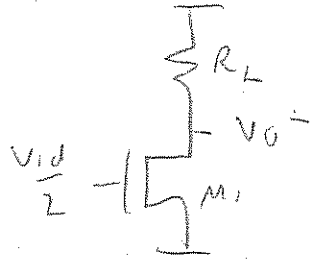


## LECTURE 7

M. H. PERROTT

1

SLIDE 12)




$$v_{o-} = -\frac{v_{id}}{2} g_m R_L, \quad v_{o+} = \frac{v_{id}}{2} g_m R_L$$

$$\Rightarrow v_{o+} - v_{o-} = \frac{1}{2} g_m R_L (v_{id} + v_{id})$$

$$= g_m R_L v_{id}$$

$$\Rightarrow \text{DIFFERENTIAL GAIN} = \boxed{a_{vd} = g_m R_L}$$

SLIDE 13)

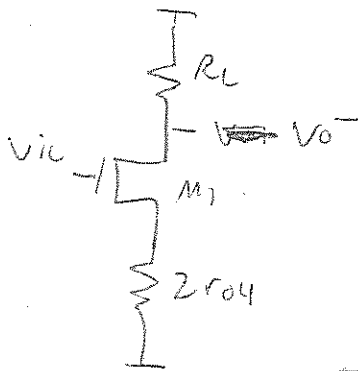

$$v_{o-} = \frac{R_L}{\frac{1}{g_m} + 2r_{o4}} v_{ic} \approx \frac{R_L}{2r_{o4}} v_{ic}$$

$$v_{o+} = \frac{R_L}{\frac{1}{g_m} + 2r_{o4}} v_{ic} \approx \frac{R_L}{2r_{o4}} v_{ic}$$

$$\Rightarrow \frac{v_{o+} + v_{o-}}{2} \approx \frac{R_L}{2r_{o4}} v_{ic}$$

$$\Rightarrow \text{COMMON MODE GAIN} = \boxed{a_{vc} \approx \frac{R_L}{2r_{o4}}}$$

SLIDE 16)

$$CMRR = 20 \log \left( \frac{a_{vd}}{a_{vc}} \right) = 20 \log \left( \frac{g_m R_L}{R_L / 2r_{o4}} \right)$$


$$\Rightarrow \boxed{CMRR = 20 \log (2 g_m r_{o4})}$$

~~PSRR~~ PSRR: SEE NEXT PAGE

SLIDE 16)  
(CONT.)

PSRR IS A COMMON MODE SIGNAL

2

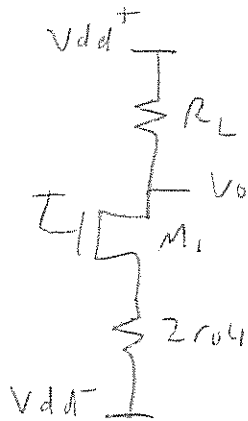

$$a_{vpt} = \frac{R_{Thd}}{R_{Thd} + R_L} V_{dd}^+$$

$$R_{Thd} \approx (g_{m1} r_{o1}) 2r_{o4}$$

(THIS IS LIKELY TO BE LARGE COMPARED TO  $R_L$ )

ASSUMING  $R_L \ll R_{Thd}$

$$\Rightarrow a_{vpt} \approx 1$$

$$\Rightarrow PSRR^+ \approx 20 \log \left( \frac{g_{m1} R_L}{\cancel{2r_{o4}}} \right)$$


$$PSRR^+ \approx 20 \log (g_{m1} R_L)$$

$$PSRR^- : a_{vp-} \approx \frac{+V_{dd}^- R_L}{2r_{o4} + \frac{1}{g_m}}$$

$$\approx \frac{R_L}{2r_{o4}} V_{dd}^-$$

$$\Rightarrow PSRR^- \approx 20 \log \left( \frac{g_{m1} R_L}{R_L / 2r_{o4}} \right)$$
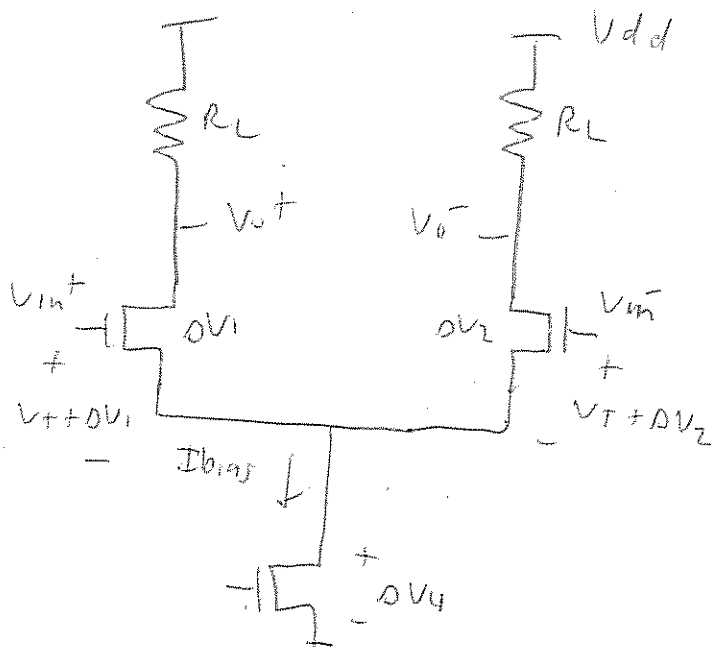
$$PSRR^- \approx 20 \log (g_{m1} 2r_{o4})$$



FOR COMMON MODE:  $V_{OC} \approx V_{O^+} = V_{O^-}$ ,  $V_{inC} = V_{in^+} = V_{in^-}$

OUTPUT RANGE:

$$V_{OC} \approx V_{DD} - \frac{I_{bias} R_L}{2}$$

→ ALWAYS THE SAME ASSUMING SATURATION IN DEVICES IN DEVICES

INPUT RANGE:

ON LOW END:  $V_{inC} > V_T + DV_1 + DV_4$

ON HIGH END:  $V_{DS1} = V_{DS2} = V_{DS}$

$$V_{DS} = V_{OC} - (V_{inC} - (V_T + DV_1)) > DV_1$$

$$= V_{OC} - V_{inC} + V_T + DV_1 > DV_1$$

$$\Rightarrow V_{OC} - V_{inC} + V_T > 0$$

$$\Rightarrow V_{inC} < V_{OC} + V_T$$

$$\Rightarrow V_T + DV_1 + DV_4 < V_{inC} < V_{OC} + V_T$$