

High Speed Communication Circuits and Systems
Lecture 4
Generalized Reflection Coefficient, Smith Chart,
Integrated Passive Components


Michael H. Perrott

February 11, 2004

Copyright © 2004 by Michael H. Perrott


All rights reserved.

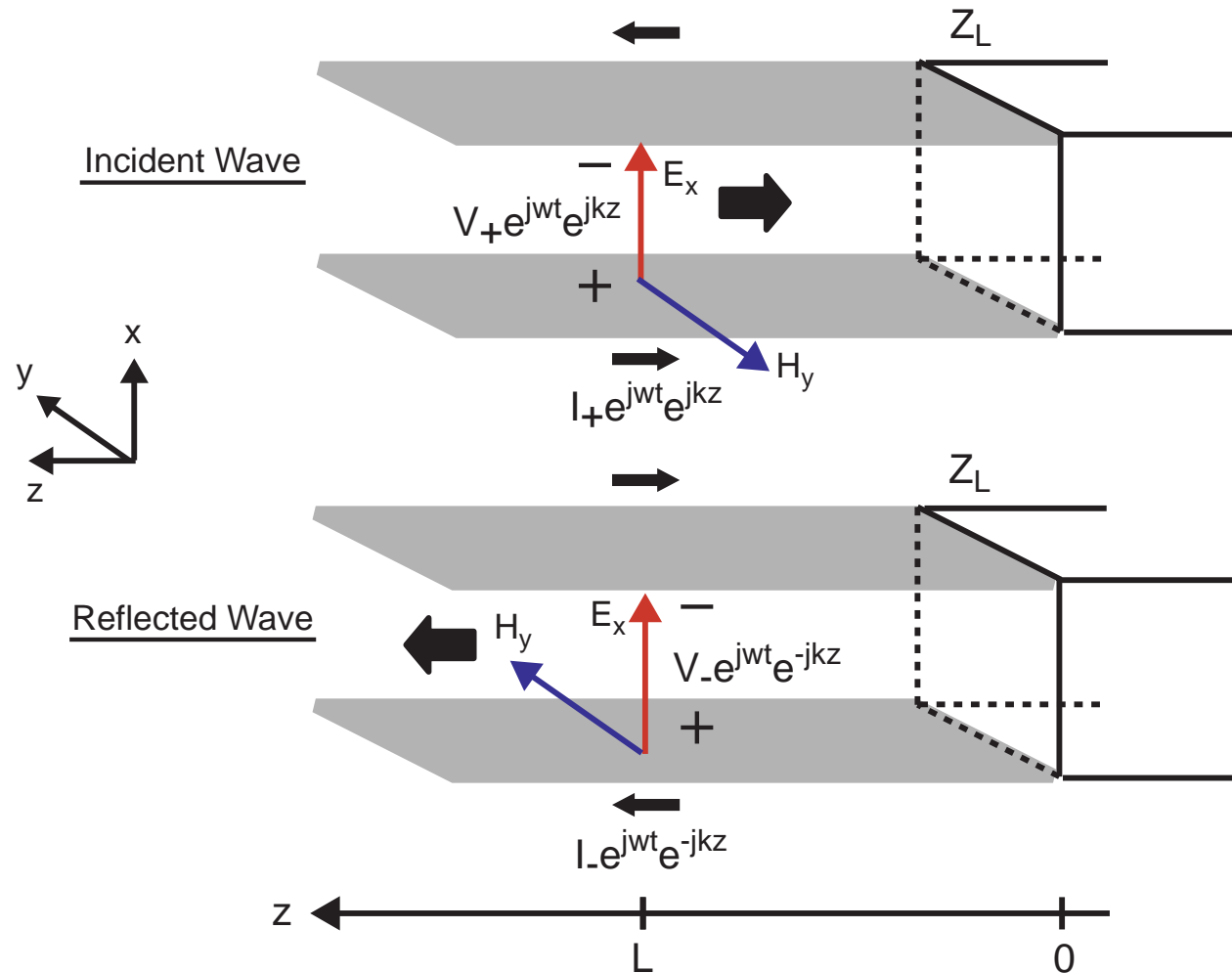Determine Voltage and Current At Different Positions



- Incident and reflected waves must be added together

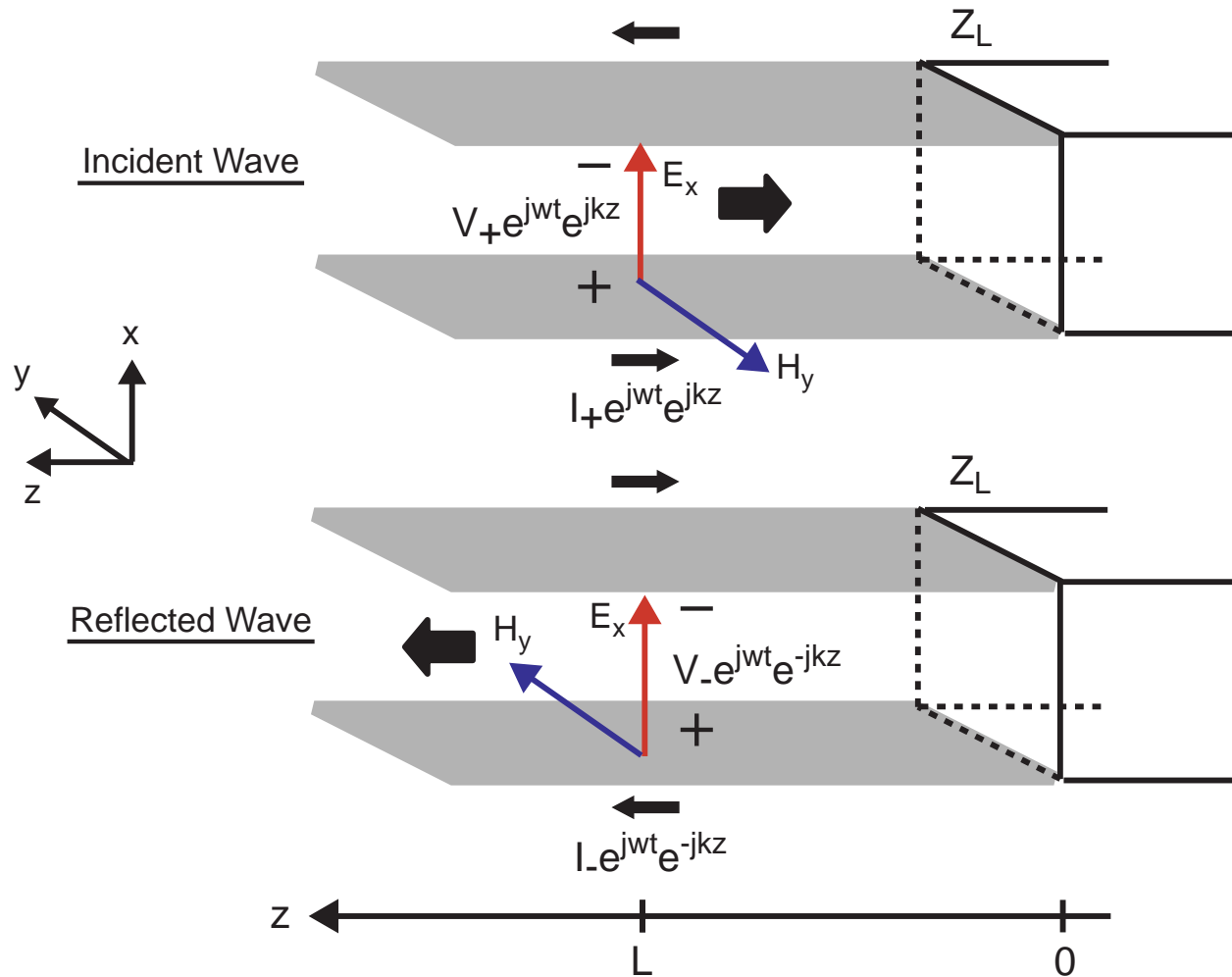Determine Voltage and Current At Different Positions



$$V(z, t) = V_+ e^{j\omega t} e^{jkz} + V_- e^{j\omega t} e^{-jkz}$$

$$I(z, t) = I_+ e^{j\omega t} e^{jkz} - I_- e^{j\omega t} e^{-jkz}$$

Define Generalized Reflection Coefficient

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} + V_- e^{j\omega t} e^{-jkz}$$

$$I(z, t) = I_+ e^{j\omega t} e^{jkz} - I_- e^{j\omega t} e^{-jkz}$$

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} \left(1 + \frac{V_-}{V_+} e^{-2jkz} \right)$$



$$V(z, t) = V_+ e^{j\omega t} e^{jkz} \left(1 + \Gamma_L e^{-2jkz} \right)$$



$$V(z, t) = V_+ e^{j\omega t} e^{jkz} (1 + \Gamma(z))$$

Similarly:

$$I(z, t) = I_+ e^{j\omega t} e^{jkz} (1 - \Gamma(z))$$

$$\Rightarrow \Gamma(z) = \Gamma_L e^{-2jkz}$$

A Closer Look at $\Gamma(z)$

- Recall Γ_L is


$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

Note: $|\Gamma_L| \leq 1$

for $\text{Re}\{Z_L/Z_o\} \geq 0$

- We can view $\Gamma(z)$ as a complex number that rotates clockwise as z (distance from the load) increases

$$\Gamma(z) = \Gamma_L e^{-2jkz}$$

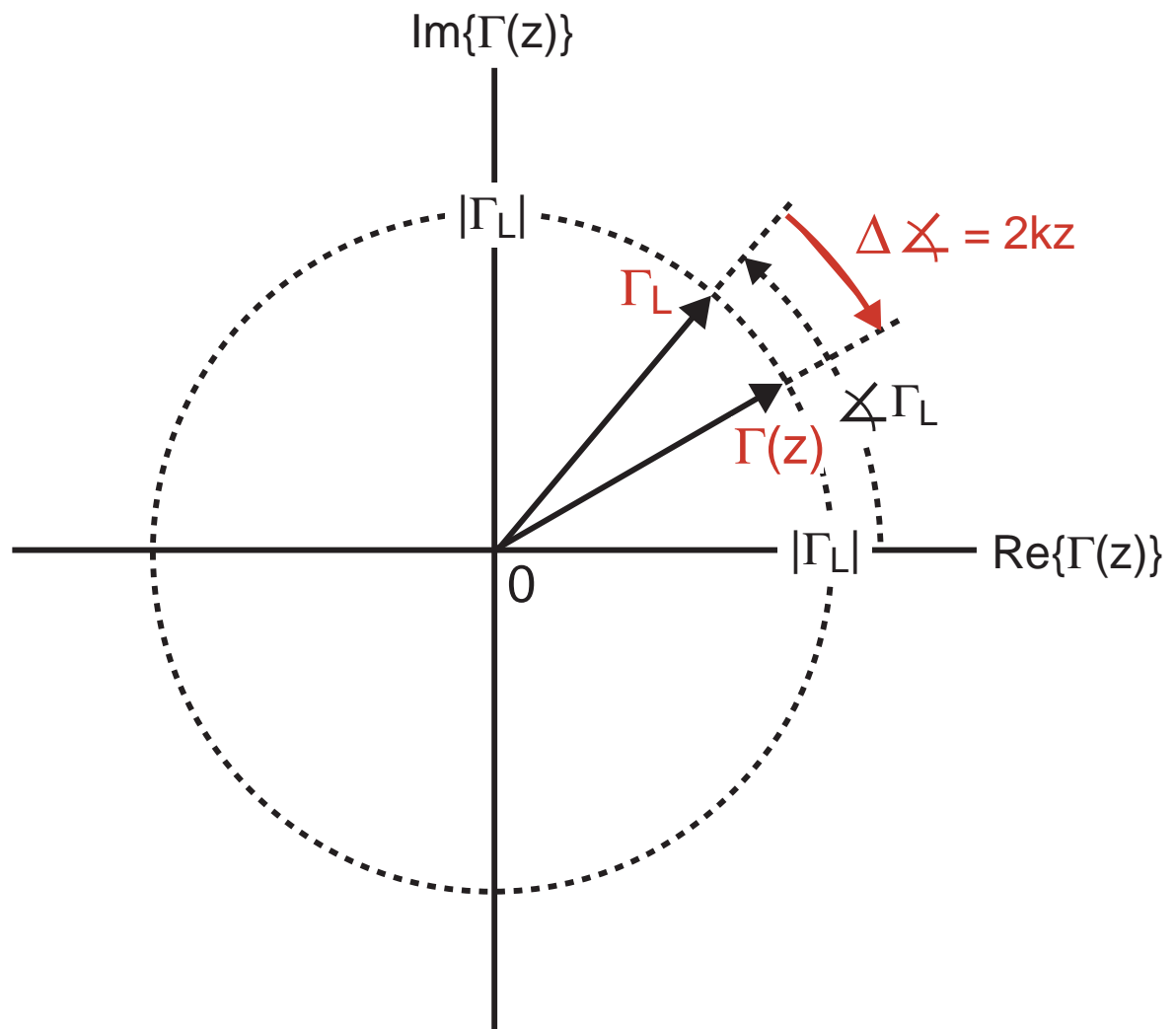

Calculate $|V_{max}|$ and $|V_{min}|$ Across The Transmission Line

- We found that

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} (1 + \Gamma(z))$$


- So that the max and min of $V(z,t)$ are calculated as

$$\Rightarrow V_{max} = \max |V(z, t)| = |V_+| \max |1 + \Gamma(z)|$$

$$\Rightarrow V_{min} = \min |V(z, t)| = |V_+| \min |1 + \Gamma(z)|$$

- We can calculate this geometrically!

A Geometric View of $|1 + \Gamma(z)|$

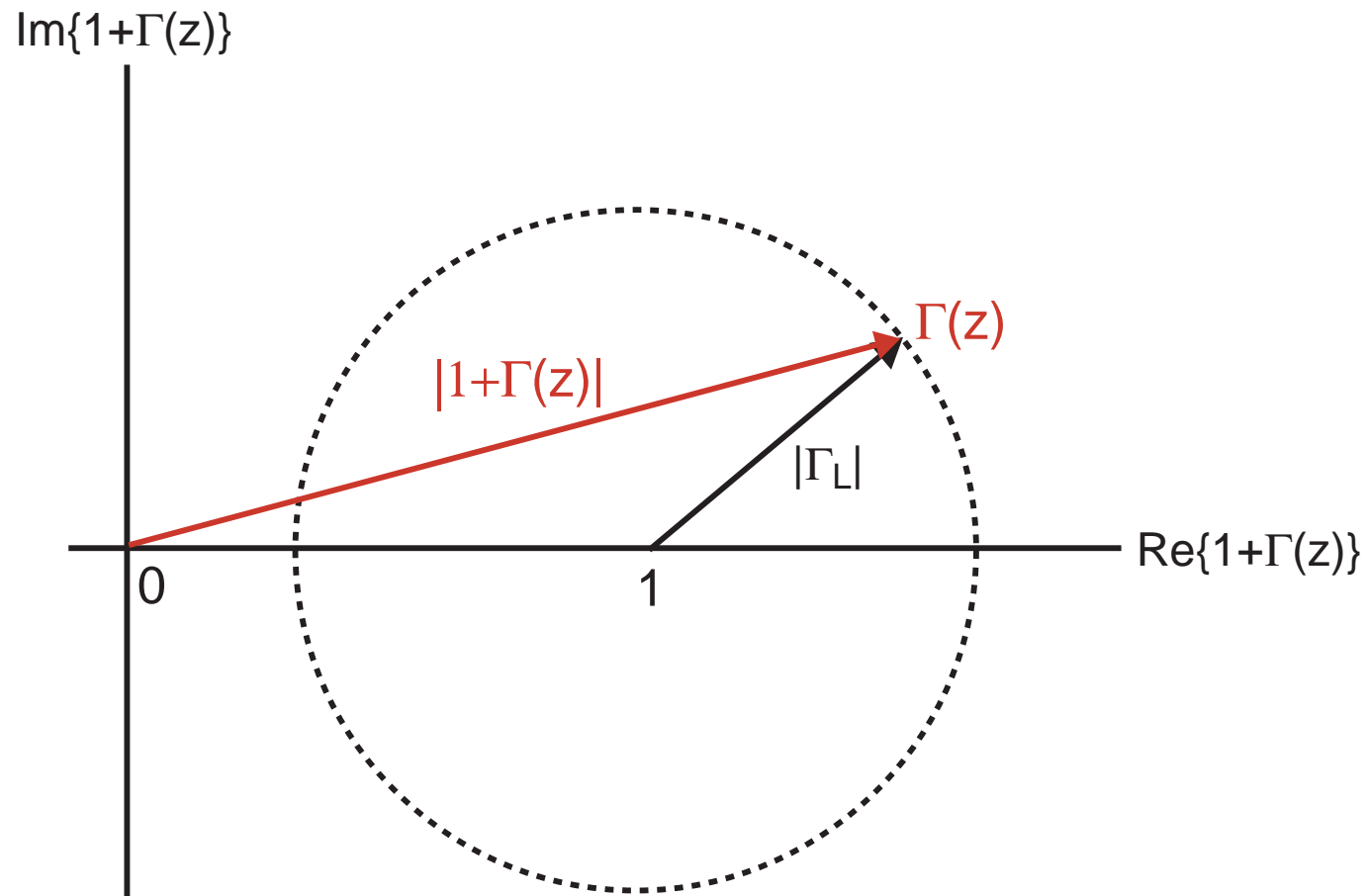


$$\Rightarrow \max |1 + \Gamma(z)| = 1 + |\Gamma_L|$$

$$\Rightarrow \min |1 + \Gamma(z)| = 1 - |\Gamma_L|$$

Reflections Cause Amplitude to Vary Across Line

- **Equation:** $V(z, t) = V_+ e^{j\omega t} e^{jkz} |1 + \Gamma(z)| e^{j\angle(1 + \Gamma(z))}$
- **Graphical representation:**

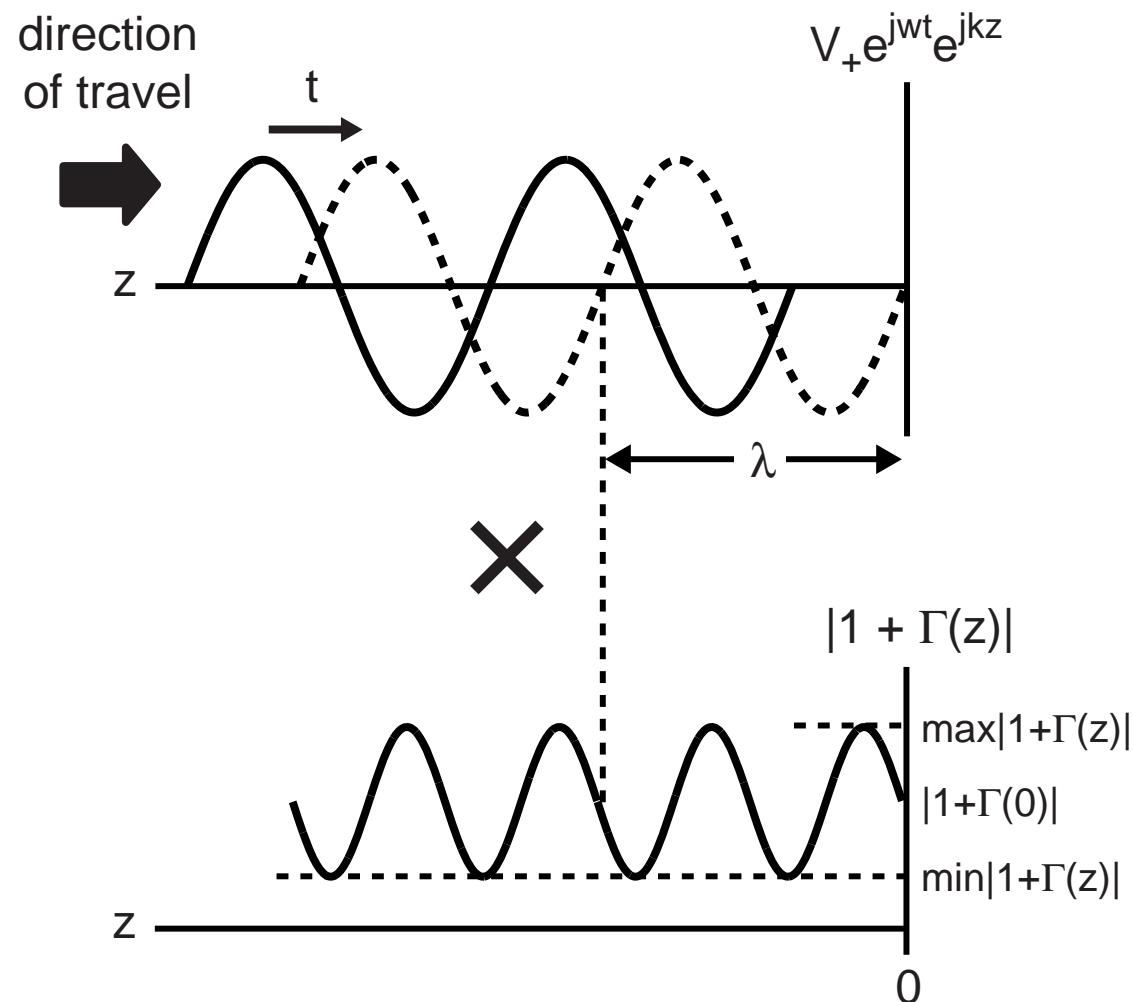


Voltage Standing Wave Ratio (VSWR)

- **Definition**

$$\text{VSWR} = \frac{V_{max}}{V_{min}} = \frac{|V_+|(1 + |\Gamma_L|)}{|V_+|(1 - |\Gamma_L|)} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

- **For passive load (and line)**

$$|\Gamma_L| \leq 1 \Rightarrow 1 \leq \text{VSWR} \leq \infty$$



$$|\Gamma_L| = 0 \qquad |\Gamma_L| = 1$$

- **We can infer the magnitude of the reflection coefficient based on VSWR**

$$|\Gamma_L| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1}$$

Reflections Influence Impedance Across The Line

- From Slide 4
$$V(z, t) = V_+ e^{j\omega t} e^{jkz} (1 + \Gamma(z))$$
$$I(z, t) = I_+ e^{j\omega t} e^{jkz} (1 - \Gamma(z))$$

$$\Rightarrow Z(z, t) = \frac{V_+(1 + \Gamma(z))}{I_+(1 - \Gamma(z))} = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$


- Note: not a function of time! (only of distance from load)

- Alternatively
$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-2jkz}}{1 - \Gamma_L e^{-2jkz}}$$

- From Lecture 2:
$$\lambda = \frac{T}{\sqrt{\mu\epsilon}} = \frac{\omega T}{\omega\sqrt{\mu\epsilon}} = \frac{2\pi f T}{k} = \frac{2\pi}{k}$$

$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-j(4\pi/\lambda)z}}{1 - \Gamma_L e^{-j(4\pi/\lambda)z}}$$

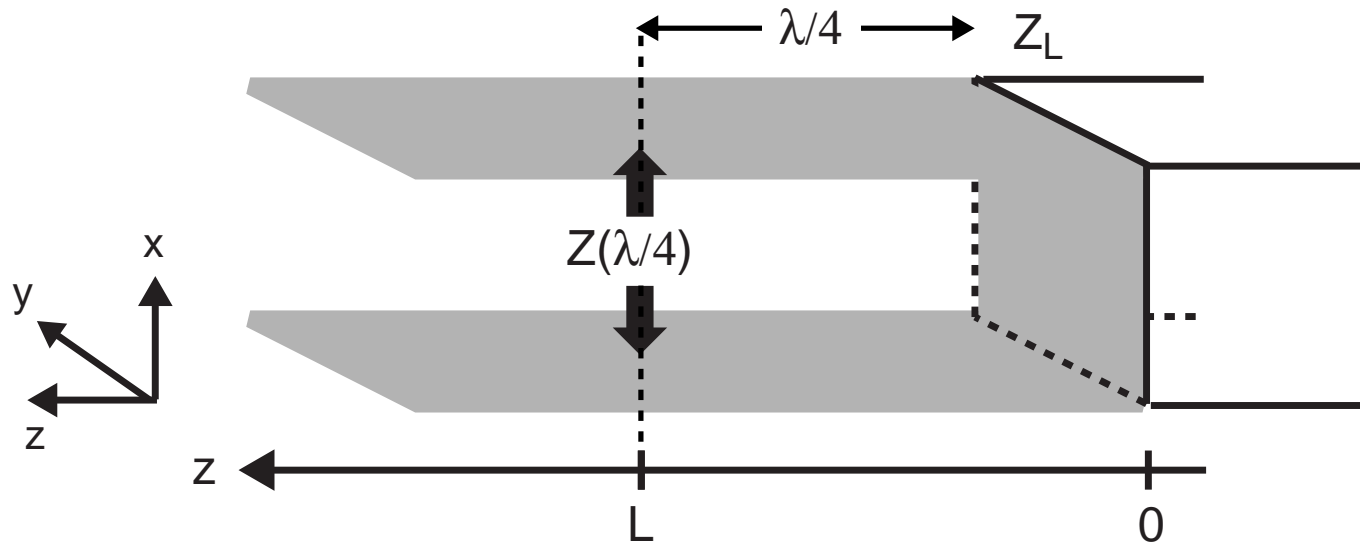Example: $Z(\lambda/4)$ with Shorted Load



- Calculate reflection coefficient

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$$

- Calculate generalized reflection coefficient

$$\Gamma(\lambda/4) = \Gamma_L e^{-j(4\pi/\lambda)(\lambda/4)} = \Gamma_L e^{-j\pi} = -\Gamma_L = 1$$

- Calculate impedance $Z(\lambda/4) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)} = \infty !$

Generalize Relationship Between $Z(\lambda/4)$ and $Z(0)$

- **General formulation**

$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-j(4\pi/\lambda)z}}{1 - \Gamma_L e^{-j(4\pi/\lambda)z}}$$

- **At load ($z=0$)**

$$Z_L = Z(0) = Z_o \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

- **At quarter wavelength away ($z = \lambda/4$)**

$$Z(\lambda/4) = Z_o \frac{1 - \Gamma_L}{1 + \Gamma_L} = \frac{Z_o^2}{Z_L}$$

- **Impedance is inverted!**

- Shorts turn into opens
- Capacitors turn into inductors

Now Look At $Z(\Delta)$ (Impedance Close to Load)

- Impedance formula (Δ very small)

$$Z(\Delta) = Z_o \frac{1 + \Gamma_L e^{-2jk\Delta}}{1 - \Gamma_L e^{-2jk\Delta}}$$

- A useful approximation: $e^{-jx} \approx 1 - jx$ for $x \ll 1$


$$\Rightarrow e^{-2jk\Delta} \approx 1 - 2jk\Delta$$

- Recall from Lecture 2: $k = w\sqrt{LC}$, $Z_o = \sqrt{\frac{L}{C}}$

- Overall approximation:

$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}{1 - \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}$$

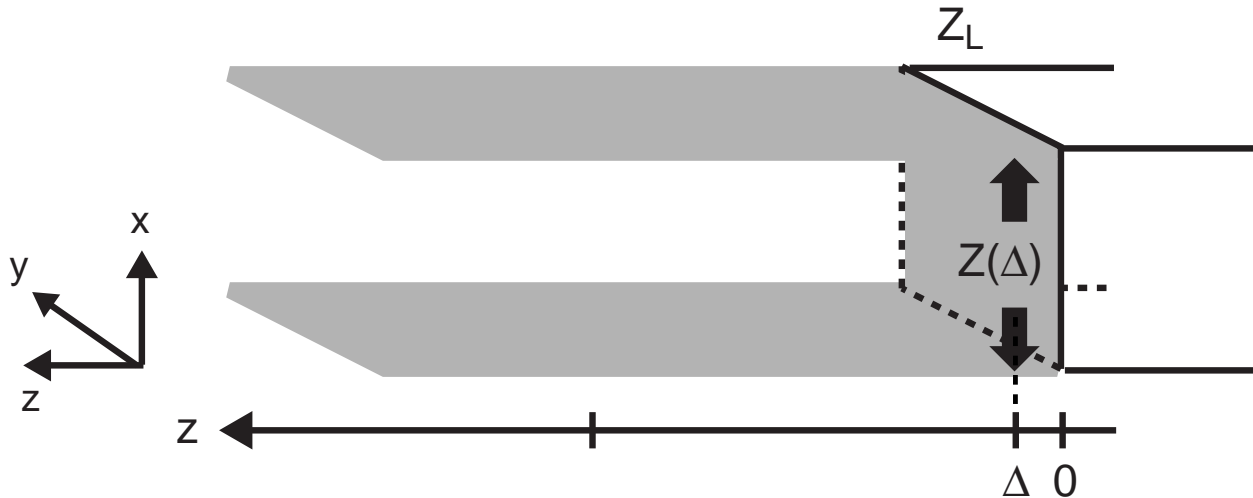Example: Look At $Z(\Delta)$ With Load Shorted




$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L(1 - 2j\omega\sqrt{LC}\Delta)}{1 - \Gamma_L(1 - 2j\omega\sqrt{LC}\Delta)}$$

- **Reflection coefficient:** $\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$
- **Resulting impedance looks inductive!**

$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 - (1 - 2j\omega\sqrt{LC}\Delta)}{1 + (1 - 2j\omega\sqrt{LC}\Delta)} \approx j\omega L\Delta$$

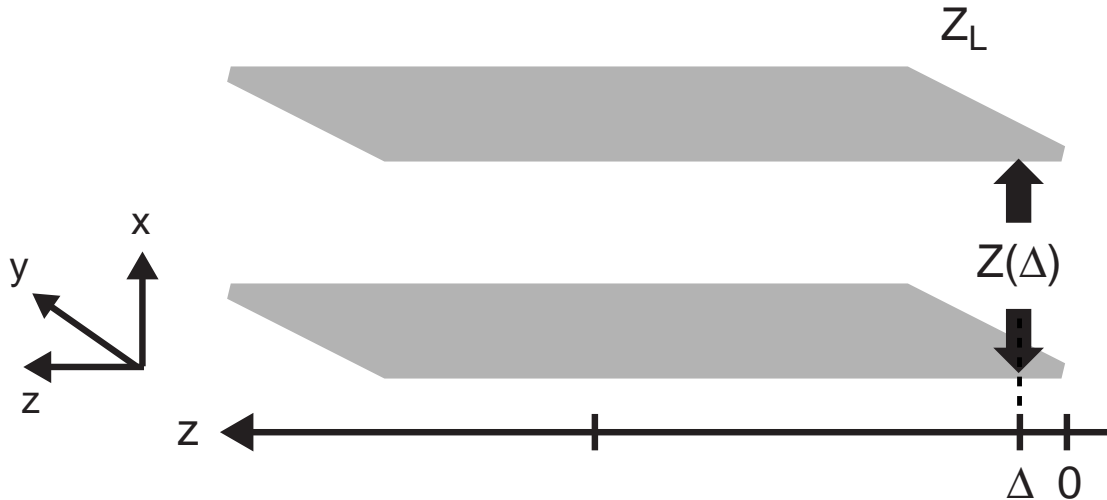Example: Look At $Z(\Delta)$ With Load Open




$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L(1 - 2j\omega\sqrt{LC}\Delta)}{1 - \Gamma_L(1 - 2j\omega\sqrt{LC}\Delta)}$$

- **Reflection coefficient:** $\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{\infty - Z_o}{\infty + Z_o} = 1$
- **Resulting impedance looks capacitive!**

$$Z(\Delta) \approx \left(\sqrt{\frac{L}{C}} \right) \frac{1 + (1 - 2j\omega\sqrt{LC}\Delta)}{1 - (1 - 2j\omega\sqrt{LC}\Delta)} \approx \frac{1}{j\omega C \Delta}$$

Consider an Ideal LC Tank Circuit

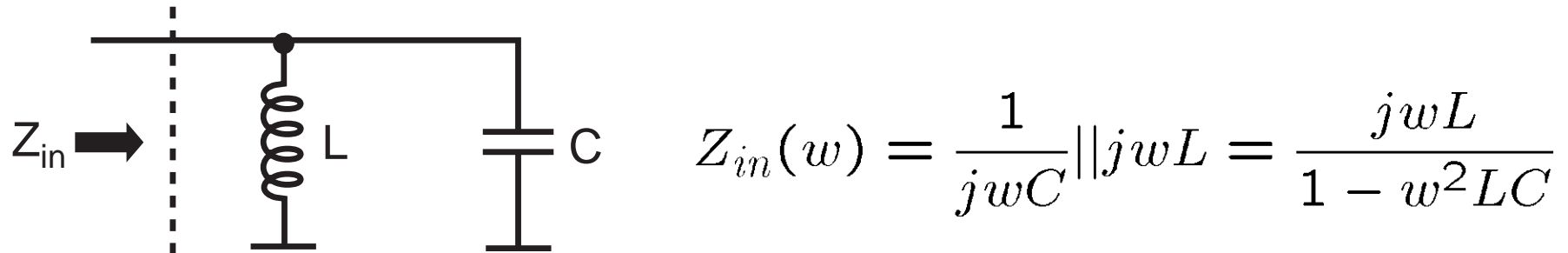


- Calculate input impedance about resonance

Consider $w = w_o + \Delta w$, where $w_o = \frac{1}{\sqrt{LC}}$

$$\begin{aligned}
 Z_{in}(\Delta w) &= \frac{j(w_o + \Delta w)L}{1 - (w_o + \Delta w)^2 LC} \\
 &= \frac{j(w_o + \Delta w)L}{\underbrace{1 - w_o^2 LC}_{= 0} - 2\Delta w(w_o LC) - \underbrace{\Delta w^2 LC}_{\text{negligible}}}
 \end{aligned}$$

$$\Rightarrow Z_{in}(\Delta w) \approx \frac{j(w_o + \Delta w)L}{-2\Delta w(w_o LC)} \approx \frac{jw_o L}{-2\Delta w(w_o LC)} = \boxed{-\frac{j}{2} \sqrt{\frac{L}{C}} \left(\frac{w_o}{\Delta w} \right)}$$

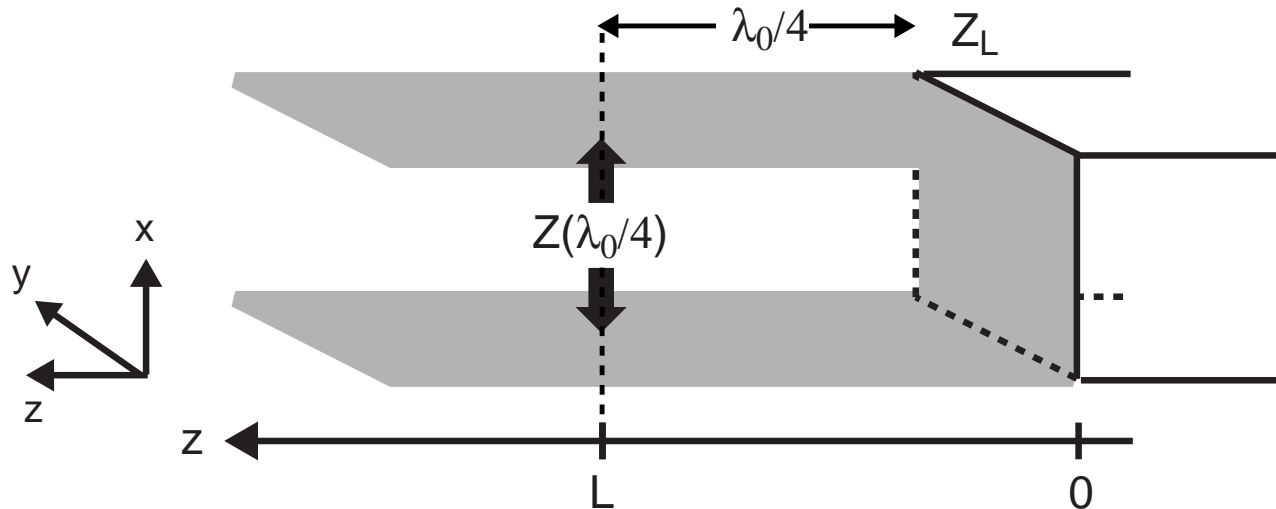Transmission Line Version: $Z(\lambda_0/4)$ with Shorted Load



- As previously calculated

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$$


- Impedance calculation

$$Z(z) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}, \quad \text{where } \Gamma(z) = \Gamma_L e^{-j(4\pi/\lambda)z}$$

- Relate λ to frequency

$$\lambda = \frac{1}{f\sqrt{\mu\epsilon}} = \frac{1}{(f_o + \Delta f)\sqrt{\mu\epsilon}}$$

Calculate $Z(\Delta f)$ – Step 1

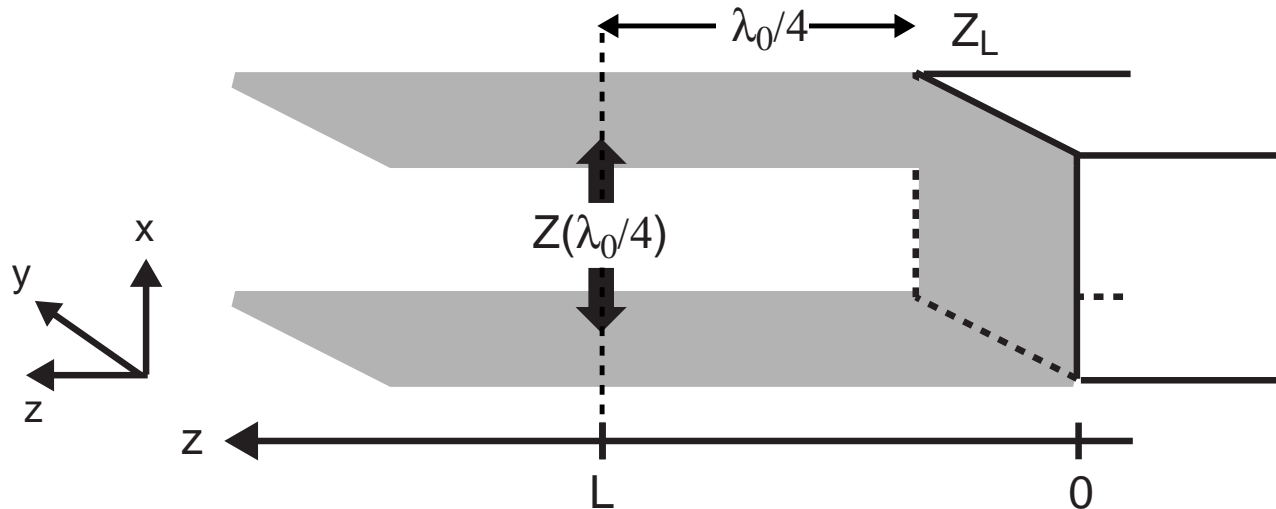

- **Wavelength as a function of Δf**


$$\lambda = \frac{1}{(f_o + \Delta f)\sqrt{\mu\epsilon}} = \frac{1}{f_o\sqrt{\mu\epsilon}(1 + \Delta f/f_o)} = \frac{\lambda_o}{1 + \Delta f/f_o}$$

- **Generalized reflection coefficient**

$$\Gamma(\lambda_o/4) = \Gamma_L e^{-j(4\pi/\lambda)\lambda_o/4} = \Gamma_L e^{-j\pi\lambda_o/\lambda} = \Gamma_L e^{-j\pi\lambda_o/\lambda}$$

$$\Rightarrow \Gamma(\lambda_o/4) = \Gamma_L e^{-j\pi(1+\Delta f/f_o)} = -\Gamma_L e^{-j\pi\Delta f/f_o}$$

Calculate $Z(\Delta f)$ – Step 2

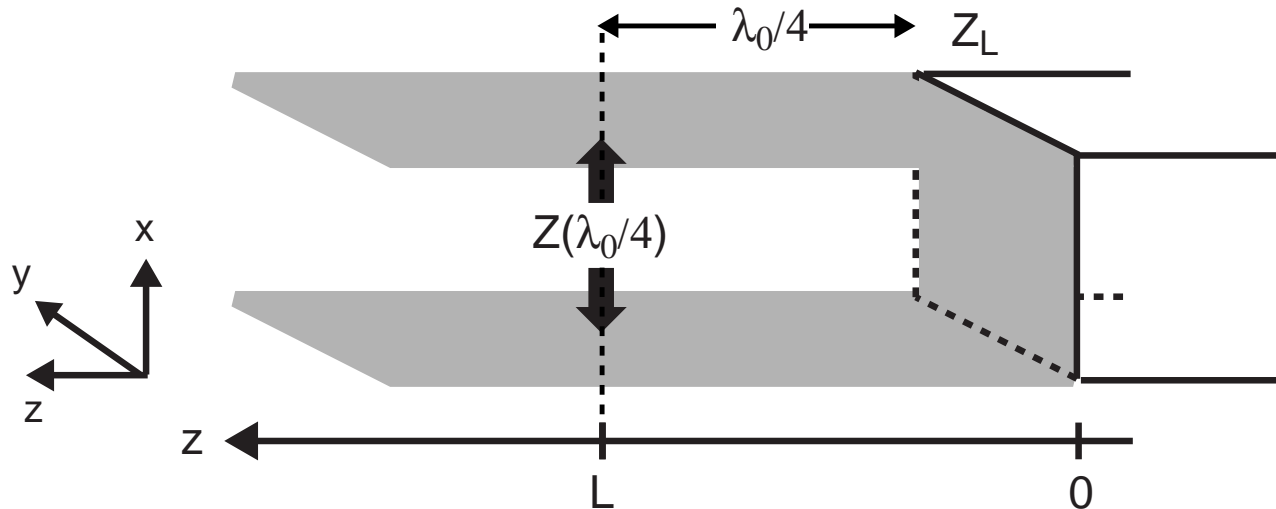

- Impedance calculation

$$Z(\lambda_0/4) = Z_0 \frac{1 - \Gamma_L e^{-j\pi\Delta f/f_0}}{1 + \Gamma_L e^{-j\pi\Delta f/f_0}} = Z_0 \frac{1 + e^{-j\pi\Delta f/f_0}}{1 - e^{-j\pi\Delta f/f_0}}$$

- Recall $e^{-j\pi\Delta f/f_0} \approx 1 - j\pi\Delta f/f_0$

$$\Rightarrow Z(z) \approx Z_0 \frac{1 + 1 - j\pi\Delta f/f_0}{1 - 1 + j\pi\Delta f/f_0} \approx Z_0 \frac{2}{j\pi\Delta f/f_0} = \boxed{-j \frac{2}{\pi} \sqrt{\frac{L}{C}} \left(\frac{w_0}{\Delta w} \right)}$$

- Looks like LC tank circuit (but more than one mode)!

Smith Chart

- Define normalized impedance

$$Z_n = \frac{Z_L}{Z_o}$$

- Mapping from normalized impedance to Γ is one-to-one

$$Z_n = \frac{1 + \Gamma_L}{1 - \Gamma_L}$$


- Consider working in coordinate system based on Γ

- Key relationship between Z_n and Γ

$$Re\{Z_n\} + jIm\{Z_n\} = \frac{1 + Re\{\Gamma_L\} + jIm\{\Gamma_L\}}{1 - (Re\{\Gamma_L\} + jIm\{\Gamma_L\})}$$


- Equate real and imaginary parts to get Smith Chart

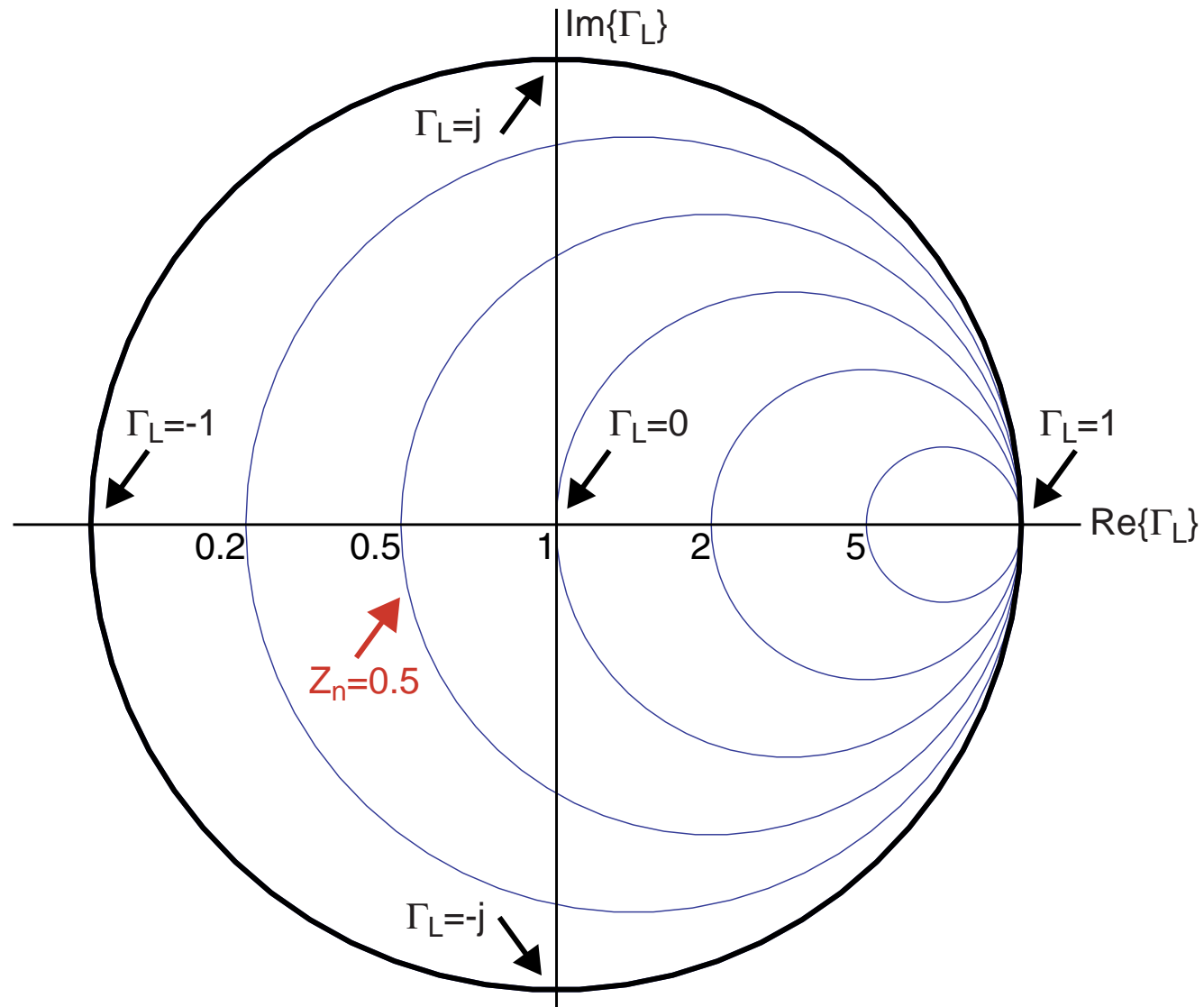Real Impedance in Γ Coordinates (Equate Real Parts)



$$\left(\text{Re}\{\Gamma_L\} - \frac{\text{Re}\{Z_n\}}{1 + \text{Re}\{Z_n\}} \right)^2 + (\text{Im}\{\Gamma_L\})^2 = \left(\frac{1}{1 + \text{Re}\{Z_n\}} \right)^2$$

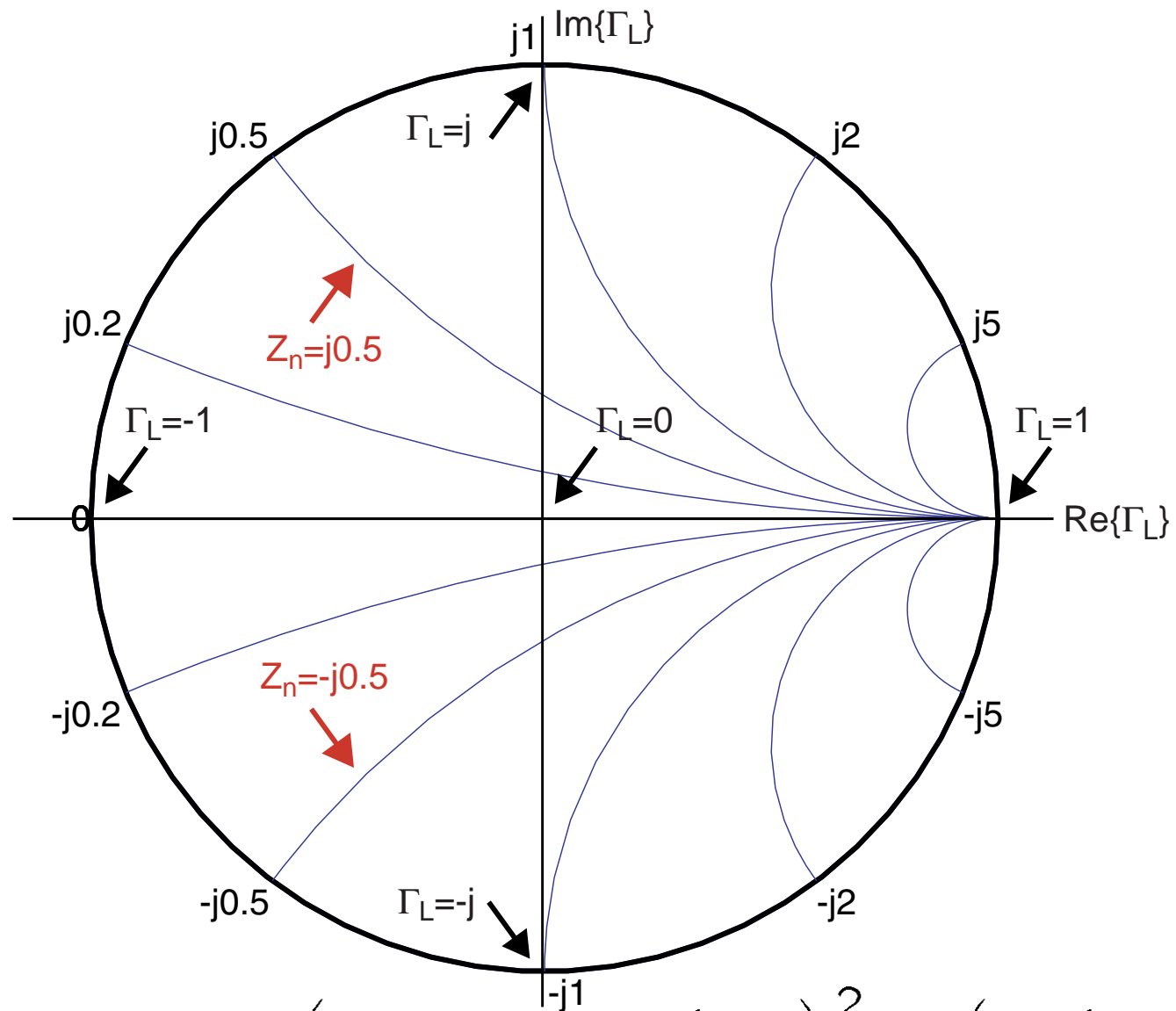Imag. Impedance in Γ Coordinates (Equate Imag. Parts)



$$\left(\operatorname{Re}\{\Gamma_L\} - 1 \right)^2 + \left(\operatorname{Im}\{\Gamma_L\} - \frac{1}{\operatorname{Im}\{Z_n\}} \right)^2 = \left(\frac{1}{\operatorname{Im}\{Z_n\}} \right)^2$$

What Happens When We Invert the Impedance?

- **Fundamental formulas**

$$Z_n = \frac{1 + \Gamma_L}{1 - \Gamma_L} \Rightarrow \Gamma_L = \frac{Z_n - 1}{Z_n + 1}$$

- **Impact of inverting the impedance**

$$Z_n \rightarrow 1/Z_n \Rightarrow \Gamma_L \rightarrow -\Gamma_L$$

- **Derivation:**

$$\frac{1/Z_n - 1}{1/Z_n + 1} = \frac{1 - Z_n}{1 + Z_n} = - \left(\frac{Z_n - 1}{Z_n + 1} \right)$$

- **We can invert complex impedances in Γ plane by simply changing the sign of Γ !**
- **How can we best exploit this?**


The Smith Chart as a Calculator for Matching Networks

- Consider constructing both impedance and admittance curves on Smith chart


$$Z_n \rightarrow 1/Z_n \Rightarrow \Gamma_L \rightarrow -\Gamma_L$$

- Conductance curves derived from resistance curves
 - Susceptance curves derived from reactance curves
-
- For series circuits, work with impedance
 - Impedances add for series circuits
 - For parallel circuits, work with admittance
 - Admittances add for parallel circuits

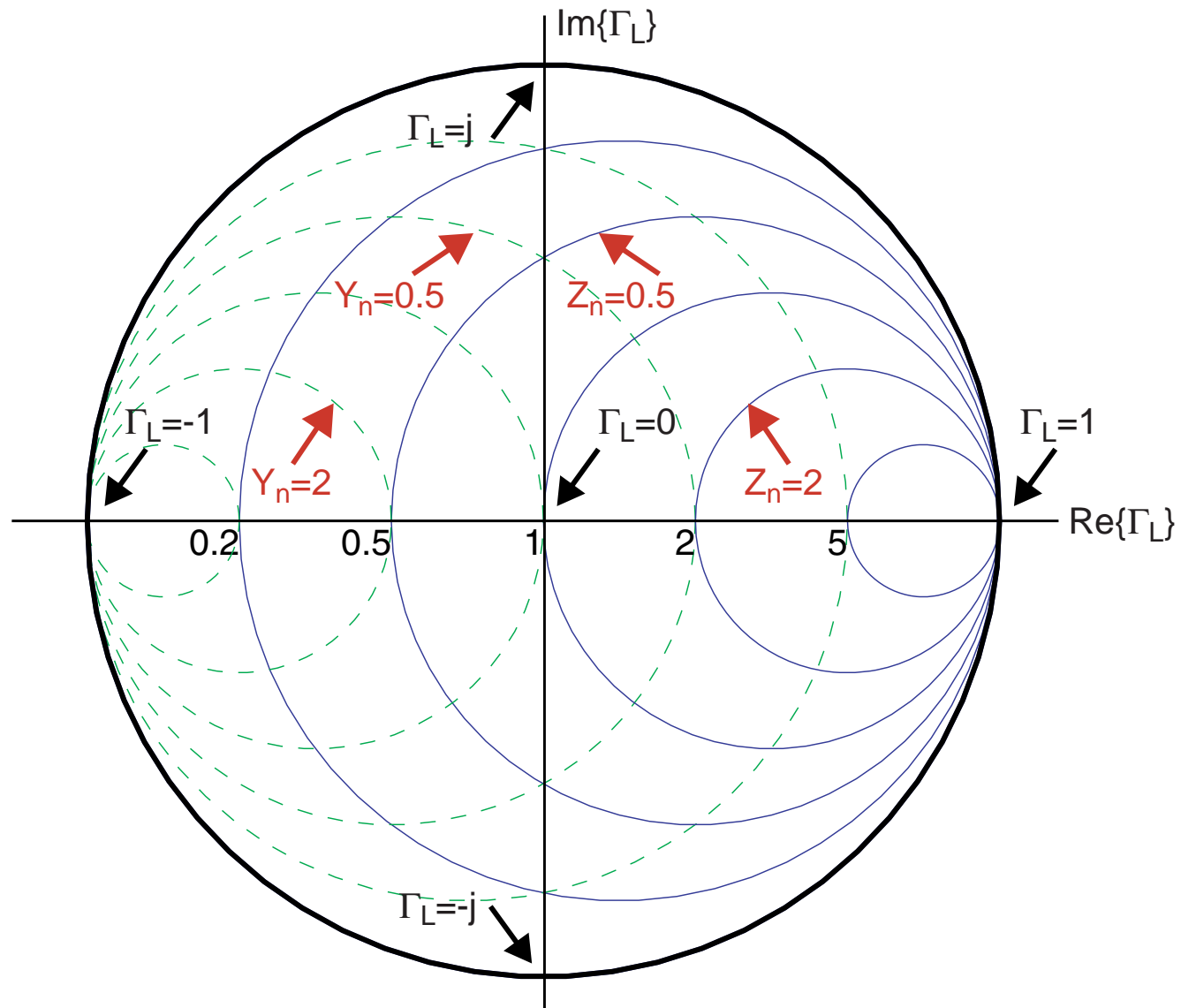
Resistance and Conductance on the Smith Chart



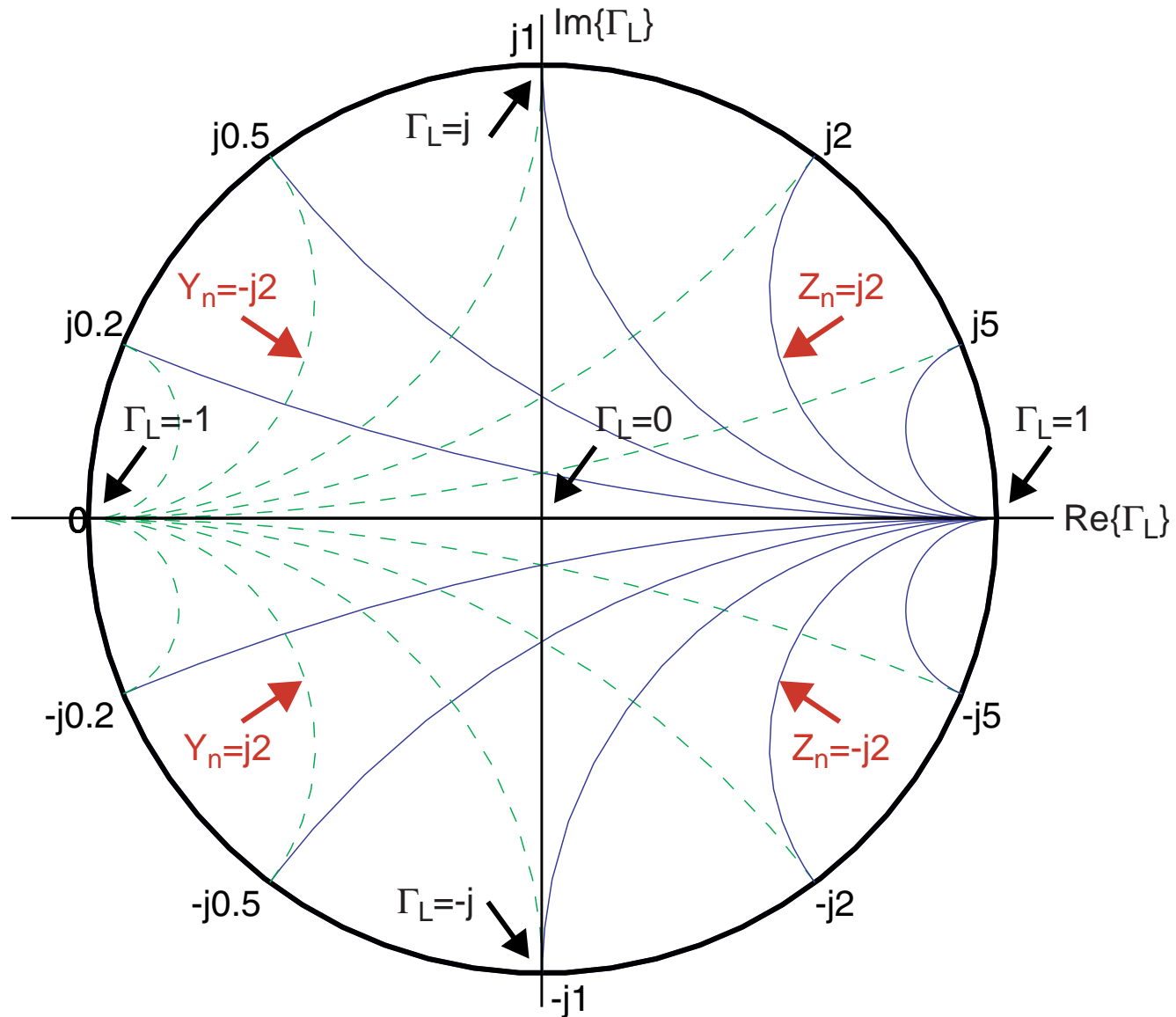Reactance and Susceptance on the Smith Chart




Overall Smith Chart

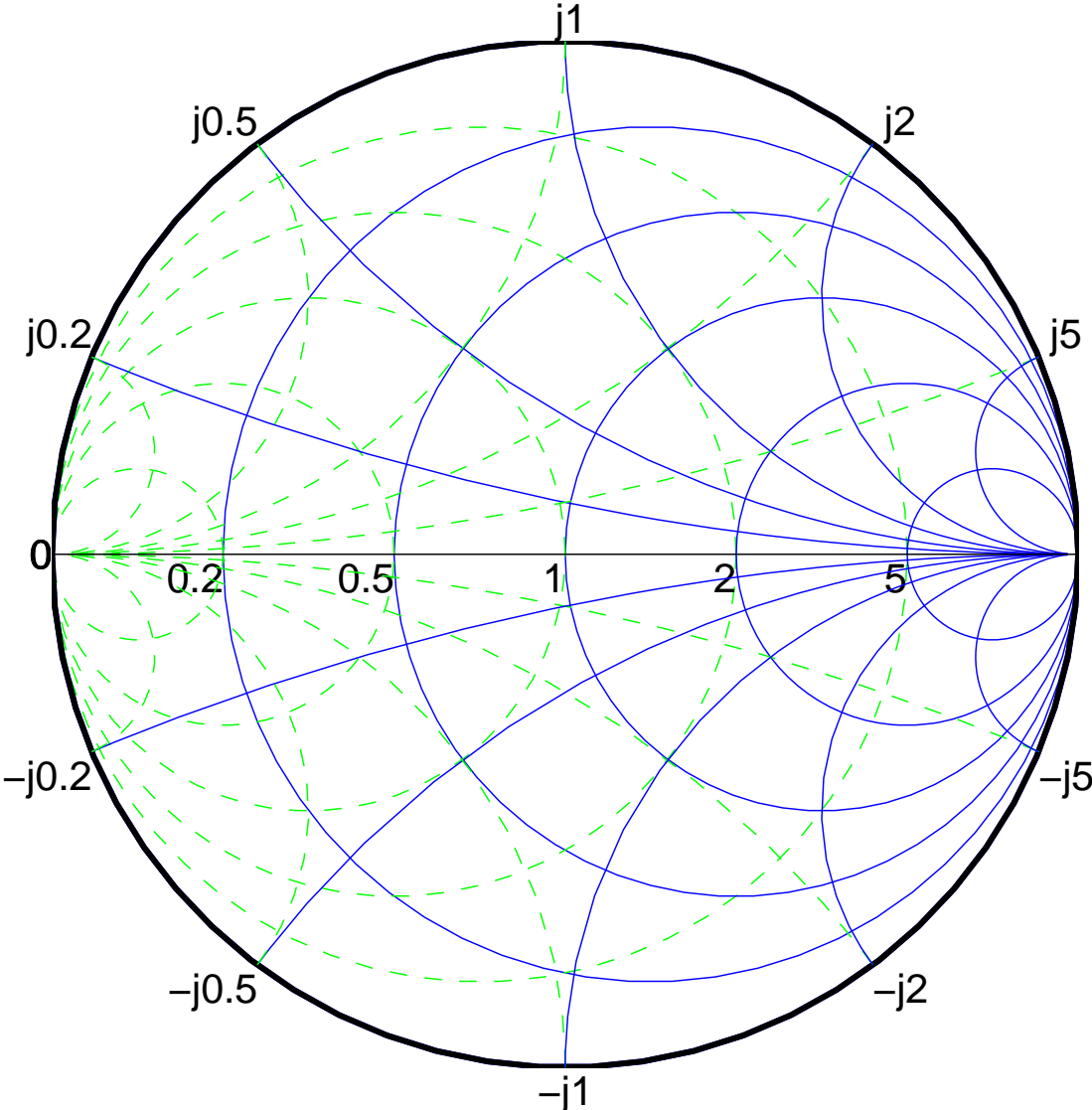

Example – Match RC Network to 50 Ohms at 2.5 GHz

■ Circuit

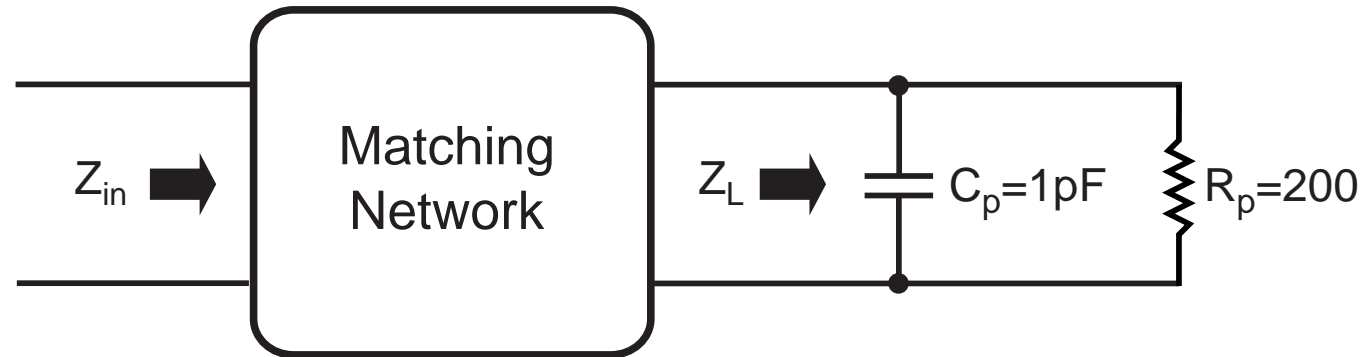


■ Step 1: Calculate Z_{Ln}

$$\begin{aligned} Z_{Ln} &= \frac{Z_L}{Z_o} = \frac{R_L || (1/j\omega C)}{50} = \frac{1}{50(1/R_L + j\omega C)} \\ &= \frac{1}{50(1/200 + j2\pi(2.5e9)10^{-12})} = \frac{1}{0.25 + j.7854} \end{aligned}$$

■ Step 2: Plot Z_{Ln} on Smith Chart (use admittance, Y_{Ln})

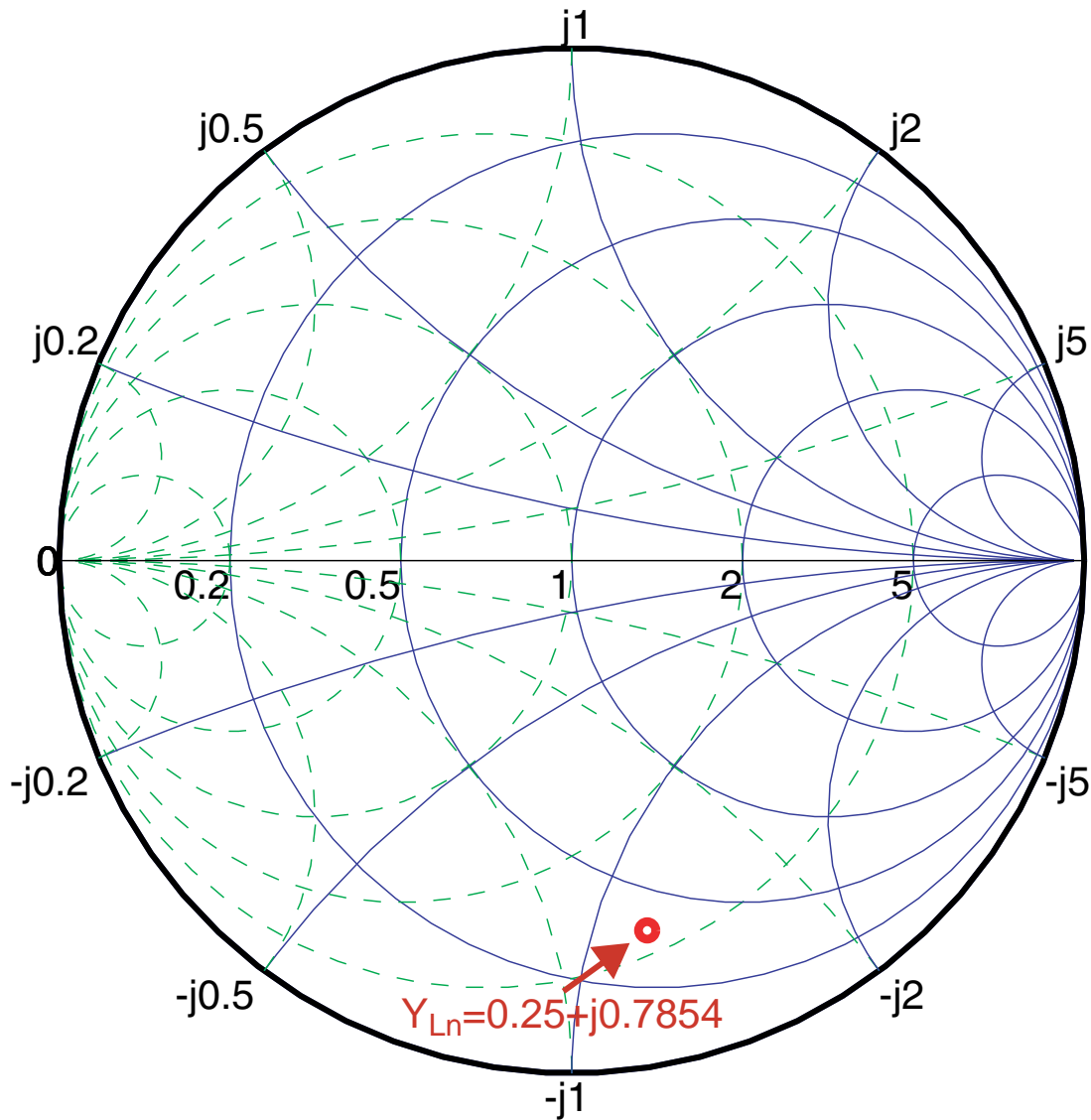
Plot Starting Impedance (Admittance) on Smith Chart



(Note: $Z_{Ln} = 0.37 - j1.16$)


Develop Matching “Game Plan” Based on Smith Chart

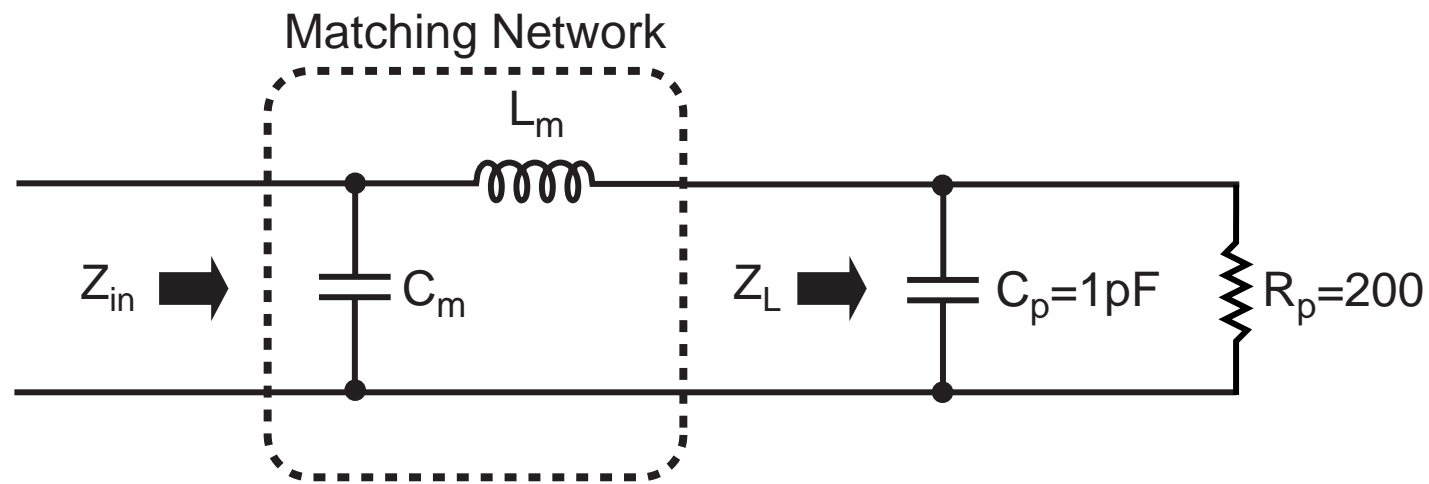- By inspection, we see that the following matching network can bring us to $Z_{in} = 50$ Ohms (center of Smith chart)



- Use the Smith chart to come up with component values
 - Inductance L_m shifts impedance up along reactance curve
 - Capacitance C_m shifts impedance down along susceptance curve

Add Reactance of Inductor L_m

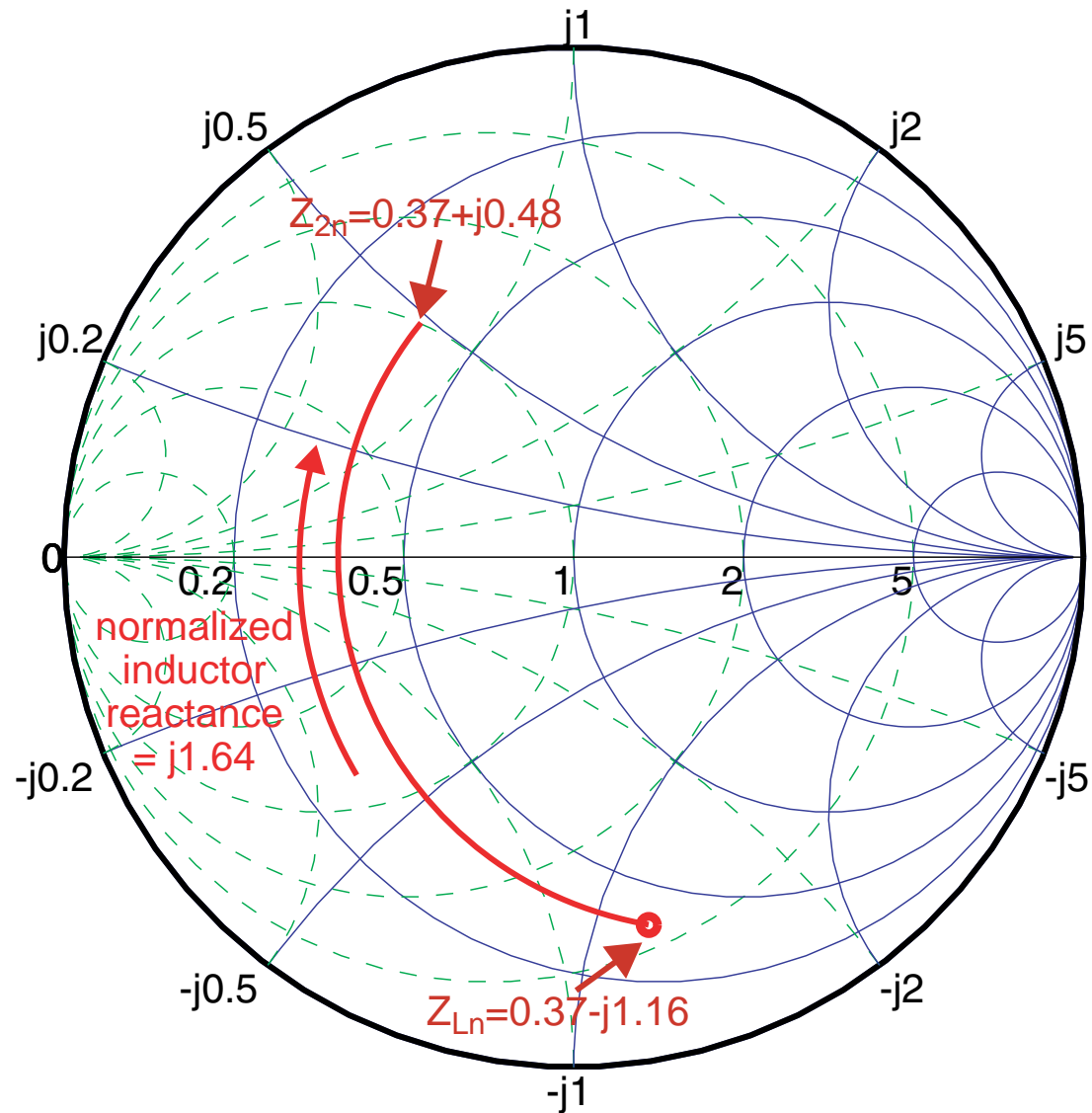

Inductor Value Calculation Using Smith Chart


- From Smith chart, we found that the desired normalized inductor reactance is

$$\frac{j\omega L_m}{Z_o} = \frac{j\omega L_m}{50} = j1.64$$

- Required inductor value is therefore

$$\Rightarrow L_m = \frac{50(1.64)}{2\pi 2.5e9} = 5.2nH$$

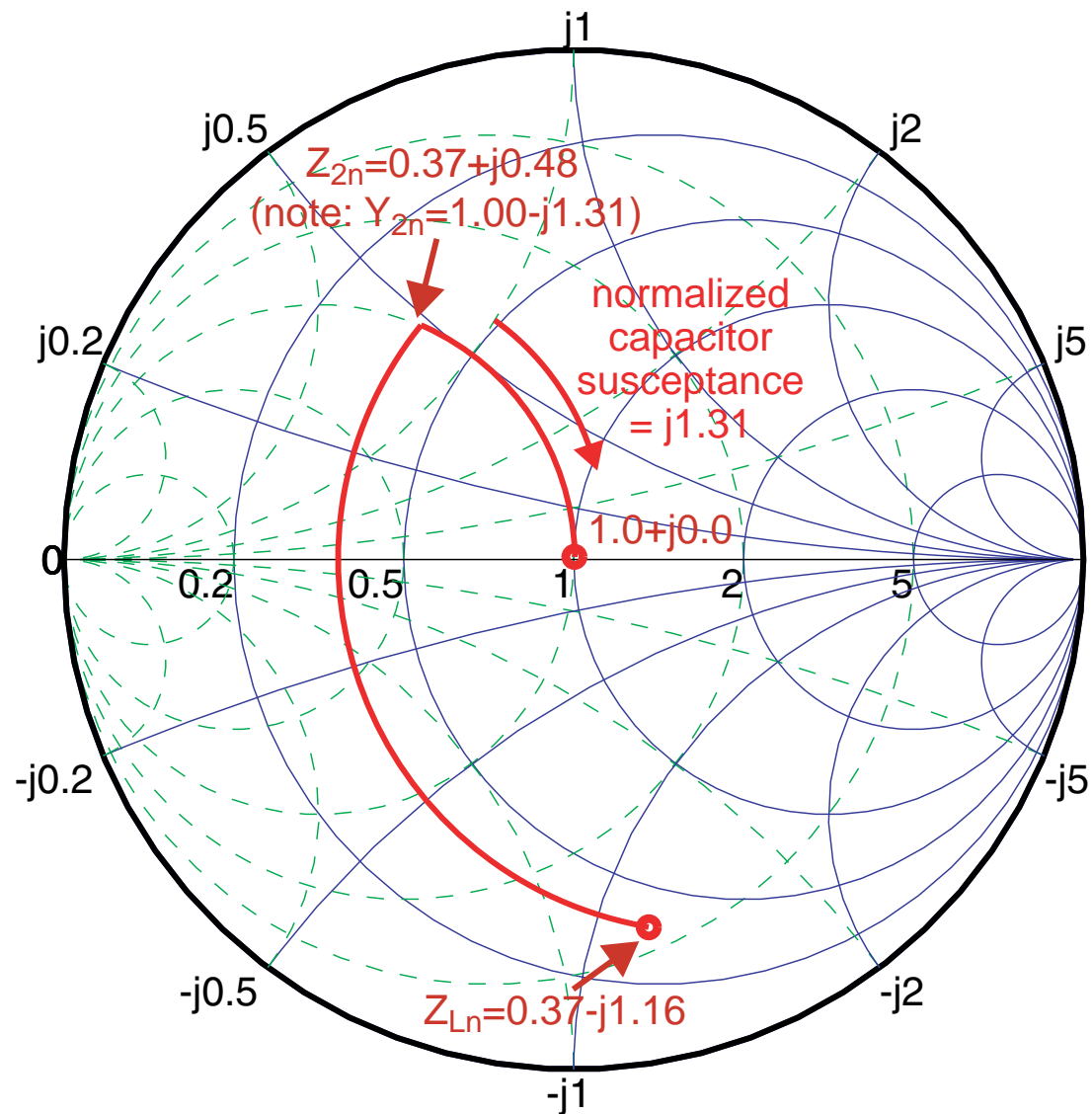Add Susceptance of Capacitor C_m (Achieves Match!)



Capacitor Value Calculation Using Smith Chart

- From Smith chart, we found that the desired normalized capacitor susceptance is

$$Z_o j\omega C_m = 50 j\omega C_m = j1.31$$

- Required capacitor value is therefore

$$\Rightarrow C_m = \frac{1.31}{50(2\pi 2.5e9)} = 1.67 pF$$

Just For Fun

- **Play the “matching game” at**


<http://contact.tm.agilent.com/Agilent/tmo/an-95-1/classes/imatch.html>

- **Allows you to graphically tune several matching networks**
- **Note: game is set up to match source to load impedance rather than match the load to the source impedance**
 - Same results, just different viewpoint

Passives

Polysilicon Resistors

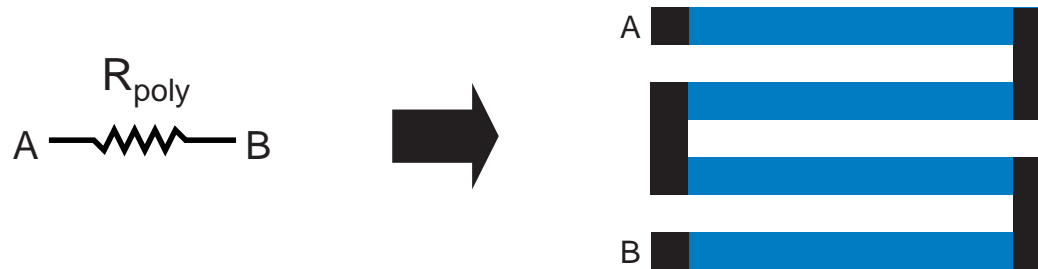
- Use unsilicided polysilicon to create resistor



- Key parameters
 - Resistance (usually 100- 200 Ohms per square)
 - Parasitic capacitance (usually small)
 - Appropriate for high speed amplifiers
 - Linearity (quite linear compared to other options)
 - Accuracy (usually can be set within $\pm 15\%$)

MOS Resistors

- Bias a MOS device in its triode region

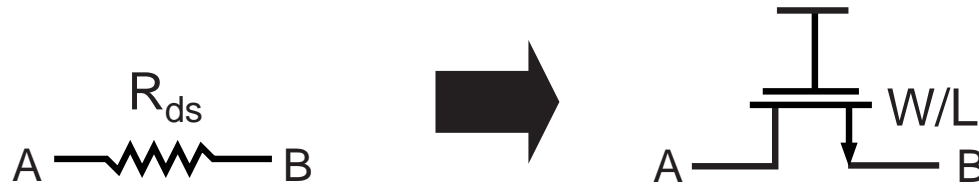


$$R_{ds} \approx \frac{1}{\mu C_{ox} W/L ((V_{gs} - V_T) - V_{DS})}$$

- High resistance values can be achieved in a small area (MegaOhms within tens of square microns)
- Resistance is quite nonlinear
 - Appropriate for small swing circuits

High Density Capacitors (Biasing, Decoupling)

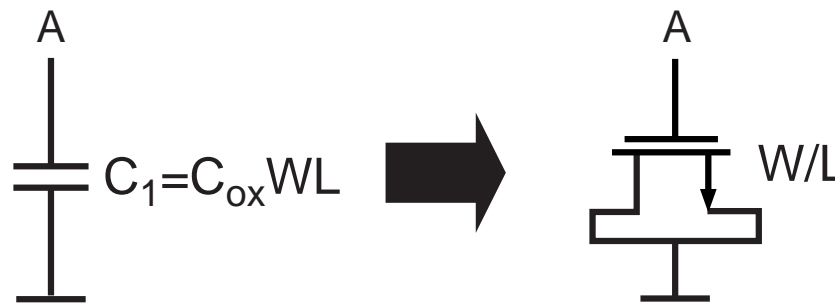
- **MOS devices offer the highest capacitance per unit area**
 - Limited to a one terminal device
 - Voltage must be high enough to invert the channel



- **Key parameters**
 - **Capacitance value**
 - Raw cap value from MOS device is $6.1 \text{ fF}/\mu \text{ m}^2$ for $0.24\mu \text{ CMOS}$
 - **Q (i.e., amount of series resistance)**
 - Maximized with minimum L (tradeoff with area efficiency)
- **See pages 39-40 of Tom Lee's book**

High Q Capacitors (Signal Path)

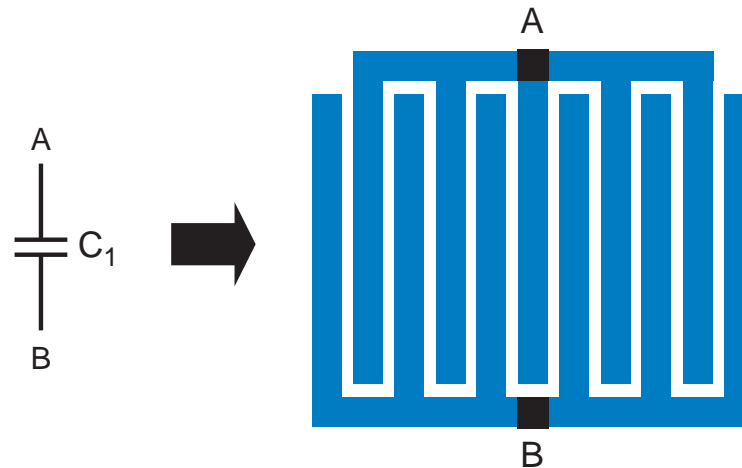
- Lateral metal capacitors offer high Q and reasonably large capacitance per unit area
 - Stack many levels of metal on top of each other (best layers are the top ones), via them at maximum density



- Accuracy often better than $\pm 10\%$
 - Parasitic side cap is symmetric, less than 10% of cap value
- Example: $C_T = 1.5 \text{ fF}/\mu\text{m}^2$ for $0.24\mu\text{m}$ process with 7 metals, $L_{\min} = W_{\min} = 0.24\mu\text{m}$, $t_{\text{metal}} = 0.53\mu\text{m}$
 - see “Capacity Limits and Matching Properties of Integrated Capacitors”, Aparicio et. al., JSSC, Mar 2002

Spiral Inductors

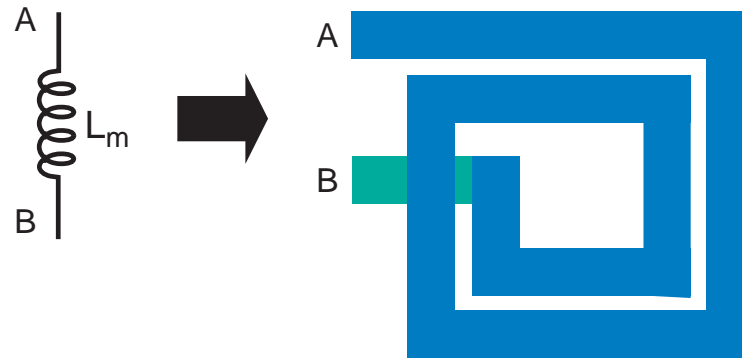
- Create integrated inductor using spiral shape on top level metals (may also want a patterned ground shield)



- Key parameters are Q (< 10), L (1-10 nH), self resonant freq.
- Usually implemented in top metal layers to minimize series resistance, coupling to substrate
- Design using Mohan et. al, "Simple, Accurate Expressions for Planar Spiral Inductances, JSSC, Oct, 1999, pp 1419-1424
- Verify inductor parameters (L , Q , etc.) using ASITIC
<http://formosa.eecs.berkeley.edu/~niknejad/asitic.html>

Bondwire Inductors


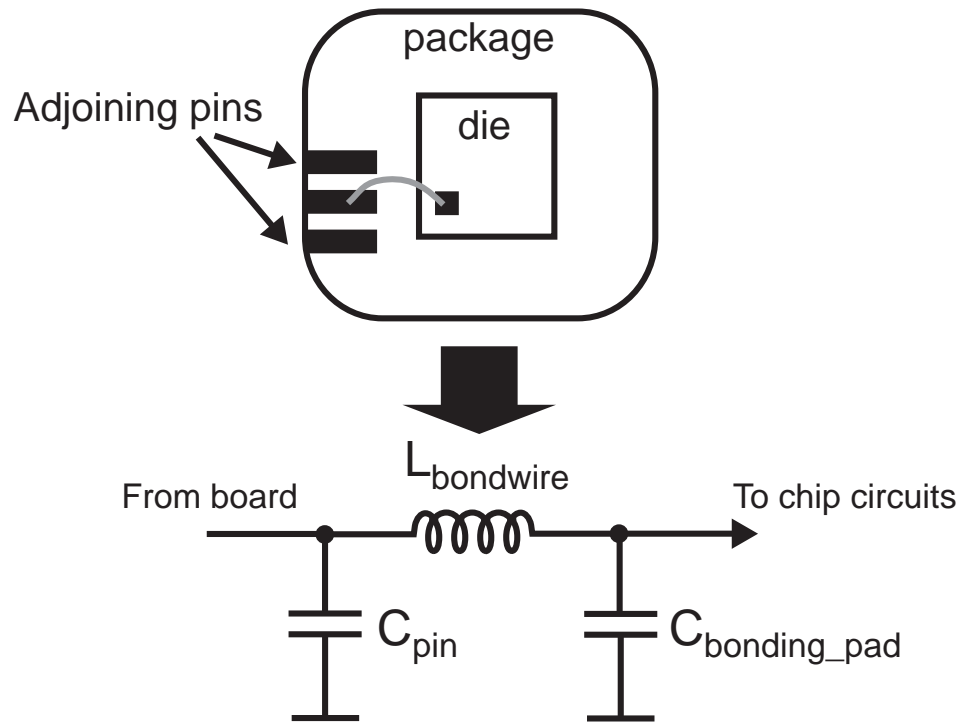
- Used to bond from the package to die
 - Can be used to advantage



- Key parameters
 - Inductance (≈ 1 nH/mm – usually achieve 1-5 nH)
 - Q (much higher than spiral inductors – typically > 40)

Integrated Transformers

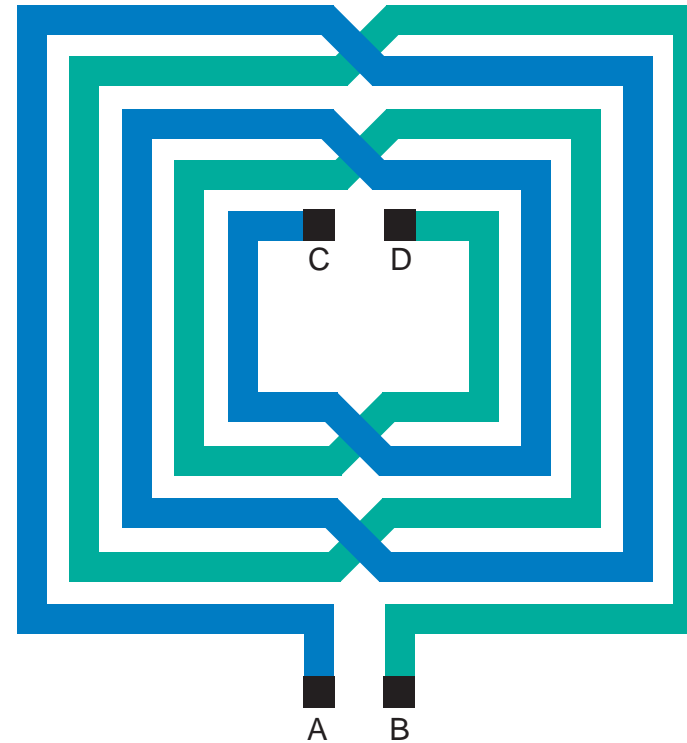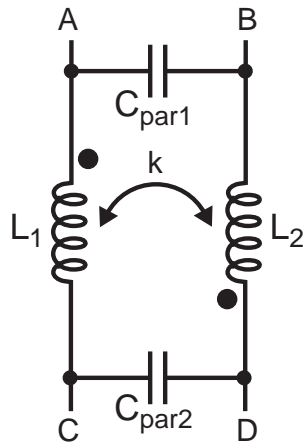- Utilize magnetic coupling between adjoining wires



- Key parameters


- L (self inductance for primary and secondary windings)
- k (coupling coefficient between primary and secondary)

Note: $k = \frac{M}{\sqrt{L_1 L_2}}$ where $M =$ mutual inductance

- Design – ASITIC, other CAD packages

High Speed Transformer Example – A T-Coil Network

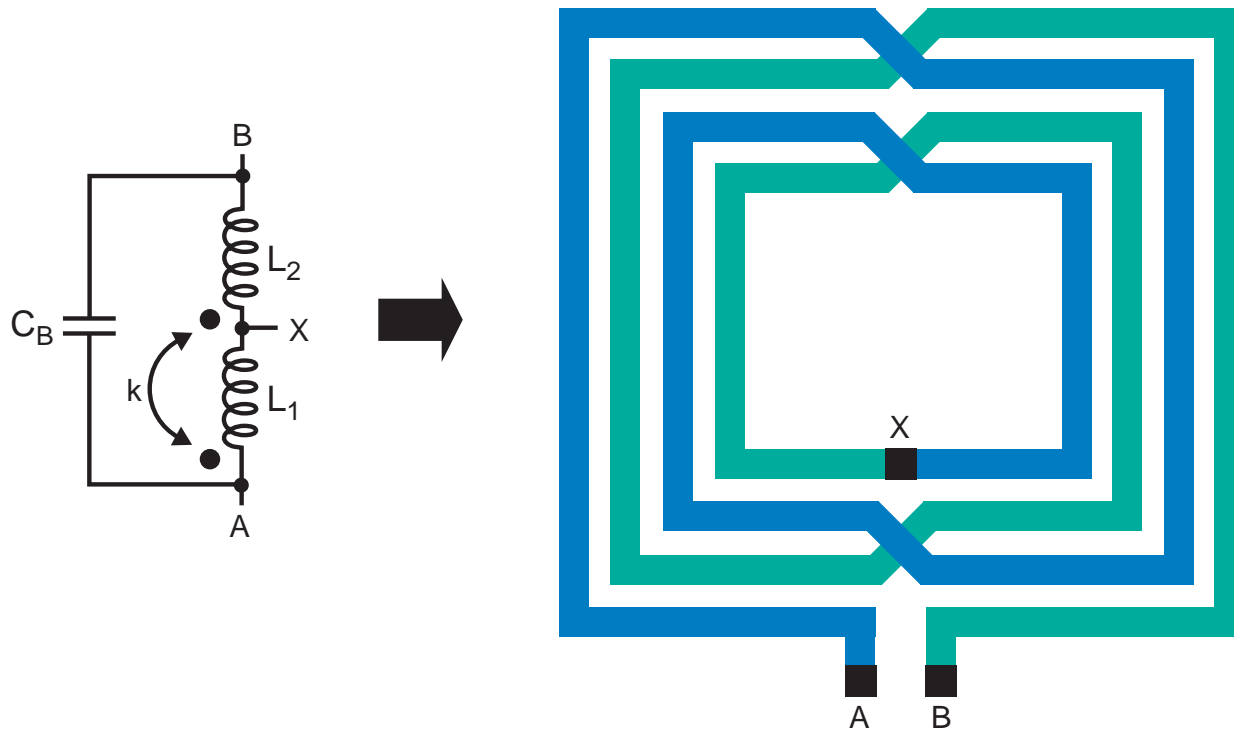- A T-coil consists of a center-tapped inductor with mutual coupling between each inductor half



- Used for bandwidth enhancement
 - See S. Galal, B. Ravazi, “10 Gb/s Limiting Amplifier and Laser/Modulator Driver in 0.18u CMOS”, ISSCC 2003, pp 188-189 and “Broadband ESD Protection ...”, pp. 182-183