

***Short Course On
Phase-Locked Loops and Their Applications
Day 4, AM Lecture***

Digital Frequency Synthesizers

Michael Perrott

August 14, 2008

Copyright © 2008 by Michael H. Perrott


All rights reserved.

Why Are Digital Phase-Locked Loops Interesting?

- PLLs are needed for a wide range of applications
 - Communication systems (both wireless and wireline)
 - Digital processors (to achieve GHz clocks)
- Performance is important
 - Phase noise can limit wireless transceiver performance
 - Jitter can be a problem for digital processors
- The standard analog PLL implementation is problematic in many applications
 - Analog building blocks on a mostly digital chip pose design and verification challenges
 - The cost of implementation is becoming too high ...

Can digital phase-locked loops offer excellent performance with a lower cost of implementation?


Integer-N Frequency Synthesizers

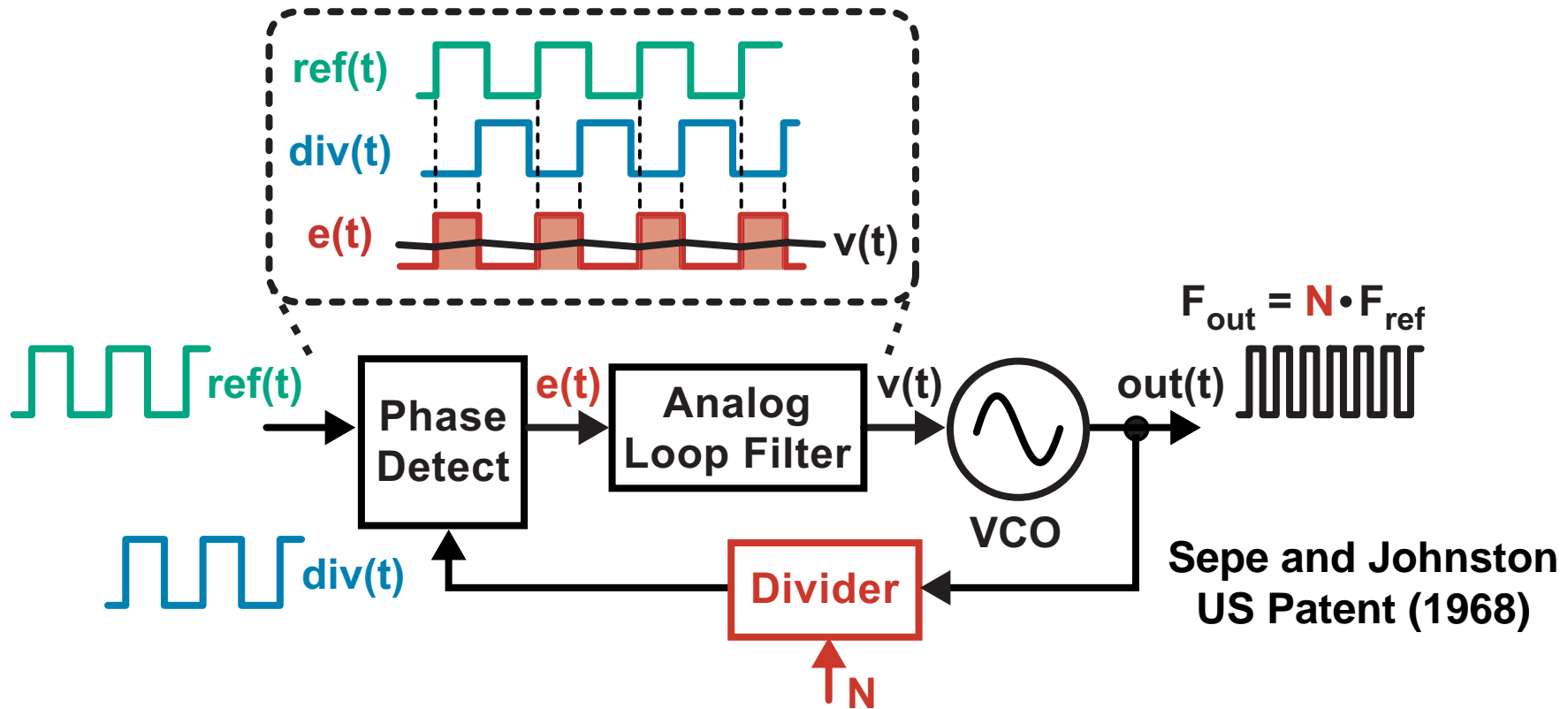

- Use digital counter structure to divide VCO frequency
 - Constraint: must divide by integer values
- Use PLL to synchronize reference and divider output

Output frequency is digitally controlled


Fractional-N Frequency Synthesizers

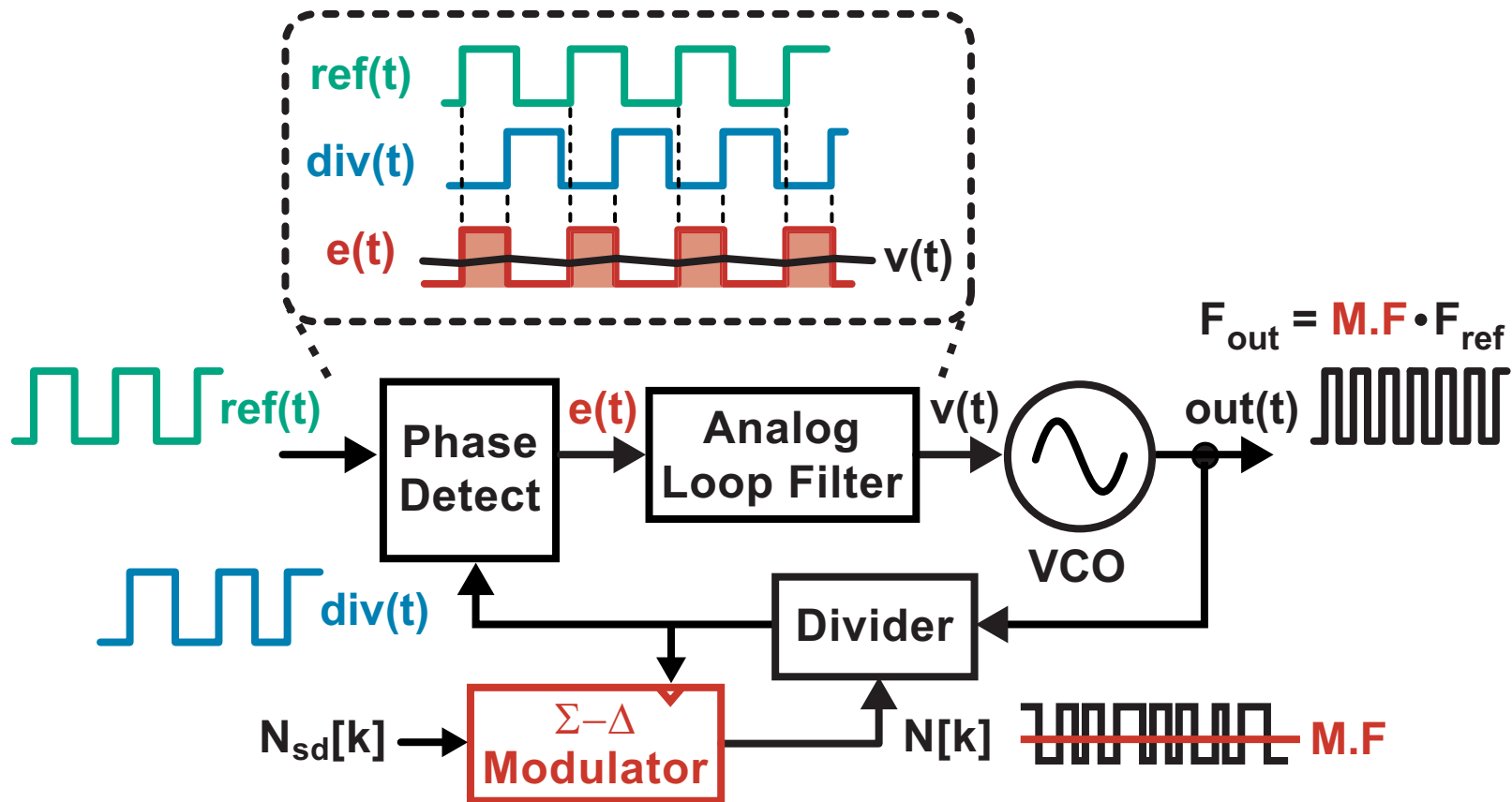


- Dither divide value to achieve fractional divide values
 - PLL loop filter smooths the resulting variations

Very high frequency resolution is achieved

The Issue of Quantization Noise


 


 - Limits PLL bandwidth
- Increases linearity requirements of phase detector




Striving for a Better PLL Implementation

Analog Phase Detection

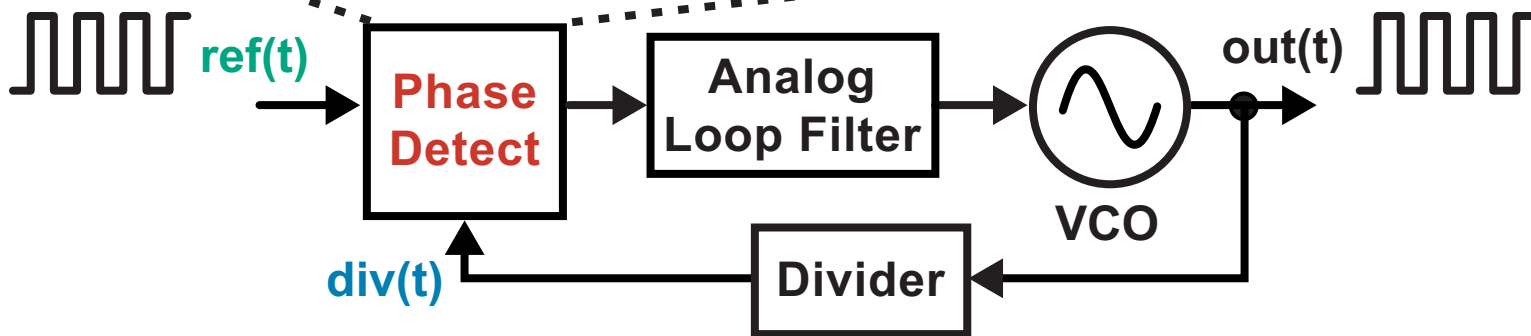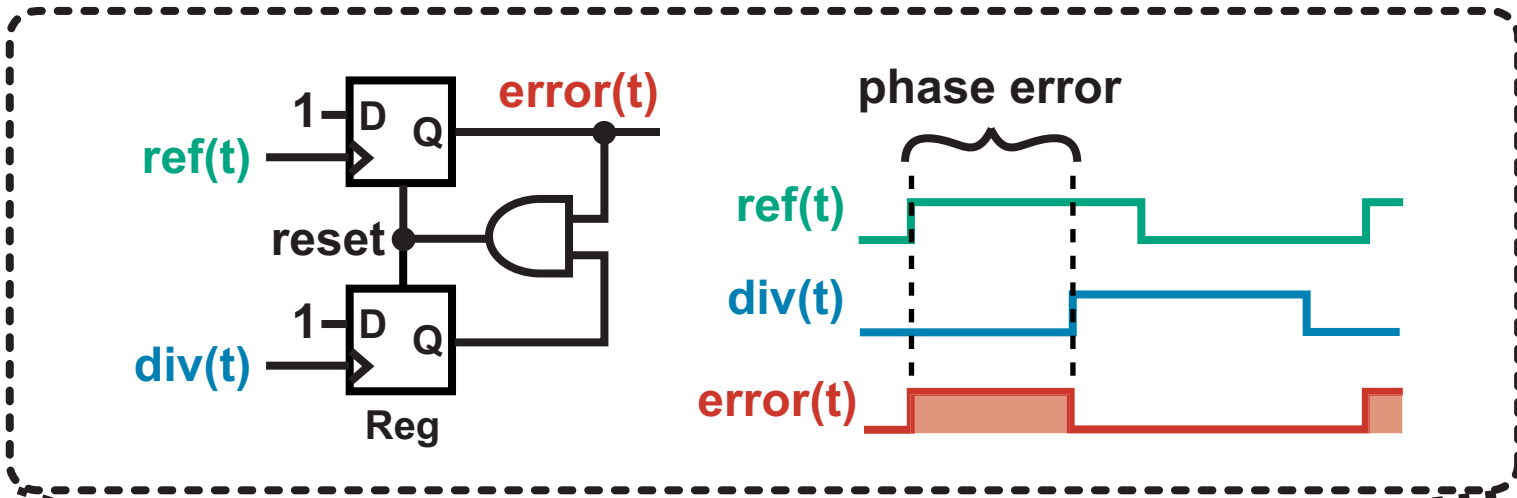


- Pulse width is formed according to phase difference between two signals
- Average of pulsed waveform is applied to VCO input

Tradeoffs of Analog Approach

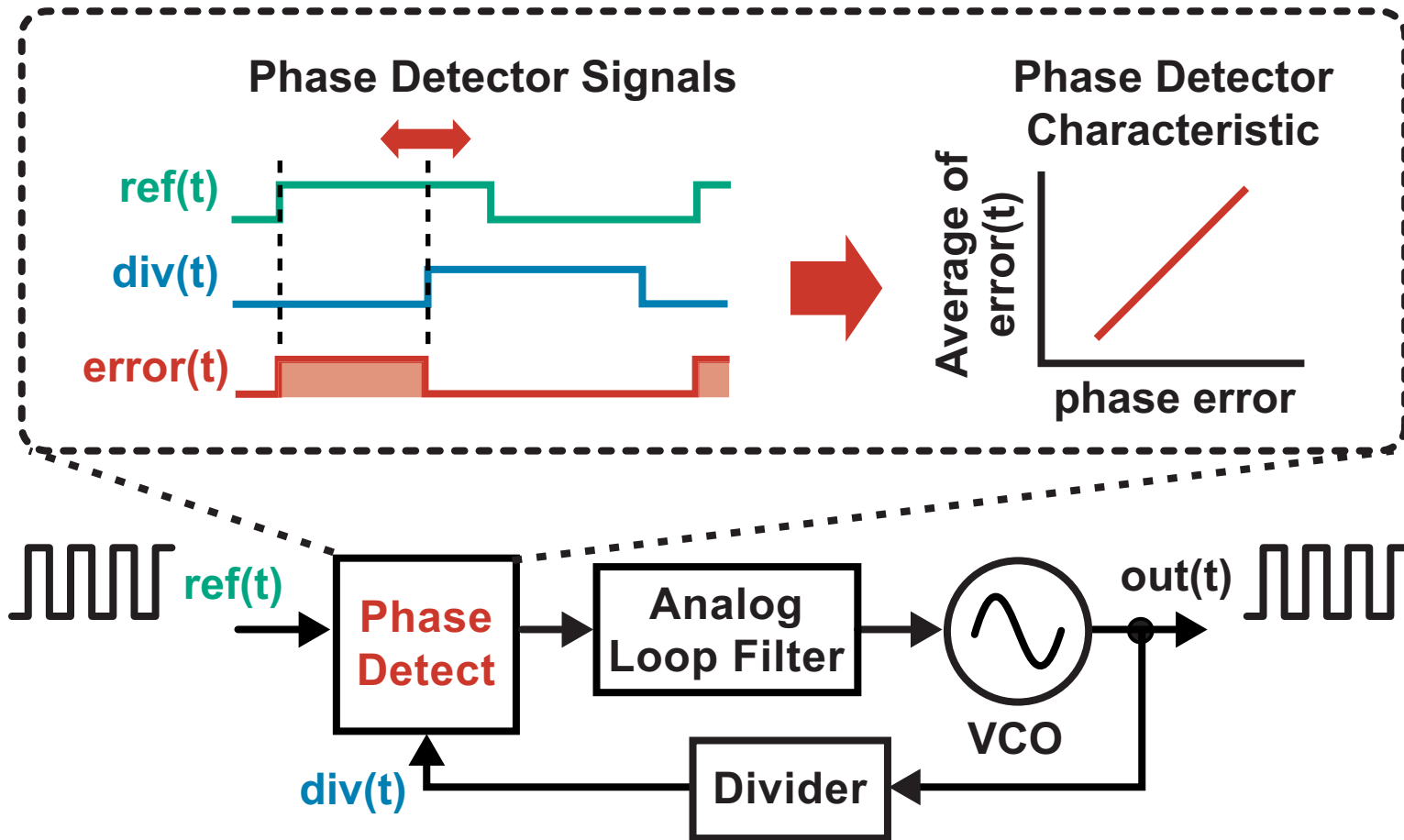



- **Benefit:** average of pulsed output is a continuous, linear function of phase error
- **Issue:** analog loop filter implementation is undesirable

Issues with Analog Loop Filter

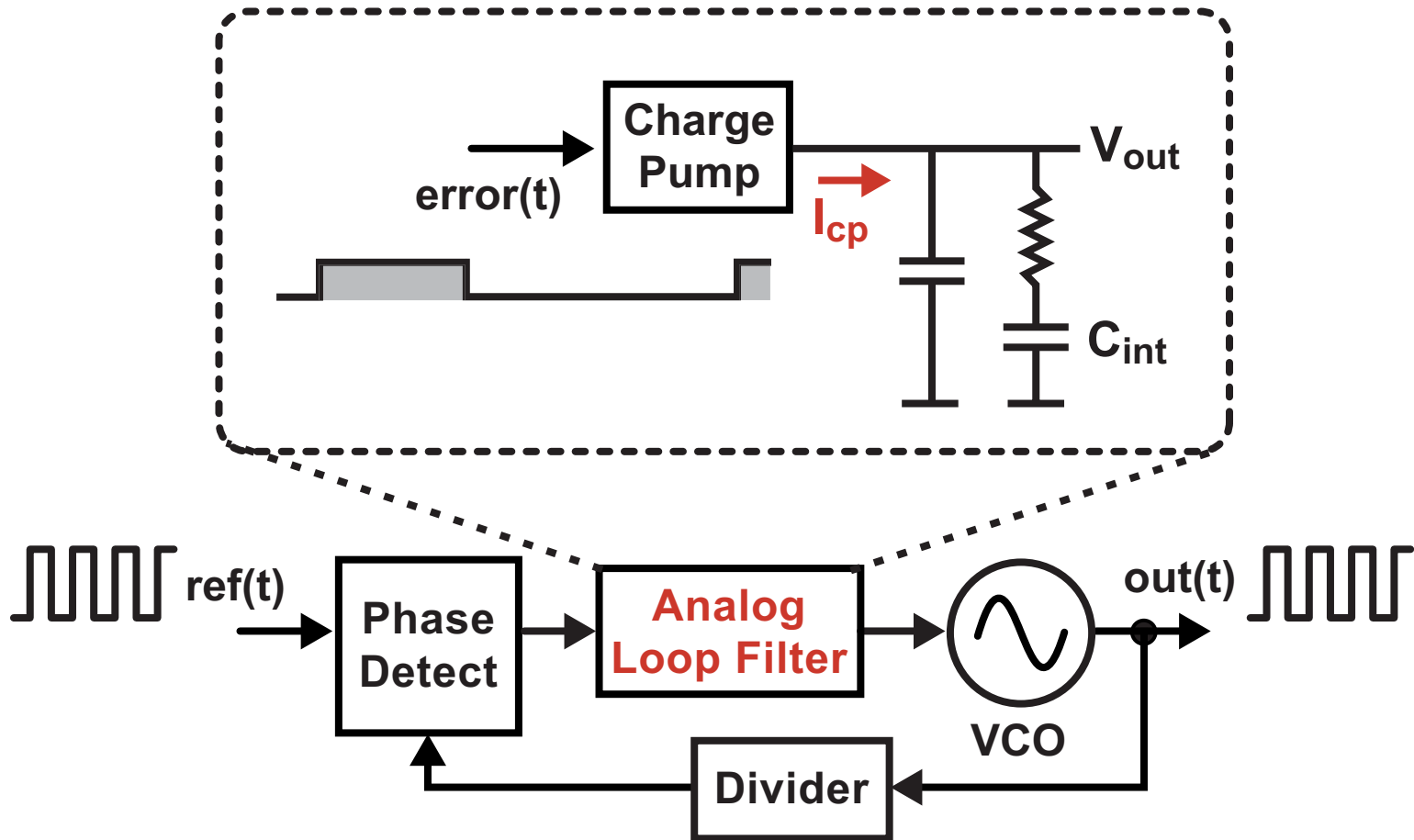

- Charge pump: output resistance, mismatch
- Filter caps: leakage current, *large area*

Going Digital ...

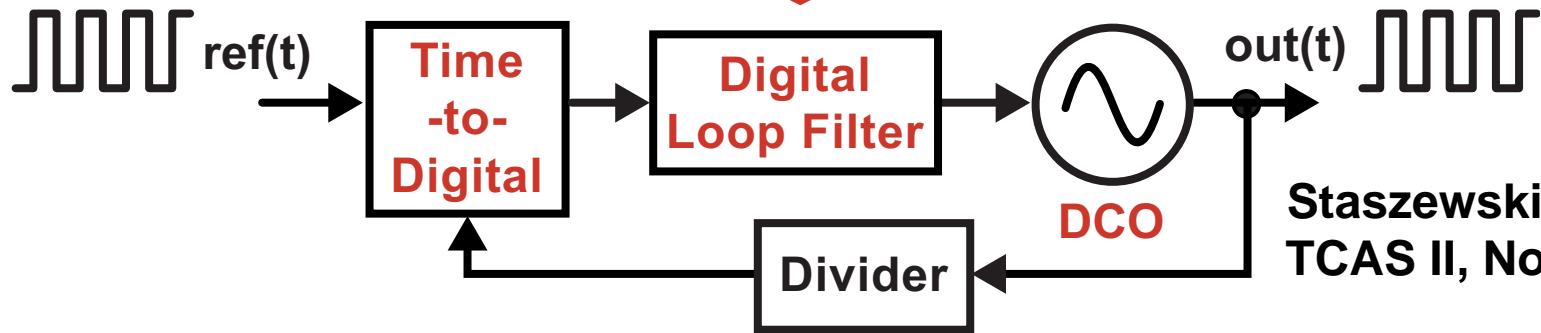
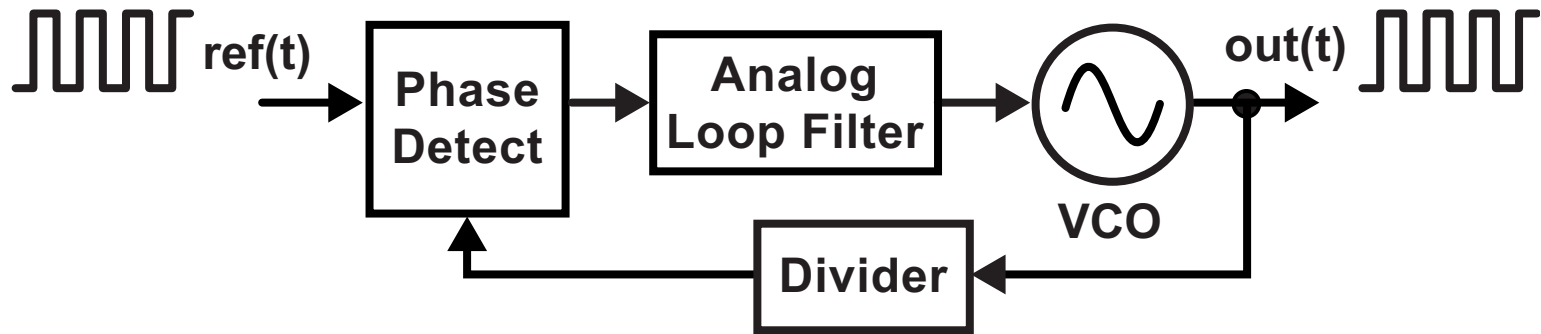


Staszewski et. al.,
TCAS II, Nov 2003

- **Digital loop filter: compact area, insensitive to leakage**
- **Challenges:**
 - **Time-to-Digital Converter (TDC)**
 - **Digitally-Controlled Oscillator (DCO)**



Time-to-Digital Conversion

Classical Time-to-Digital Converter

 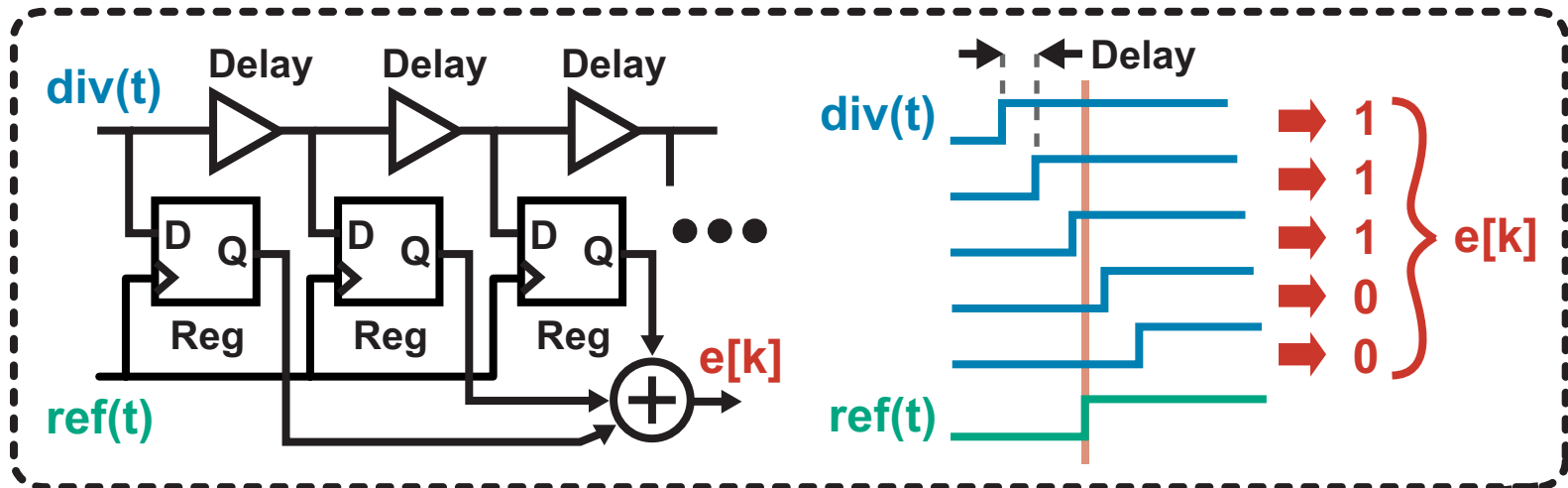



- Resolution set by a “Single Delay Chain” structure
 - Phase error is measured with delays and registers
- Corresponds to a flash architecture

 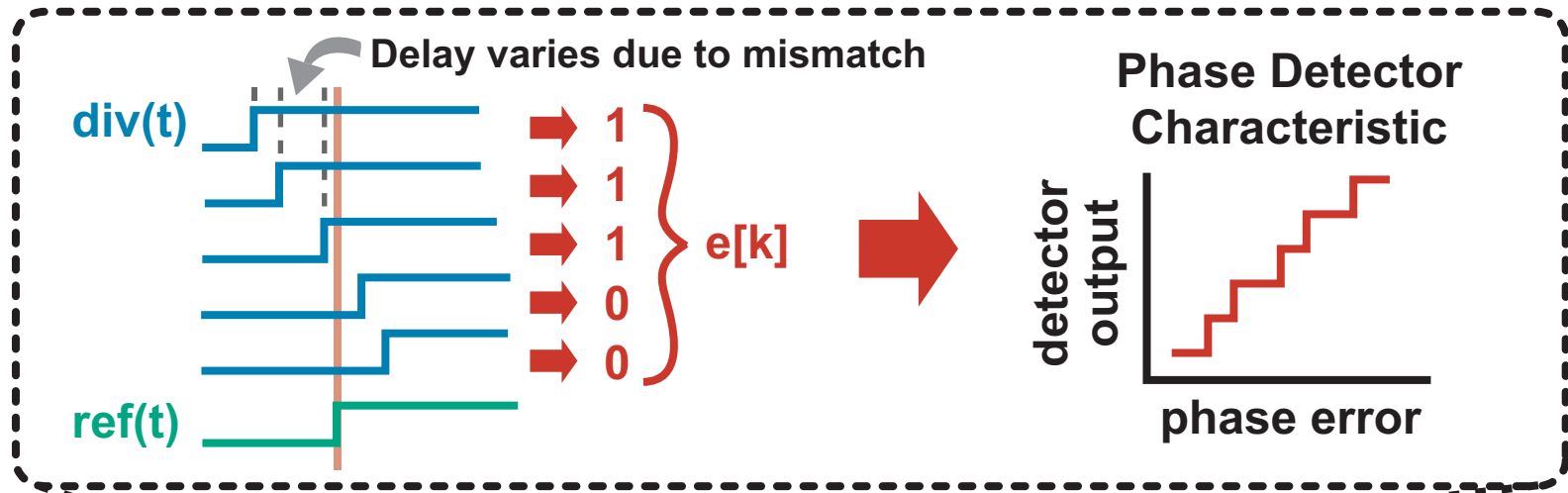Impact of Limited Resolution and Delay Mismatch



- Integer-N PLL
 - Limit cycles due to limited resolution (unless high ref noise)
- Fractional-N PLL
 - Fractional spurs due to non-linearity from delay mismatch

Modeling of TDC

 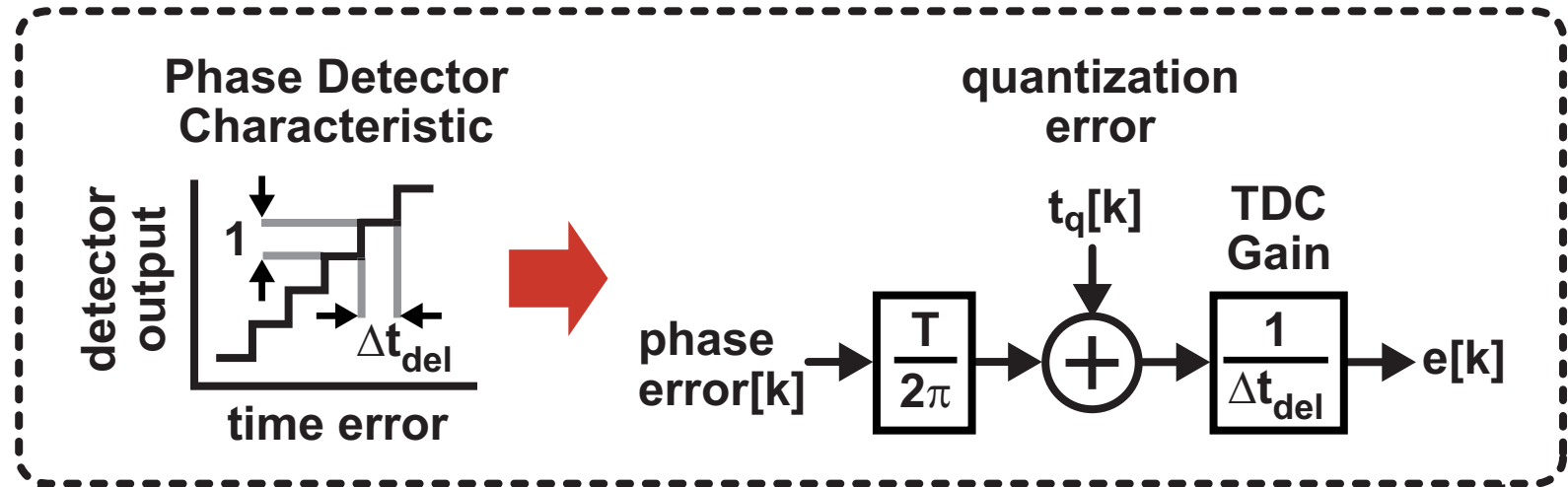





- Phase error converted to time error by scale factor: $T/2\pi$
- TDC introduces quantization error: $t_q[k]$
- TDC gain set by average delay per step: Δt_{del}

How Do We Improve Performance?

Two Key Issues:

- **TDC resolution**
- **Mismatch**

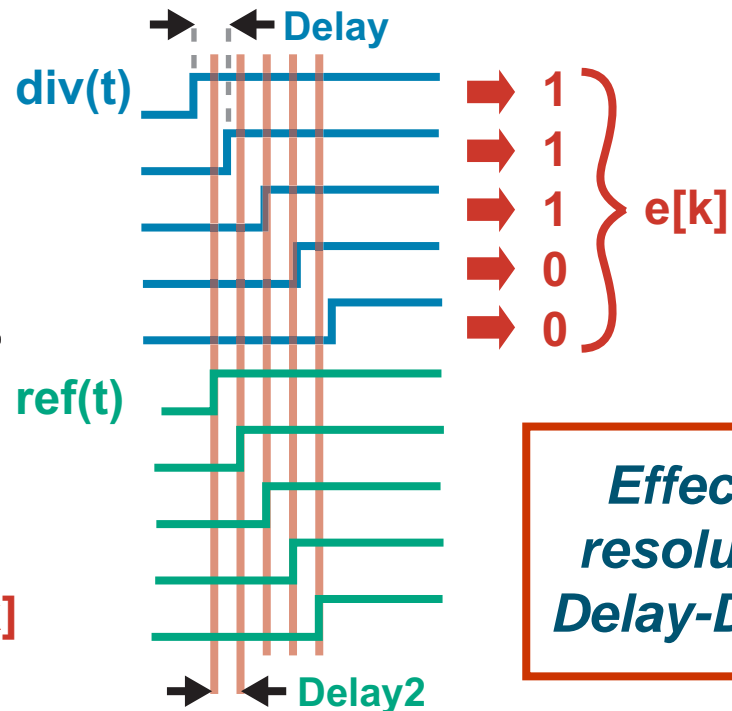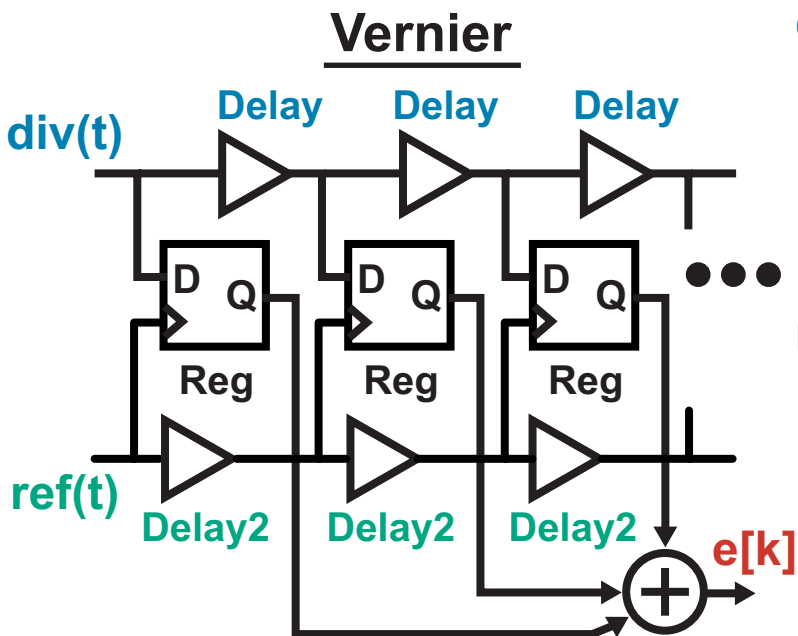 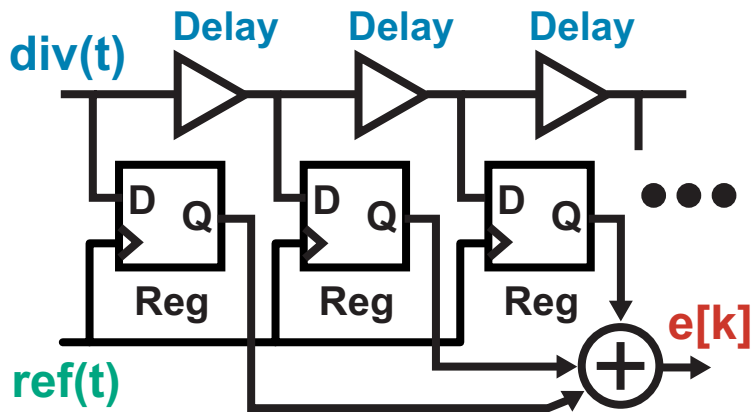
Improve Resolution with Vernier Delay Technique




**Effective resolution:
Delay-Delay2**

Issues with Vernier Approach

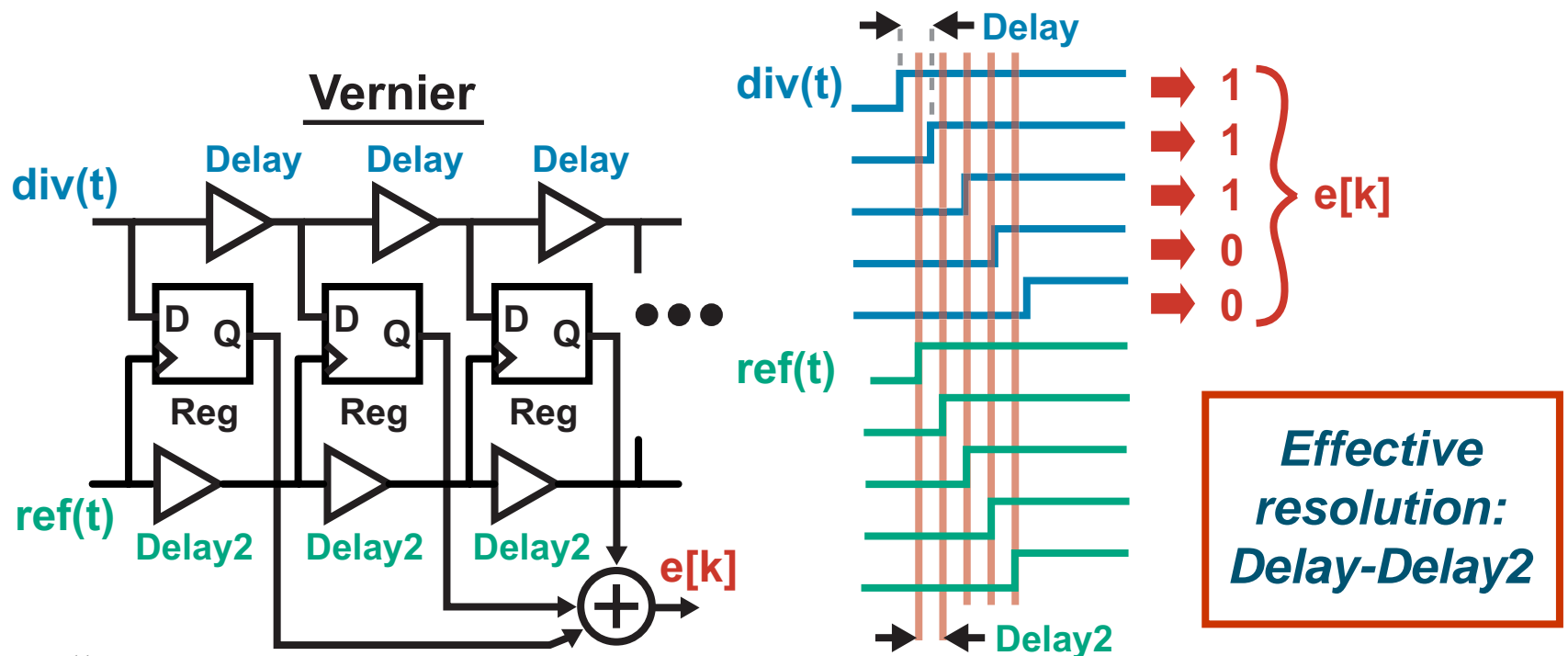- Mismatch issues are more severe than the single delay chain TDC
 - Reduced delay is formed as *difference* of two delays
- Large measurement range requires large area
 - Initial PLL frequency acquisition may require a large range




 Two-Step TDC Architecture Allows Area Reduction




Ramakrishnan, Balsara
VLSID '06

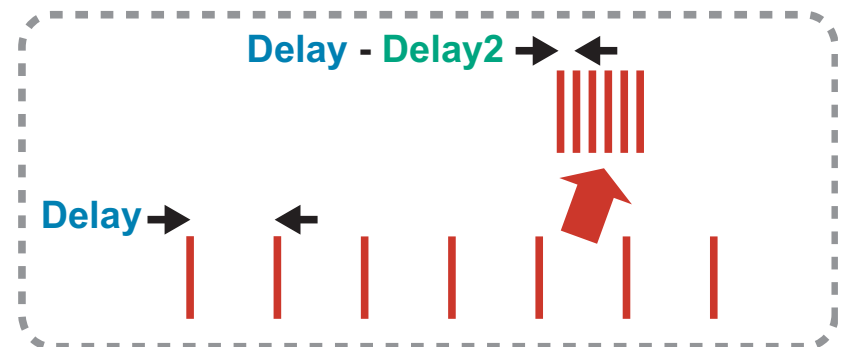- Single delay chain provides coarse resolution
- (Folded) Vernier provides fine resolution




Two-Step TDC Using Time Amplification

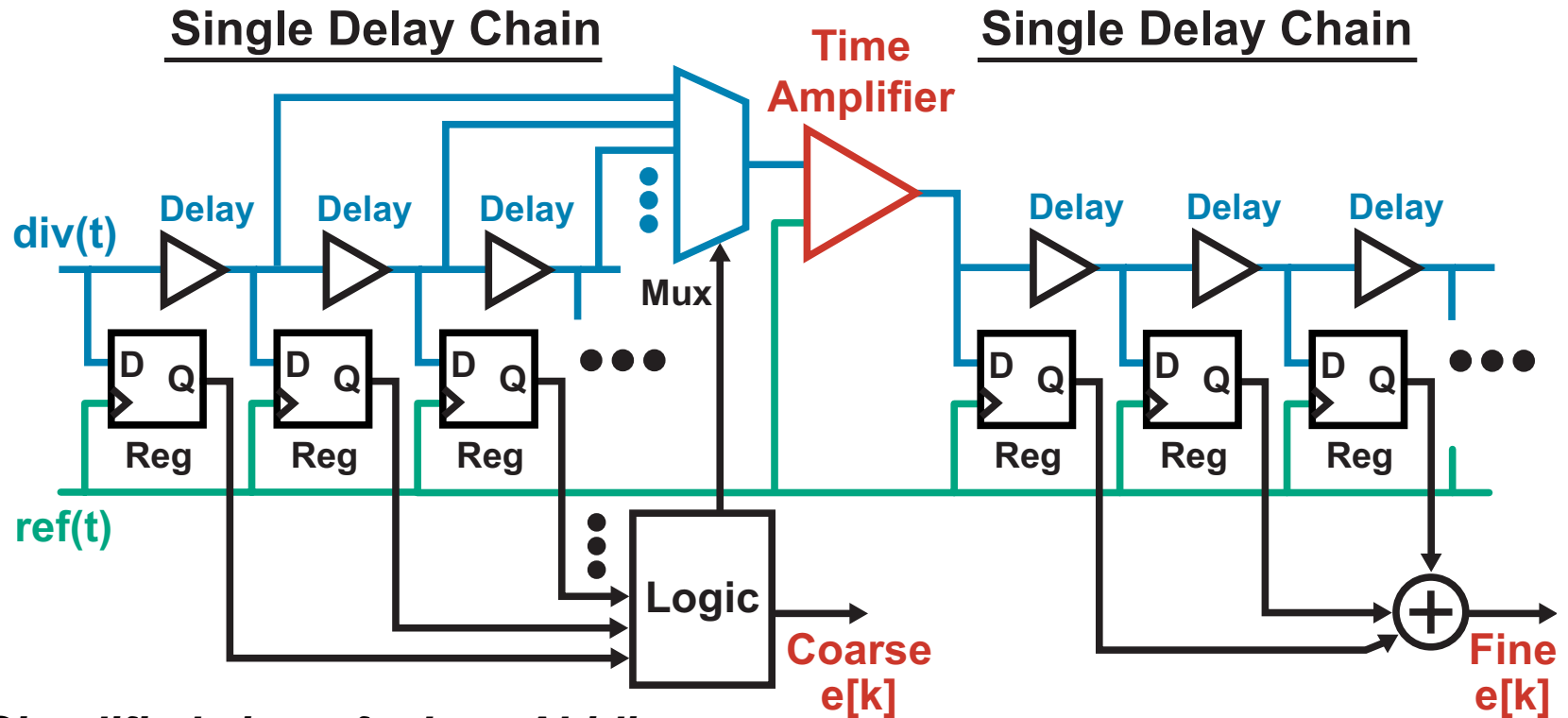


Simplified view of: Lee, Abidi
VLSI 2007

 - Single delay chain provides coarse and fine resolution
- Time amplification is used to improve resolution



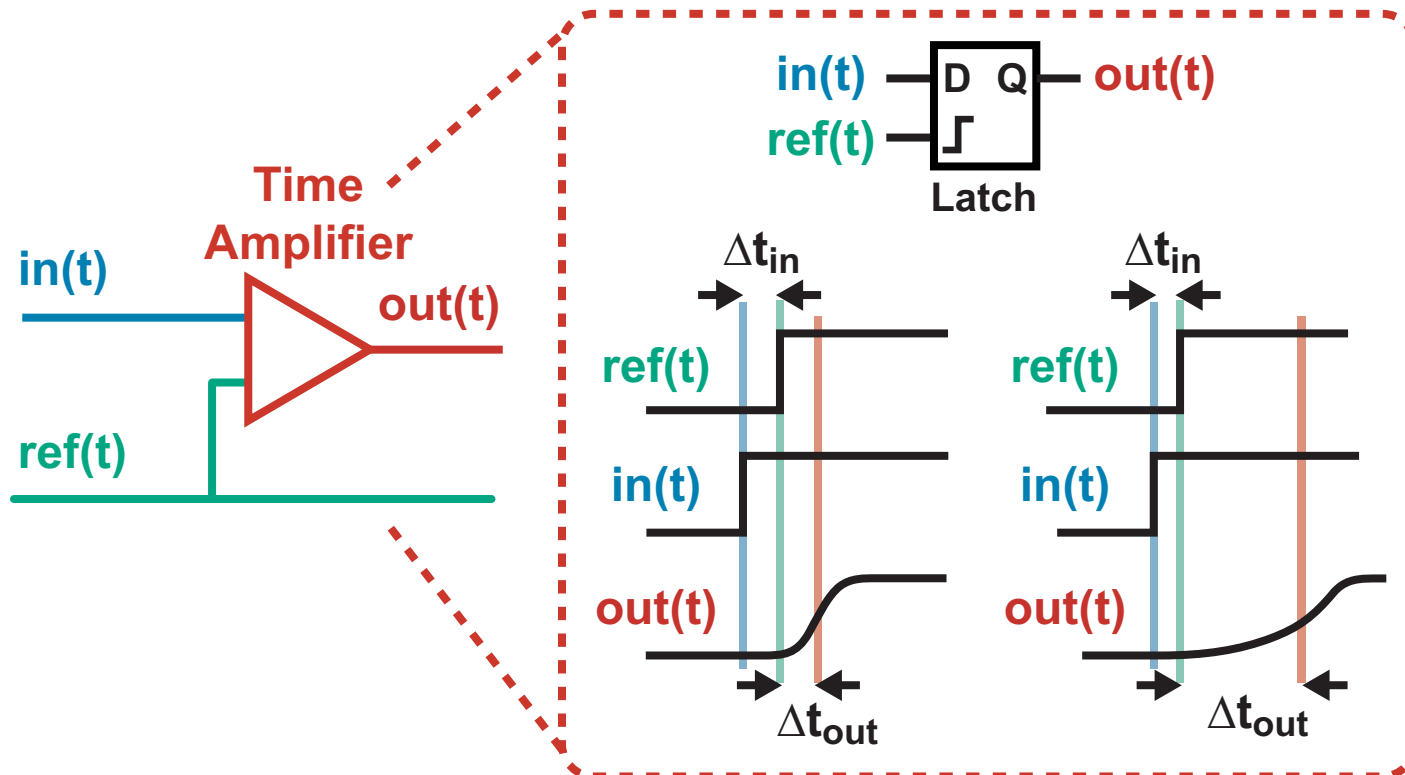
Leveraging Metastability to Create a Time Amplifier



*Simplified view of: Abas, et al., Electronic Letters, Nov 2002
(note that actual implementation uses SR latch)*


- **Metastability leads to progressively slower output transitions as setup time on latch is encroached upon**
 - Time difference at input is amplified at output

Interpolating time-to-digital converter

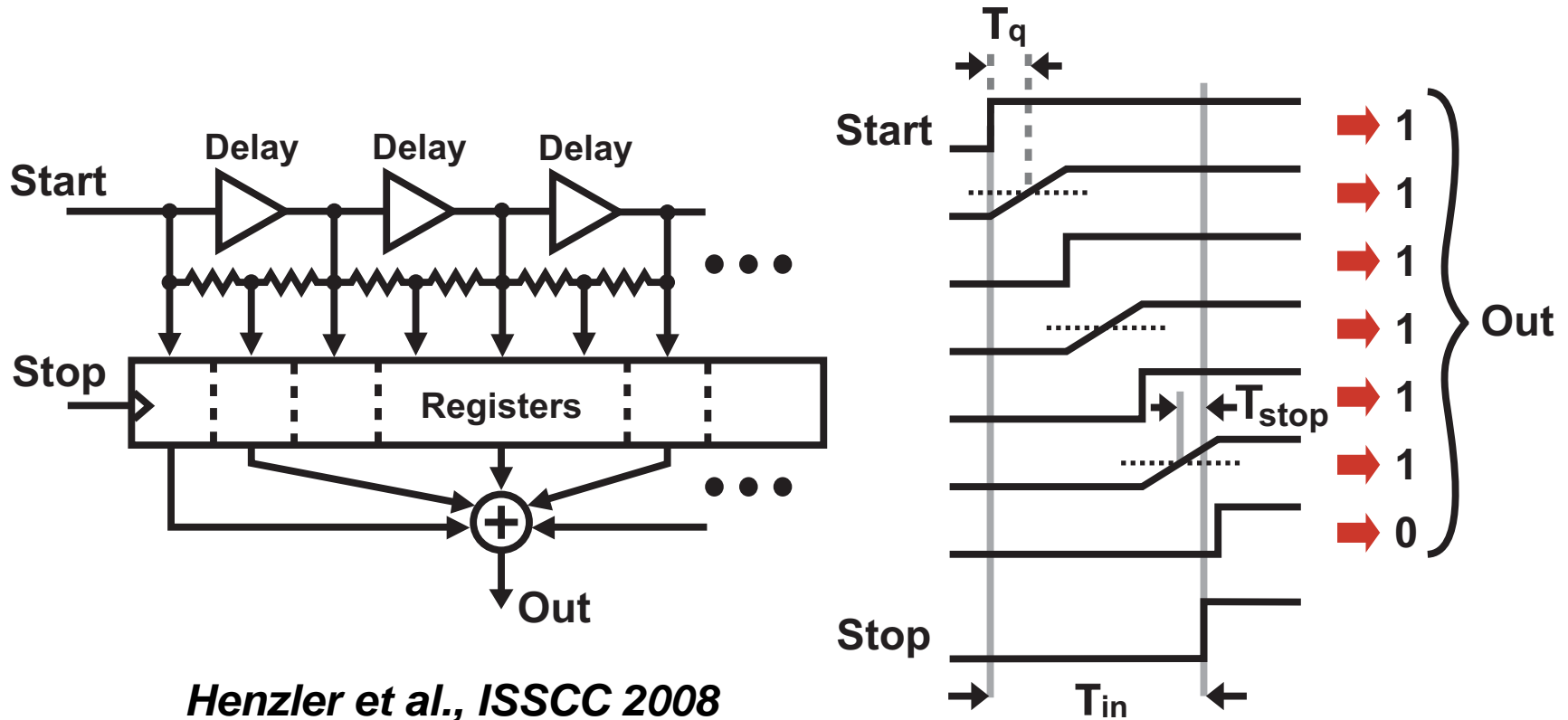


- Interpolate between edges to achieve fine resolution
- Cyclic approach can also be used for large range

An Oscillator-Based TDC

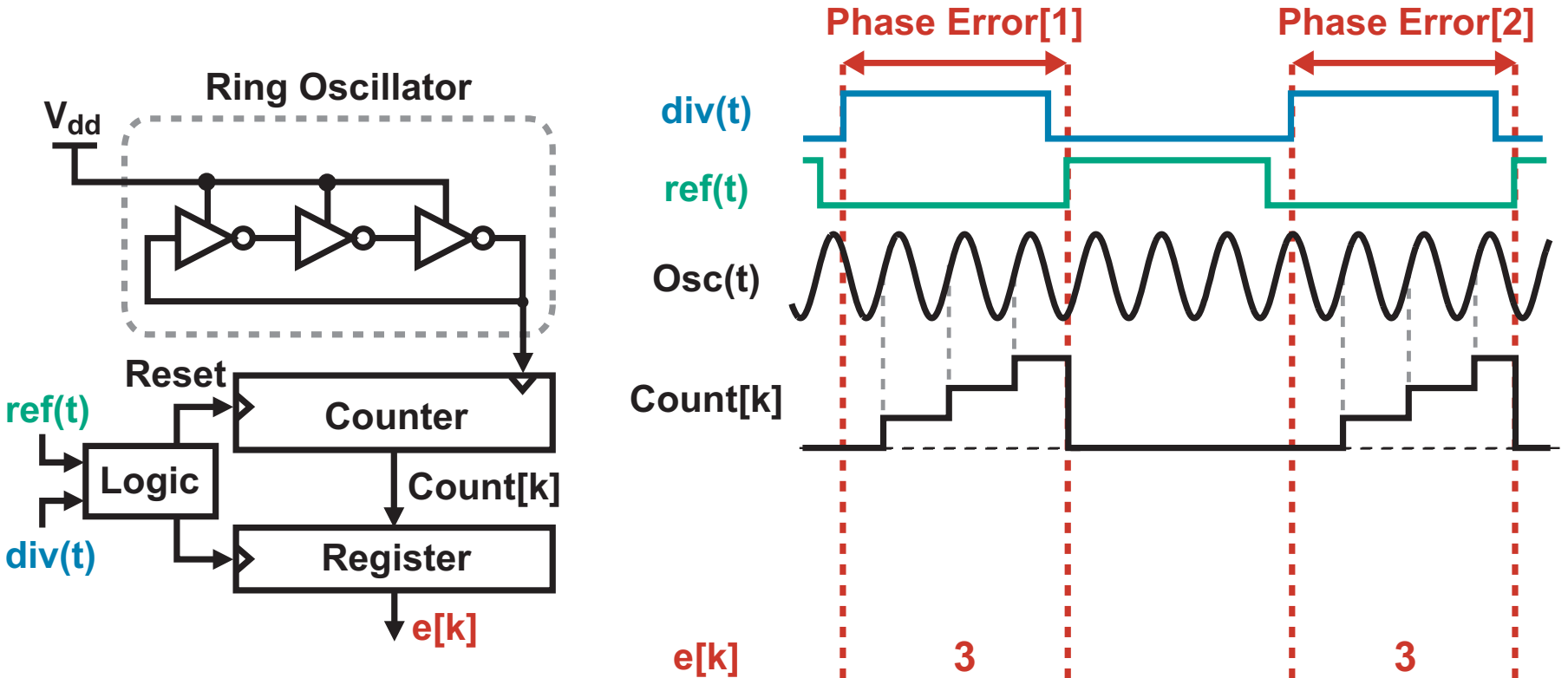


- Output $e[k]$ corresponds to the number of oscillator edges that occur during the measurement time window
- Advantages
 - Extremely large range can be achieved with compact area
 - Quantization noise is scrambled across measurements

 A Closer Look at Quantization Noise Scrambling



- Quantization error occurs at beginning and end of each measurement interval
- As a rough approximation, assume error is uncorrelated between measurements
- Averaging of measurements improves effective resolution

 
Deterministic quantizer error vs. scrambled error



- **Deterministic TDC do not provide inherent scrambling**
- **For oversampling benefit, *TDC error must be scrambled!***
- **Some systems provide input scrambling ($\Delta\Sigma$ fractional-N PLL), while some others do not (integer-N PLL)**


Proposed GRO TDC Structure

A Gated Ring Oscillator (GRO) TDC

 

- Enable ring oscillator only during measurement intervals
 - Hold the state of the oscillator between measurements
- Quantization error becomes first order noise shaped!
 - $e[k] = \text{Phase Error}[k] + q[k] - q[k-1]$
 - Averaging dramatically improves resolution!

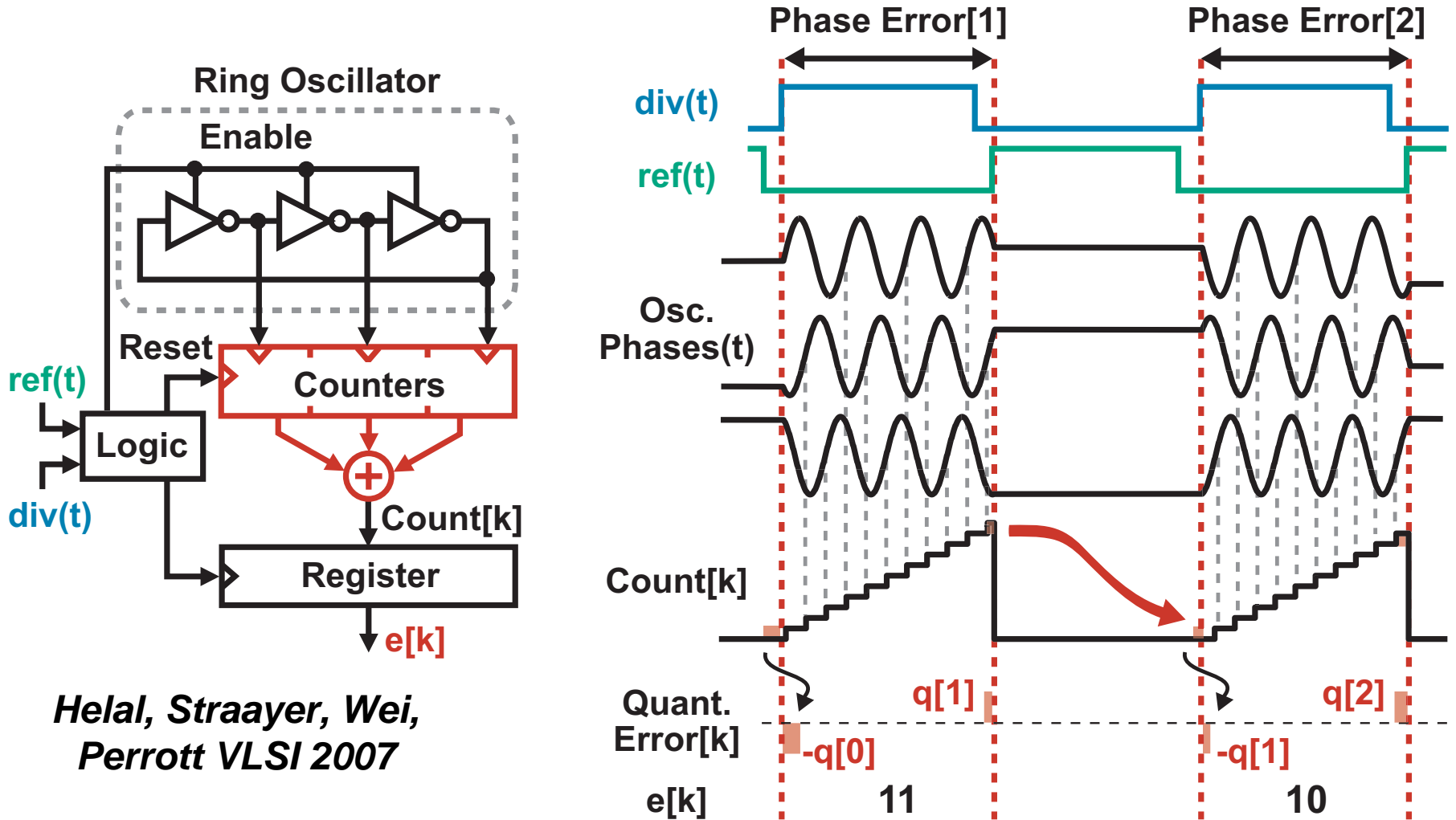
Improve Resolution By Using All Oscillator Phases




Helal, Straayer, Wei,
Perrott VLSI 2007

- Raw resolution is set by inverter delay
- Effective resolution is dramatically improved by averaging

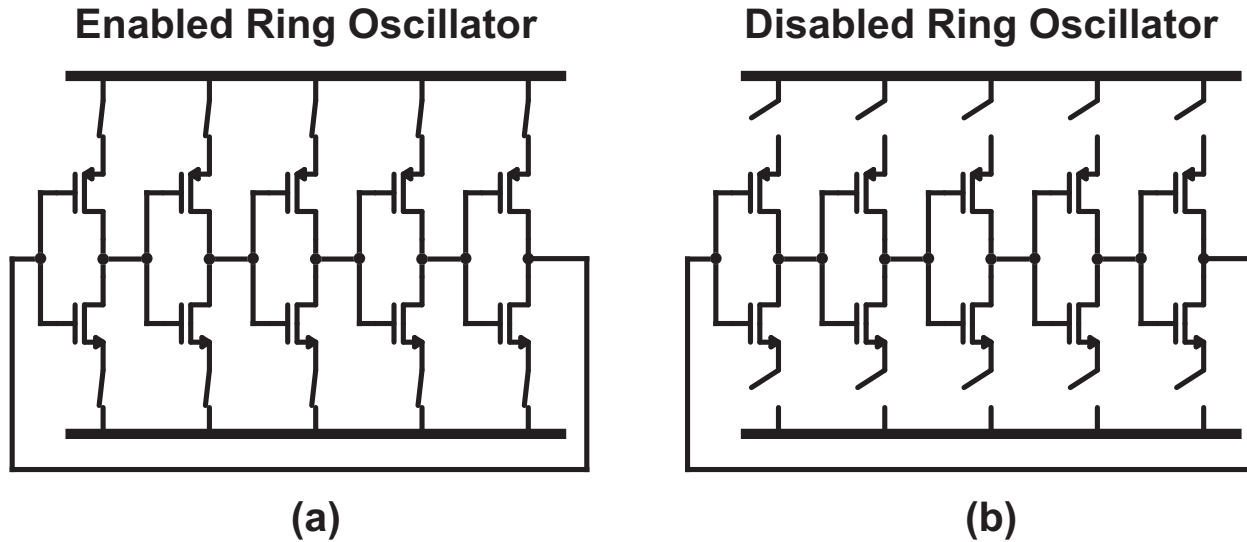
Simple gated ring oscillator inverter-based core



 
Gate the oscillator by switching the inverter cores to the power supply






GRO Prototype

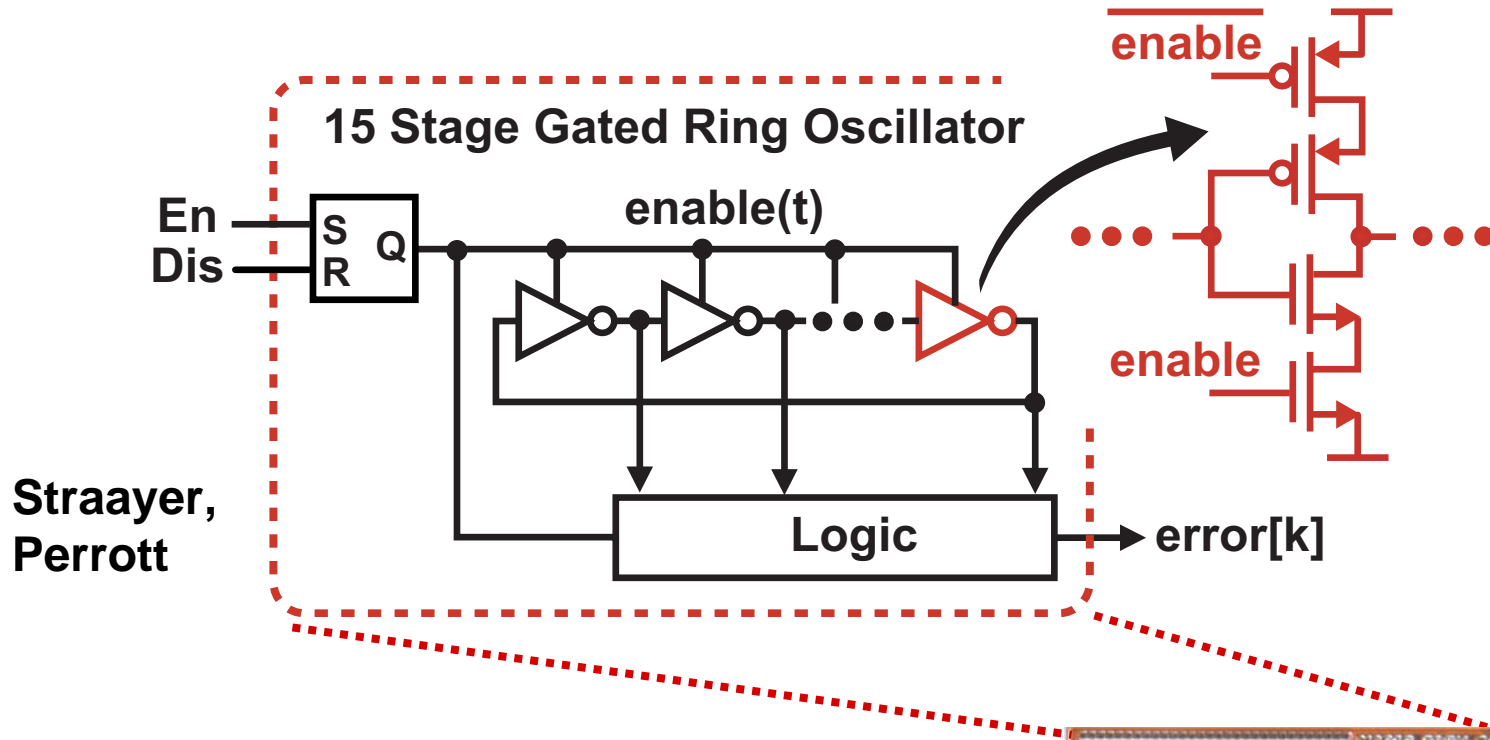

 
- GRO implemented as a custom 0.13 μm CMOS IC



  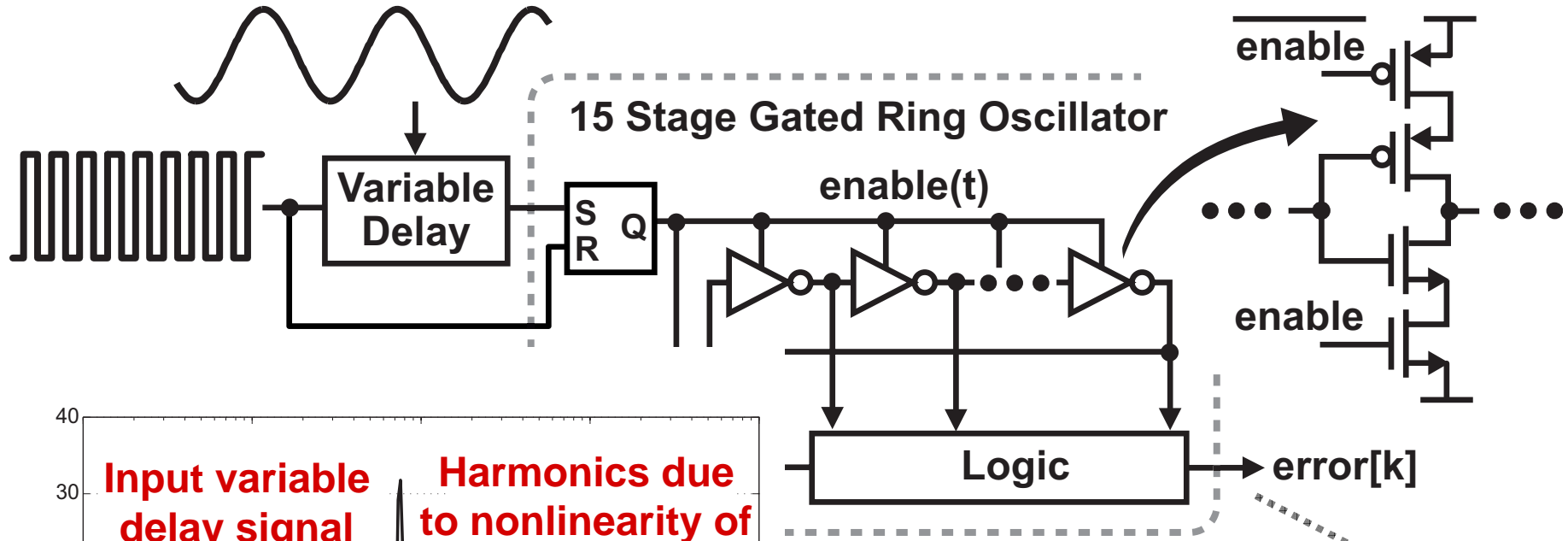
Measured GRO Results Confirm Noise Shaping



 Measured deadzone behavior of inverter-based GRO




(a)

 

(b)


- Deadzones were caused by errors in gating the oscillator
- GRO “injection locked” to an integer ratio of F_s
- Behavior occurred for almost all integer boundaries, and some fractional values as well
- Noise shaping benefit was limited by this gating error

The issue of gating non-idealities...

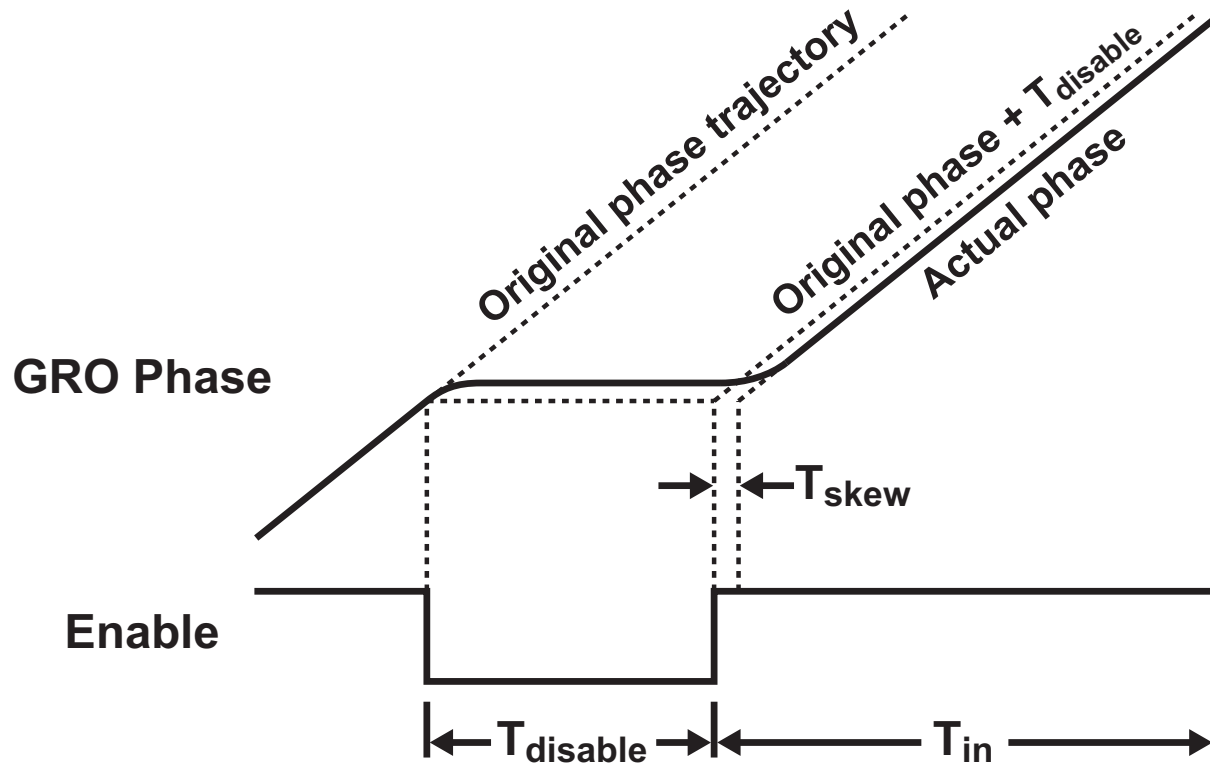


- Oscillator does not stop and start instantly
- Actual phase trajectory deviates from ideal trajectory by a time defined as " T_{skew} "

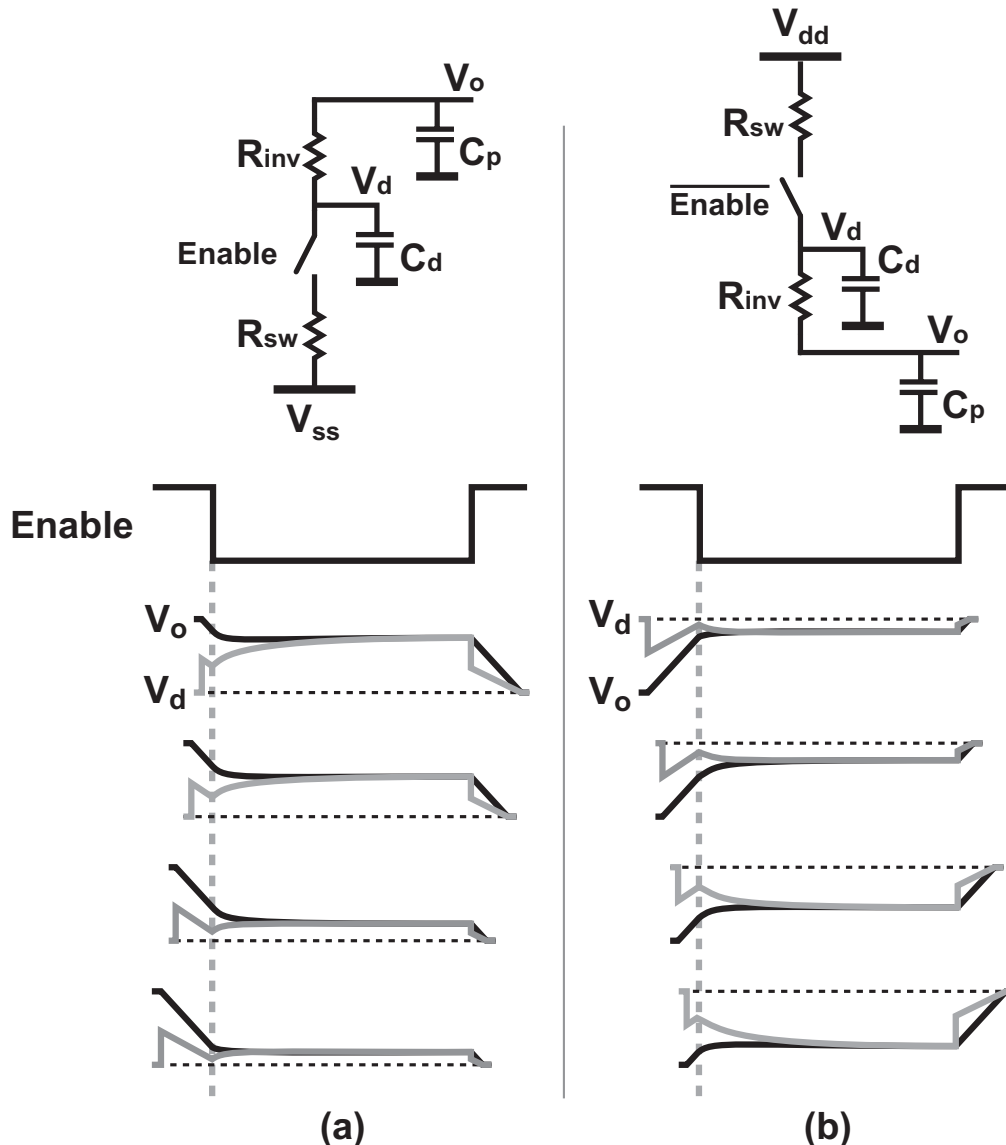Interrupted transition causes charge redistribution



- Charge redistribution depends on when the transition is stopped
- Positive and negative transitions are not perfectly symmetric
- Gating skew (T_{skew}) then depends on GRO phase (θ_{GRO}) when $Enable$ transitions low

 
Cartoon depicting the error from individual stages




- Only one stage in transition at a time
- T_{skew} is the sum of error from each of the individual stages
- Periodic with $2T_q$ due to positive and negative transition asymmetry

Next Generation GRO: Multi-path oscillator concept

Single Input
Single Output

 


Multiple Inputs
Single Output

 


- Use multiple inputs for each delay element instead of one
- Allow each stage to optimally begin its transition based on information from the entire GRO phase state
- Key design issue is to ensure primary mode of oscillation

Multi-path inverter core

 


Lee, Kim, Lee
JSSC 1997

(a) Asymmetrically skewed inverter


 


(b) Multiple skewed inverters

 


(c) Unrestricted connections

Mohan, et. al.,
CICC 2005

  

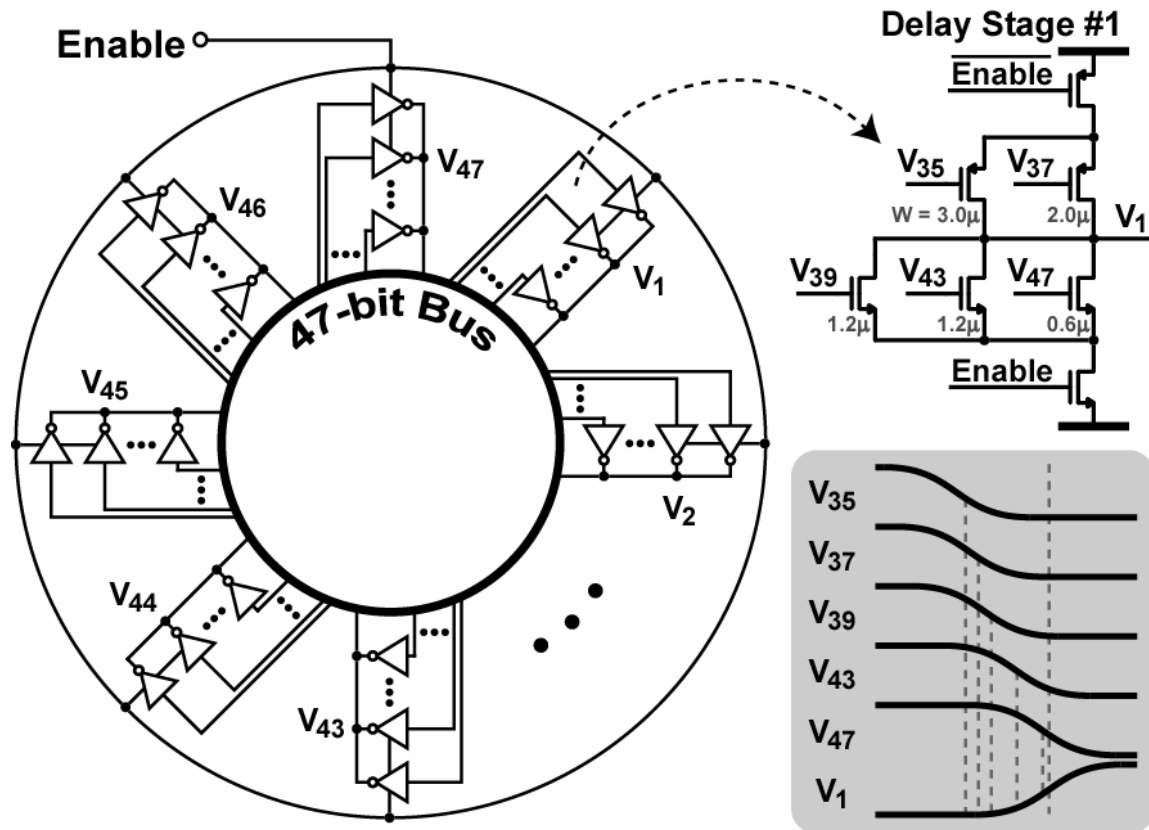
Proposed multi-path gated ring oscillator



Hsu, Straayer, Perrott
ISSCC 2008

- Oscillation frequency near 2GHz with 47 stages...
- Reduces effective delay per stage by a factor of 5-6!
- Represents a factor of 2-3 improvement compared to previous multi-path oscillators


A simple measurement approach...

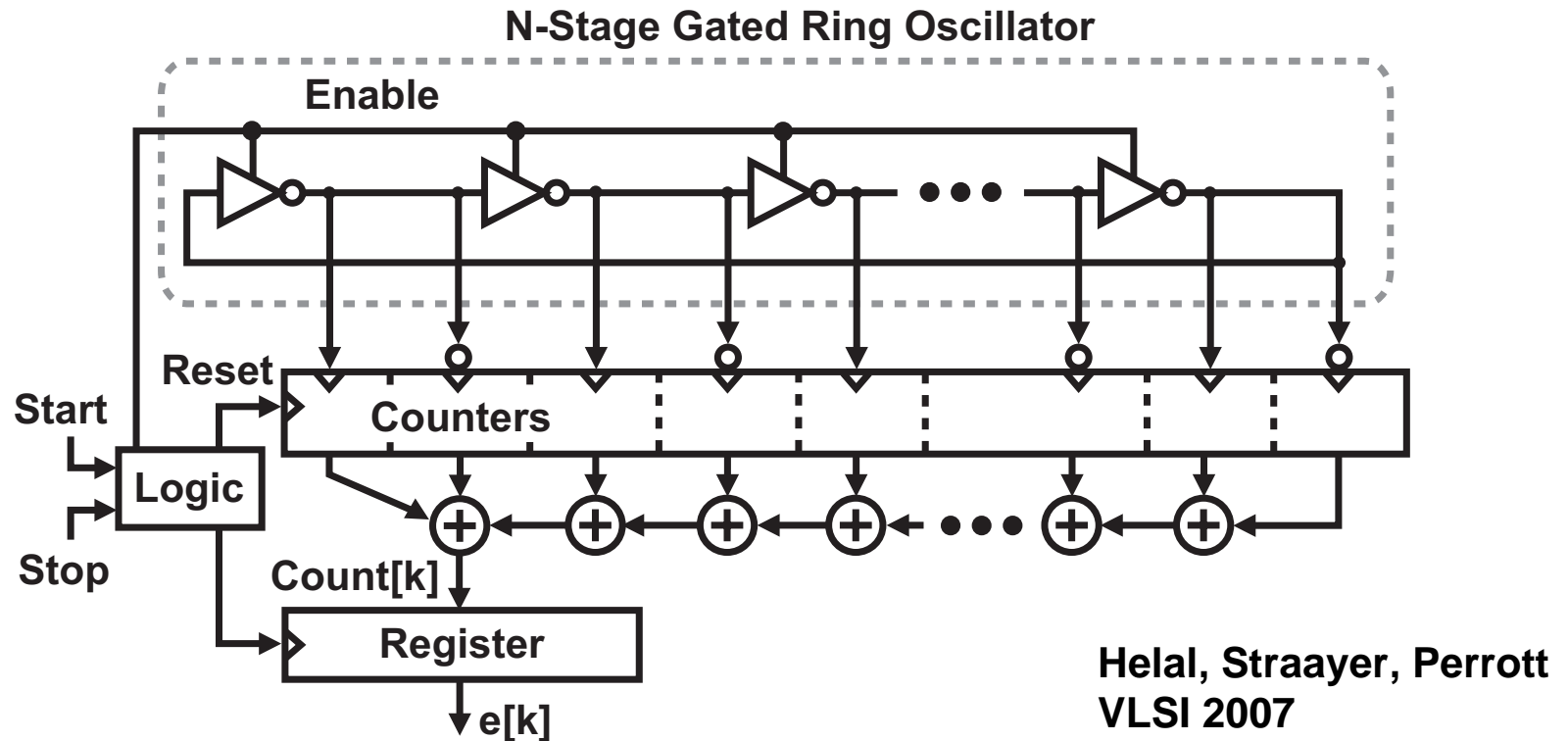


- 2 counters per stage * 47 stages = 94 counters each at 2GHz
- Power consumption for these counters is unreasonable

Need a more efficient way to measure the multi-path GRO



Phase-based measurement for a simple GRO

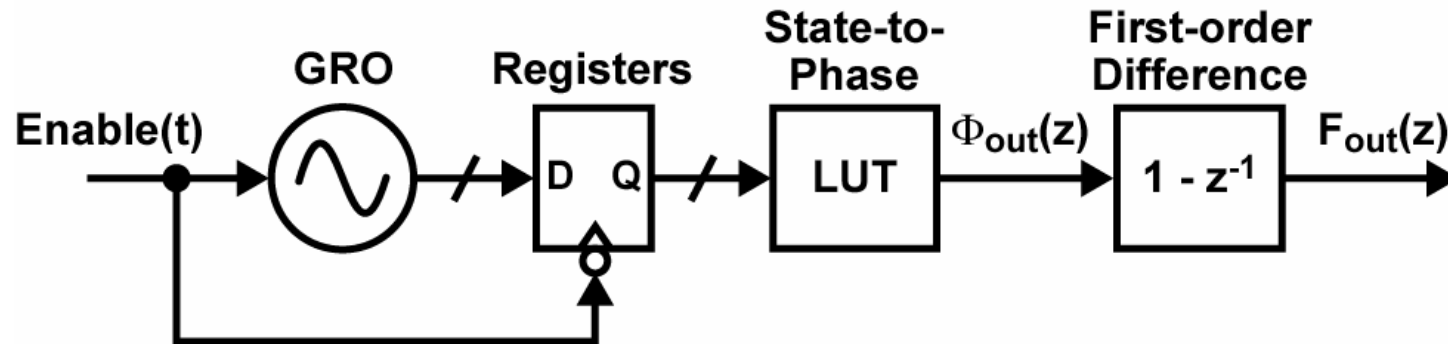

 - Simple logic provides map from GRO output state to phase
- Transition sequence is predictable, unambiguous




Accounting for phase wrapping...

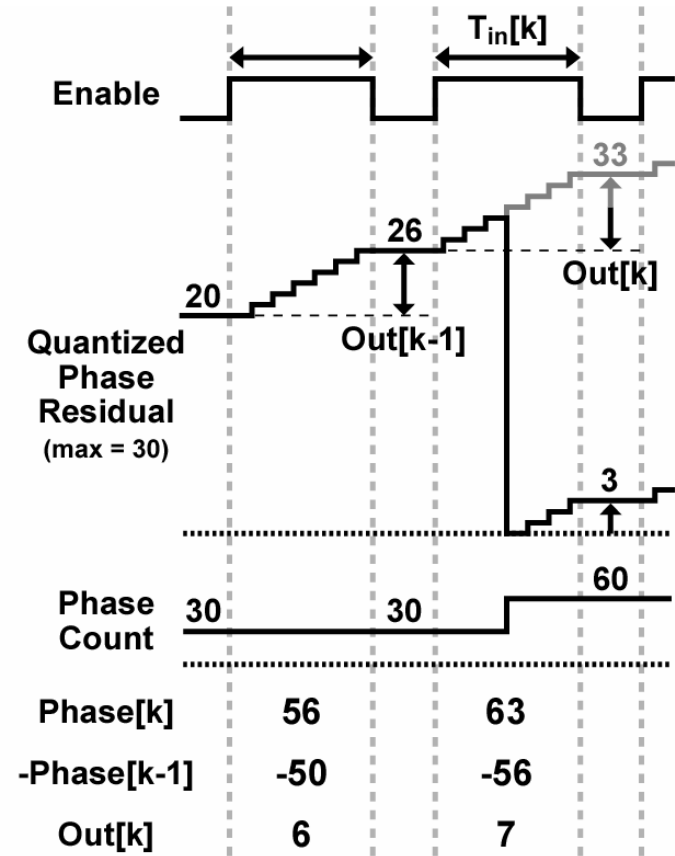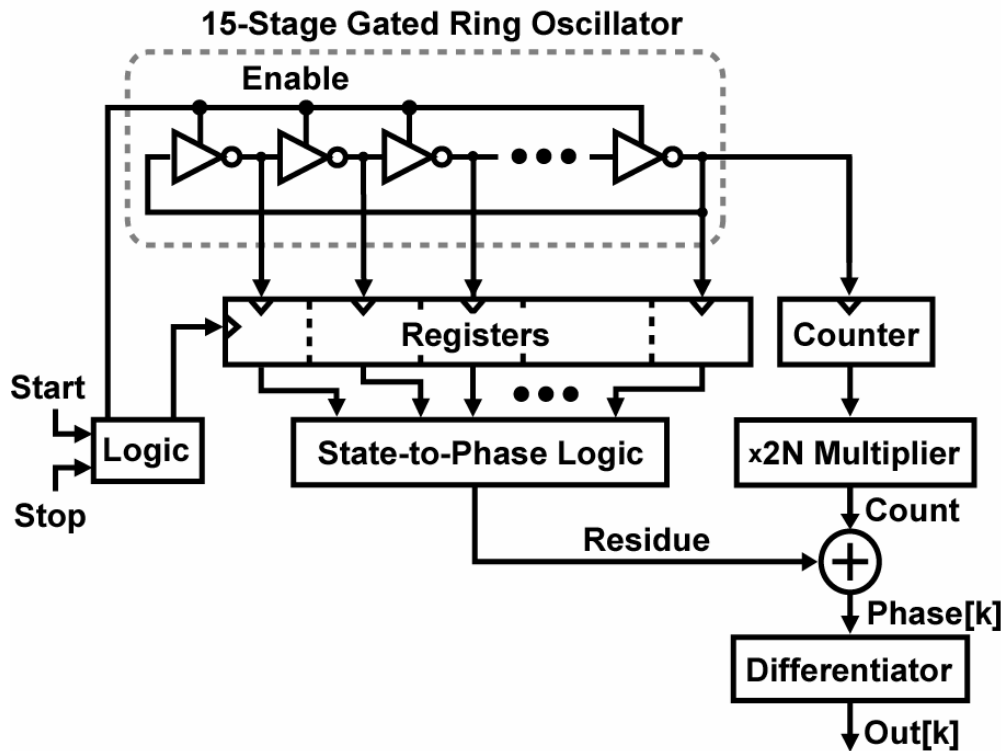


- Calculate phase from:
 - A single counter for coarse phase information
 - GRO output state for fine phase residual
- 1 counter and N registers → much more efficient

Accuracy considerations...

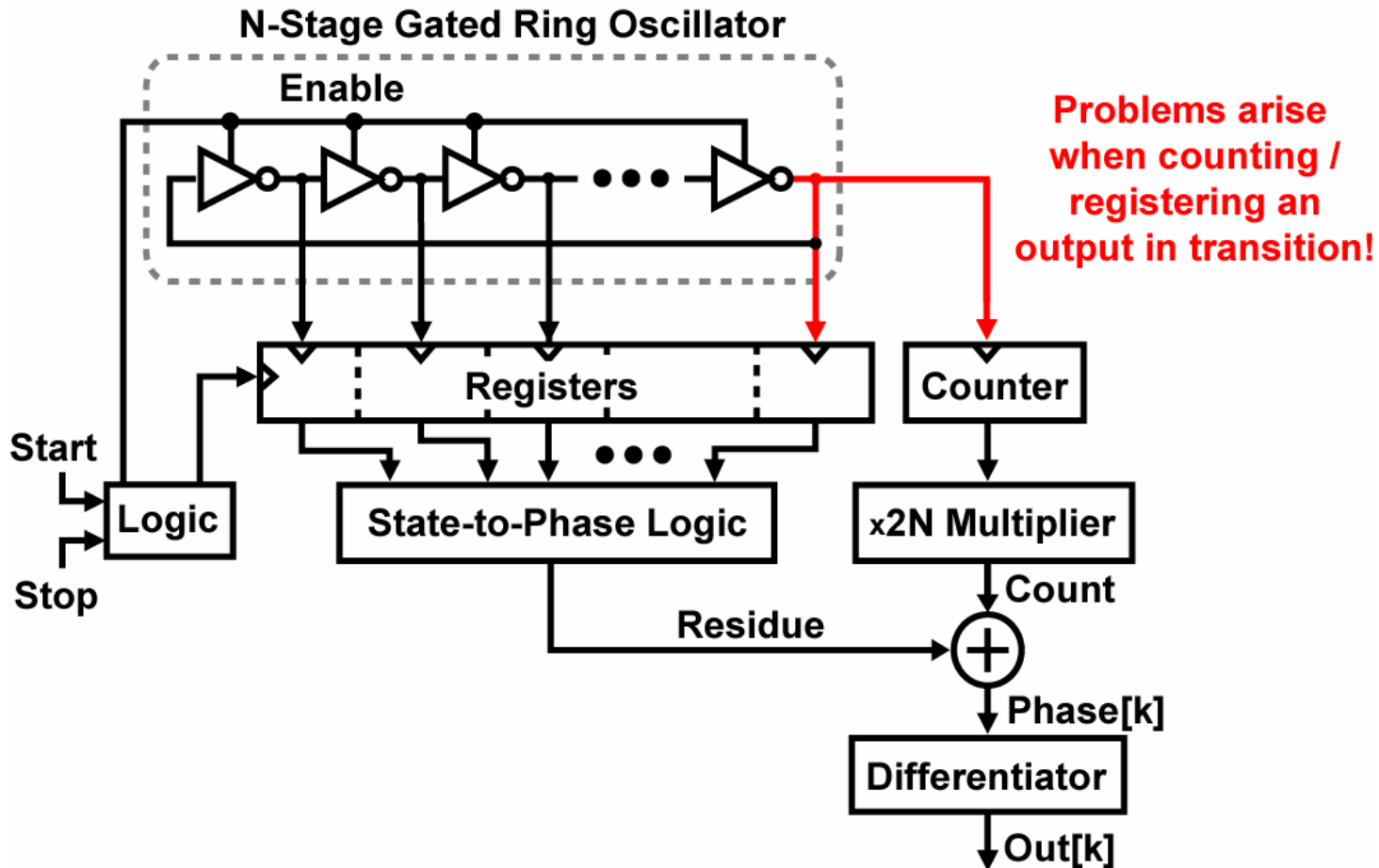


- Counter and registers need to have the same state
- Cannot allow counters to double-count a single transition

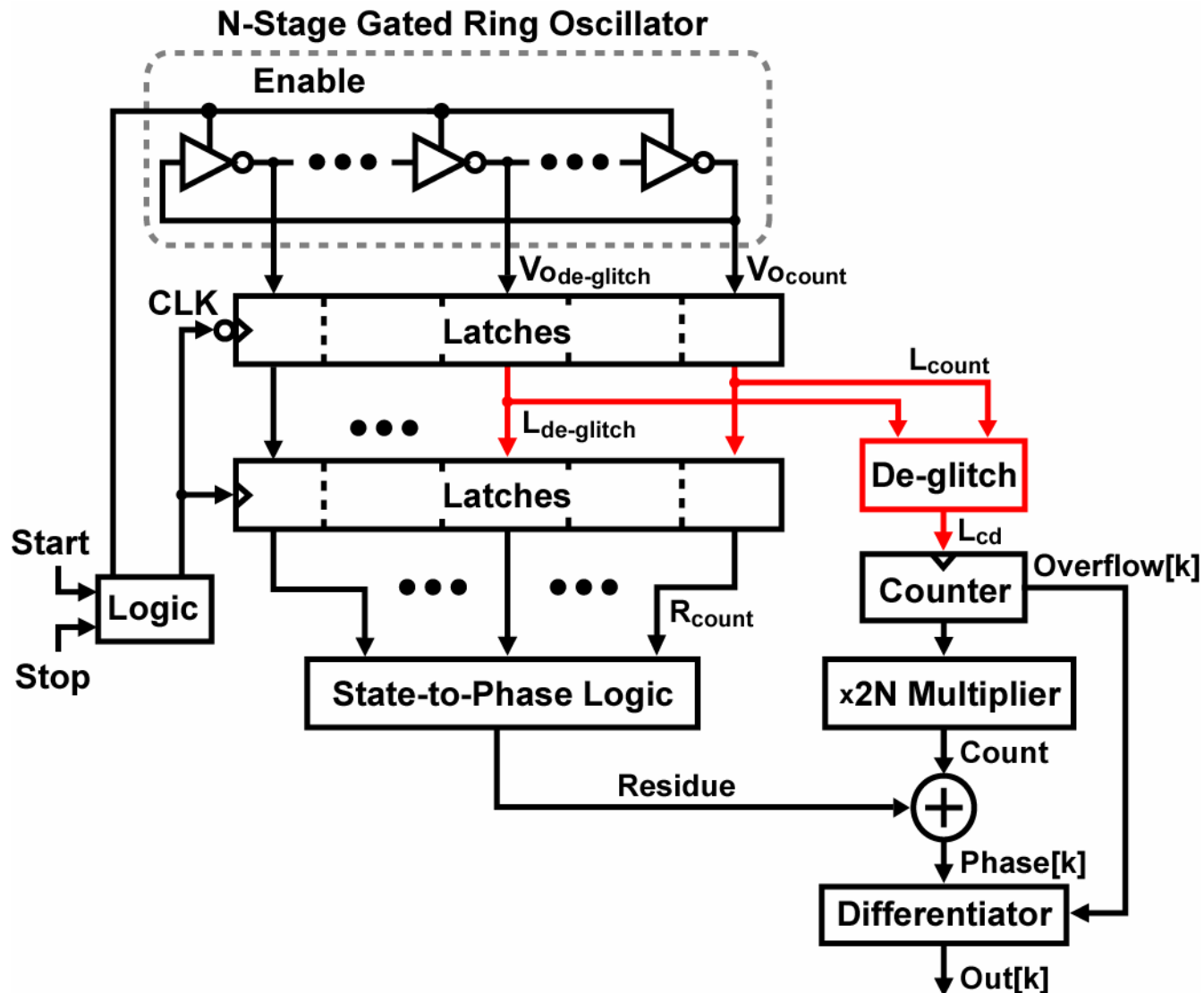De-glitch circuits to ensure accurate measurements




 Key issue with scheme for an multi-path GRO...





- More than one delay element output is logically uncertain
- Transition sequence is unpredictable and ambiguous
- Cannot map from entire GRO output state to phase

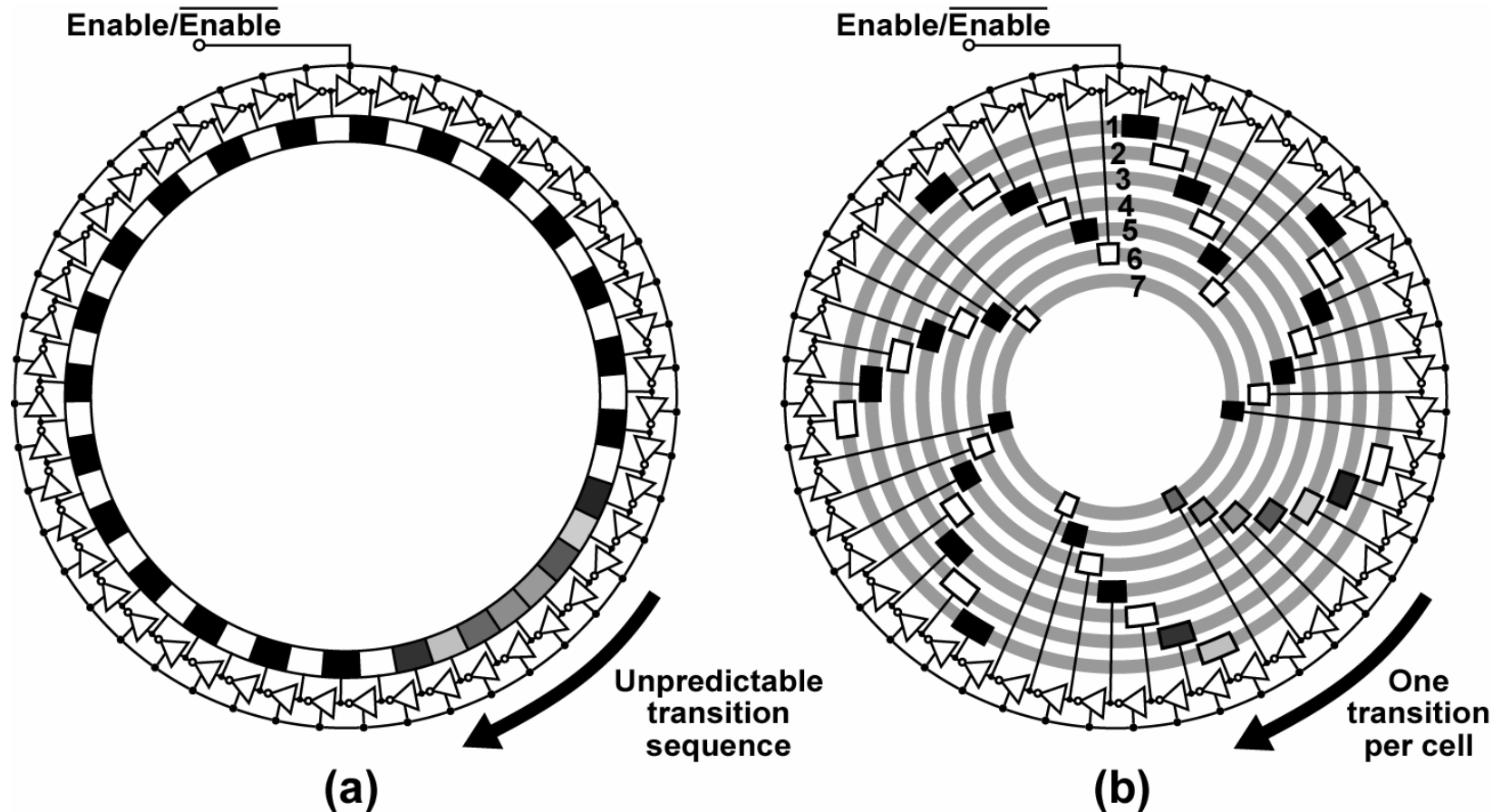Restoring the predictable relationship...





- Calculate phase contribution from each cell independently
- Transition sequence within each cell is now predictable

 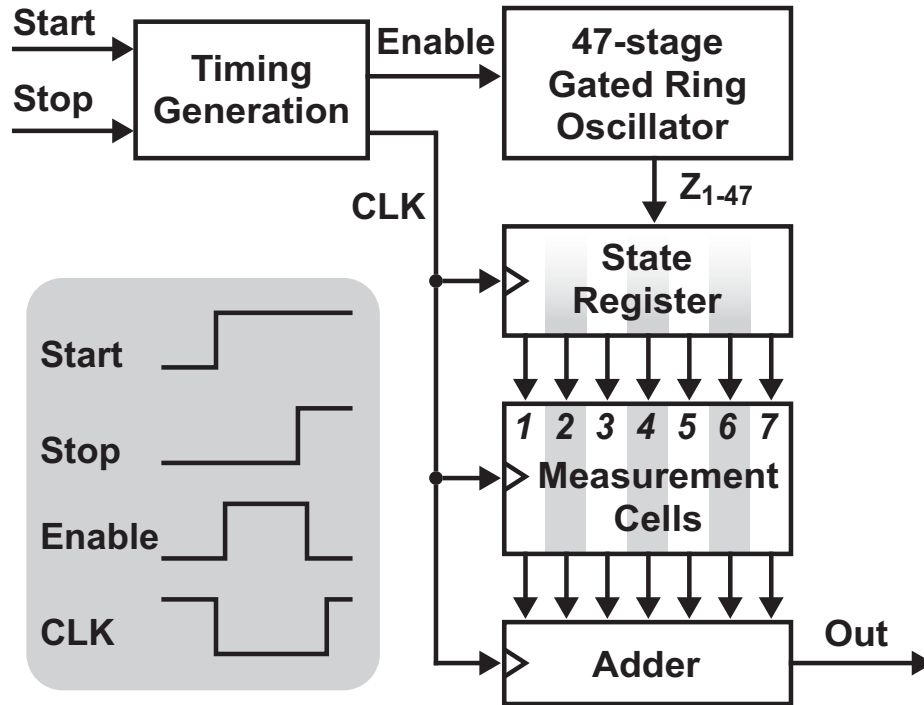Prototype 0.13 μm CMOS multi-path GRO-TDC




- **Two implemented versions:**
 - 8-bit, 500MSPs
 - 11-bit, 100MSPs version
- **2-21mW power consumption depending on input duty cycle**

Measured noise-shaping of multi-path GRO

 
 


- Data collected at 50Mps
- More than 20dB of noise-shaping benefit
- 80fs_{rms} integrated error from 2kHz-1MHz
- Floor primarily limited by 1/f noise (up to 0.5-1MHz)

Measured 11-bit range of multi-path GRO

 


  Measured deadzone behavior for multi-path GRO



- Only deadzones for outputs that are multiples of $2N$
 - 94, 188, 282, etc.
 - No deadzones for other even or odd integers, fractional output
- Size of deadzone is reduced by 10x

 Revised gating skew cartoon for the multi-path GRO



- At least **13** stages in transition at a time
 - Most of the mismatch from positive and negative transitions is cancelled
- T_{skew} is the **average** of error from each of the individual stages
 - GRO phase trajectory is determined by many stages, not just one

11-bit GRO-TDC performance summary


Sampling Frequency	<100 MHz
Raw delay resolution	6ps
Effective resolution	1ps @ 50Msps
Integrated noise	80fs-rms, 2kHz-1MHz
Dynamic range	95dB, 1MHz BW
Power	2.2-21mW (<4mW typical)
Area	157 x 258μm
Technology	0.13μm CMOS

Summary of Time to Digital Conversion

- **Key performance metrics are**
 - Resolution: want low quantization noise
 - Mismatch: want high linearity
 - Power and area: want long battery life, low cost
- **Many structures have been introduced**
 - Classical, Vernier, Two-Step, Time Amplifiers, Re-cycling, Gated Ring Oscillator
- **Comparable to ADCs but suffers from lack of “time memory element”**
 - Cyclic conversion and pipeline structures have not been achieved
- **A very promising research area!**



Digitally-Controlled Oscillators

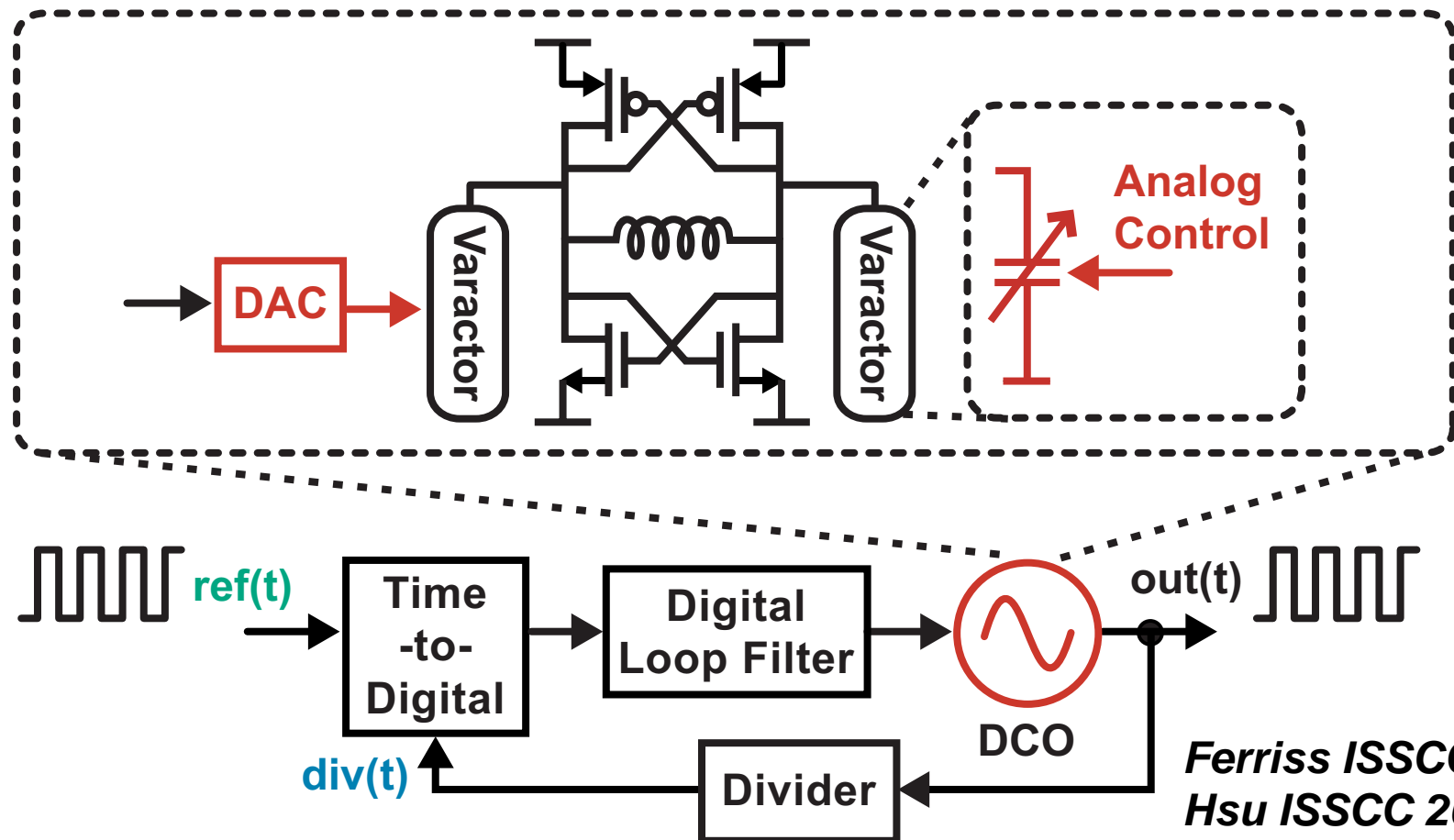A Straightforward Approach for Achieving a DCO




- Use a DAC to control a conventional LC oscillator
 - Allows the use of an existing VCO within a digital PLL
 - Can be applied across a broad range of IC processes

A Much More Digital Implementation

  


- Adjust frequency in an LC oscillator by switching in a variable number of small capacitors
 - Most effective for CMOS processes of 0.13u and below

 Leveraging Segmentation in Switched Capacitor DCO




- Similar in design as *segmented* capacitor DAC structures
 - Binary array: efficient control, but may lack monotonicity
 - Unit element array: monotonic, but complex control
- Coarse and fine control segmentation of DCO
 - Coarse control: active only during initial frequency tuning (leverage binary array)
 - Fine control: controlled by PLL feedback (leverage unit element array to guarantee monotonicity)

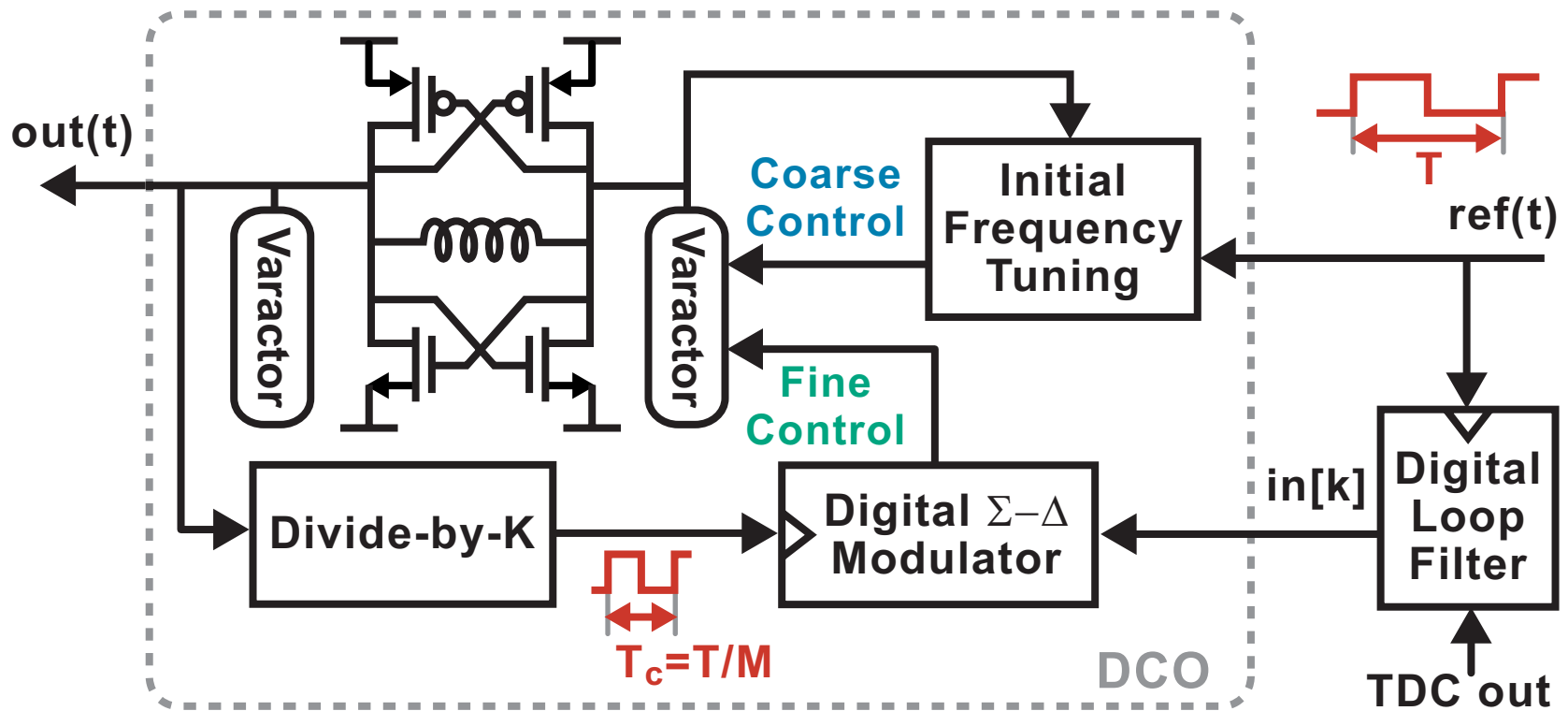Leveraging Dithering for Fine Control of DCO




- Increase resolution by $\Sigma-\Delta$ dithering of fine cap array
- Reduce noise from dithering by
 - Using small unit caps in the fine cap array
 - Increasing the dithering frequency (defined as $1/T_c$)
 - We will assume $1/T_c = M/T$ (i.e. M times reference frequency)

Time-Domain Modeling of the DCO

 


- **Input to the DCO is supplied by the loop filter**
 - Clocked at $1/T$ (i.e., reference frequency)
- **Switched capacitors are dithered by $\Sigma-\Delta$ at a higher rate**
 - Clocked at $1/T_c = M/T$
 - Held at a given setting for duration T_c
- **Fine cap element value determines K_v of VCO**
 - Units of K_v are Hz/unit cap

Frequency Domain Modeling of DCO

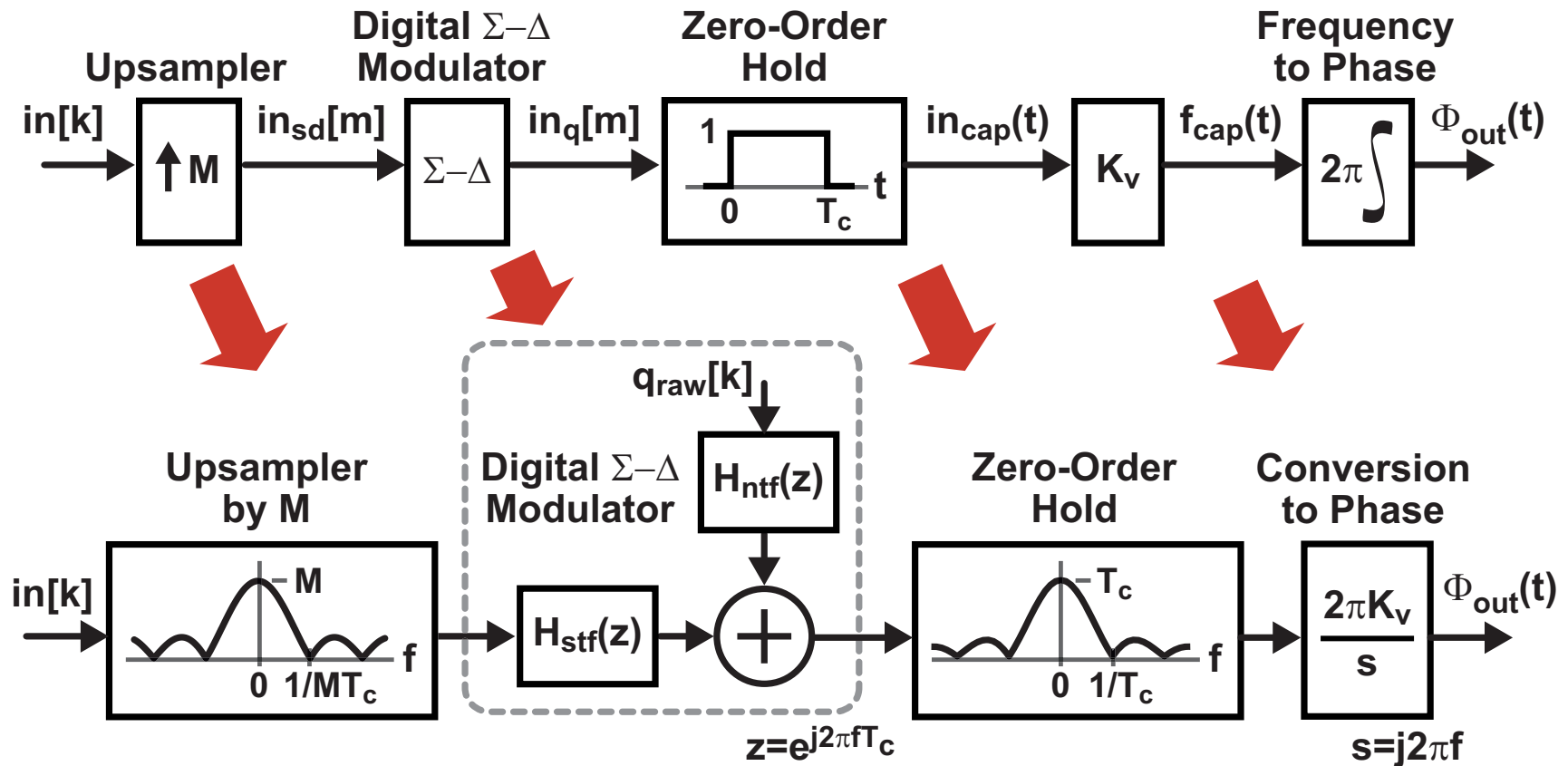


- Upsampler and zero-order hold correspond to discrete and continuous-time *sinc* functions, respectively
- $\Sigma-\Delta$ has signal and noise transfer functions ($H_{stf}(z)$, $H_{ntf}(z)$)
 - Note: $var(q_{raw}[k]) = 1/12$ (uniformly distributed from 0 to 1)

Simplification of the DCO Model

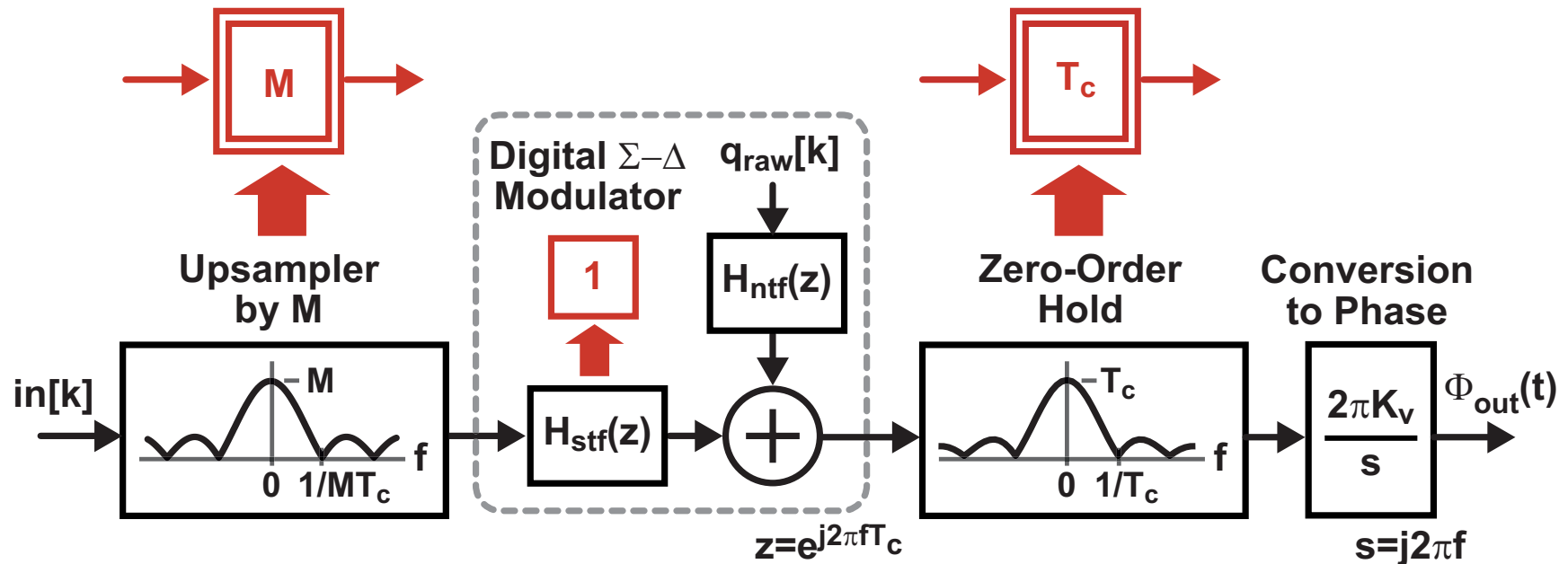


- Focus on low frequencies for calculations to follow
 - Assume *sinc* functions are relatively flat at the low frequencies of interest
 - Upsampler is approximated as a gain of M
 - Zero-order hold is approximated as a gain of T_c
- Assume $H_{stf}(z) = 1$
 - True for $\Sigma-\Delta$ structures such as MASH (ignoring delays)

Spectral Density Calculations

 

- **CT → CT** $S_y(f) = |H(f)|^2 S_x(f)$
- **DT → DT** $S_y(e^{j2\pi fT}) = |H(e^{j2\pi fT})|^2 S_x(e^{j2\pi fT})$
- **DT → CT** $S_y(f) = \frac{1}{T} |H(f)|^2 S_x(e^{j2\pi fT})$

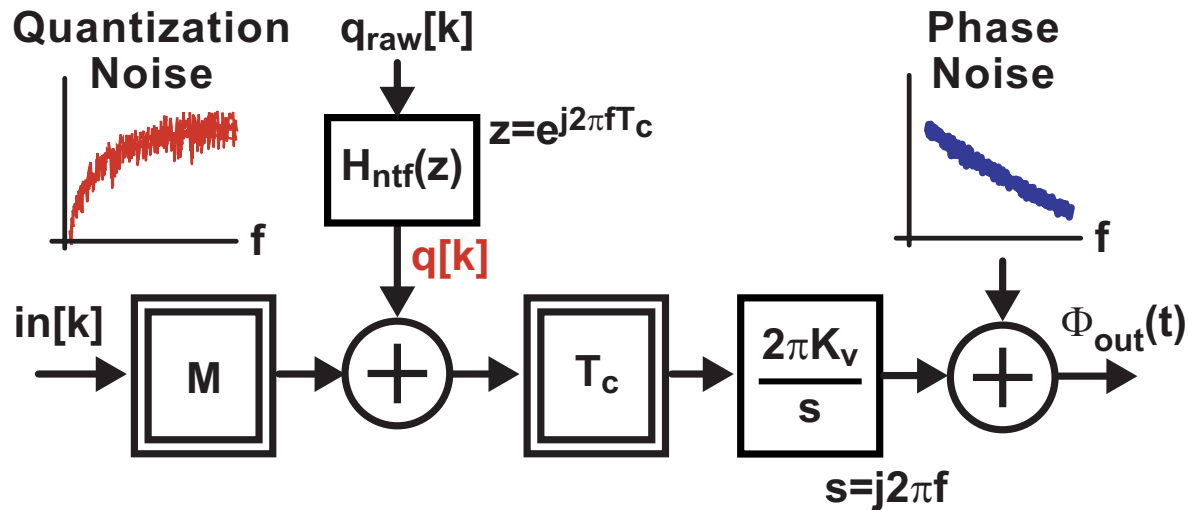Calculation of Quantization Noise from Cap Dithering



■ DT to CT spectral calculation:

$$\begin{aligned}
 S_{\Phi_{out}}(f) \Big|_{dco, quant} &= \frac{1}{T_c} \left| T_c \frac{2\pi K_v}{j2\pi f} \right|^2 \left| H_{ntf}(e^{j2\pi f T_c}) \right|^2 S_{q_{raw}}(f) \\
 &= T_c \left| \frac{K_v}{f} \right|^2 \left| H_{ntf}(e^{j2\pi f T_c}) \right|^2 \frac{1}{12}
 \end{aligned}$$

- $S_{q_{raw}}(f) = 1/12$ since $q_{raw}[k]$ uniformly distributed from 0 to 1
- $H_{ntf}(z)$ is often $1-z^{-1}$ (first order) or $(1-z^{-1})^2$ (second order)

Example Calculation for DCO Quantization Noise

- Assumptions (Out freq = 3.6 GHz)
 - Dithering frequency is 200 MHz (i.e., $1/T_c = 200e6$)
 - $\Sigma\text{-}\Delta$ has first order shaping (i.e., $H_{ntf}(z) = 1 - z^{-1}$)
 - Fine cap array yields 12 kHz/unit cap (i.e., $K_v = 12e3$)

$$S_{\Phi_{out}}(f)|_{\text{dco, quant}} = T_c \left| \frac{K_v}{f} \right|^2 \left| H_{ntf}(e^{j2\pi f T_c}) \right|^2 \frac{1}{12}$$
$$= \frac{1}{200e6} \left| \frac{12e3}{f} \right|^2 \left| 1 - e^{j2\pi f / 200e6} \right|^2 \frac{1}{12}$$


- At a frequency offset of $f = 20$ MHz:

$$= \frac{1}{200e6} \left| \frac{12e3}{20e6} \right|^2 \left| 1 - e^{j2\pi 1/10} \right|^2 \frac{1}{12} = 5.73 \cdot 10^{-17}$$

$$10 \log(5.73 \cdot 10^{-17}) = -162.4 \text{ dBc/Hz (at 20 MHz offset)}$$

Below the phase noise (-153 dBc/Hz at 20 MHz) in the example


Further Simplification of DCO Model

 


- Proper design of DCO will yield quantization noise that is below that of the intrinsic phase noise (set by tank Q , etc.)

- Assume $q[k] = 0$ for simplified model

- Note that $T = M\phi T_c$

 


Overall Digital PLL Model

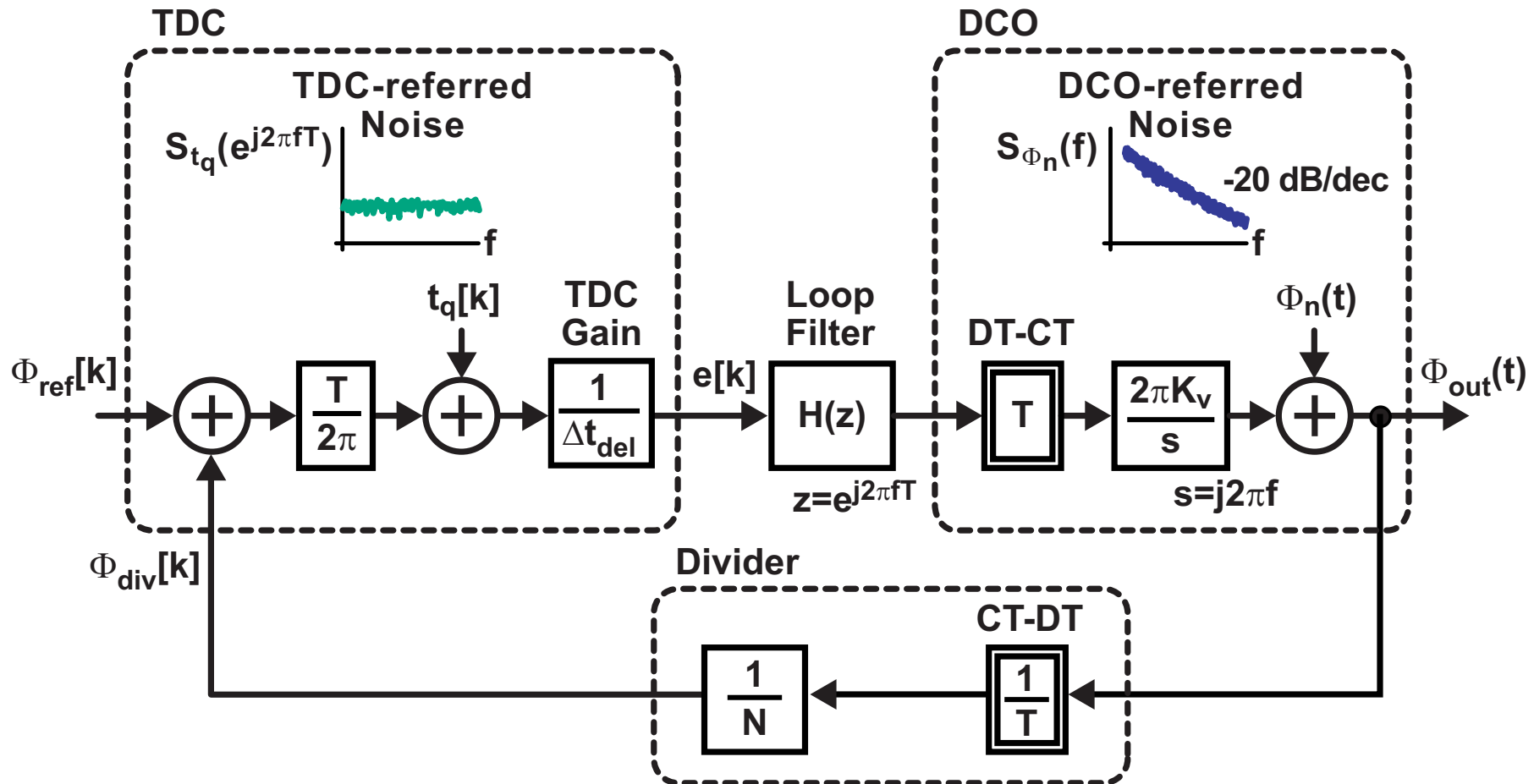

- TDC and DCO-referred noise influence overall phase noise according to associated transfer functions to output
- Calculations involve both discrete *and* continuous time

Key Transfer Functions

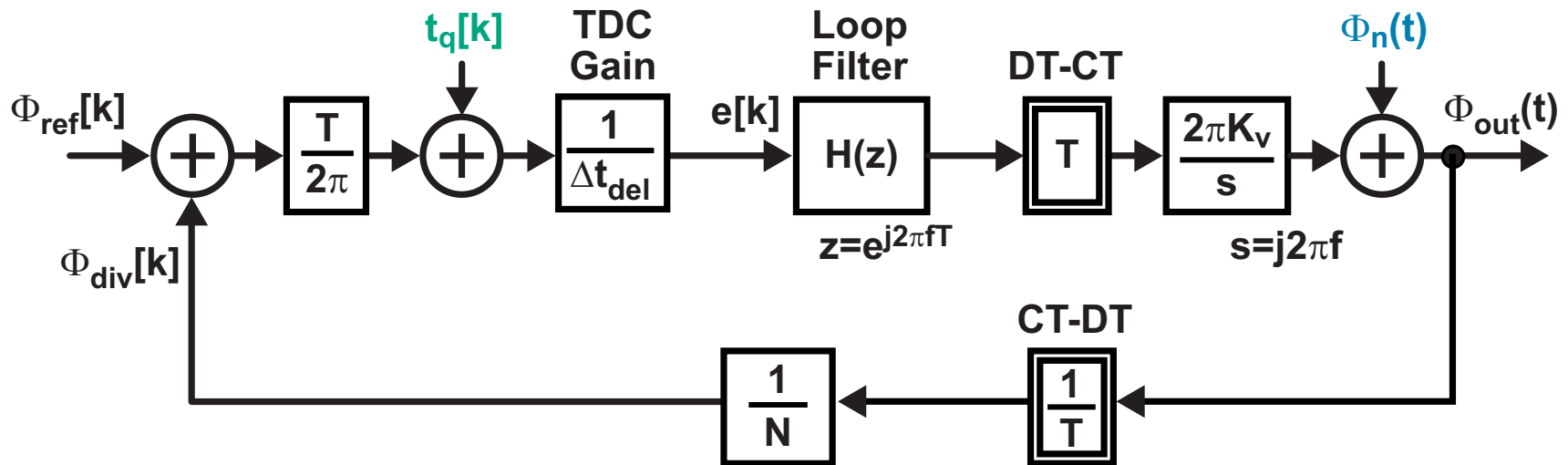


- **TDC-referred noise**

$$\frac{\Phi_{out}}{t_q} = \frac{(1/\Delta t_{del})H(e^{j2\pi fT})T2\pi K_v/(2\pi jf)}{1 + (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)}$$

- **DCO-referred noise**

$$\frac{\Phi_{out}}{\Phi_n} = \frac{1}{1 + (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)}$$

Introduce a Parameterizing Function

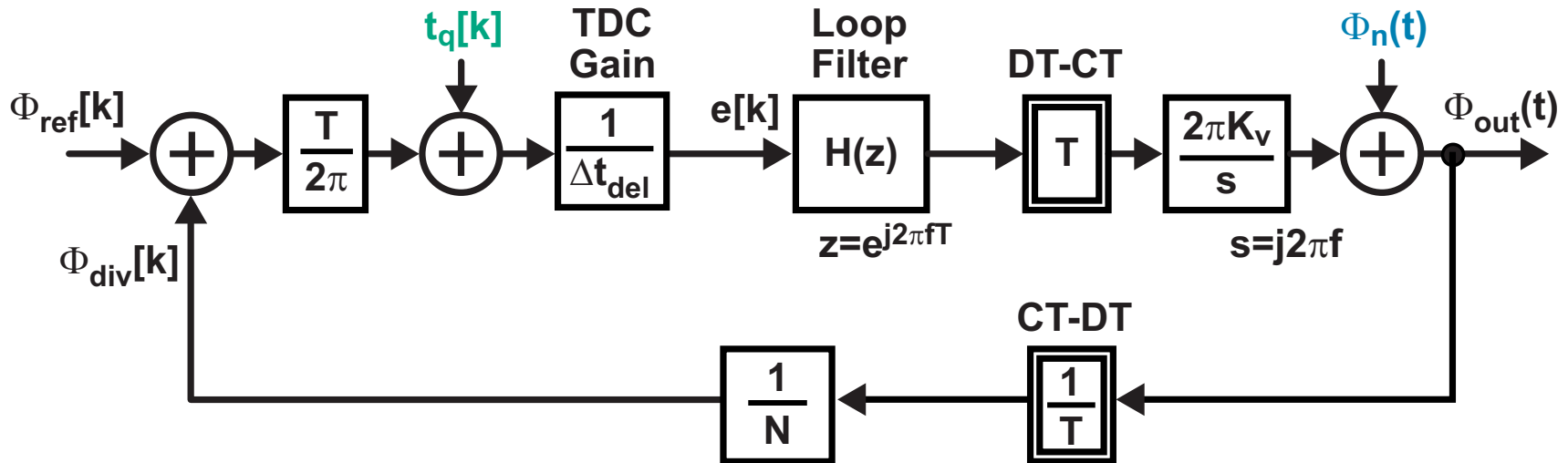

- Define open loop transfer function $A(f)$ as:

$$A(f) = (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)$$

- Define closed loop parameterizing function $G(f)$ as:

$$G(f) = \frac{A(f)}{1 + A(f)}$$

- Note: $G(f)$ is a lowpass filter with DC gain = 1

Transfer Function Parameterization Calculations


- TDC-referred noise

$$\begin{aligned}\frac{\Phi_{out}}{t_q} &= \frac{(1/\Delta t_{del})H(e^{j2\pi fT})T2\pi K_v/(2\pi jf)}{1 + (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)} \\ &= \frac{2\pi NA(f)}{1 + A(f)} = 2\pi NG(f)\end{aligned}$$

- DCO-referred noise

$$\begin{aligned}\frac{\Phi_{out}}{\Phi_n} &= \frac{1}{1 + (1/\Delta t_{del})H(e^{j2\pi fT})TK_v/(2\pi jf)(1/N)} \\ &= \frac{1}{1 + A(f)} = \frac{1 + A(f) - A(f)}{1 + A(f)} = 1 - G(f)\end{aligned}$$

Key Observations

 

- **TDC-referred noise**

$$\frac{\Phi_{out}}{t_q} = 2\pi N G(f)$$



Lowpass with a DC gain of $2\pi N$

- **DCO-referred noise**


$$\frac{\Phi_{out}}{\Phi_n} = 1 - G(f)$$



Highpass with a high frequency gain of 1

How do we calculate the output phase noise?

Phase Noise Calculation

 


■ TDC noise


- DT to CT calculation
- Dominates PLL phase noise at low frequency offsets

■ DCO noise

 - CT to CT calculation
- Dominates PLL phase noise at high frequency offsets




Impact of PLL Bandwidth

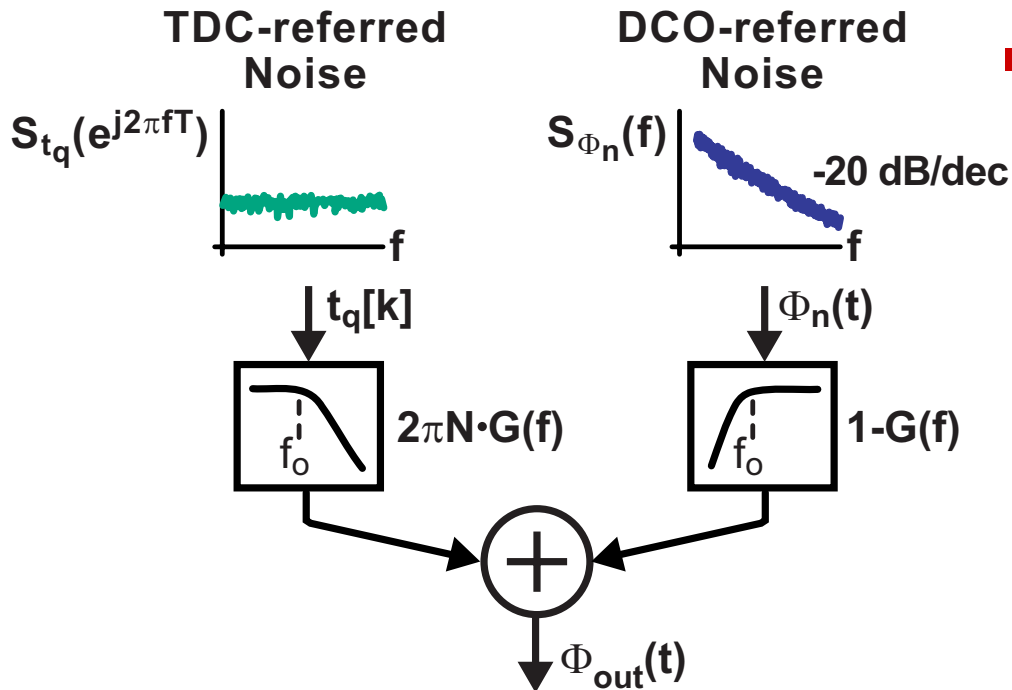

- PLL bandwidth dramatically influences relative impact of TDC and VCO noise


Want high PLL bandwidth?

➔ Need low TDC Noise

 

System Level Design

Closed Loop PLL Design Approach

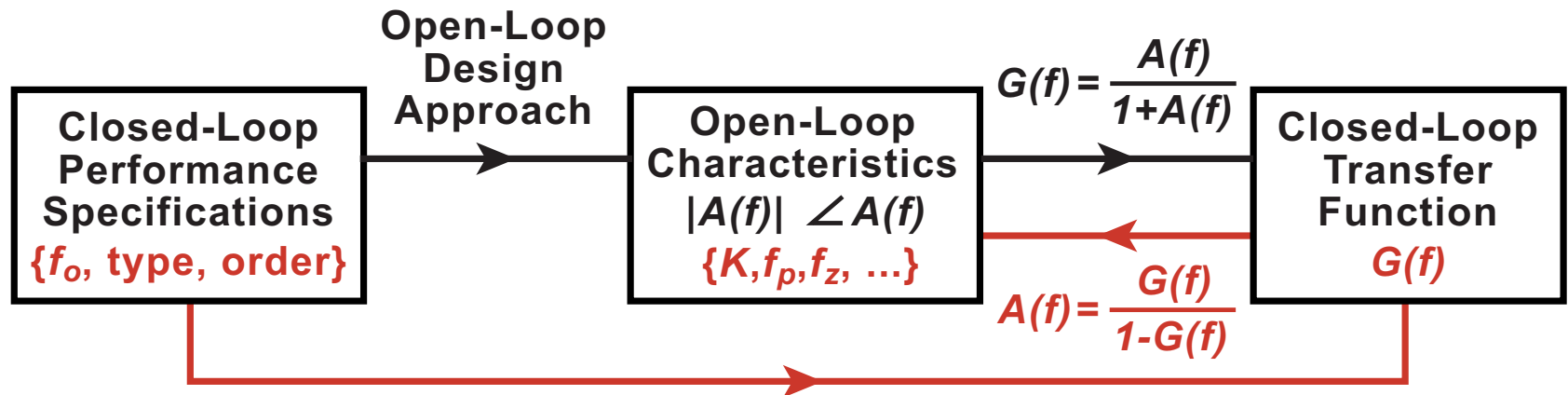

Proposed Closed Loop Design Approach

Lau and Perrott,
DAC, June 2003

- **Classical open loop approach**
 - Indirectly design $G(f)$ using bode plots of $A(f)$
- **Proposed closed loop approach**
 - Directly design $G(f)$ by examining impact of its specifications on phase noise (and settling time)
 - Solve for $A(f)$ that will achieve desired $G(f)$


Implemented in *PLL Design Assistant Software*

<http://www.cppsim.com>

Transfer Function Design using PLL Design Assistant


- PLL Design Assistant assumes continuous-time open loop transfer function $A_{calc}(s)$:
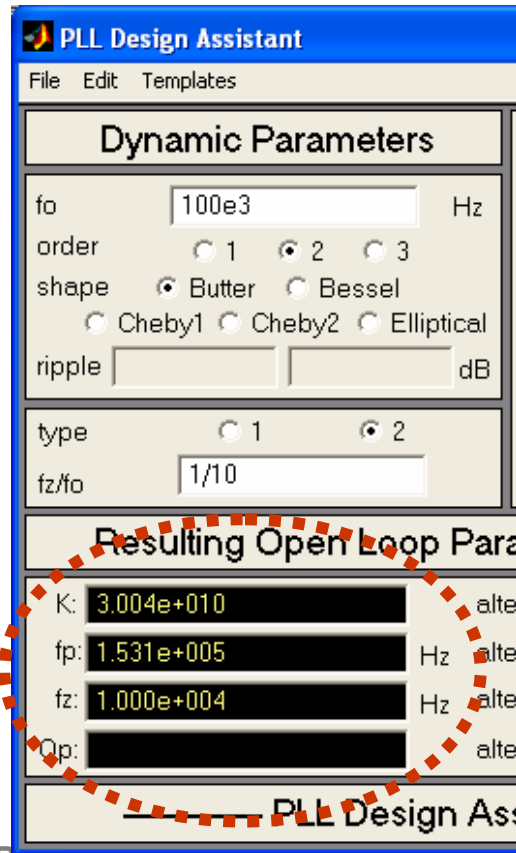
$$A_{calc}(s) = \frac{K}{s^{type}} \frac{1 + s/w_z}{1 + s/w_p}$$



- Above parameters are calculated based on the desired closed loop PLL *bandwidth, type, and order of rolloff* (which specify $G(s)$)
- For 100 kHz bandwidth, $type = 2$, 2nd order rolloff, we have:
 - $K = 3.0 \times 10^{10}$
 - $w_p = 2\pi(153 \text{ kHz})$
 - $w_z = 2\pi(10 \text{ kHz})$

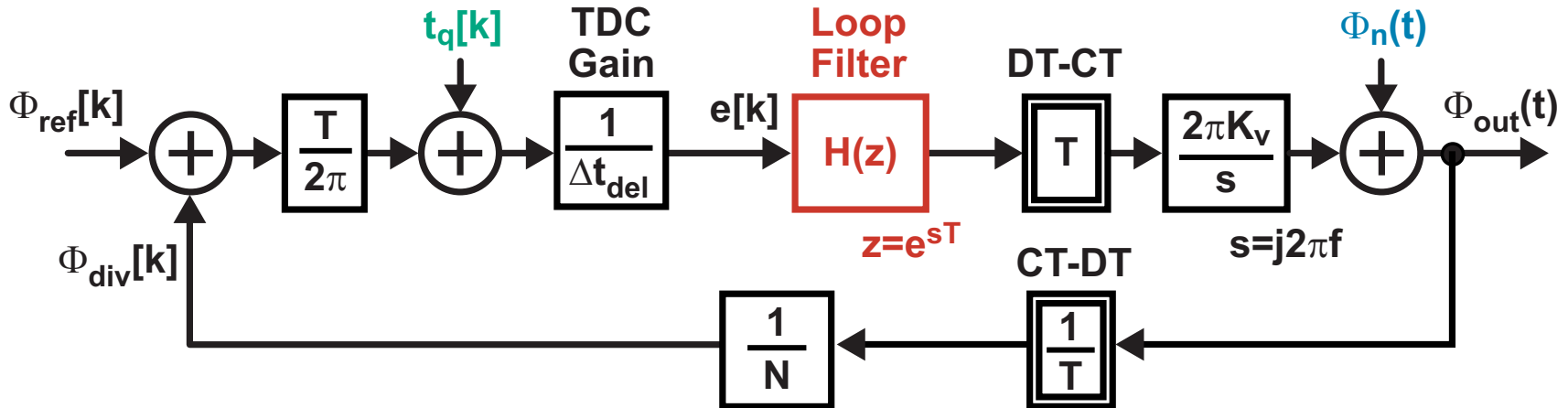Continuous-Time Approximation of Digital PLL



- At low frequencies (i.e., $|sT| \ll 1$), we can use the first order term of a Taylor series expansion to approximate

$$z^{-1} = e^{-sT} \approx 1 - sT$$

- Resulting continuous-time approximation of open loop transfer function of digital PLL:

$$A(s) \approx \frac{T}{\Delta t_{del}} \frac{K_v}{N} \frac{1}{s} H(z) \Big|_{z^{-1} \approx 1 - sT}$$

Applying PLL Design Assistant to Digital PLL Design

- Given the continuous-time approximation of $A(s)$, we then leverage the PLL Design Assistant calculation:

$$A(s) = A_{calc}(s)$$

- Also note that:

$$z^{-1} = 1 - sT \Rightarrow s = \frac{1 - z^{-1}}{T}$$

- Given the above, we obtain:

$$\frac{T}{\Delta t_{del}} \frac{K_v}{N} \frac{1}{s} H(z) \Big|_{s=\frac{1-z^{-1}}{T}} = \frac{K}{s^{type}} \frac{1 + s/w_z}{1 + s/w_p} \Big|_{s=\frac{1-z^{-1}}{T}}$$

$$\Rightarrow H(z) = \frac{\Delta t_{del}}{T} \frac{N}{K_v} \left(\frac{K}{s^{type-1}} \right) \frac{1 + s/w_z}{1 + s/w_p} \Big|_{s=\frac{1-z^{-1}}{T}}$$

Simplified Form for Digital Loop Filter (Type II PLL)

- From previous slide:

$$H(z) = \frac{\Delta t_{del}}{T} \frac{N}{K_v} \left(\frac{K}{s^{type-1}} \right) \frac{1 + s/w_z}{1 + s/w_p} \Bigg|_{s = \frac{1-z^{-1}}{T}}$$

- Simplified form with $type = 2$ (assume $order = 2$)

$$H(z) = K_{LF} \left(\frac{1}{1 - z^{-1}} \right) \frac{1 - b_1 z^{-1}}{1 - a_1 z^{-1}}$$

- Where:

$$a_1 = \frac{1}{1 + w_p T} \quad b_1 = \frac{1}{1 + w_z T}$$

$$K_{LF} = \left(\frac{\Delta t_{del}}{T/N} \right) \frac{K}{K_v} \left(\frac{w_p}{w_z} \right) \frac{a_1}{b_1} T$$

*

Note:


$$T_{dco} = T/N$$

* Typically implemented by gain normalization circuit

Summary of Loop Filter Design

- **PLL Design Assistant allows fast loop filter design**

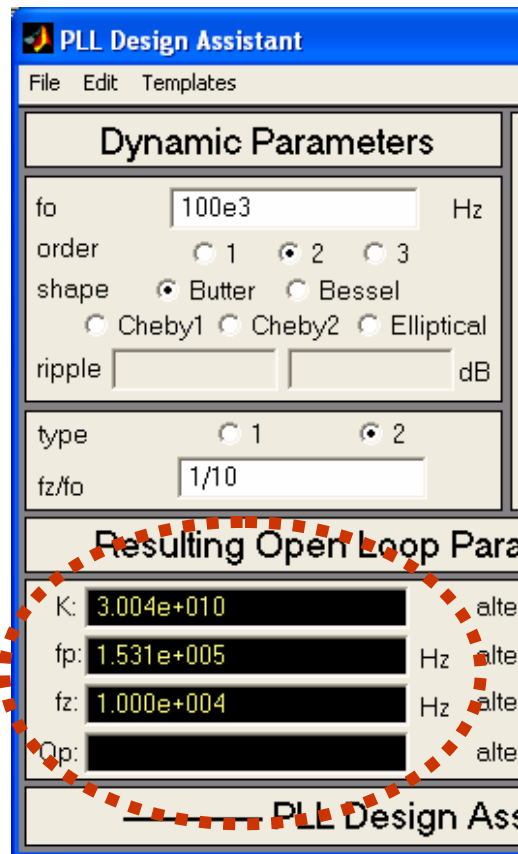- Assumption: $Type = 2$, 2^{nd} order rolloff



$$H(z) = K_{LF} \left(\frac{1}{1 - z^{-1}} \right) \frac{1 - b_1 z^{-1}}{1 - a_1 z^{-1}}$$

- Where:

$$a_1 = \frac{1}{1 + w_p T} \quad b_1 = \frac{1}{1 + w_z T}$$

$$K_{LF} = \left(\frac{\Delta t_{del}}{T/N} \right) \frac{K}{K_v} \left(\frac{w_p}{w_z} \right) \frac{a_1}{b_1} T$$

*


* implemented by gain normalization circuit

- **PLL Design Assistant provides the values of K , $w_p = 2\pi f_p$, $w_z = 2\pi f_z$**

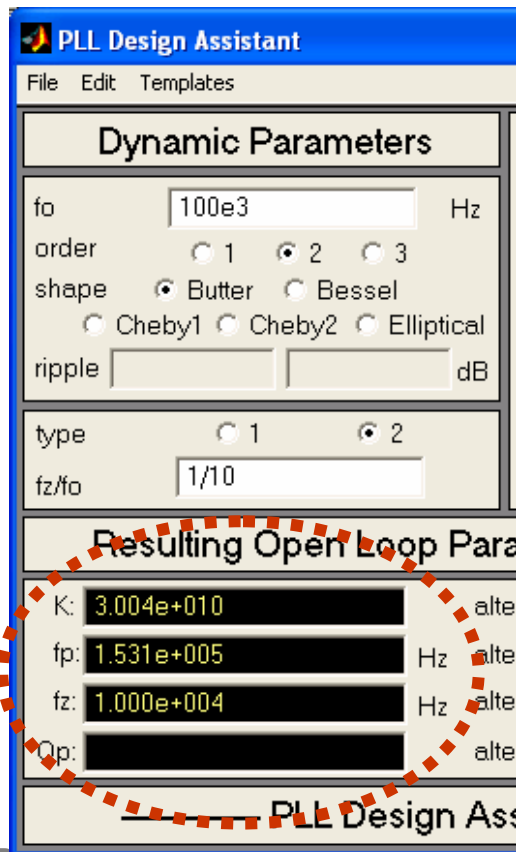Example Digital Loop Filter Calculation

Assumptions

- Ref freq ($1/T$) = 50 MHz, Out freq = 3.6 GHz (so $N = 72$)
- $\Delta t_{del} = 20$ ps, $K_v = 12$ kHz/unit cap
- 100 kHz bandwidth, Type = 2, 2nd order rolloff



$$H(z) = K_{LF} \left(\frac{1}{1 - z^{-1}} \right) \frac{1 - b_1 z^{-1}}{1 - a_1 z^{-1}}$$

$$b_1 = \frac{1}{1 + 2\pi 10\text{kHz}/50\text{MHz}} = .9987$$


$$a_1 = \frac{1}{1 + 2\pi 153\text{kHz}/50\text{MHz}} = .9811$$

$$K_{LF} = \left(\frac{\Delta t_{del}}{T/N} \right) \frac{3 \cdot 10^{10}}{12\text{kHz}} \frac{153}{10} \frac{.9811}{.9987} \frac{1}{50\text{MHz}}$$

$$= \left(\frac{\Delta t_{del}}{T/N} \right) 0.75 = \left(\frac{\Delta t_{del}}{T_{dco}} \right) 0.75$$

Overall PLL Noise Analysis

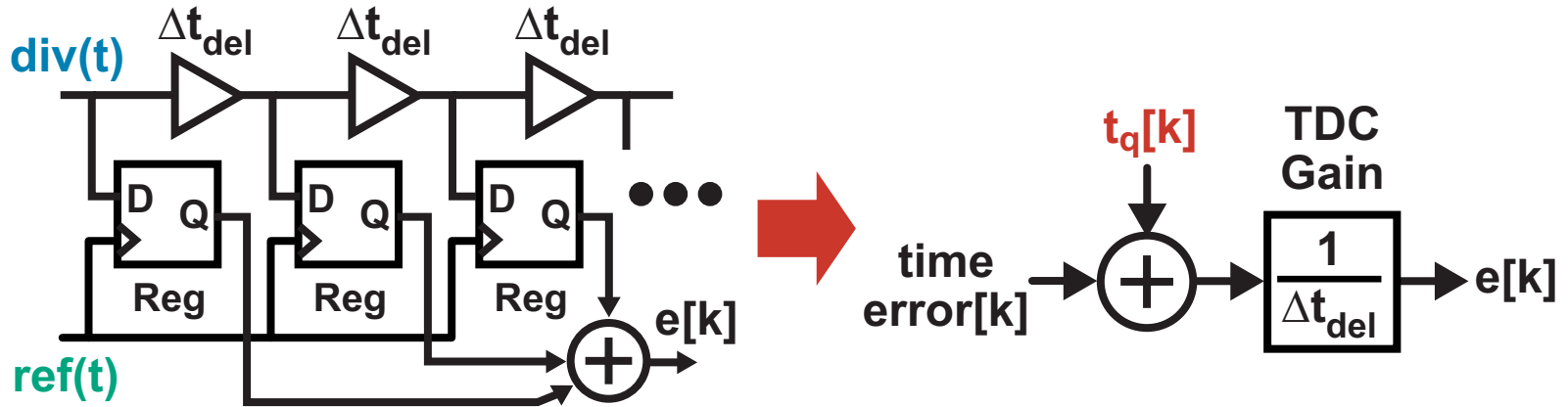
Calculation of TDC Noise Spectrum: Delay Chain TDC




- Under the assumption that quantization error is uniformly distributed across time interval Δt_{del} :

$$S_{t_q}(e^{j2\pi fT}) = \frac{(\Delta t_{del})^2}{12}$$

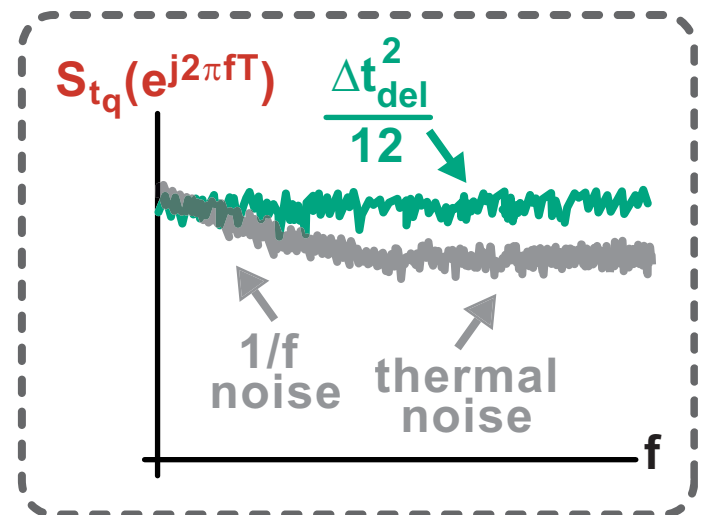- Key issue: quantization error may not be white for this TDC!
 - Use behavioral simulations to get a more accurate view
- $1/f$ noise may have impact



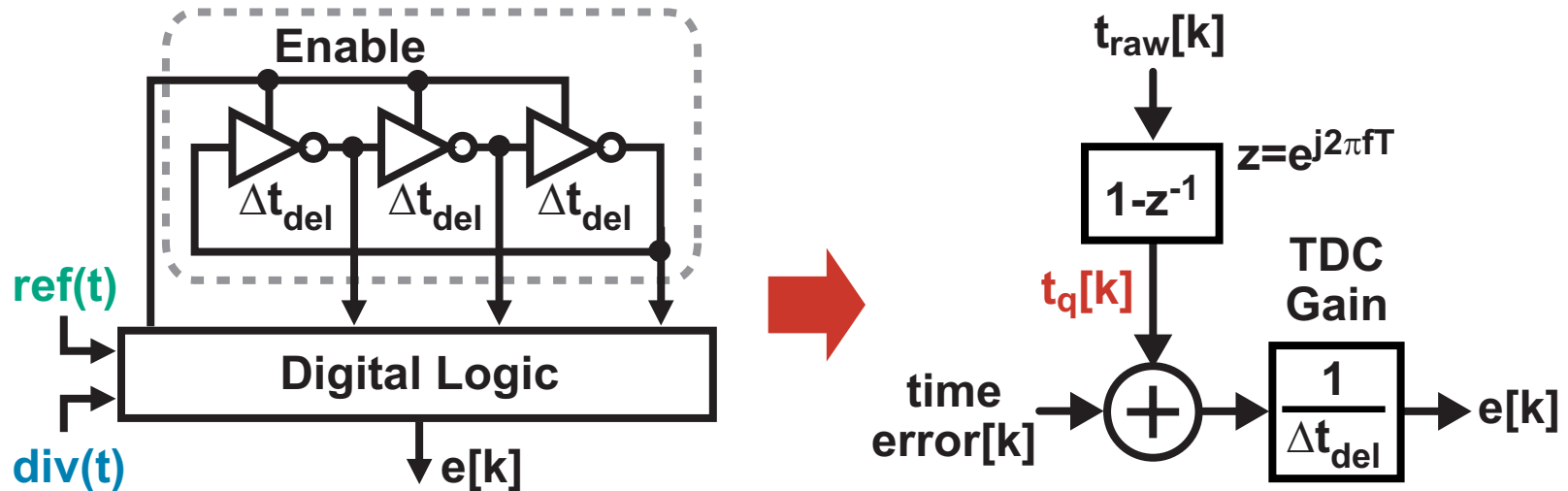
Calculation of TDC Noise Spectrum: GRO TDC



- **GRO achieves noise shaping:**

$$S_{t_q}(e^{j2\pi fT}) = \frac{|1 - e^{-j2\pi fT}|^2 (\Delta t_{del})^2}{12}$$

 - **1/f and thermal noise limit noise performance at low frequency offsets**



Example Calculation for Delay Chain TDC

- Ref freq = $1/T = 50$ MHz,
Out freq = 3.6 GHz


$$\Rightarrow N = \frac{3600}{50} = 72$$

- Inverter delay = $\Delta t_{del} = 20$ ps


$$\begin{aligned} S_{\Phi_{out}}(f) \Big|_{tdc} &= \frac{1}{T} |2\pi N G(f)|^2 \frac{\Delta t_{del}^2}{12} \\ &= 3.4 \cdot 10^{-10} |G(f)|^2 \end{aligned}$$

- Note: $G(f) = 1$ at low offset frequencies
 
$$10 \log(3.4 \cdot 10^{-10}) = -94.7 \text{ dBc/Hz (at low offset freq.)}$$



 Calculation of Noise Spectrum: Switched Cap DCO




Phase noise

- Same as for conventional VCO (tank Q, etc.)

Quantization noise from dithering

- Design to be less than VCO phase noise

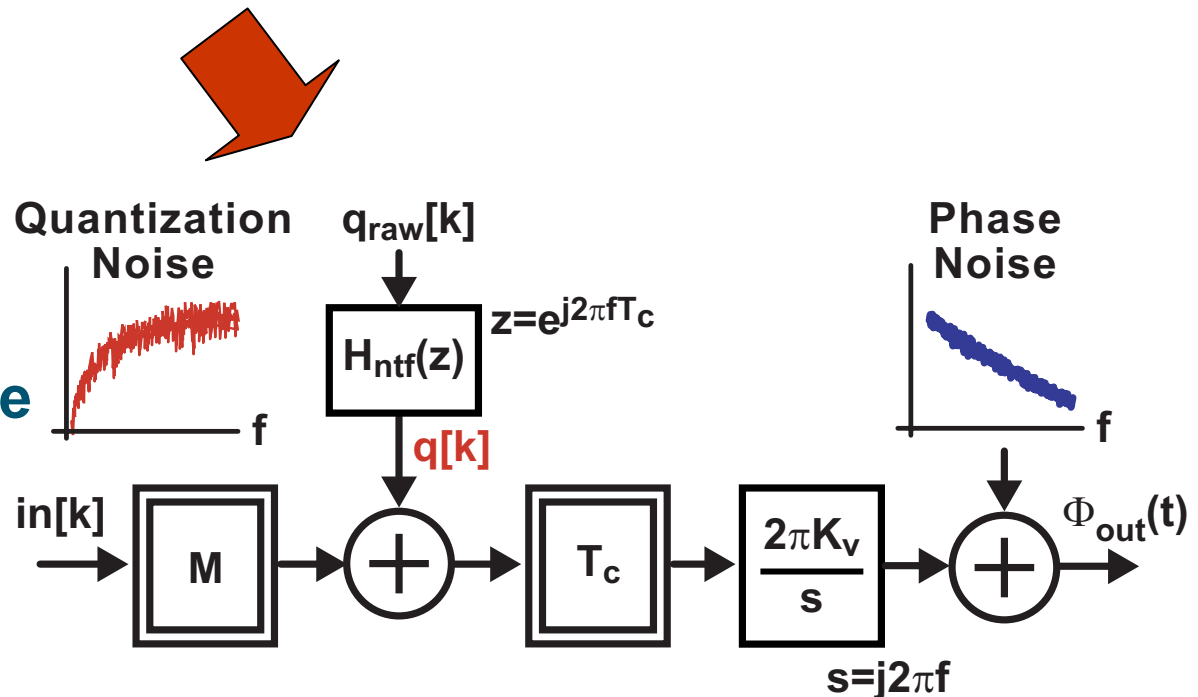

Evaluate Phase Noise with 500 kHz PLL Bandwidth

■ Key PLL parameters:

- $G(f)$: 500 kHz BW, Type II, 2nd order rolloff
- TDC noise: -94.7 dBc/Hz
- DCO noise: -153 dBc/Hz at 20 MHz offset (3.6 GHz carrier)


The screenshot shows the PLL Design Assistant software interface. The window title is "PLL Design Assistant". The interface is divided into several sections:

- Dynamic Parameters:** Contains fields for f_o (500e3 Hz), order (radio buttons 1, 2, 3), shape (radio buttons Butter, Bessel, Cheby1, Cheby2, Elliptical), ripple (dB), type (radio buttons 1, 2), and f_z/f_o (1/10).
- Noise Parameters:** Contains fields for ref. freq (50e6 Hz), out freq. (3.6e9 Hz), Detector (-94.7 dBc/Hz), VCO (-153 dBc/Hz), and freq. offset (20e6 Hz). There are also S-D radio buttons (1, 2, 3, 4, 5) and On/Off checkboxes.
- Resulting Open Loop Parameters:** Shows K (7.509e+011), fp (7.655e+005 Hz), fz (5.000e+004 Hz), and Qp. Each has an "alter:" field and an "On/Off" checkbox.
- Resulting Plots and Jitter:** Includes an "Apply" button, radio buttons for Pole/Zero Diagram, Transfer Function, Step Response, and Noise Plot (selected), and a field for rms jitter (980.788 fs).

A red dashed circle highlights the Dynamic Parameters and Noise Parameters sections.

PLL Design Assistant
Written by Michael Perrott (<http://www-mtl.mit.edu/~perrott>)

 Calculated Phase Noise Spectrum with 500 kHz BW



TDC noise too high for GSM mask with 500 kHz PLL bandwidth

Change PLL Bandwidth to 100 kHz

■ Key PLL parameters:


- **G(f): 100 kHz BW**, Type = 2, 2nd order rolloff
- TDC noise: -94.7 dBc/Hz
- DCO noise: -153 dBc/Hz at 20 MHz offset (3.6 GHz carrier)

The screenshot shows the PLL Design Assistant software interface. The window title is "PLL Design Assistant". The interface is divided into several sections:

- Dynamic Parameters:** Contains fields for f_o (set to 100e3 Hz), order (set to 2), shape (Butter selected), ripple (dB), type (set to 2), and f_z/f_o (set to 1/10).
- Noise Parameters:** Contains fields for ref. freq (50e6 Hz), out freq. (3.6e9 Hz), Detector (-94.7 dBc/Hz), VCO (-153 dBc/Hz), and freq. offset (20e6 Hz). There are also S-D options (1, 2, 3, 4, 5) and On/Off buttons.
- Resulting Open Loop Parameters:** Shows calculated values for K (3.004e+010), f_p (1.531e+005 Hz), f_z (1.000e+004 Hz), and Qp. Each has an "alter:" field and an On/Off button.
- Resulting Plots and Jitter:** Includes an "Apply" button, plot type options (Pole/Zero Diagram, Transfer Function, Step Response, Noise Plot), and numerical values for jitter (1e3, 40e6, -160, -60) and rms jitter (464.961 fs).

At the bottom of the window, it says "PLL Design Assistant" and "Written by Michael Perrott (<http://www-mtl.mit.edu/~perrott>)".


 
Calculated Phase Noise Spectrum with 100 kHz BW



GSM mask is met with 100 kHz PLL bandwidth



Digital Fractional-N Synthesis

  A First Glance at Fractional-N Signals ($F_{out} = 4.25F_{ref}$)



- Constant *divide value* of $N = 4$ leads to frequency error
- Phase error accumulates in unbounded manner


TI Approach to Fractional Division

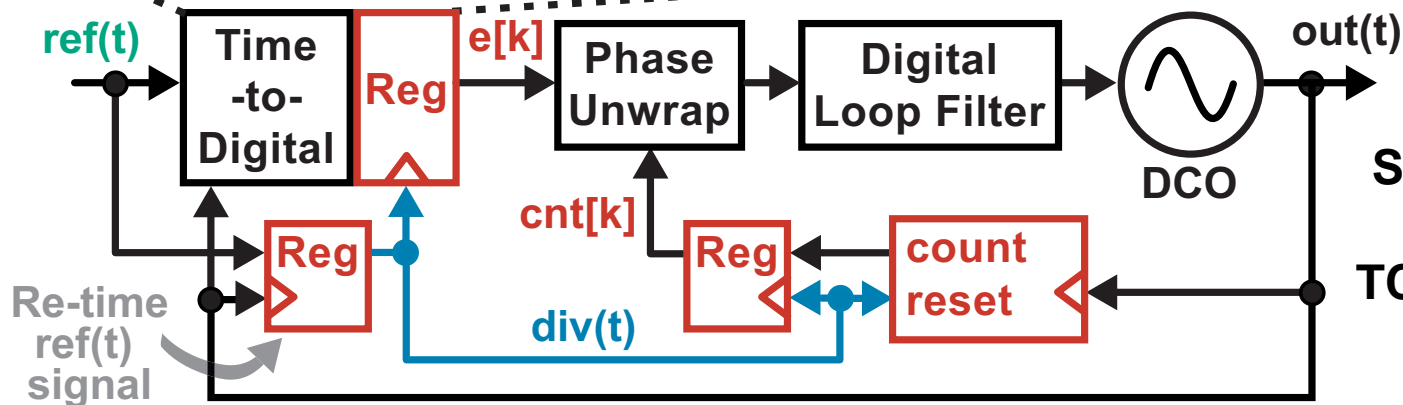 

Staszewski
et. al.,
TCAS II, Nov
2003



- Wrap $e[k]$ by feeding delay chain in TDC with $out(t)$
- Counter provides information of *when* wrapping occurs

Key Issues

 

- Counter, re-timing register, and delay stages of TDC must operate at very high speeds
 - Power consumption can be an issue
- Calibration of TDC scale factor required to achieve proper unwrapping of $e[k]$
 - Can be achieved continuously with relative ease
 - See Staszewski et. al, JSSC, Dec 2005

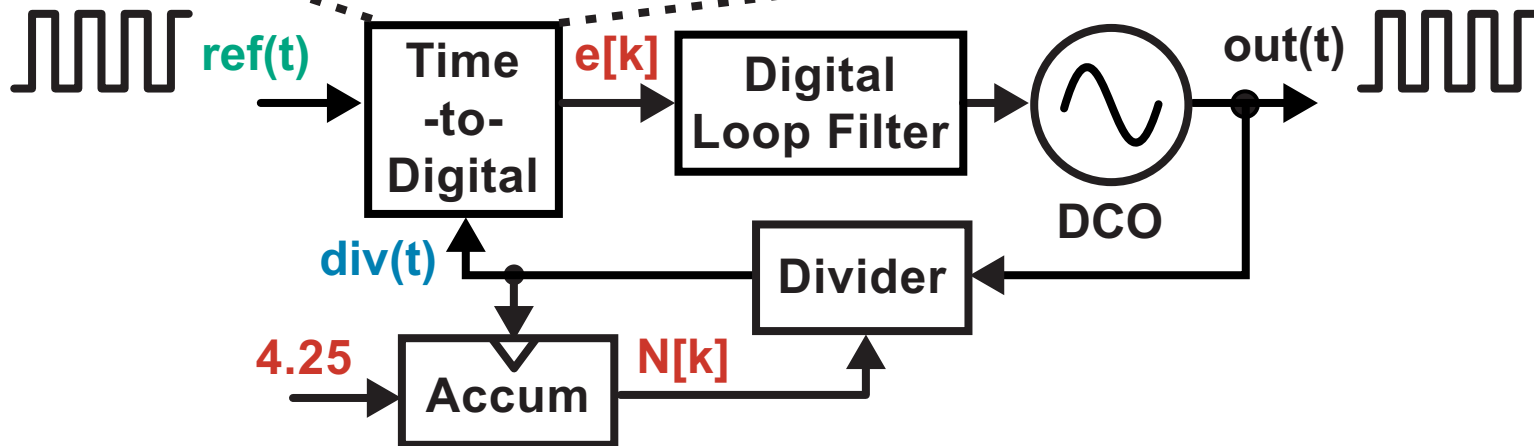 
Fractional-N Synthesizer Approach ($F_{out} = 4.25F_{ref}$)



- Accumulator guides the “swallowing” of VCO cycles
- Average divide value of $N = 4.25$ is achieved in this case


The Accumulator as a Phase “Observer”

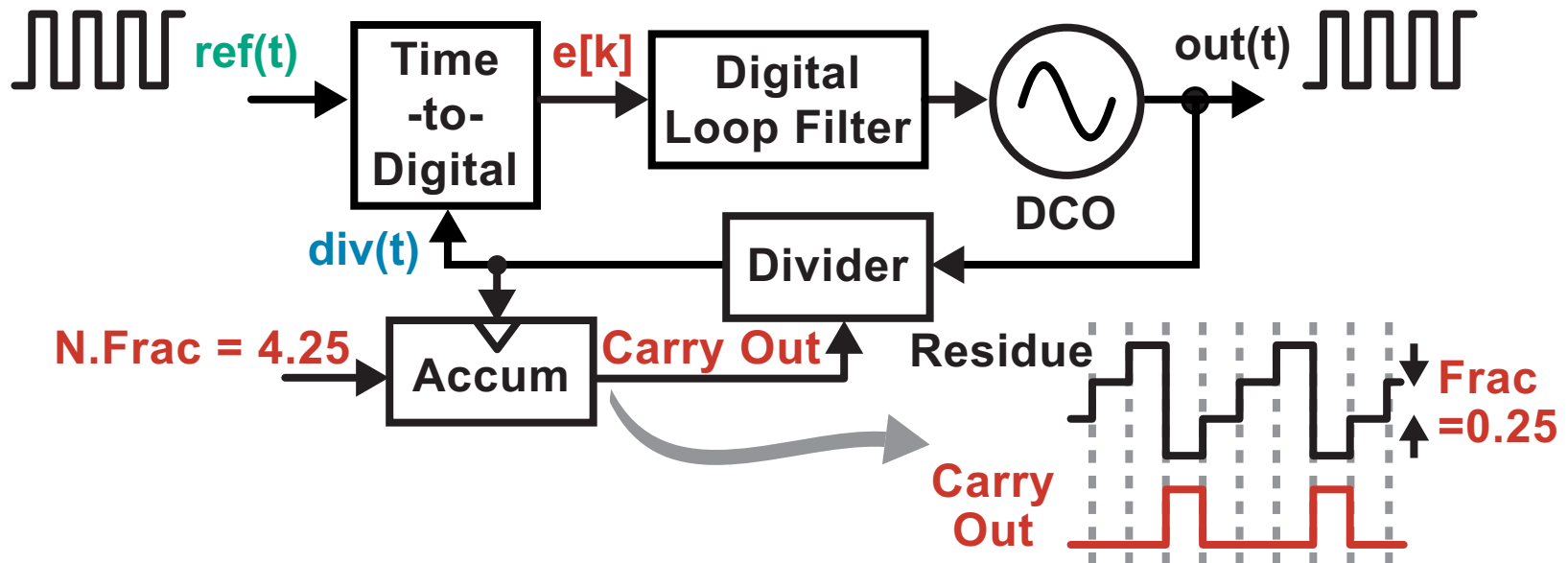- Accumulator residue corresponds to an estimate of the instantaneous phase error of the PLL
 - Fractional value (i.e., 0.25) yields the slope of the residue
- Carry out signal is asserted when the phase error deviation (i.e. residue) exceeds one VCO cycle
 - Carry out signal accurately predicts when a VCO cycle should be “swallowed”




Improve Dithering Using Sigma-Delta Modulation

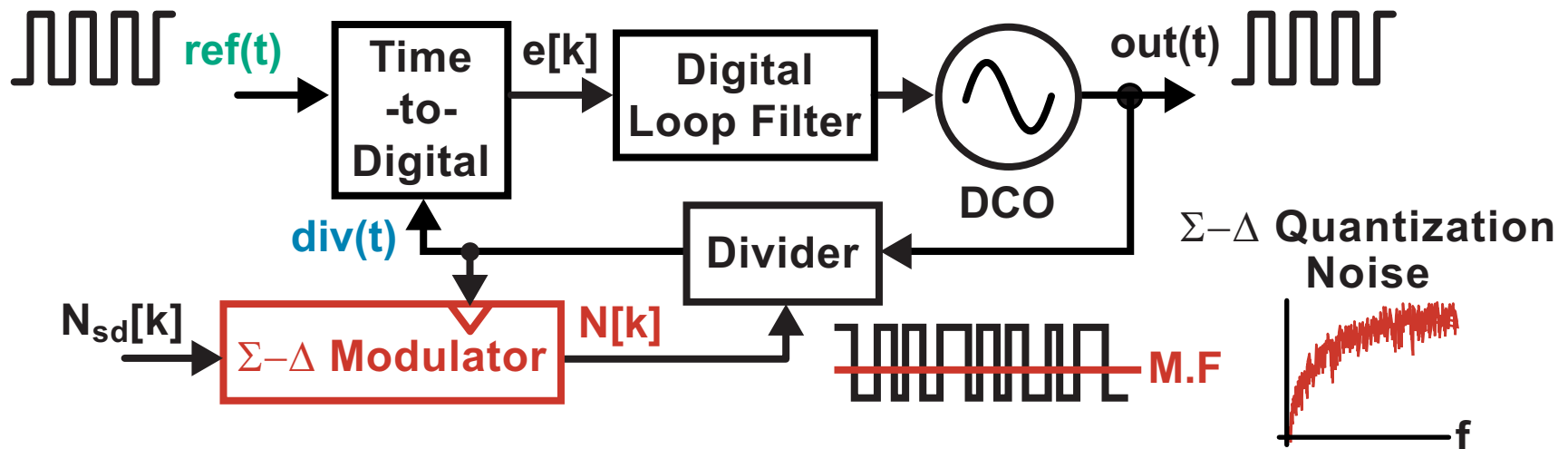- Provides improved noise performance over accumulator-based divide value dithering
 - Dramatic reduction of spurious noise
 - Noise shaping for improved in-band noise
 - Maintains bounded phase error signal
- Digital $\Sigma-\Delta$ fractional-N synthesizer architecture is directly analogous to analog $\Sigma-\Delta$ fractional-N synth.




 Model of Digital $\Sigma\text{-}\Delta$ Fractional-N PLL




- Divider model is expanded to include the impact of divide value variations

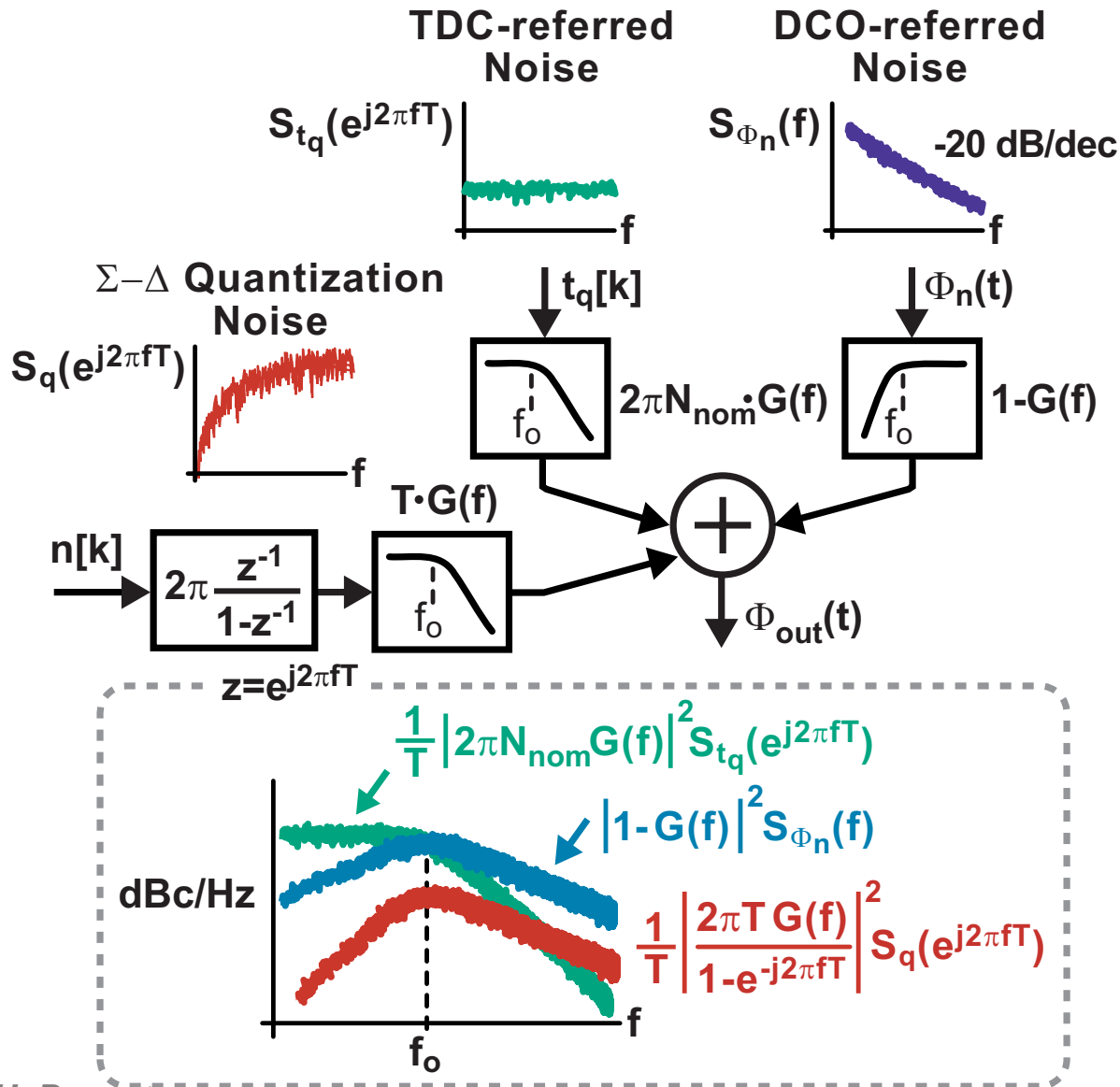Transfer Function View of Digital $\Sigma\text{-}\Delta$ Fractional-N PLL




- $\Sigma\text{-}\Delta$ quantization noise now impacts the overall PLL phase noise
 - High PLL bandwidth will increase its impact
- Digital PLL implementation simplifies quantization noise cancellation

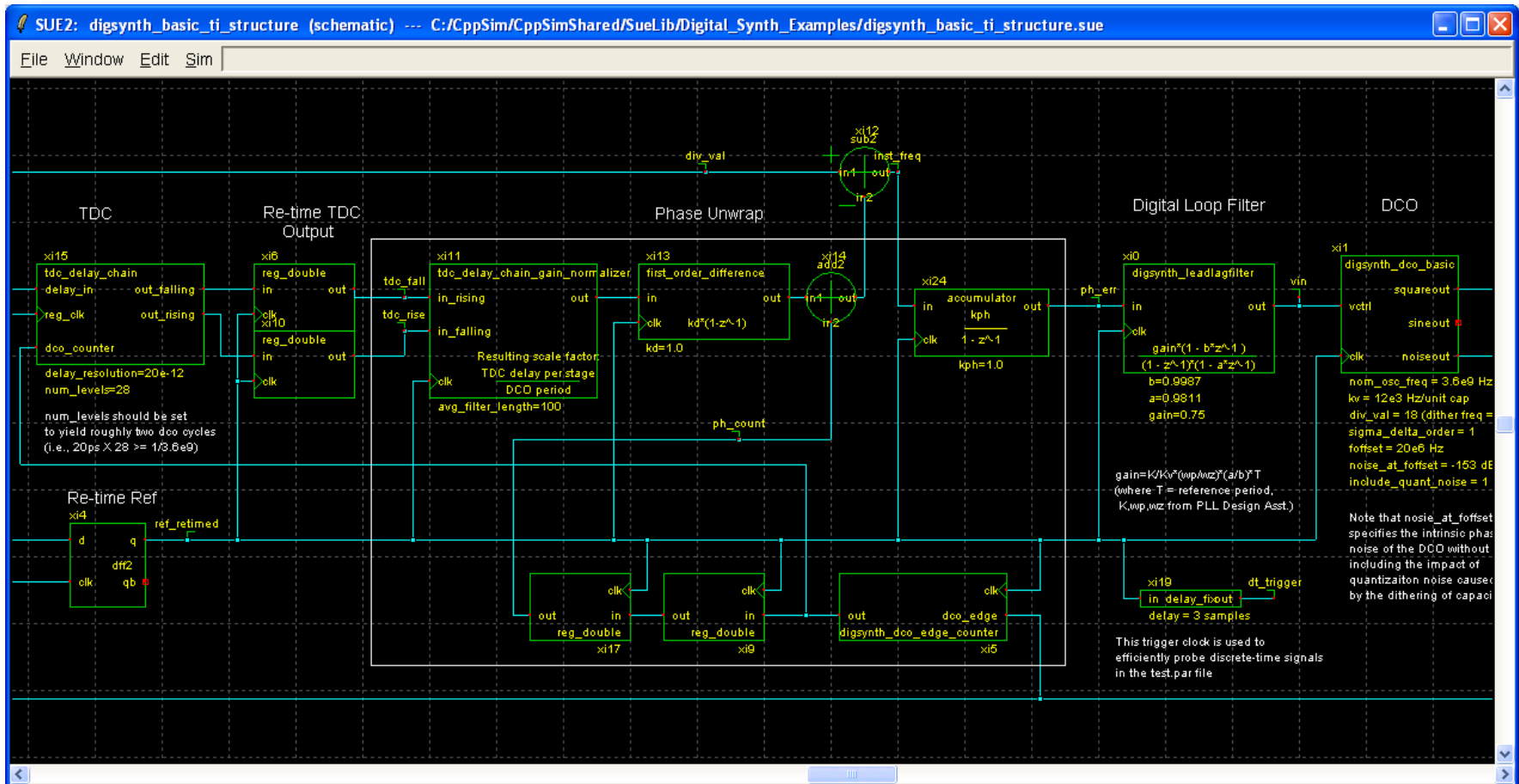CppSim Behavioral Model of TI Digital Synthesizer




- Implements basic version of TI “all-digital” synthesizer with parameters we calculated in this tutorial

 Comparing Behavioral Simulation to Calculations



■ **Calculations validated by simulation results!**

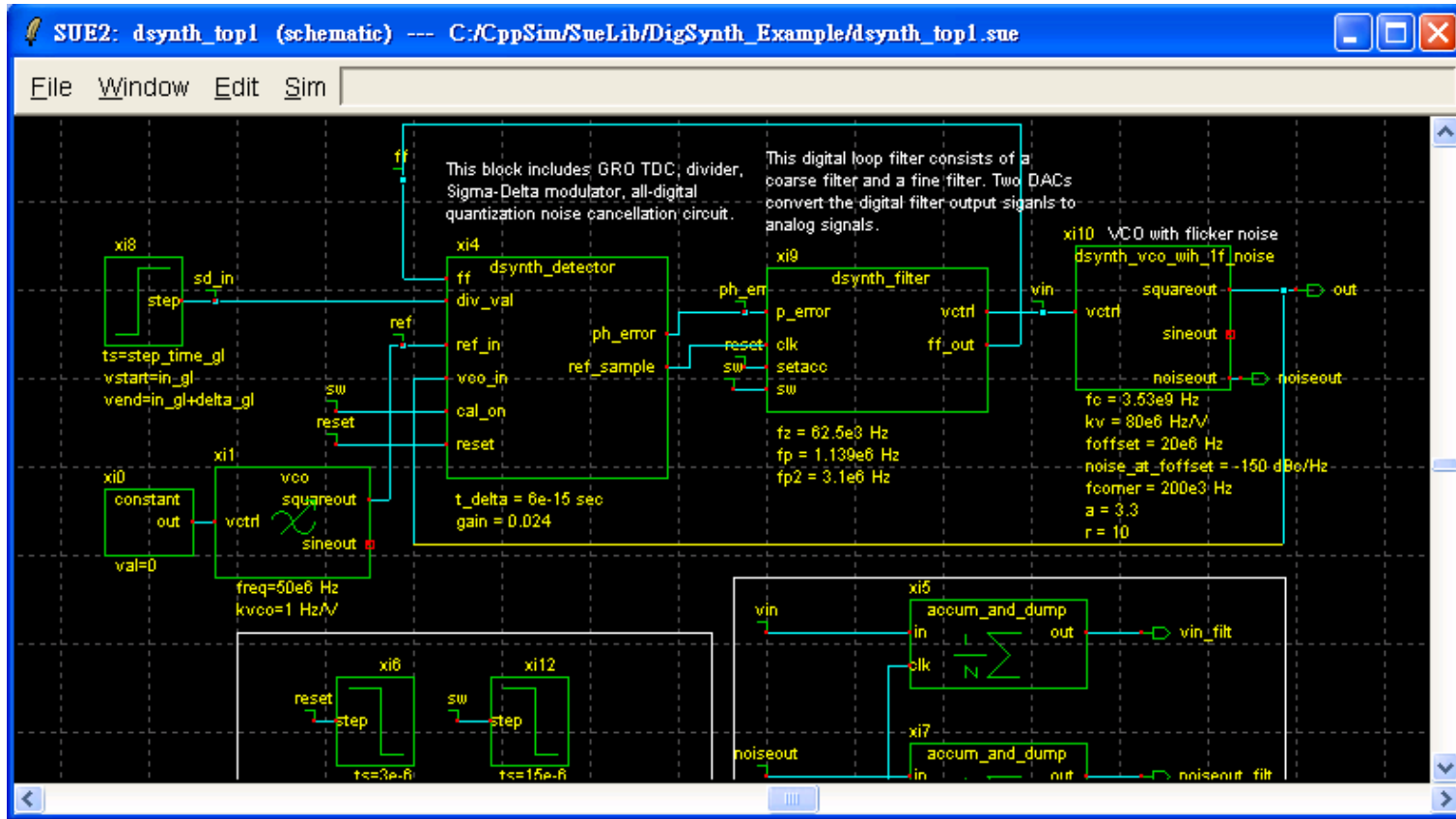Behavioral Simulation of a Digital Fractional-N PLL



- Check out the CppSim tutorial:
 - Design of a Low-Noise Wide-BW 3.6GHz Digital Σ - Δ Fractional-N Frequency Synthesizer Using the PLL Design Assistant and CppSim

<http://www.cppsim.com>

Summary of Digital Frequency Synthesizers

- **Digital Phase-Locked Loops look extremely promising for future applications**
 - Very amenable to future CMOS processes
 - Excellent performance can be achieved
- **TDC structures are an exciting research area**
 - Ideas from A-to-D conversion can be applied
- **Analysis of digital PLLs is similar to analog PLLs**
 - PLL bandwidth is often chosen for best noise performance
 - TDC (or Ref) noise dominates at low frequency offsets
 - DCO noise dominates at high frequency offsets
- **Behavioral simulation tools such as CppSim allow architectural investigation and validation of calculations**

Innovation of future digital PLLs will involve joint circuit/algorithm development