

***Short Course On
Phase-Locked Loops and Their Applications
Day 4, PM Lecture***

Examples of Leveraging Digital Techniques in PLLs



**Michael Perrott
August 14, 2008**

**Copyright © 2008 by Michael H. Perrott
All rights reserved.**

Outline

- **Example of high performance digital frequency synthesizer**
 - **Goal: wide bandwidth (500 kHz) and low phase noise**
 - **Techniques to achieve low implementation complexity**
- **Example of high performance mixed-signal clock and data recovery**
 - **Goal: low jitter and full integration with compact area**
 - **Techniques to achieve low implementation complexity**

Going Digital ...

  


Staszewski et. al.,
TCAS II, Nov 2003

- Digital loop filter: compact area, insensitive to leakage
- Challenges:
 - Time-to-Digital Converter (TDC)
 - Digitally-Controlled Oscillator (DCO)

Examine Noise Performance: *Narrow-Bandwidth Case*

 
- **Assumptions:**
 - **delay = 20ps**
 - **carrier freq. = 3.6GHz**
 - **reference freq. = 50MHz**
 - **PLL BW = 50kHz**
 - **3rd order $\Delta\Sigma$**



- VCO noise dominates performance everywhere ...
- Don't need very high TDC resolution
- $\Delta\Sigma$ fractional-N quantization noise is not an issue

Examine Noise Performance: *Wide-Bandwidth Case*

 - **Assumptions:**
 - delay = 20ps
 - carrier freq. = 3.6GHz
 - reference freq. = 50MHz
 - PLL BW = 500kHz
 - 3rd order $\Delta\Sigma$




- Noise dominated by TDC at low frequencies
- Noise dominated by $\Delta\Sigma$ fractional-N noise at high frequencies

To Meet High Performance Applications like GSM....


Assumptions:

- delay = 6ps
- carrier freq. = 3.6GHz
- reference freq. = 50MHz
- PLL BW = 500kHz
- 3rd order $\Delta\Sigma$ (20dB lower)

 




Need 6-ps TDC resolution and 20dB cancellation of $\Delta-\Sigma$ fractional-N noise to achieve 500kHz bandwidth

Proposed Digital Wide BW Synthesizer

 


- **Gated-ring-oscillator (GRO) TDC** achieves low in-band noise
- **All-digital quantization noise cancellation** achieves low out-of-band noise
- **Design goals:**
 - 3.6-GHz carrier, 500-kHz bandwidth
 - <-100dBc/Hz in-band, <-150 dBc/Hz at 20 MHz offset

  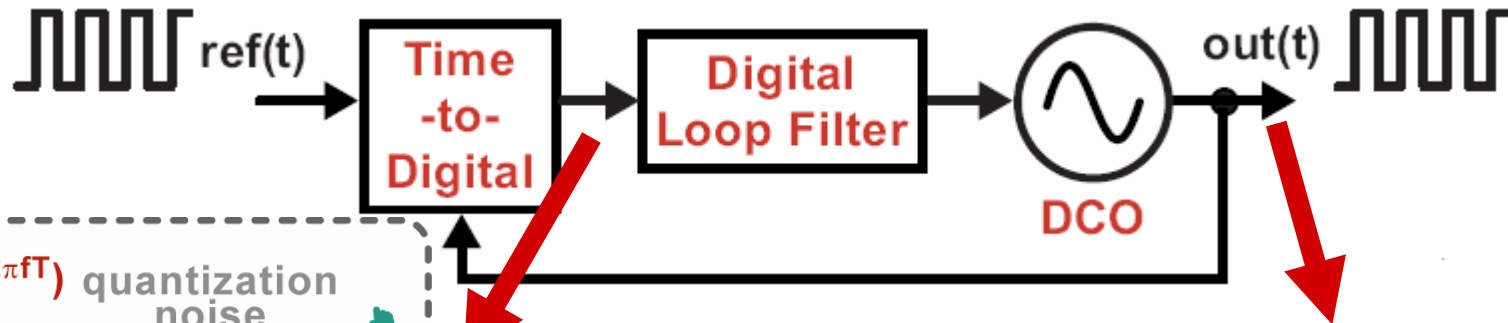Key Enablers: GRO and $\Delta\Sigma$ Frac-N Noise Cancellation



- GRO offers low noise at low frequency offsets
- $\Delta\Sigma$ fractional-N noise cancellation offers low noise at high frequency offsets


Proposed Multi-Path GRO TDC

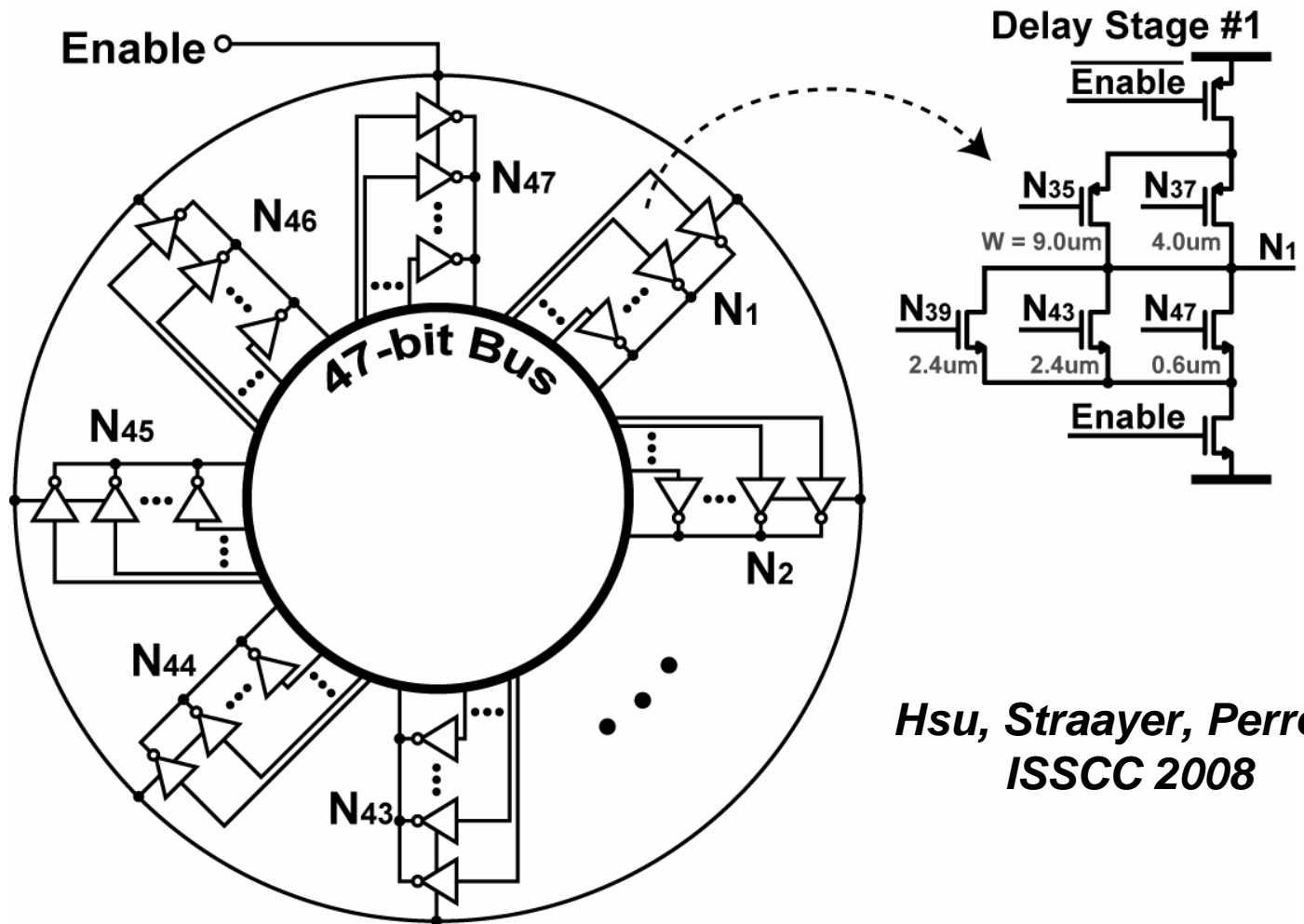

Hsu, Straayer, Perrott
ISSCC 2008


- Average delay per stage is reduced from 35ps to 6ps
- Noise shaping further improves effective resolution

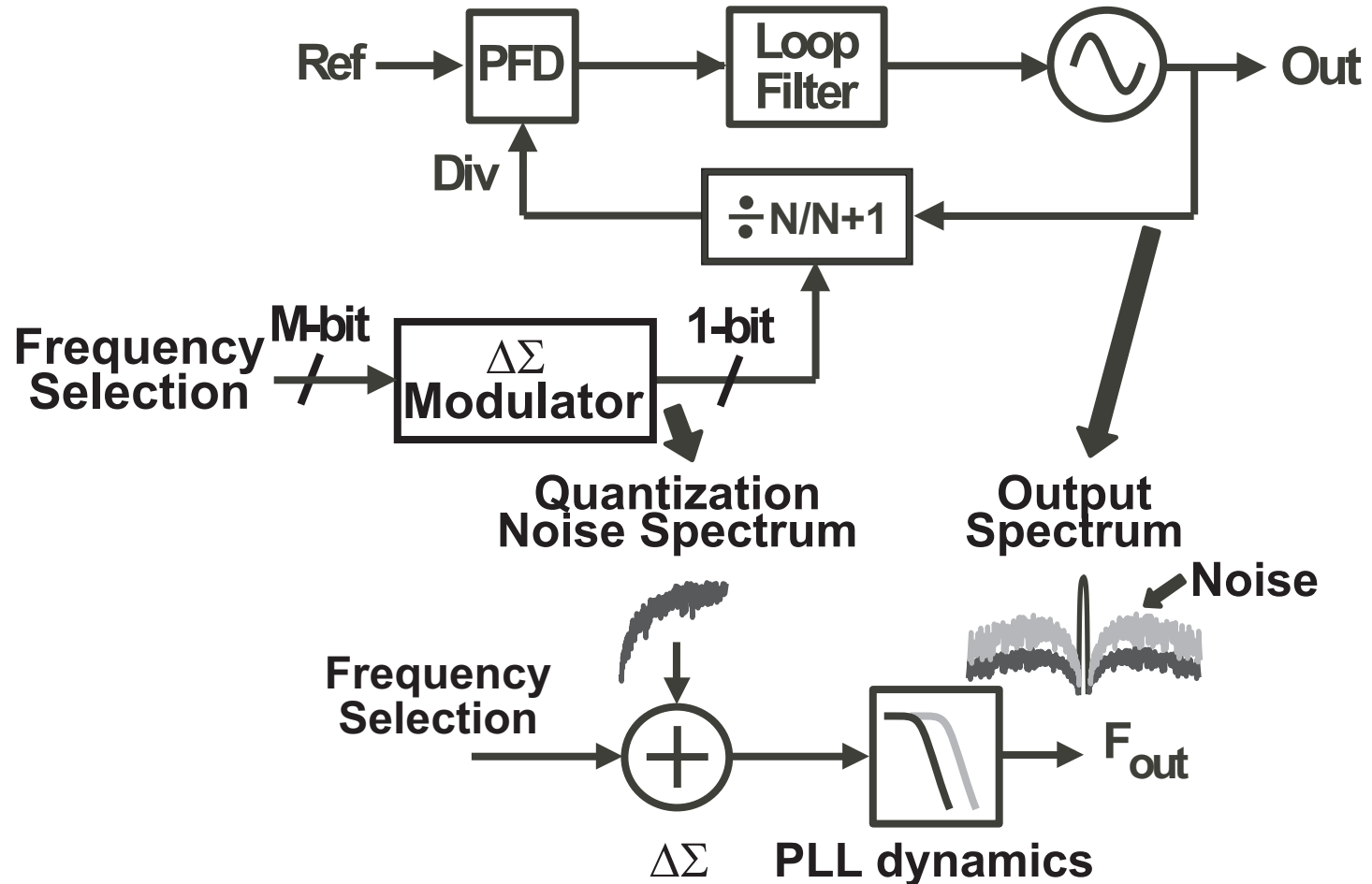Reduction of Fractional-N Quantization Noise



- Increasing PLL bandwidth increases impact of $\Delta\Sigma$ fractional-N noise
 - Cancellation offers a way to counter this effect

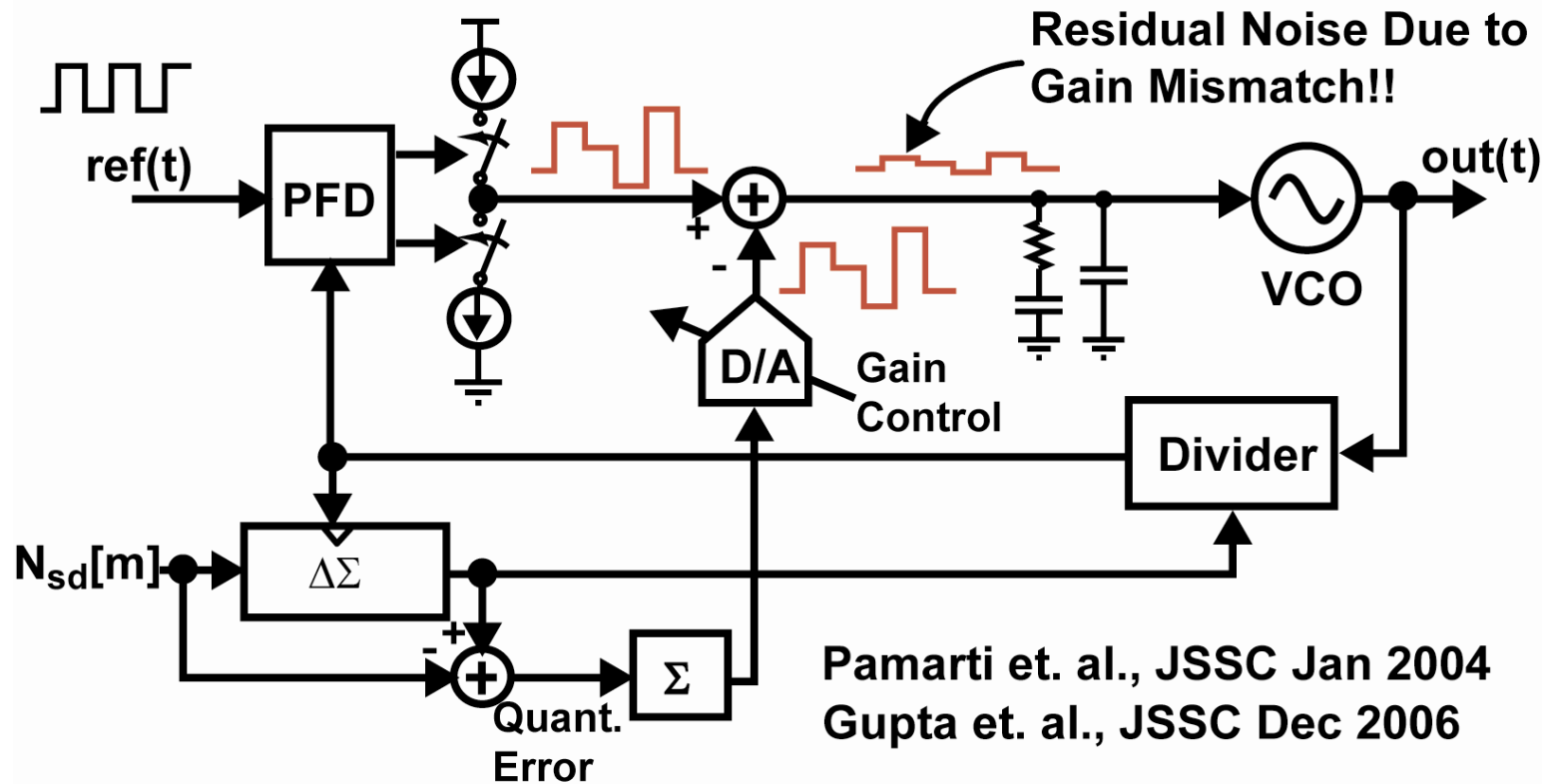
Previous Analog Quantization Noise Cancellation



- Phase error due to $\Delta\Sigma$ is predicted by accumulating $\Delta\Sigma$ quantization error
- Gain matching between PFD and D/A must be precise


Matching in *analog* domain limits performance

 Proposed All-digital Quantization Noise Cancellation




- Scale factor determined by simple digital correlation
- Analog non-idealities such as DC offset are completely eliminated

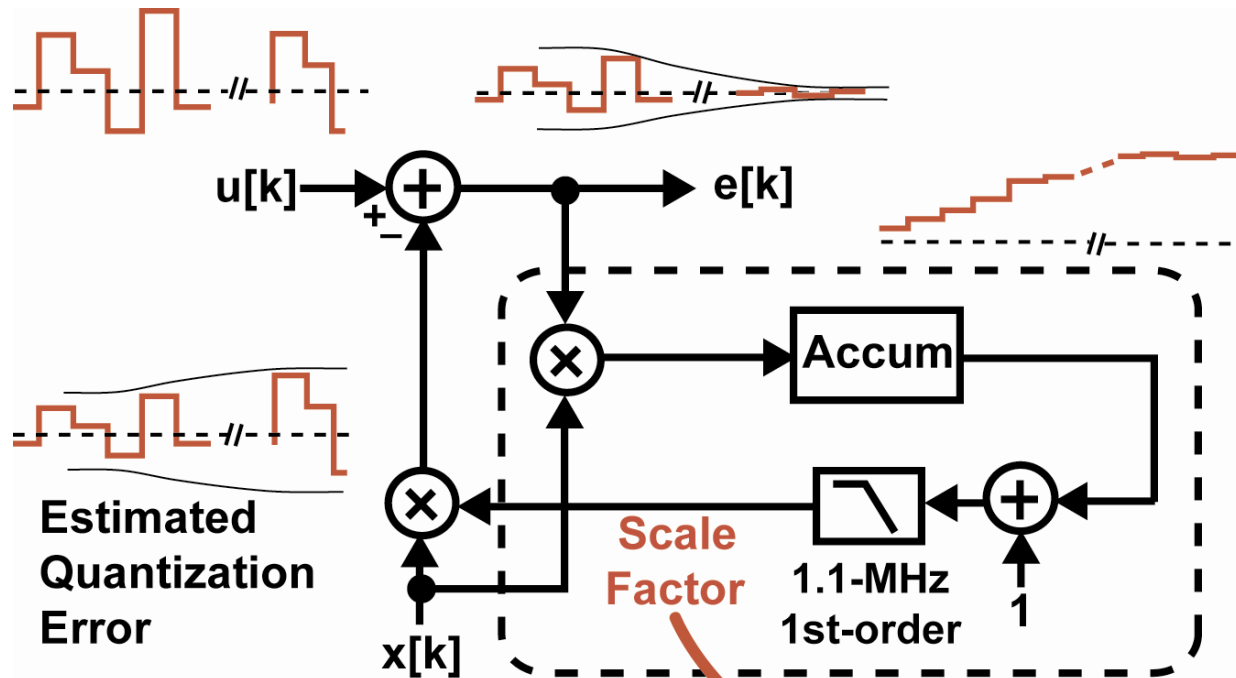
Details of Proposed Quantization Noise Cancellation



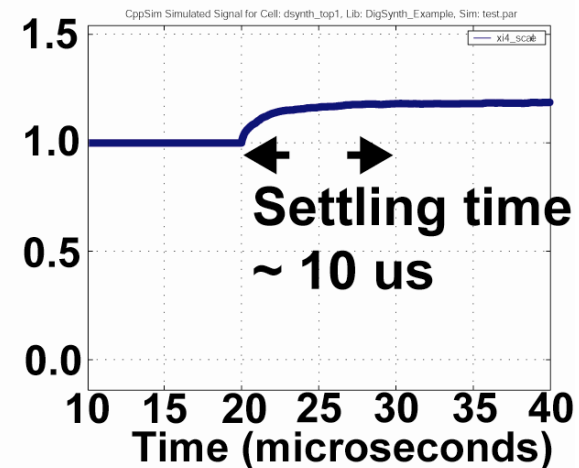- Correlator out is accumulated and filtered to achieve scale factor
 - Settling time chosen to be around 10 us
- See *analog* version of this technique in *Swaminathan et.al., ISSCC 2007*




Overall Synthesizer Architecture

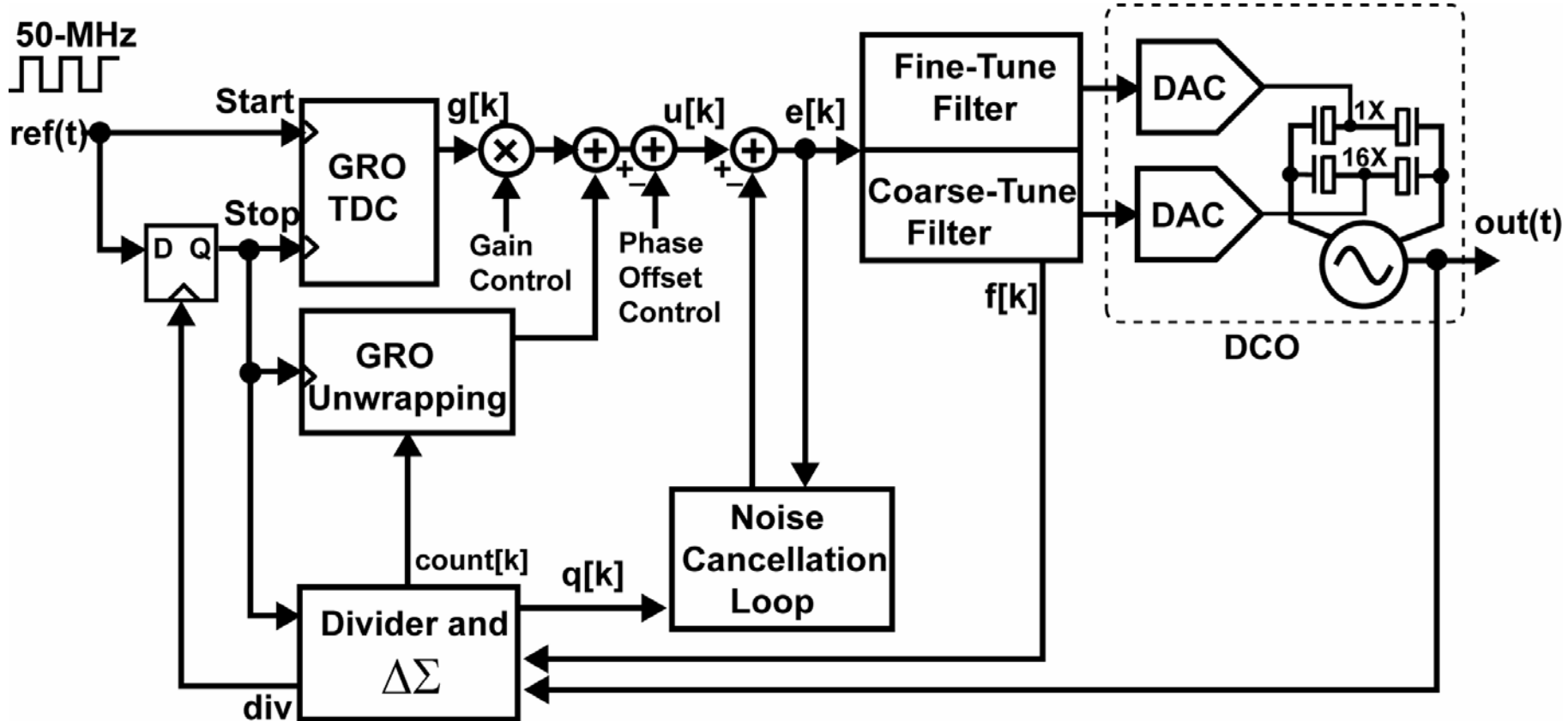

Note: Detailed behavioral simulation model available at <http://www.cppsim.com>


Dual-Port LC VCO

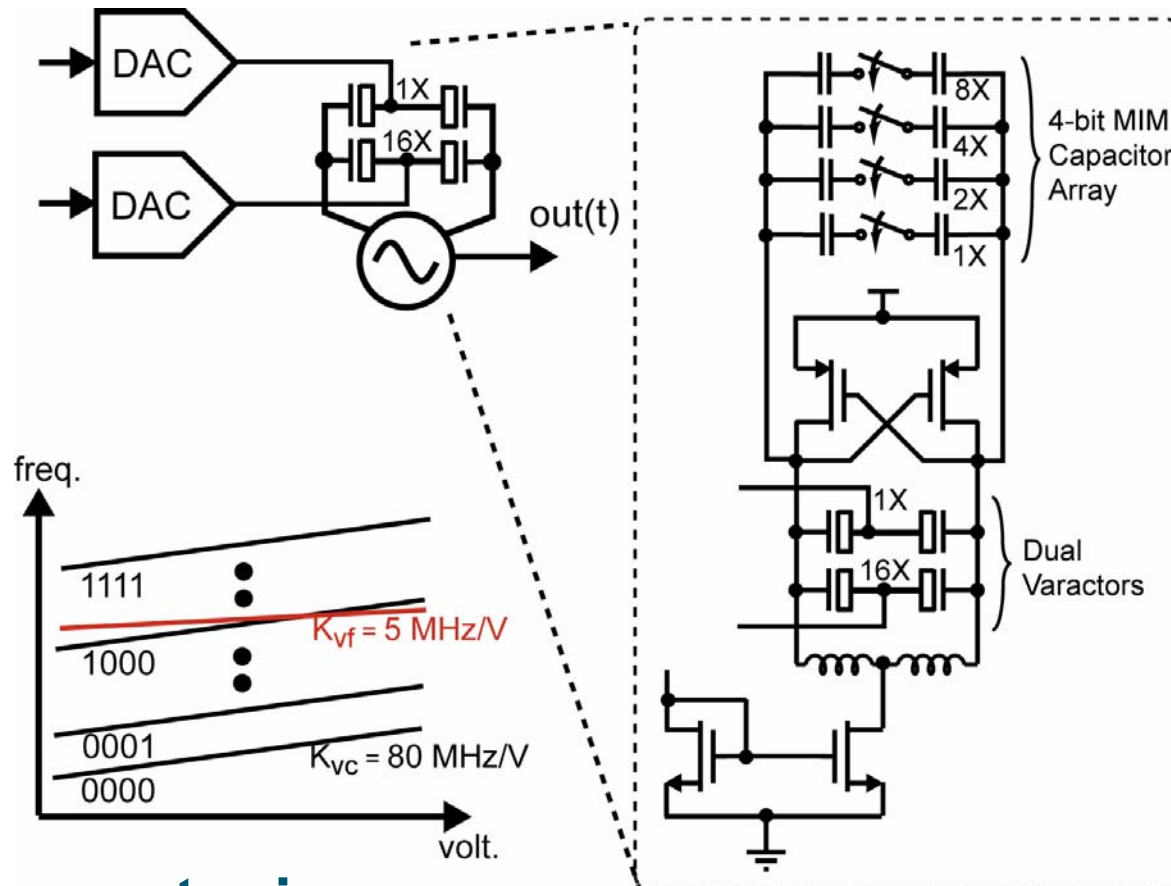

■ Frequency tuning:


- Use a small 1X varactor to minimize noise sensitivity
- Use another 16X varactor to provide moderate range
- Use a four-bit capacitor array to achieve 3.3-4.1 GHz range

VCO Varactor

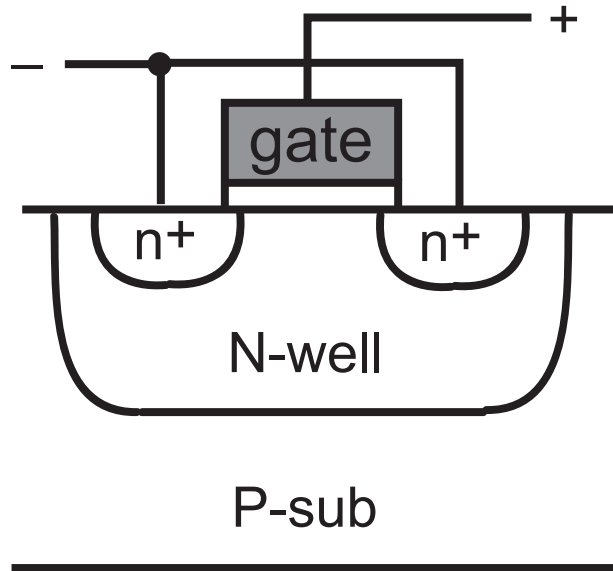


- **Accumulation-mode varactor used for both coarse and fine frequency tuning**
 - Coarse varactor is 16 times the size of fine varactor
 - Provides good ratio of capacitance versus voltage variation with limited supply voltage

Switched Structure for Coarse Cap Tuning

 

- **Ma0 provides low differential resistance for caps**
 - Ma3 and Ma4 provide low bias voltage to minimize Ma0 channel resistance when Ma0 is turned on
 - Minimizes impact on Q of tank
- **Ma2 provides high bias when Ma0 is turned off**
 - Keeps voltage at n1 and n2 defined and prevents turn-on of Ma0

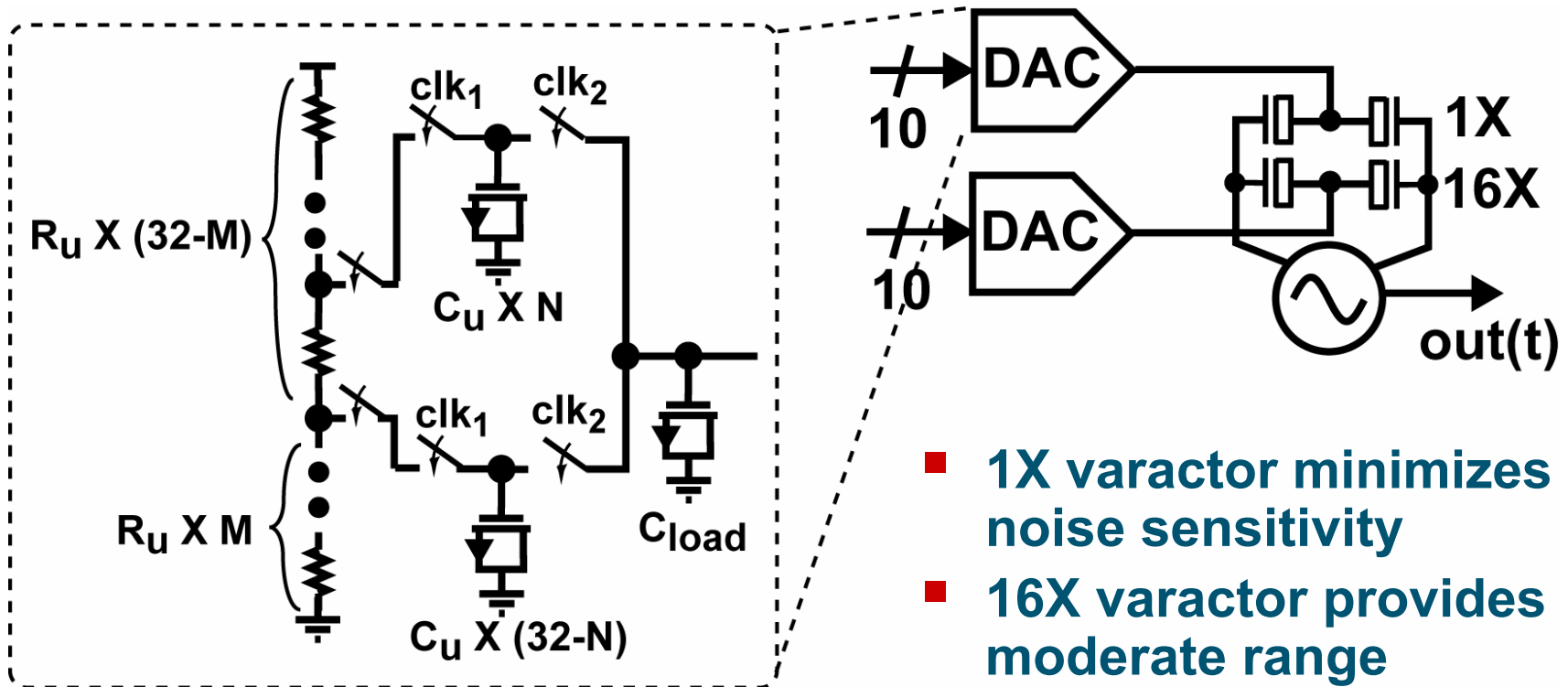Digitally-Controlled Oscillator with Passive DAC




- **Goals of 10-bit DAC**

- Monotonic
- Minimal active circuitry and no transistor bias currents
- Full-supply output range


- **1X varactor minimizes noise sensitivity**
- **16X varactor provides moderate range**
- **A four-bit capacitor array covers 3.3-4.1GHz**

Operation of 10-bit Passive DAC (Step 1)

 


- 5-bit resistor ladder; 5-bit switch-capacitor array
- Step 1: *Capacitors Charged*
 - Resistor ladder forms $V_L = M/32 \cdot V_{DD}$ and $V_H = (M+1)/32 \cdot V_{DD}$, where M ranges from 0 to 31
 - N unit capacitors charged to V_H , and $(32-N)$ unit capacitors charged to V_L

Operation of 10-bit Passive DAC (Step 2)

 

- **Step 2: Disconnect Capacitors from Resistors, Then Connect Together**
 - Achieves DAC output with first-order filtering
 - Bandwidth = $32 \cdot C_u / (2\pi \cdot C_{load}) \cdot 50\text{MHz}$
 - Determined by capacitor ratio
 - Easily changed by using different C_{load}


Now Let's Examine Divider ...

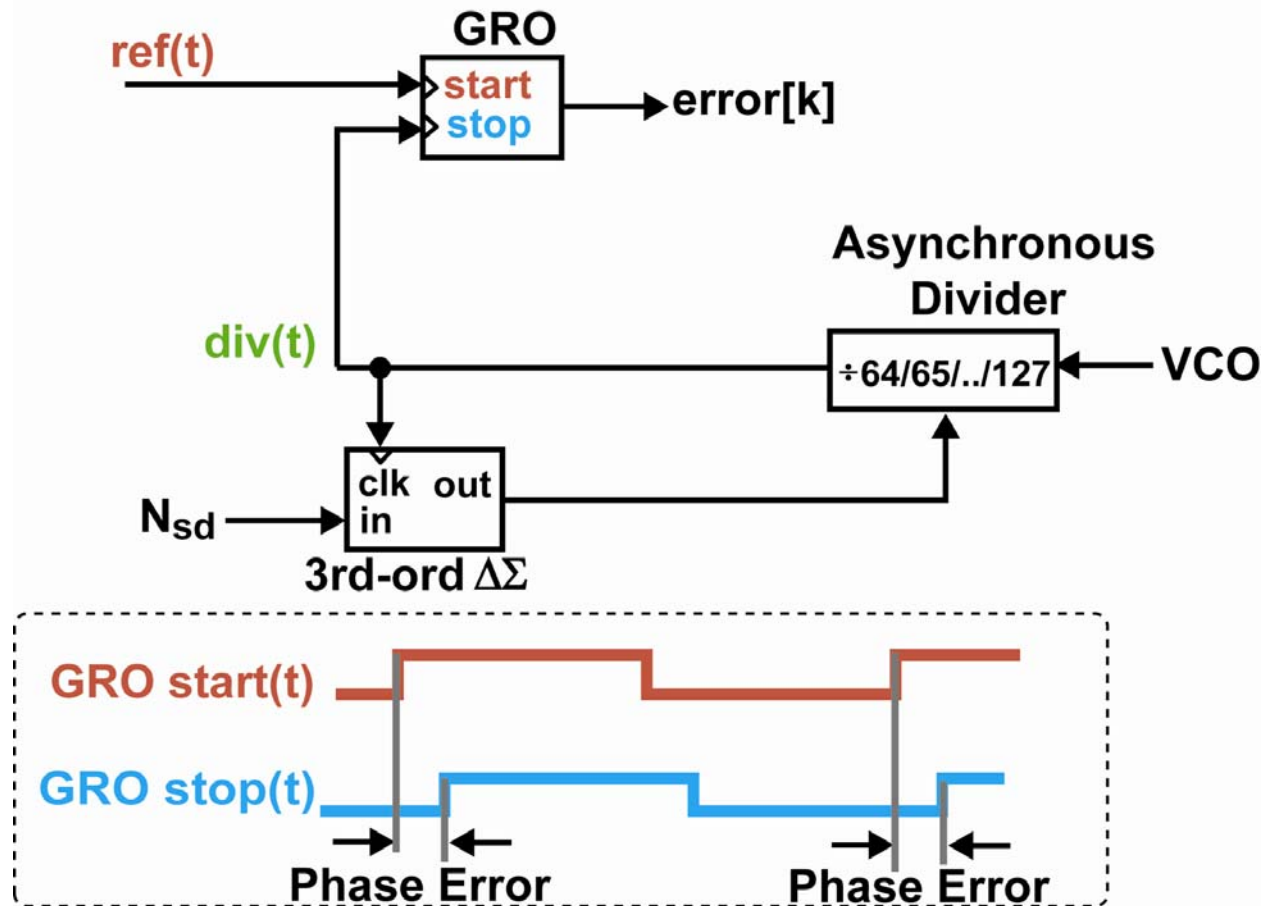

■ Issues:


- GRO range must span entire reference period during initial lock-in

Proposed Divider Structure

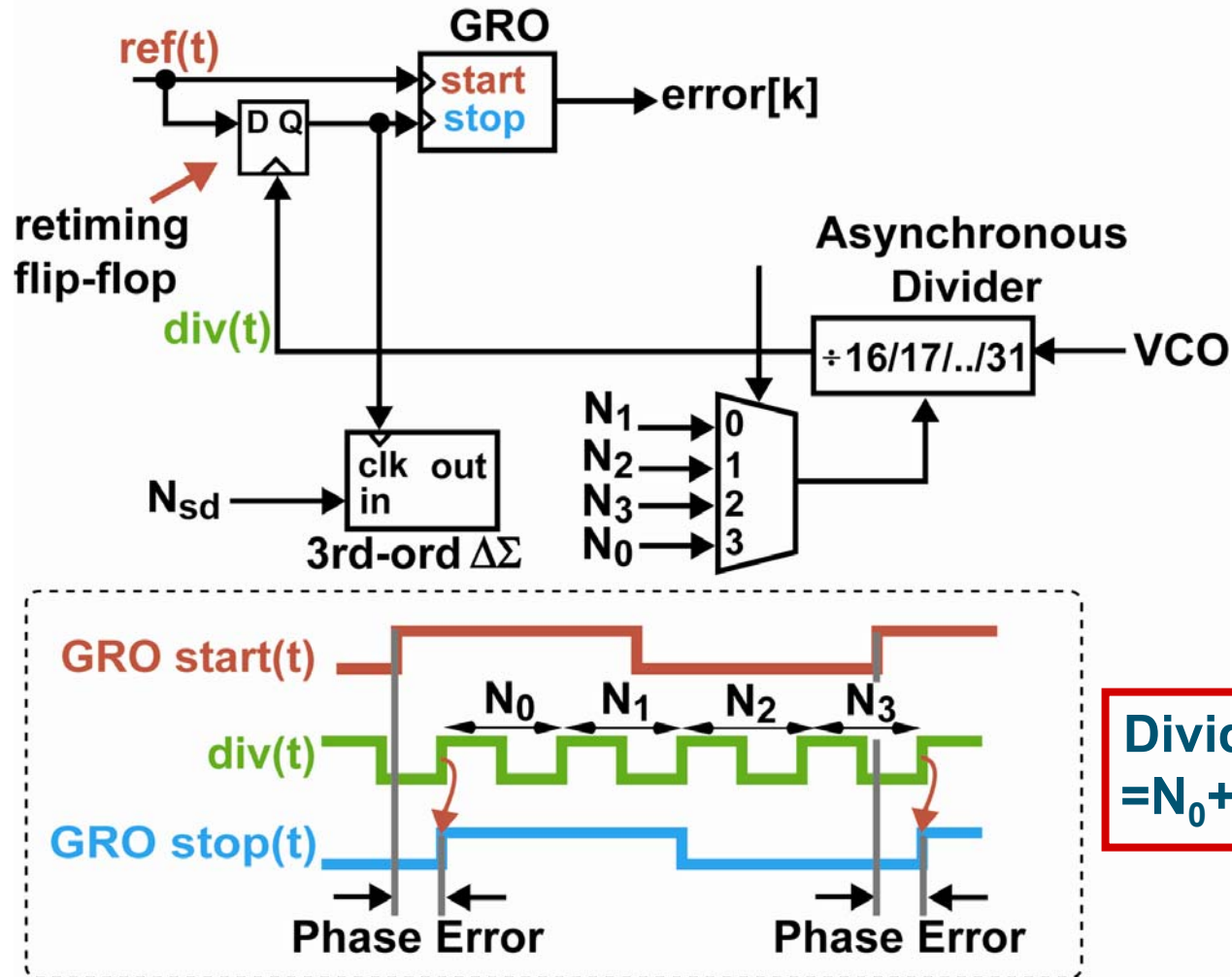


- Resample reference with 4x division frequency
 - Lowers GRO range to one fourth of the reference period

Proposed Divider Structure (cont'd)

 


- Place $\Delta\Sigma$ dithered edge away from GRO edge
 - Prevents extra jitter due to divide-value dependent delay

Asynchronous Divider Structure

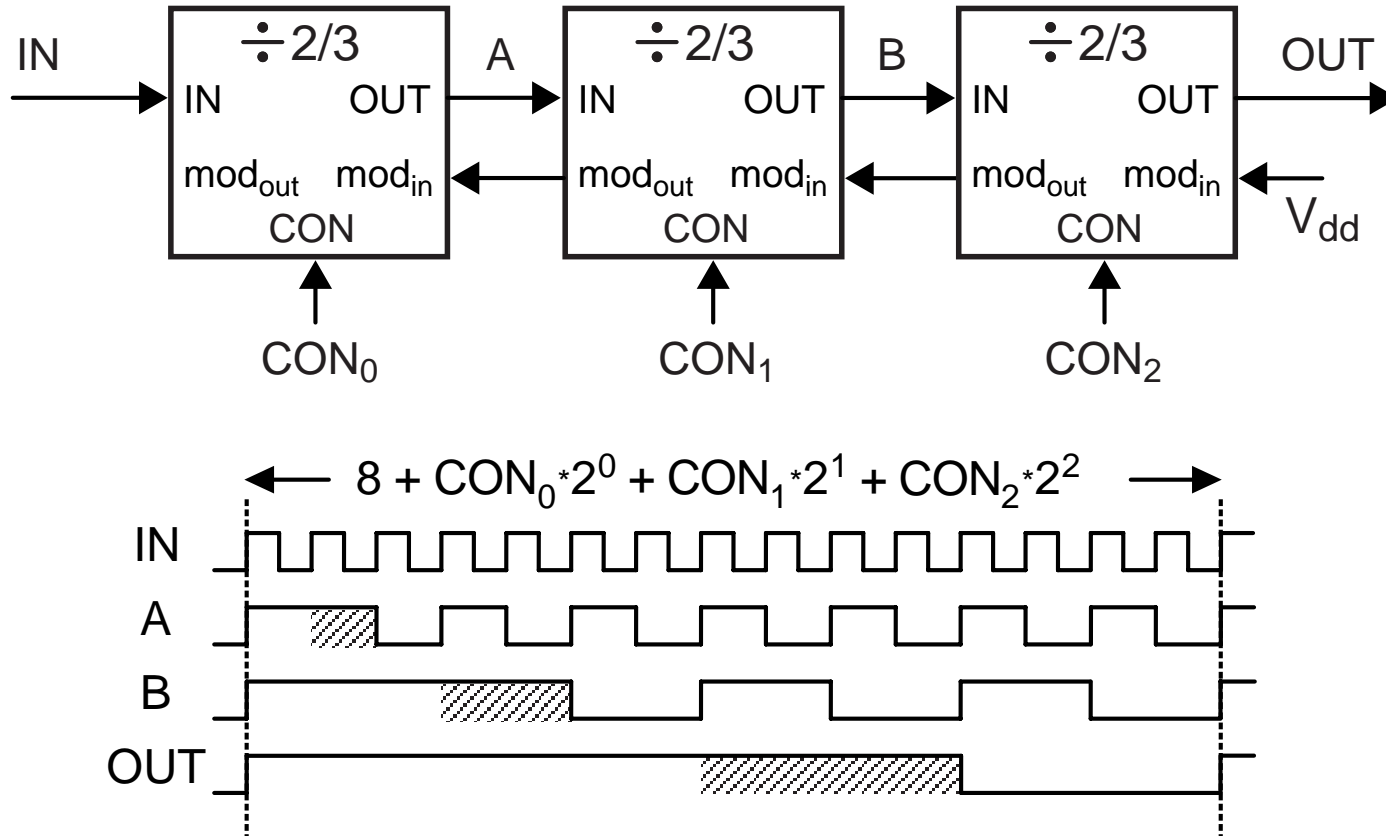


- Vaucher et. al., “A Family of Low-Power Truly Modular Programmable Dividers ...”, JSSC, July 2000

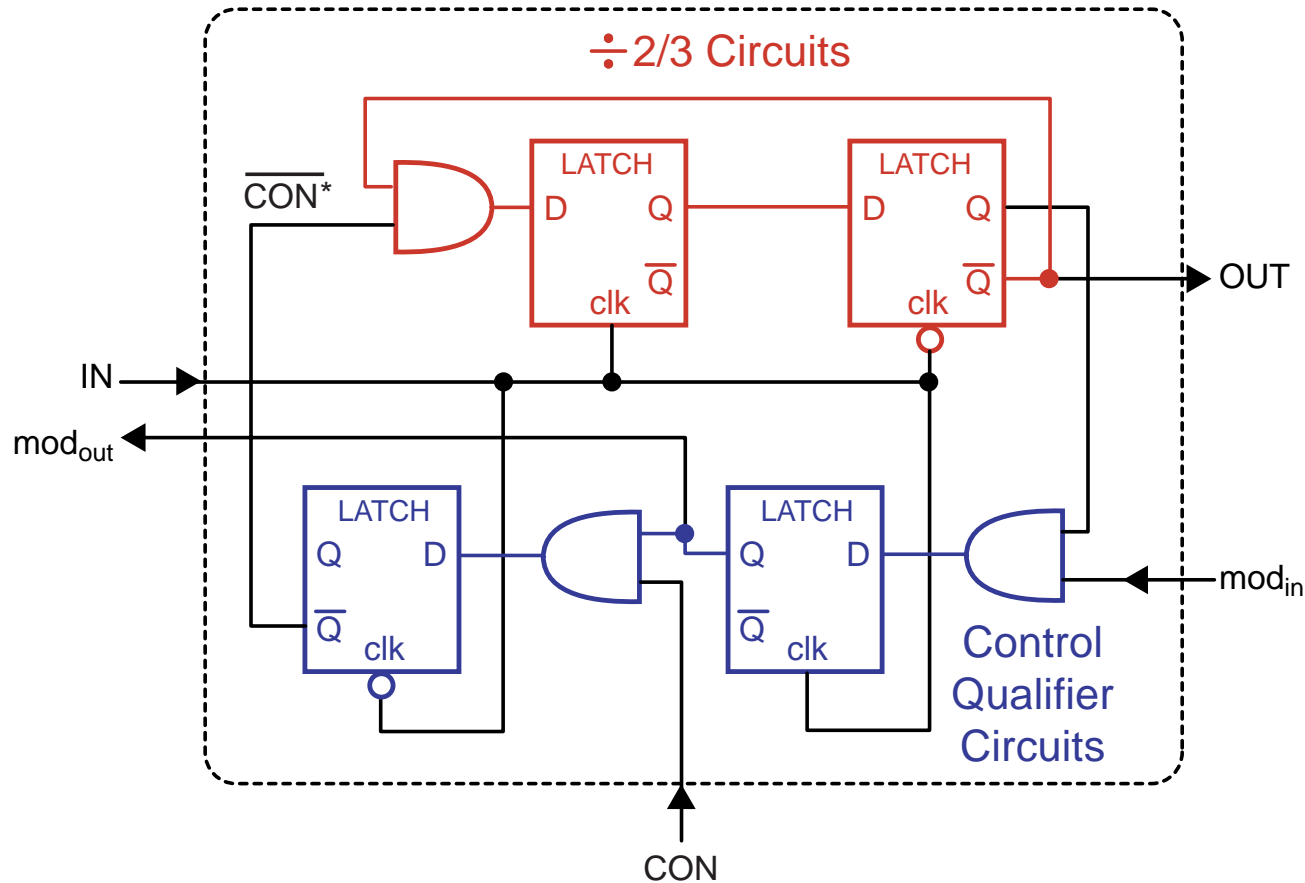Implementation of 2/3 Sections in Modular Approach




- Same as discussed on day 2 of this class

Implementation of 2/3 Section

 


- Combines logic gates into TSPC latches
 - Requires only 1 ma at 3.6 GHz operation in 0.13u CMOS!

Dual-Path Loop Filter

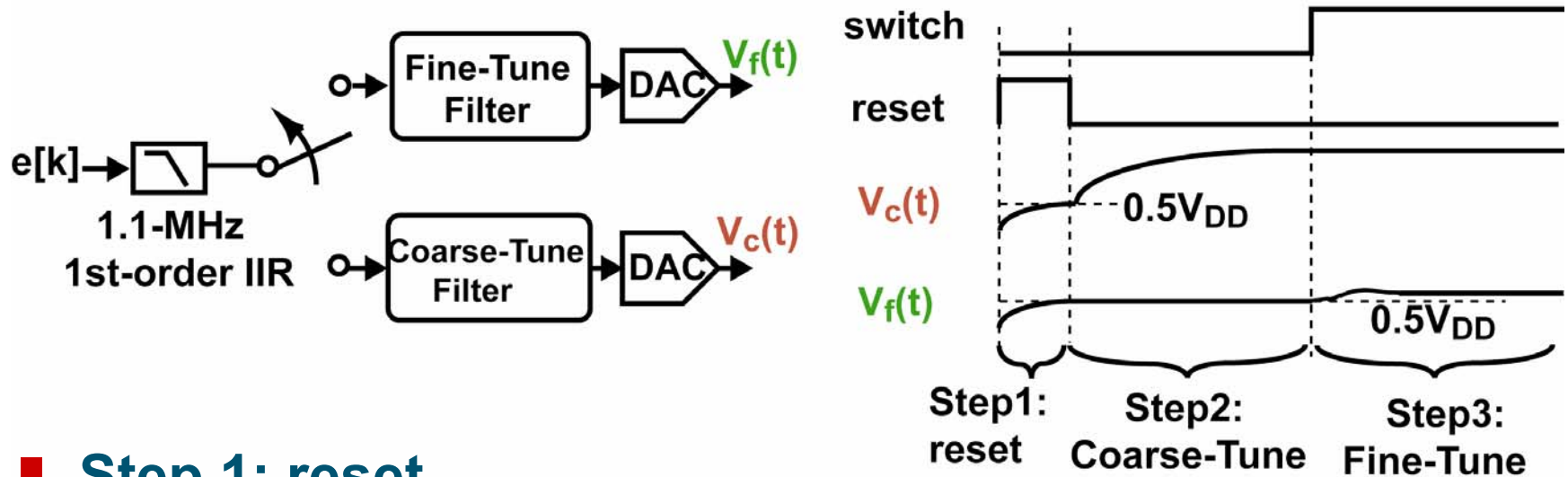



- **Step 1: reset**
- **Step 2: frequency acquisition**
 - $V_c(t)$ varies
 - $V_f(t)$ is held at midpoint
- **Step 3: steady-state lock conditions**
 - $V_c(t)$ is frozen to take quantization noise away
 - $\Delta\Sigma$ quantization noise cancellation is enabled

Fine-Path Loop Filter

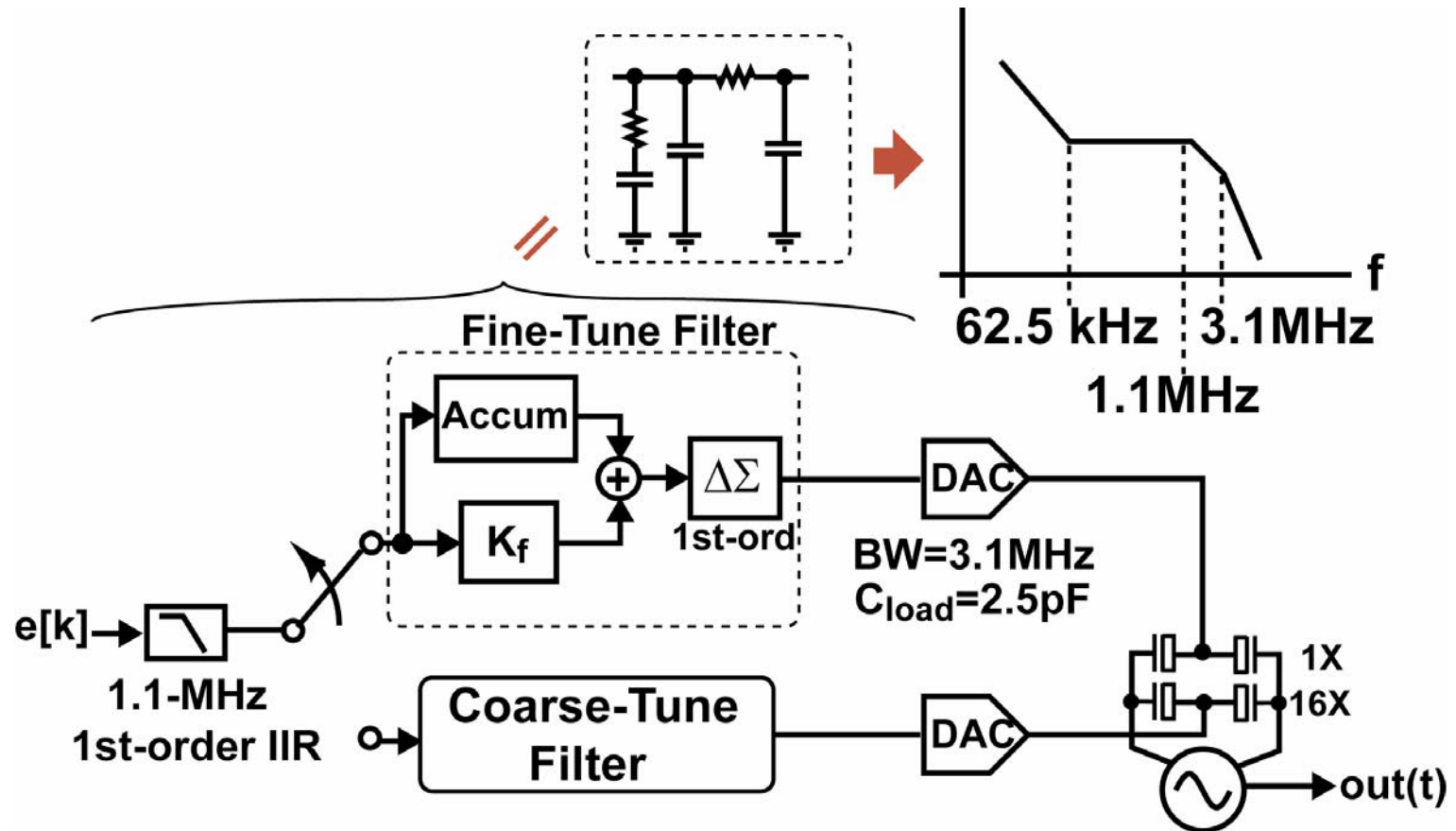


- Equivalent to an analog lead-lag filter
 - Set zero (62.5kHz) and first pole (1.1MHz) digitally
 - Set second pole (3.1MHz) by capacitor ratio
- First-order $\Delta\Sigma$ reduces in-band quantization noise

 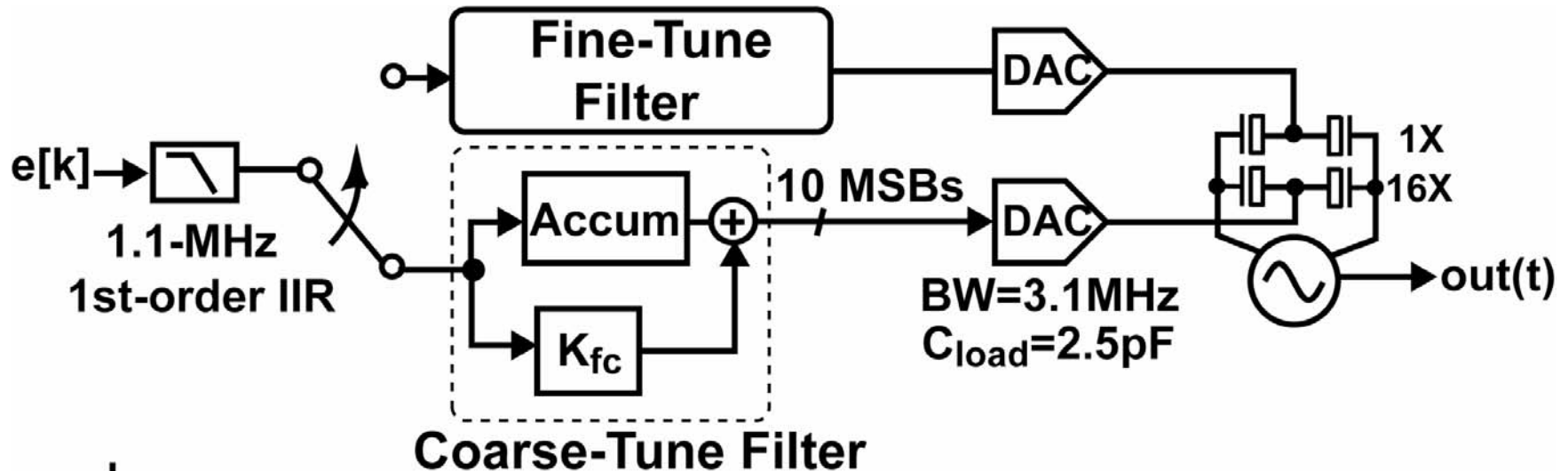Same Technique Poses Problems for Coarse-Tune




- DAC thermal noise impacts performance due to the higher coarse VCO gain
 - Can we somehow lower the DAC bandwidth?

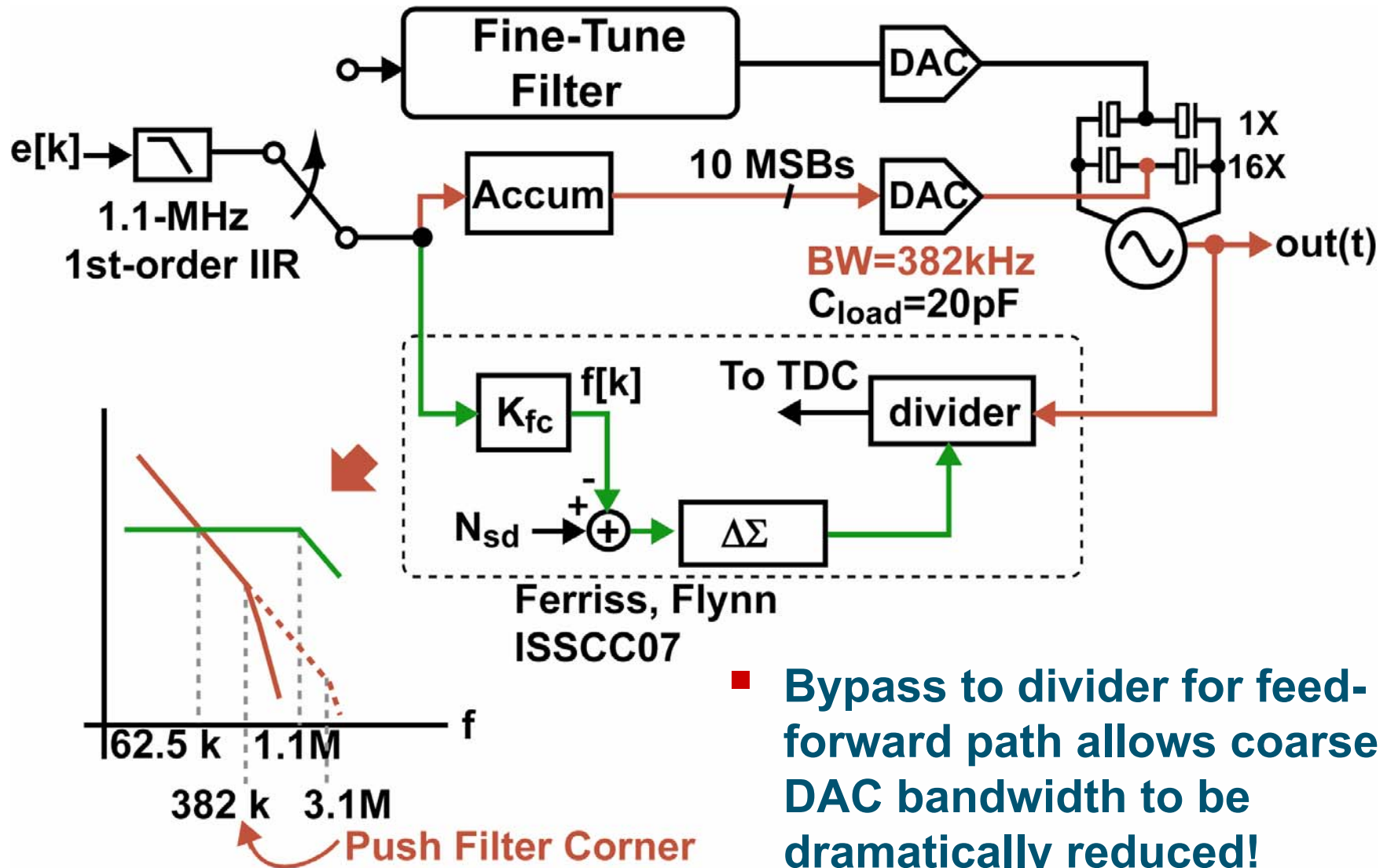Fix: Leverage the Divider as a Signal Path




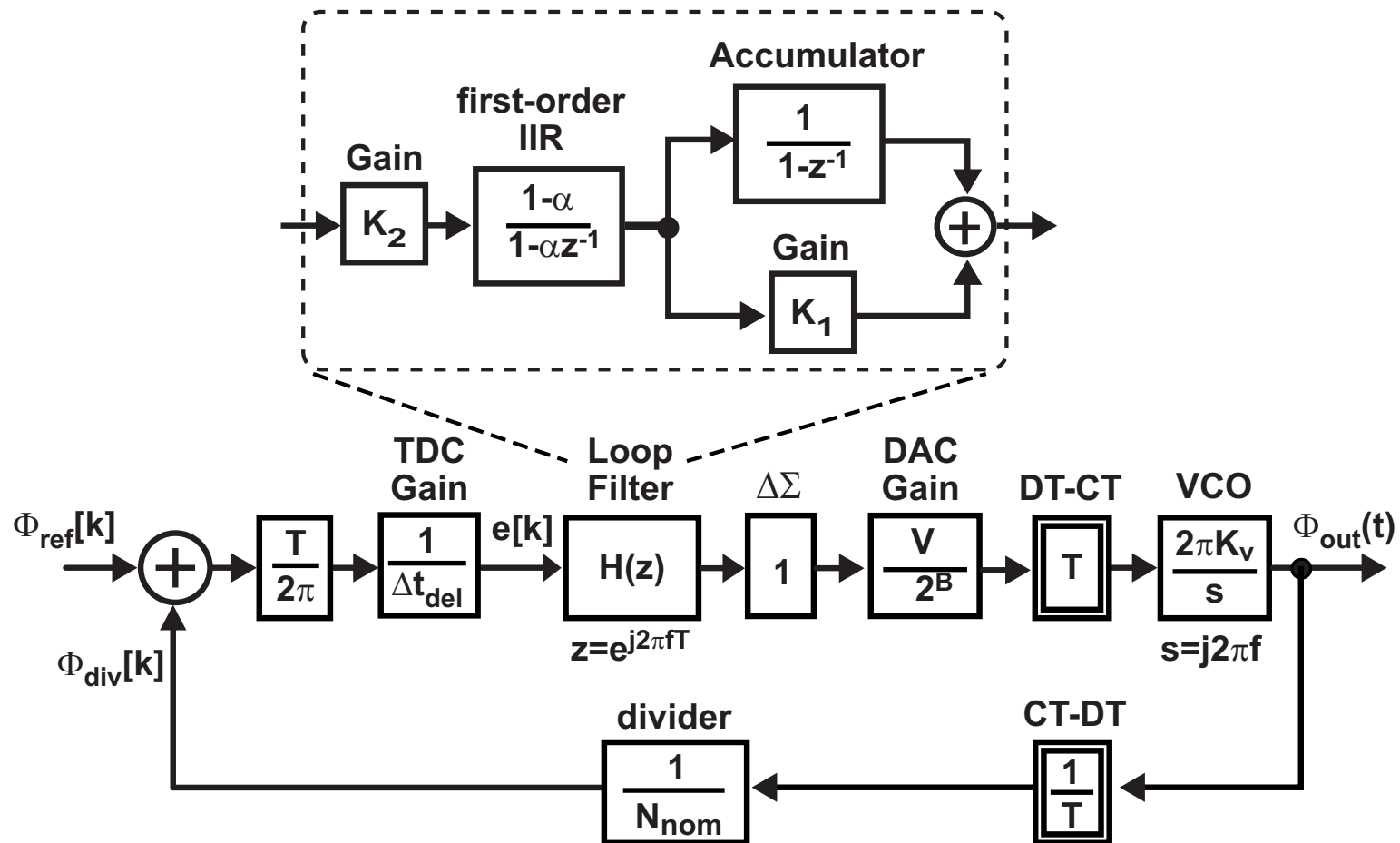Linearized Model of PLL Under Fine-Tune Operation




- Standard lead-lag filter topology but implemented in digital domain
 - Consists of accumulator plus feedforward path

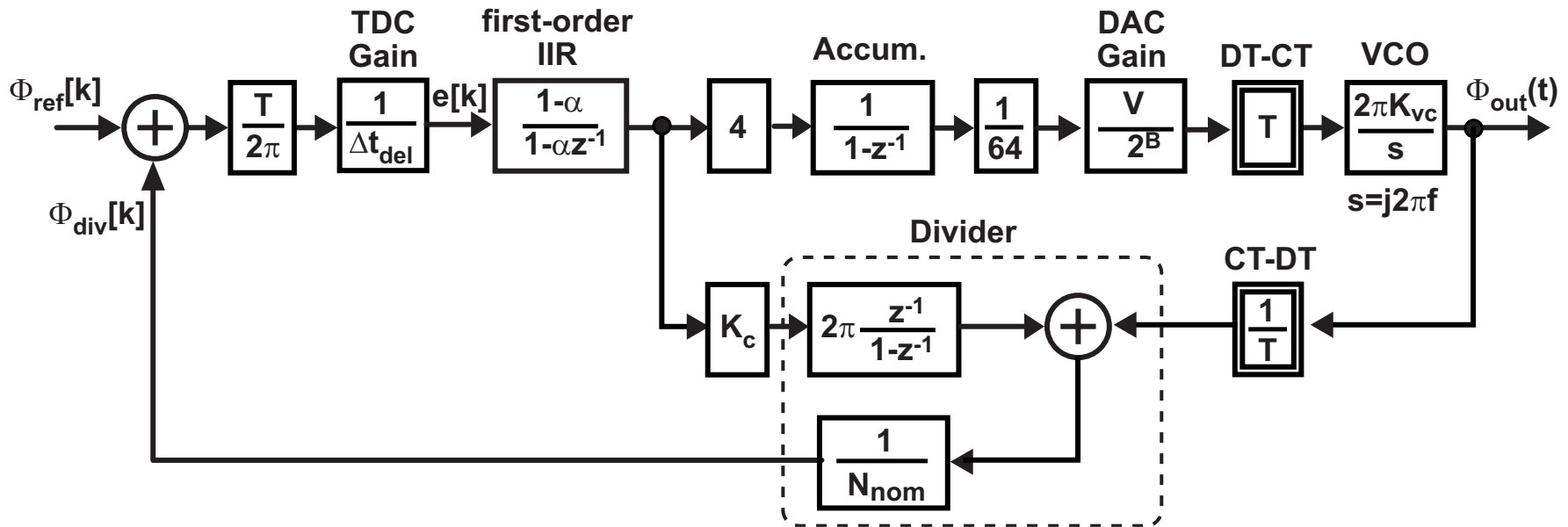Linearized Model of PLL Under Coarse-Tune Operation




- **Routing of signal path into Sigma-Delta controlling the divider yields a feedforward path**
 - Adds to accumulator path as both signals pass back through the divider
 - Allows reduction of coarse DAC bandwidth
 - Noise impact of coarse DAC on VCO is substantially lowered

VCO Buffer Implementation

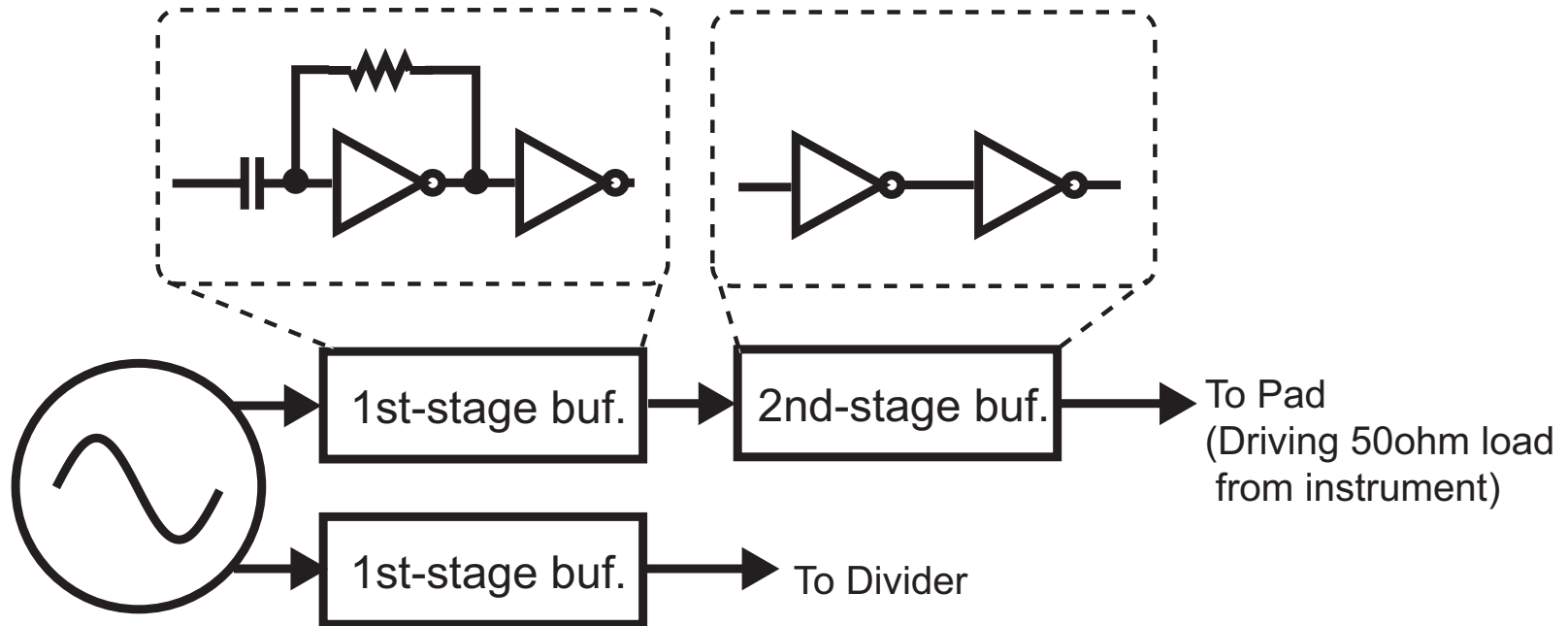

- **Consists of inverters with self-biased first stage**
 - AC coupling from VCO output into buffer
 - Achieves low noise (as will be seen in far-out phase noise in measured results)

Die Photo

 


- 0.13- μm CMOS
- Active area: 0.95 mm²
- Chip area: 1.96 mm²
- V_{DD} : 1.5V
- Current:
 - 26mA (Core)
 - 7mA (VCO output buffer at 1.1V)

GRO-TDC:


- 2.3mA
- 157X252 μm^2

Power Distribution of Prototype IC

 


- Notice GRO and digital quantization noise cancellation have only minor impact on power (and area)

Measured Phase Noise at 3.67GHz

 


- Suppresses quantization noise by more than 15 dB
- Achieves 204 fs (0.27 degree) integrated noise (jitter)
- Reference spur: -65dBc

Calculation of Phase Noise Components

 

- See wideband digital synthesizer tutorial available at <http://www.cppsim.com>

Measured Worst Spurs over Fifty Channels

 

- Tested from 3.620 GHz to 3.670 GHz at intervals of 1 MHz
 - Worst spurs observed close to integer-N boundary (multiples of 50 MHz)
- -42dBc worst spur observed at 400kHz offset from boundary


Conclusions

- Digital Phase-Locked Loops look extremely promising for future applications
 - Very amenable to future CMOS processes
 - Excellent performance can be achieved
- A low-noise, wide-bandwidth digital $\Delta\Sigma$ fractional-N frequency synthesizer is achieved with
 - High performance *noise-shaping* GRO TDC
 - Quantization noise cancellation in *digital* domain
- Key result: < 250 fs integrated noise with 500 kHz bandwidth

Innovation of future digital PLLs will involve joint circuit/algorithm development


Mixed Signal CDR Example

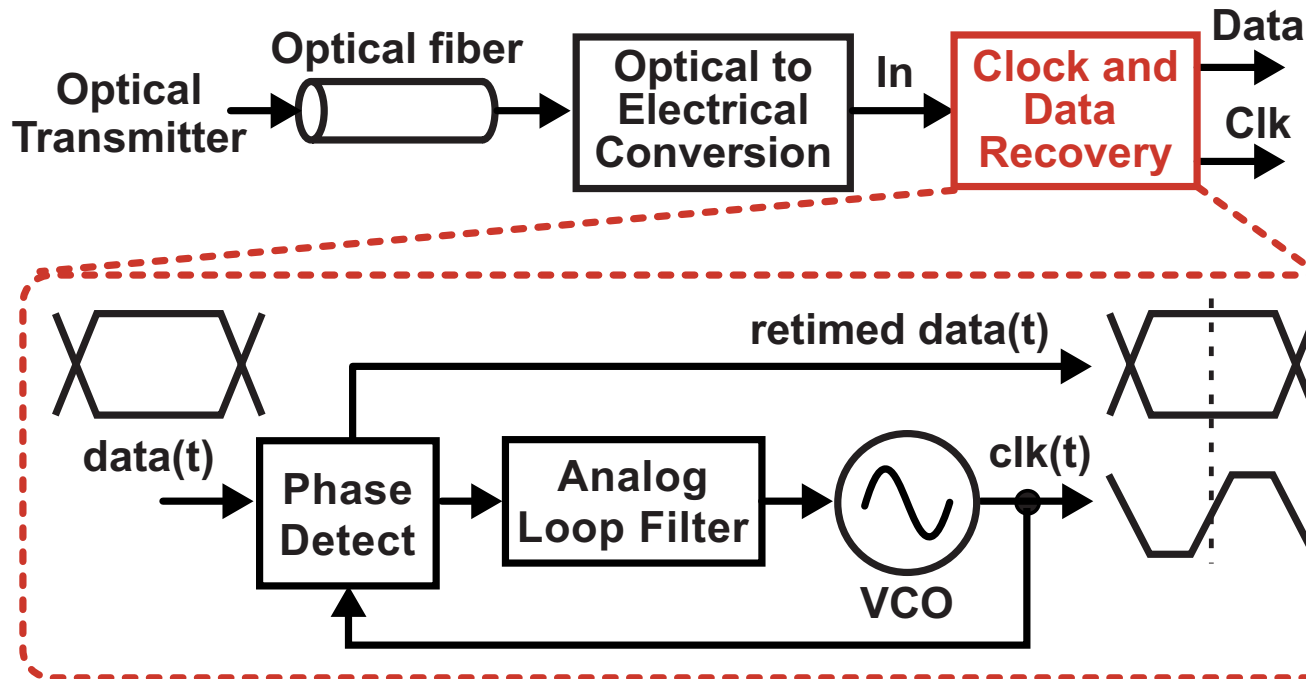Clock and Data Recovery Circuits for SONET




- **Function:** recover clock from input NRZ data stream
 - Want to support multi-rates: 2.5 Gb/s, GbE, 622 Mb/s, 155 Mb/s
- **Structure:** phase-locked loop with an appropriate phase detector
- **Focus:** analog, digital, or hybrid (i.e., mixed-signal) implementation?

Key Jitter Performance Metrics for SONET

 


- **Jitter generation:** amount of jitter produced by PLL
 - Achieved by designing low noise PLL
- **Jitter tolerance:** amount of input jitter tolerated by PLL
 - Achieved through appropriate design of phase detector
- **Jitter transfer:** required filtering of input jitter
 - Achieved by properly designing transfer function of PLL
 - Key challenge: need < 0.1 dB peaking in transfer function

The Woes of an Analog PLL Implementation

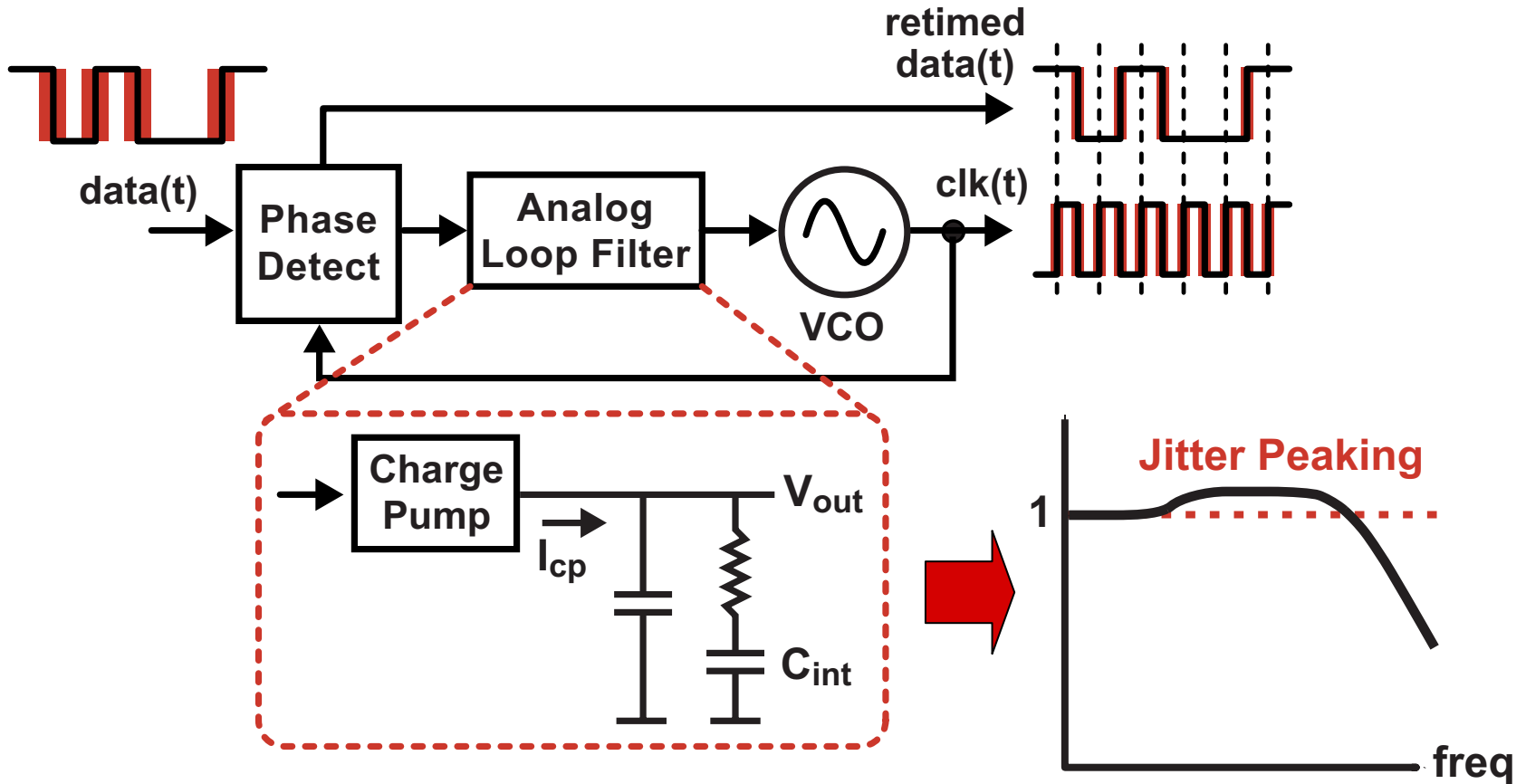


- **Goal: integrated loop filter**
- **Issue: required cap value too large (100 uA charge pump):**
 - 2.5 Gb/s (OC-48): 4 nF
 - 155 Mb/s (OC-3): 64 nF

Consider A Digital CDR ...

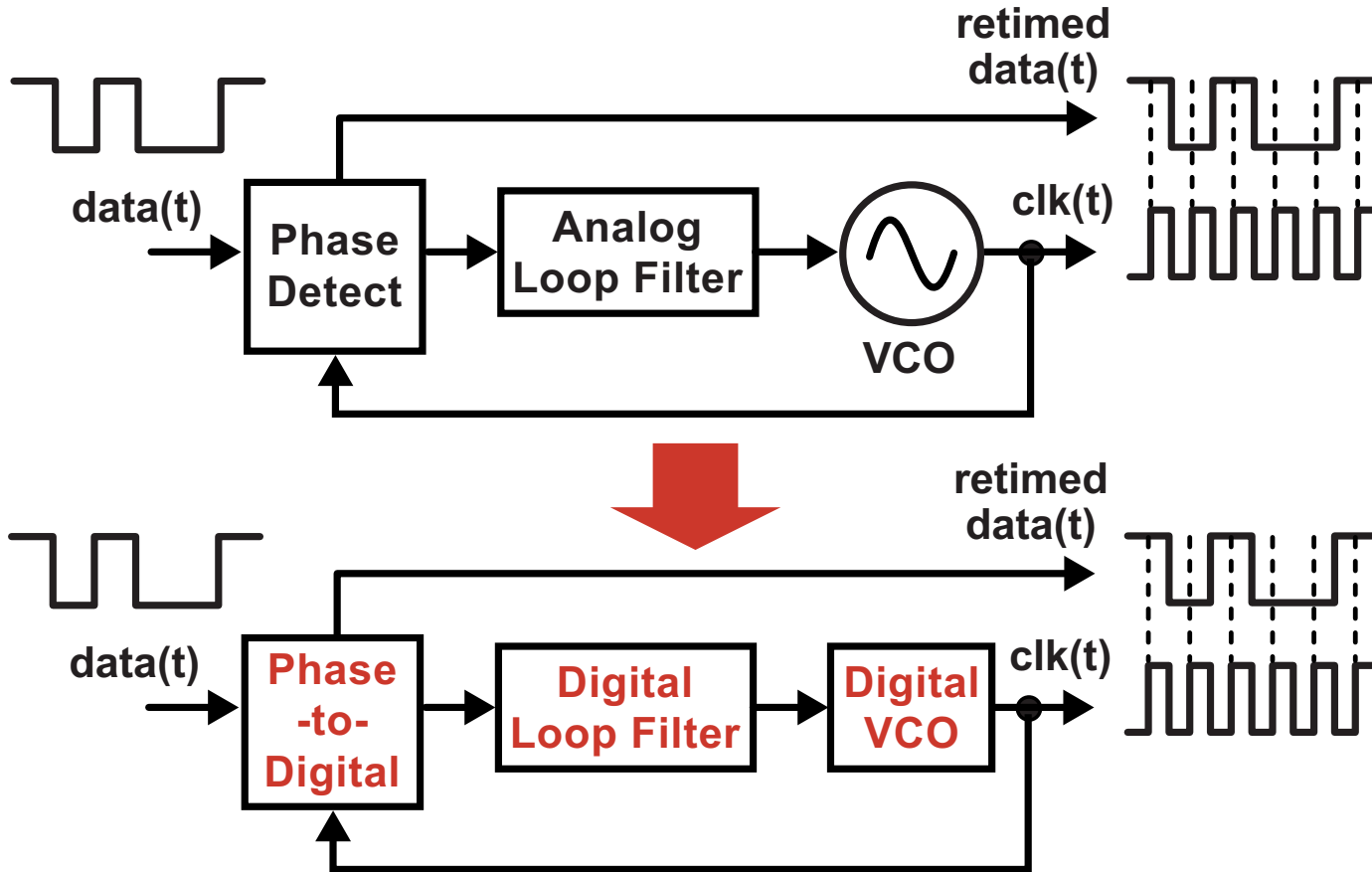

- **Digital loop filter allows:**
 - Easy integration of loop filter
 - Easy configurability for multi-rate operation



Digital VCO Implementation

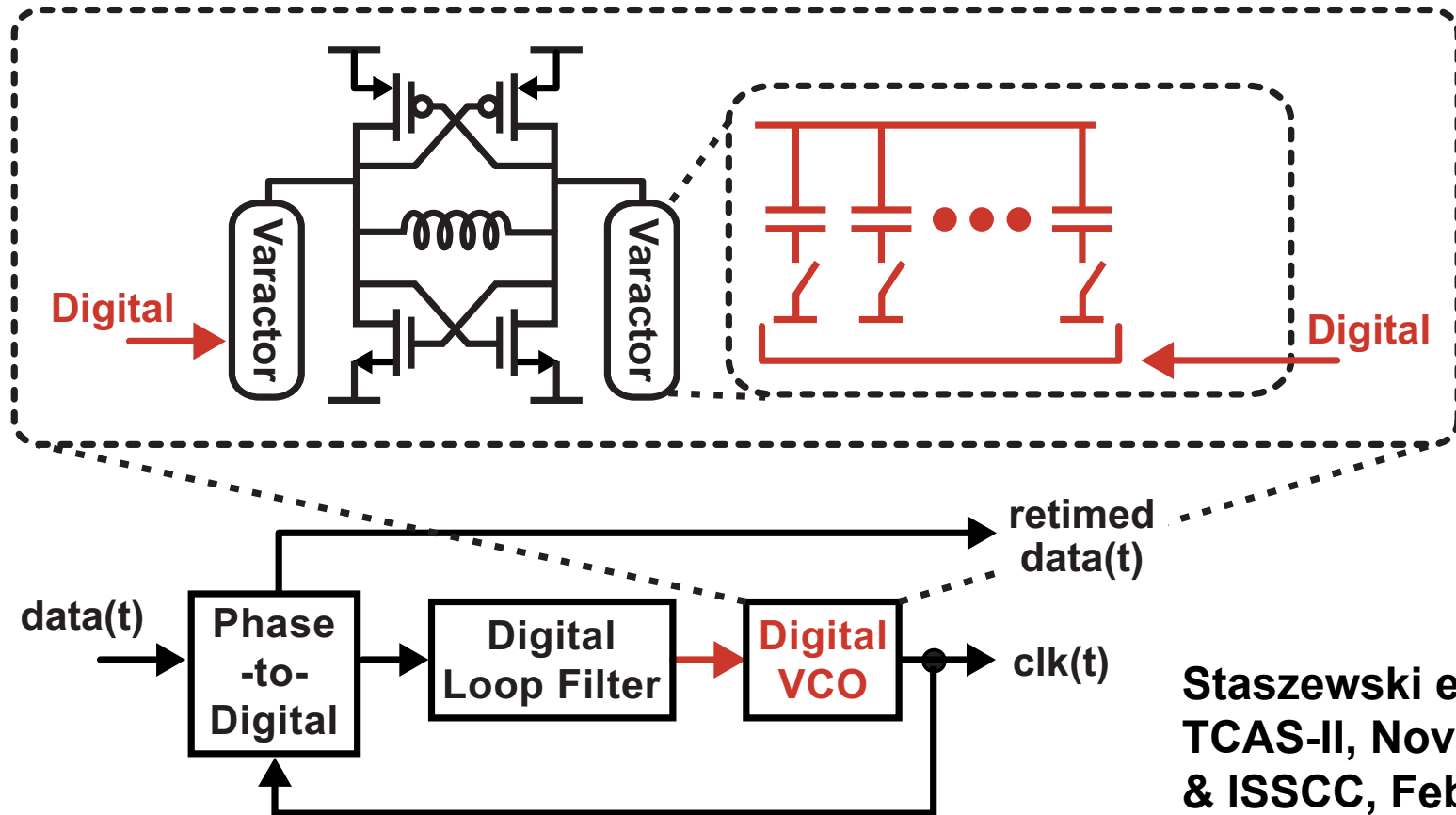

Staszewski et. al.,
TCAS-II, Nov 2003
& ISSCC, Feb 2004

- Other researchers have demonstrated a “digital” LC VCO using a switched capacitor bank
- Issue: better suited for 0.09 μ rather than 0.25 μ CMOS

Hybrid VCO Implementation

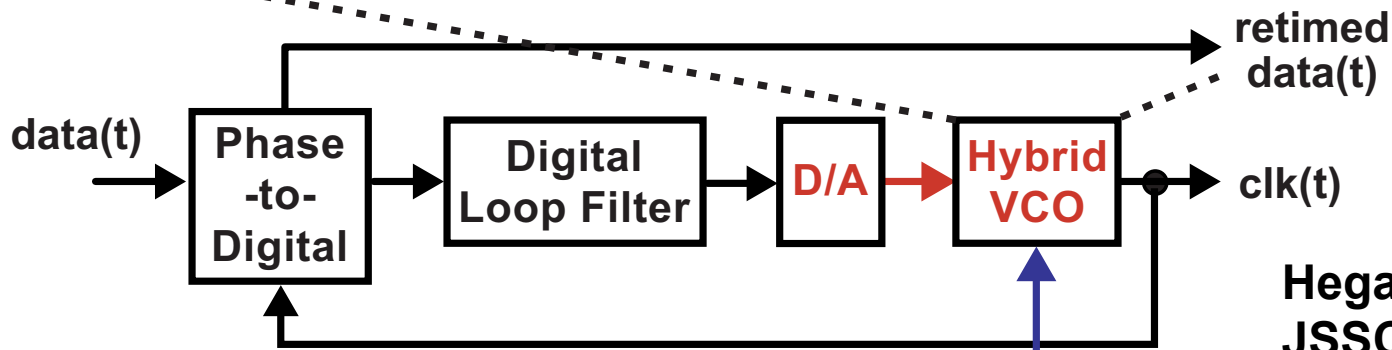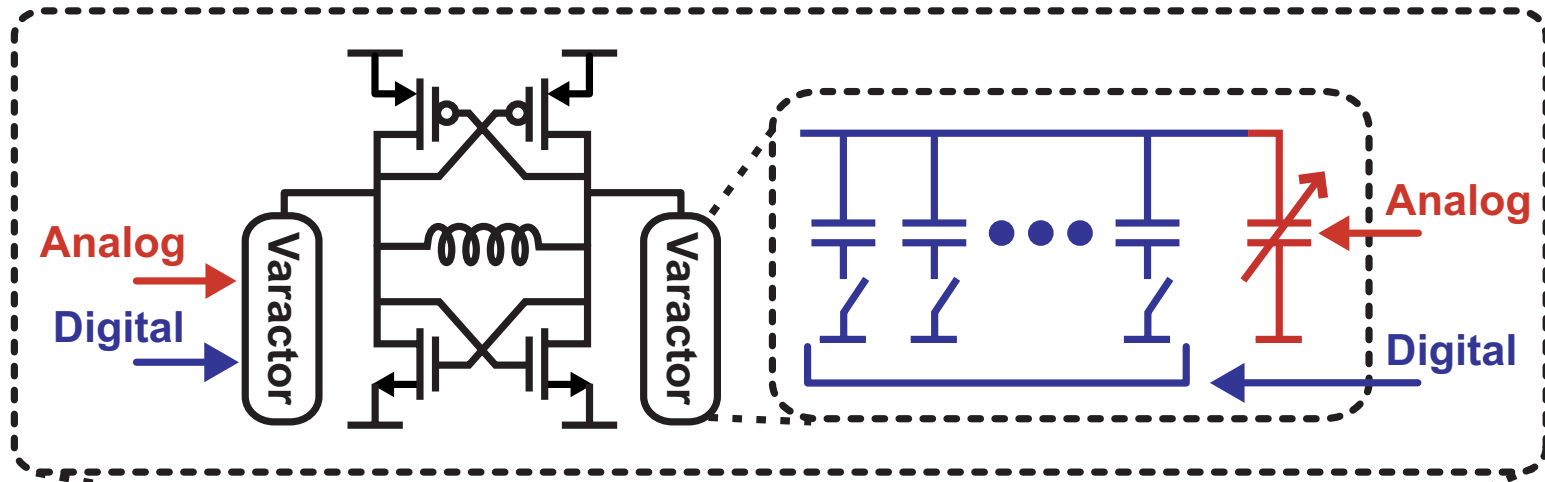


Hegazi et. al.
JSSC, Dec 2001

Advantages


- Low phase noise, easy implementation in 0.25u CMOS

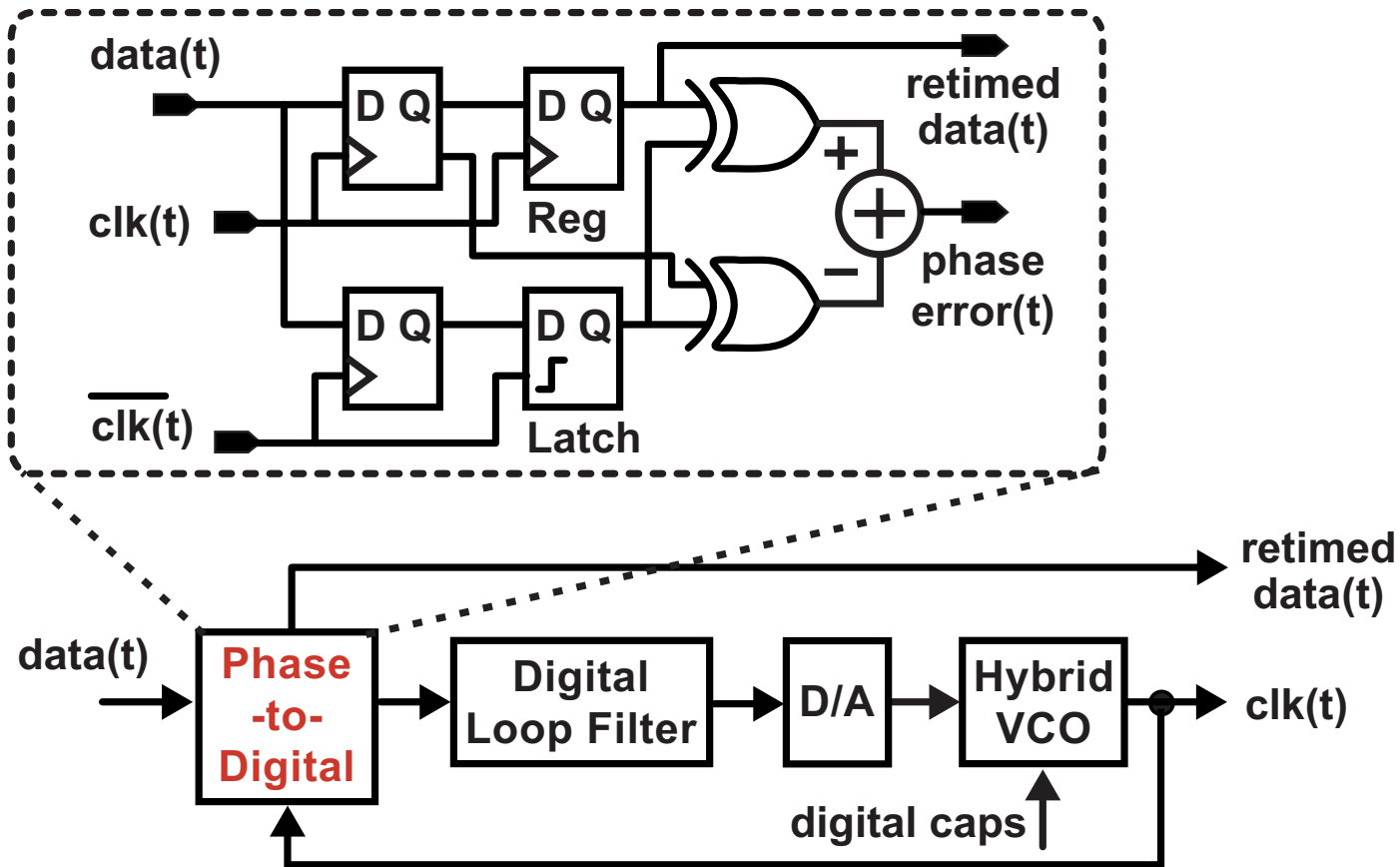Bang-Bang Structure as Digital Phase Detector?




- **Advantages:** purely digital implementation with low complexity and low clock loading
- **Issue:** leads to nonlinear CDR behavior

A Closer Look at the Bang-Bang Detector

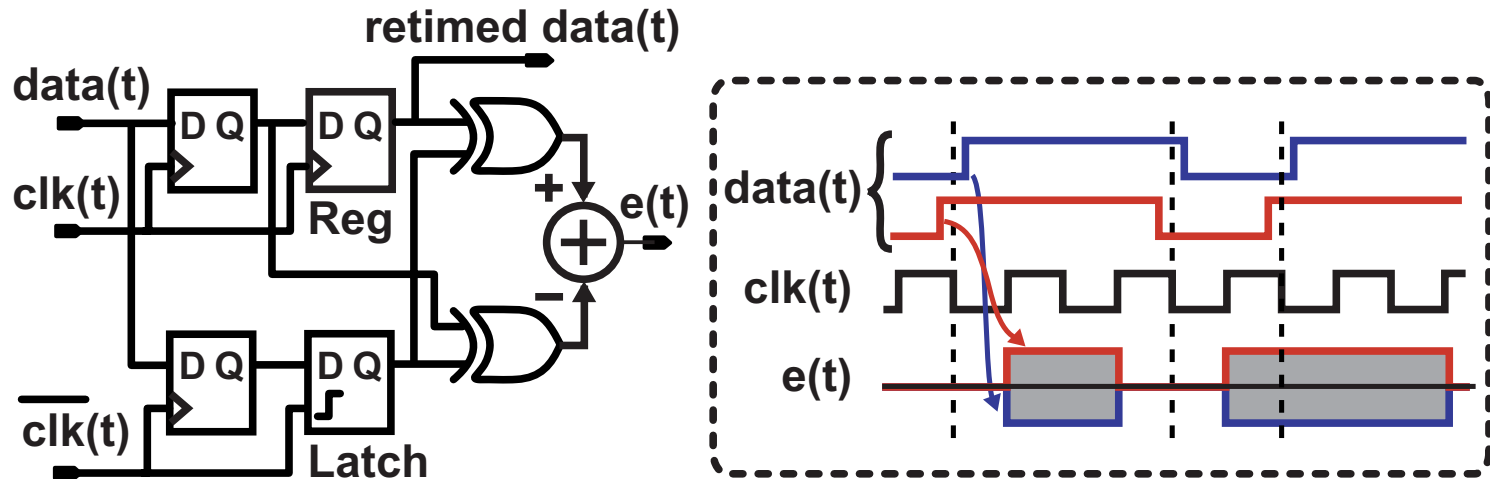



- Phase error output consists of pulses of *fixed* area that are either positive or negative
 - Nonlinear phase detection!
- Issue: PLL dynamics become nonlinear
 - Difficult to meet SONET Jitter Transfer Specification
 - Prone to limit cycle issues

A Flash Phase-to-Digital Converter?

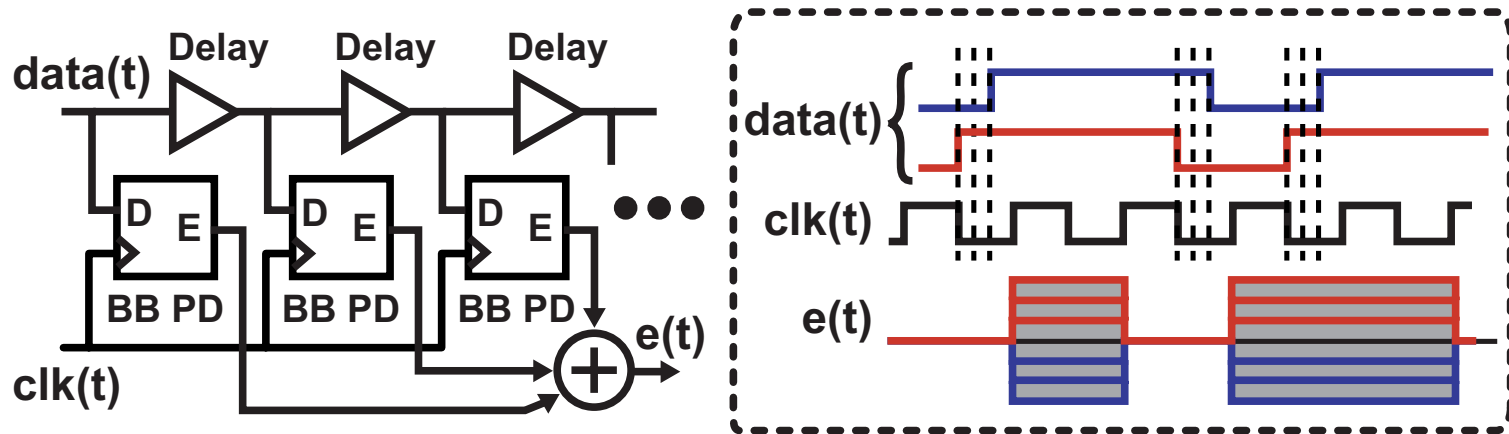


- **Chain several bang-bang detectors through delays**
 - Allows multi-level phase detection with digital structure
 - Similar to time-to-digital converters of other researchers
 - Staszewski et. al., TCAS-II, Nov 2003 & ISSCC, Feb 2004
- **Issues:**
 - High power consumption (multi-GHz operation required)
 - High clock loading (complicates VCO buffer design)
 - Prone to limit cycle issues

An Analog Phase Detector?

 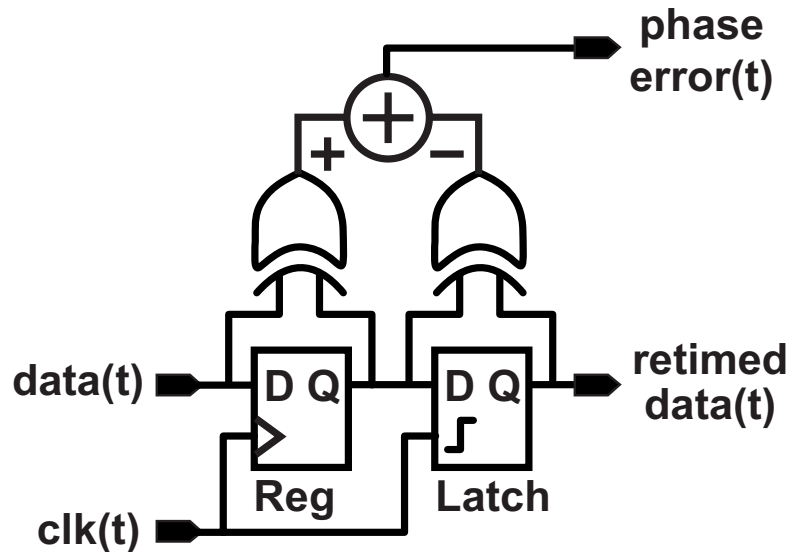


- Hogge detector popular in analog CDR designs
- Advantages
 - Low complexity, power consumption, and clock loading
 - Leads to linear PLL dynamics
- Issue
 - We need a digital output!

Proposed Phase-to-Digital Converter

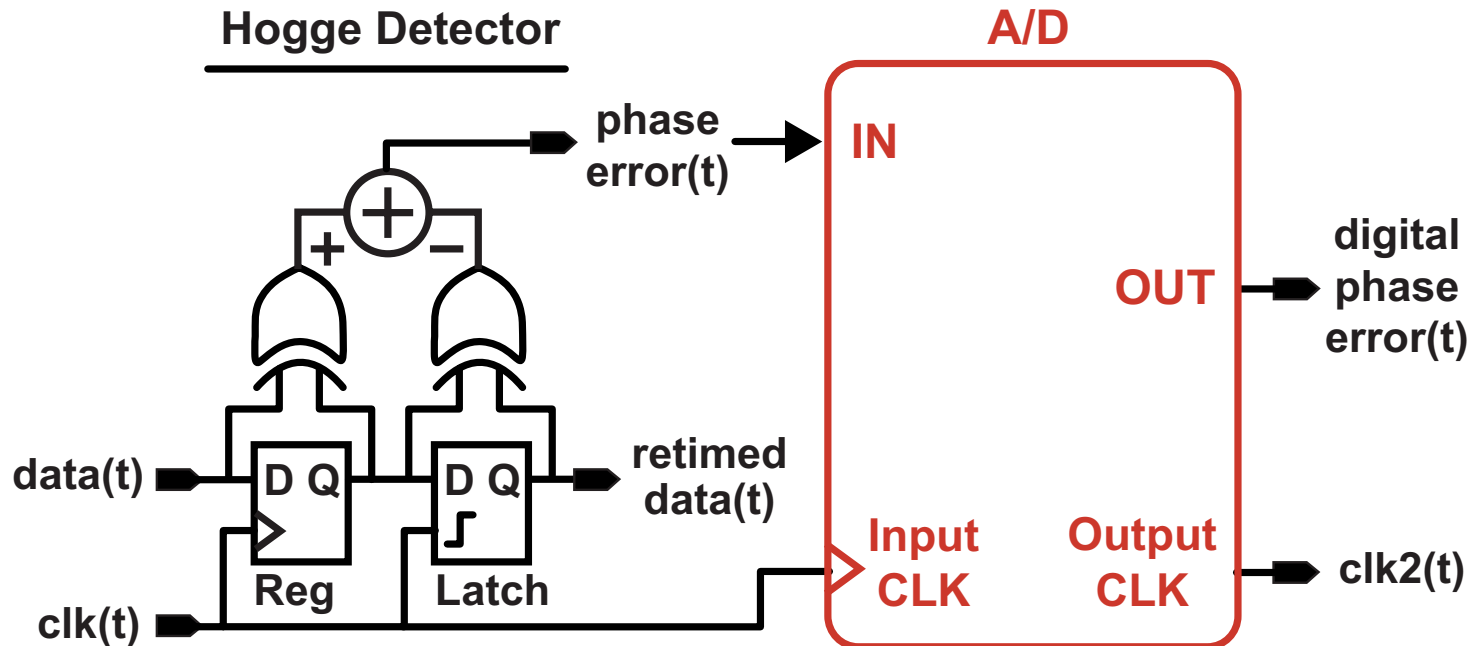

- **Combine Hogge Detector with a high speed A/D**
- **Issues:**
 - Want high resolution (i.e., to achieve high linearity)
 - Want low power, low clock loading, and compact area



Proposed A/D Approach

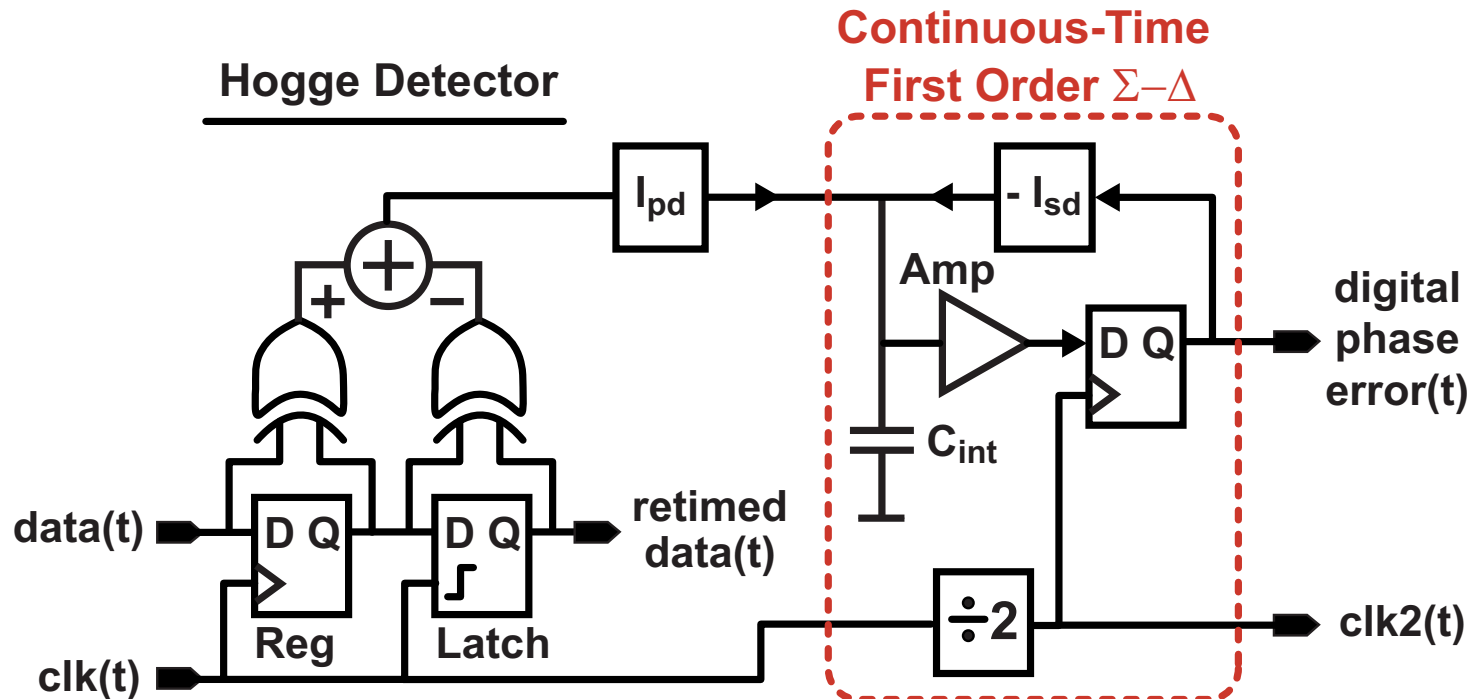

- **A first order continuous-time Sigma-Delta A/D**
 - Achieves high resolution, low power, low clock loading, compact area
- **How could this work??**
 - Can easily clock at GHz speeds (i.e., high oversampling)
 - Hogge output provides random dithering source for free


Phase-to-Digital Converter Implementation Details

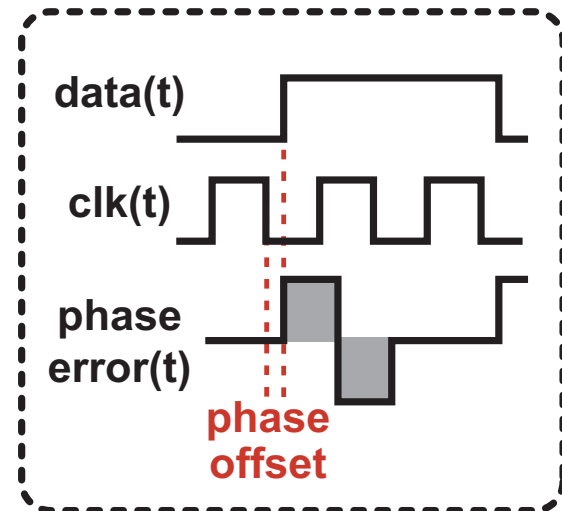 - Start with Hogge Detector/Charge Pump implementation




- Issue 1: Hogge detector is prone to phase offsets
 - Caused by unequal delays for XOR input signals
 - Degrades jitter tolerance performance

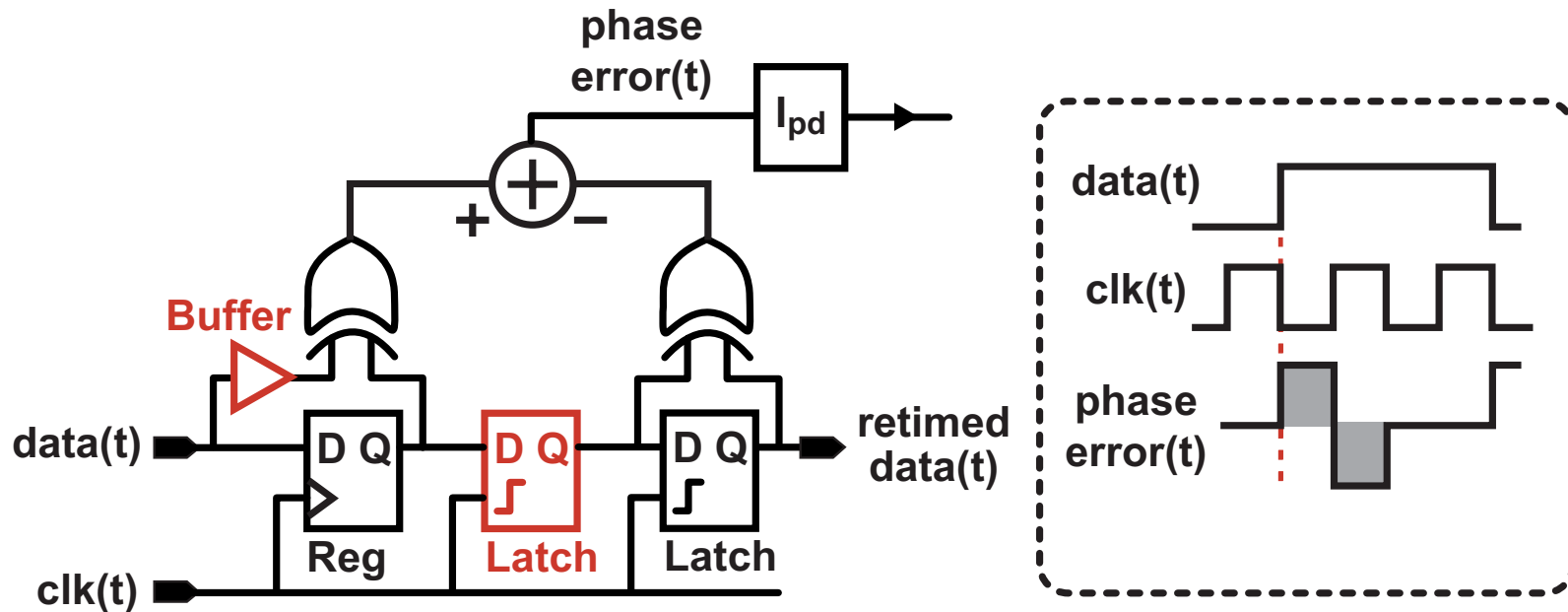Improvement of Phase Offset of Hogge Detector




- Extra latch improves matching of loads of Reg and Latch
- Extra buffer ideally matches clk-to-Q delay of Reg

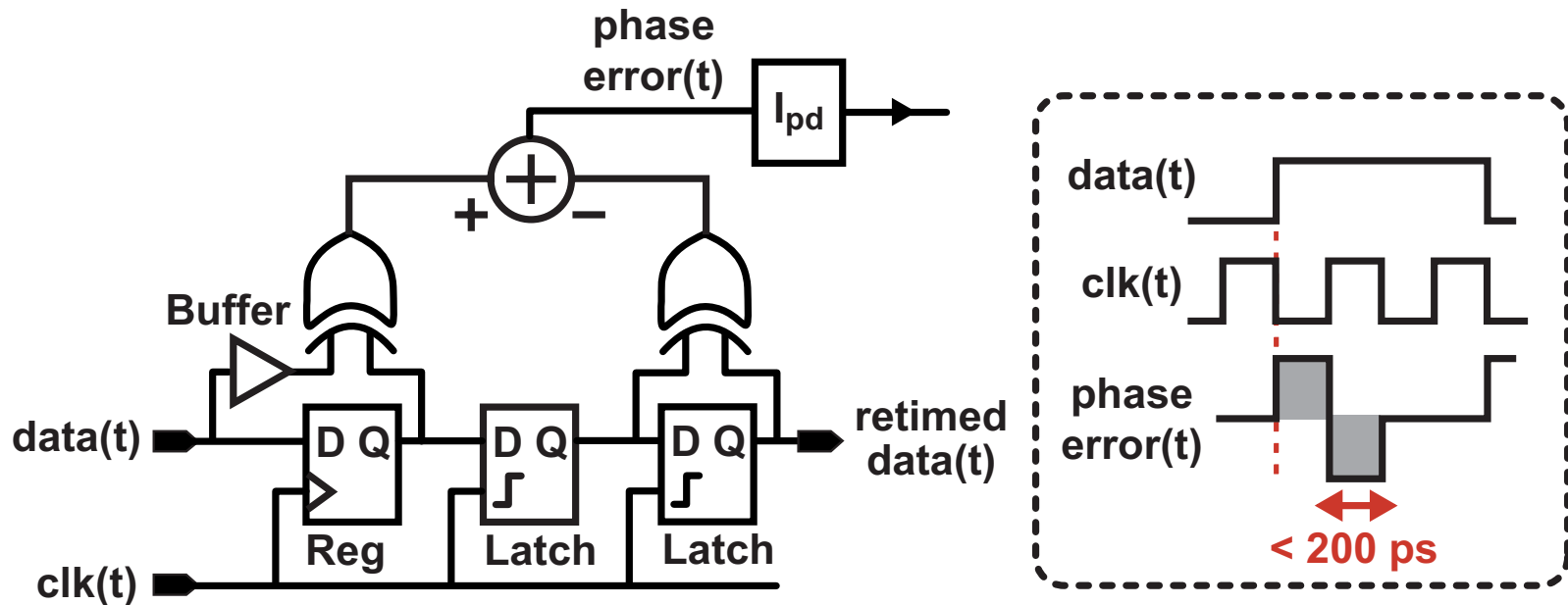Challenge of 2.5 Gb/s Operation in 0.25u CMOS




- XOR outputs have pulse widths < 200 ps at 2.5 Gb/s
 - Complicates efforts to achieve reasonable linearity and phase detector range

A Combined XOR/Charge Pump Topology

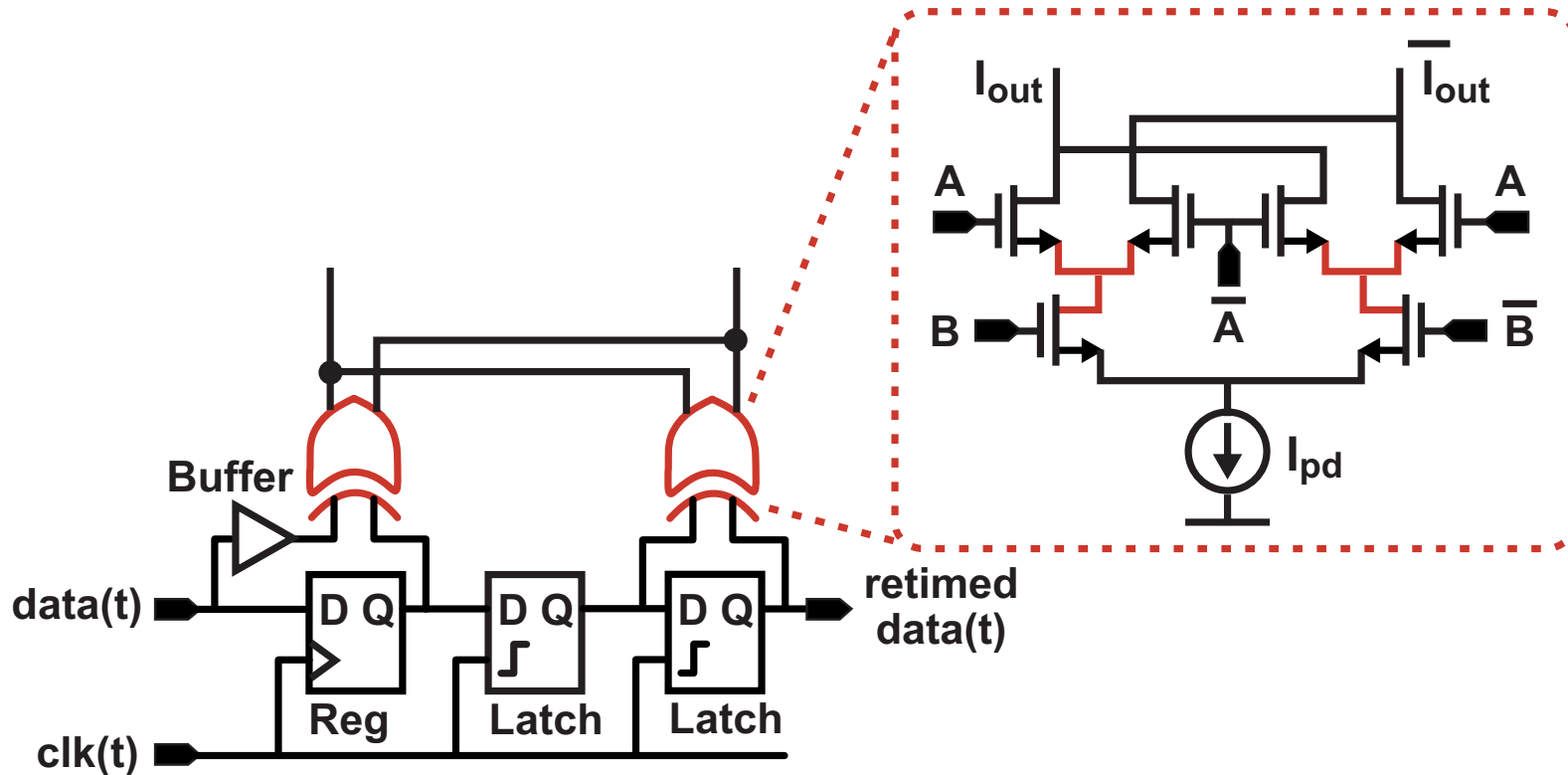


- Limits short pulse width signals to low impedance nodes
 - Fast pulses occur at source nodes of devices
 - Note: XOR outputs feed into “low impedance” capacitor
- Combined implementation saves power and area

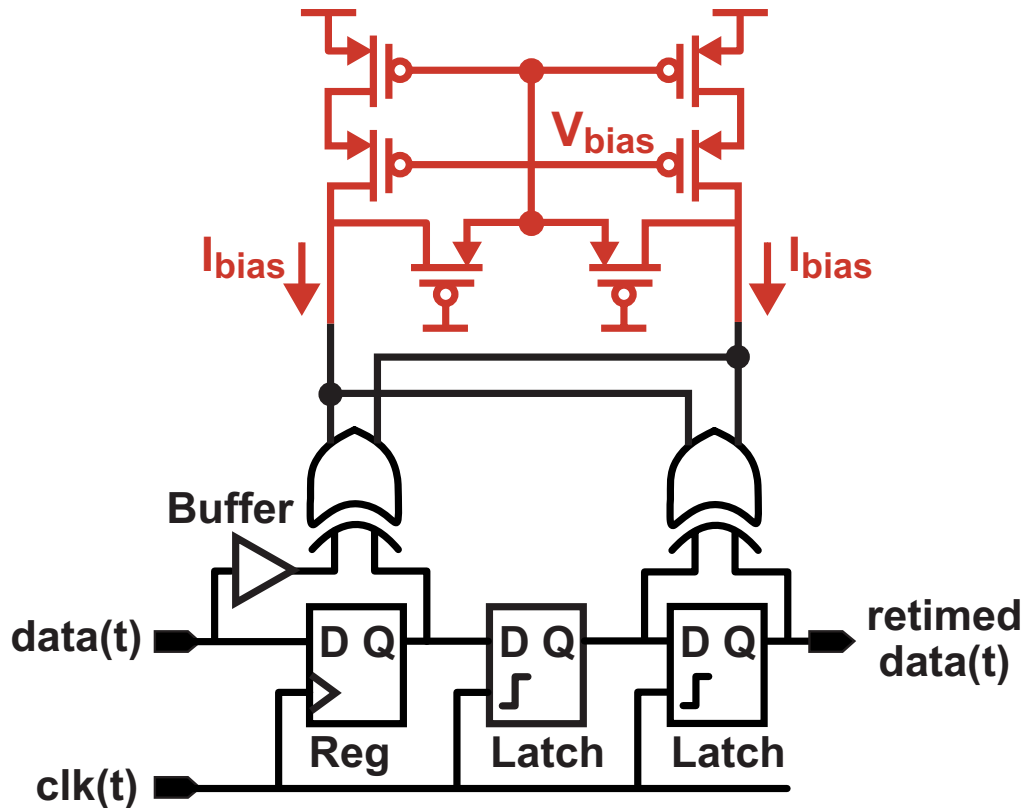Bias Network with Simple Common-Mode Feedback




- Common-mode feedback sets voltage according to voltage of top PMOS devices
 - Size PMOS devices appropriately for desired voltage
- Achieves high impedance with compact design

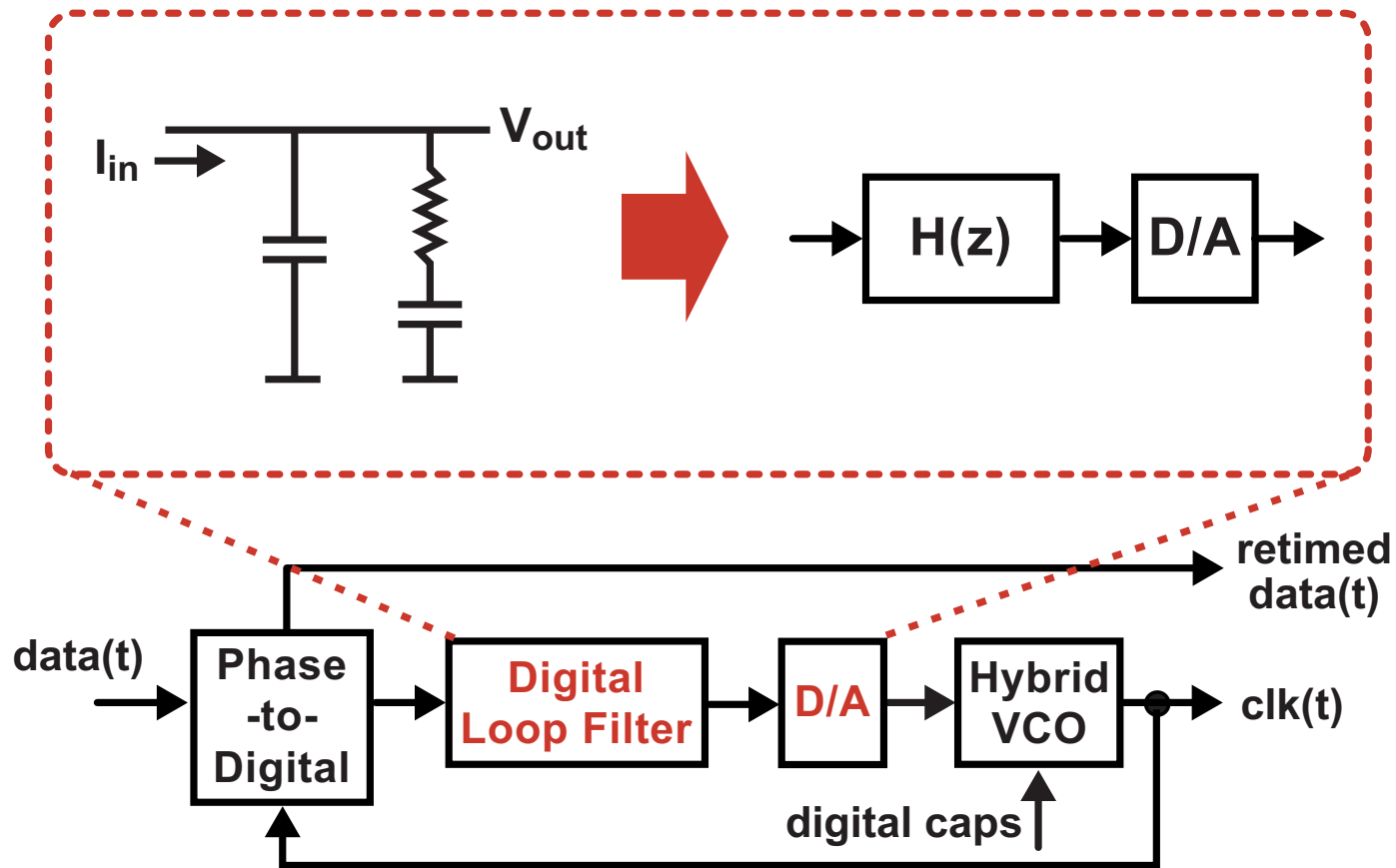Digital Loop Filter and D/A Implementation




- Goal: digital implementation of analog lead/lag filter
- Issue: requires D/A with $\gg 1$ MHz bandwidth, high resolution
 - An easier D/A implementation is preferred ...

Proposed Hybrid Loop Filter Approach

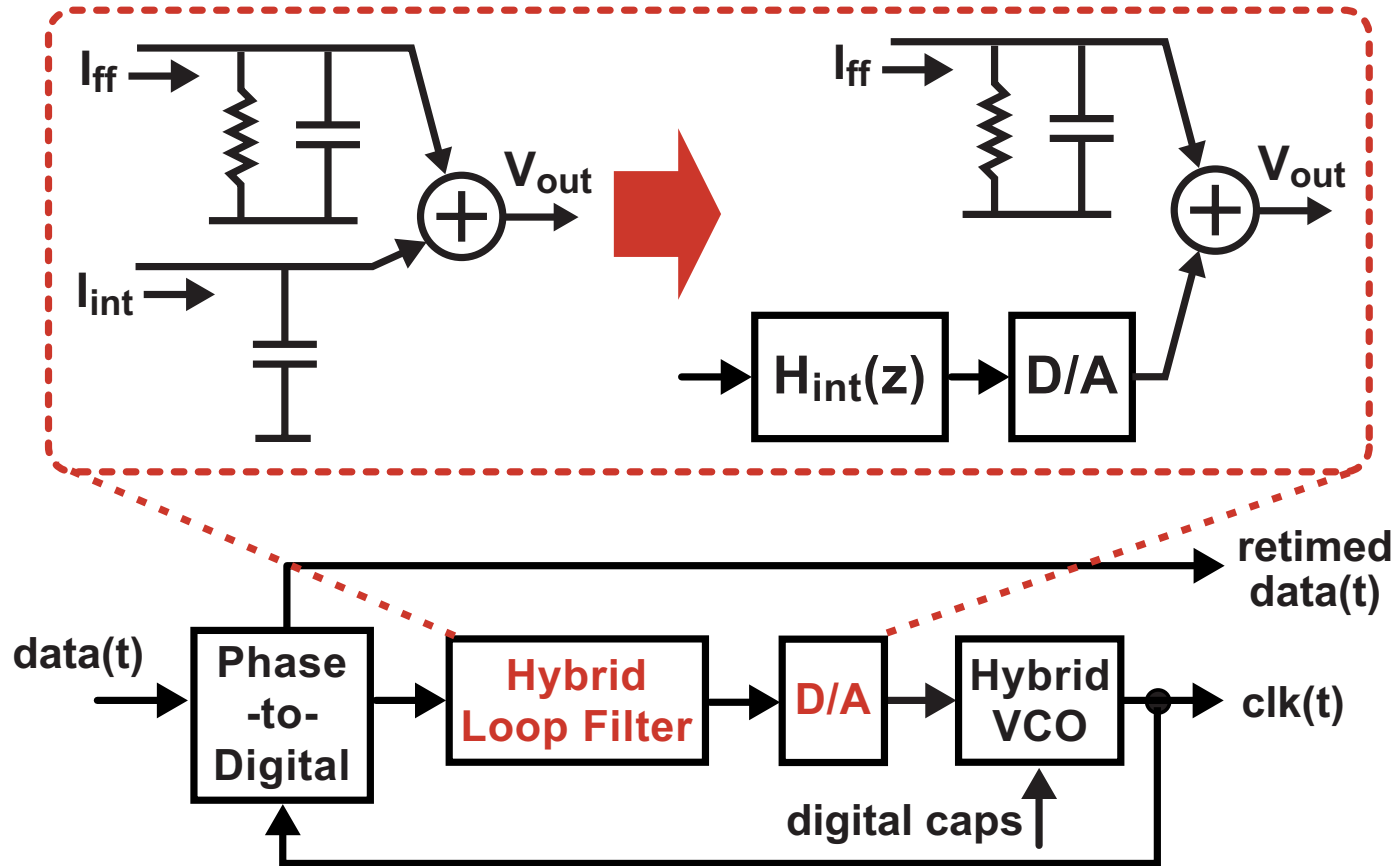


- Lead/Lag filter can be decomposed into two paths
 - Feedforward path (high bandwidth, easy in analog domain)
 - Integrating path (low bandwidth, hard in analog domain)
 - Digital domain provides a compact implementation

Overall Hybrid Loop Filter Structure

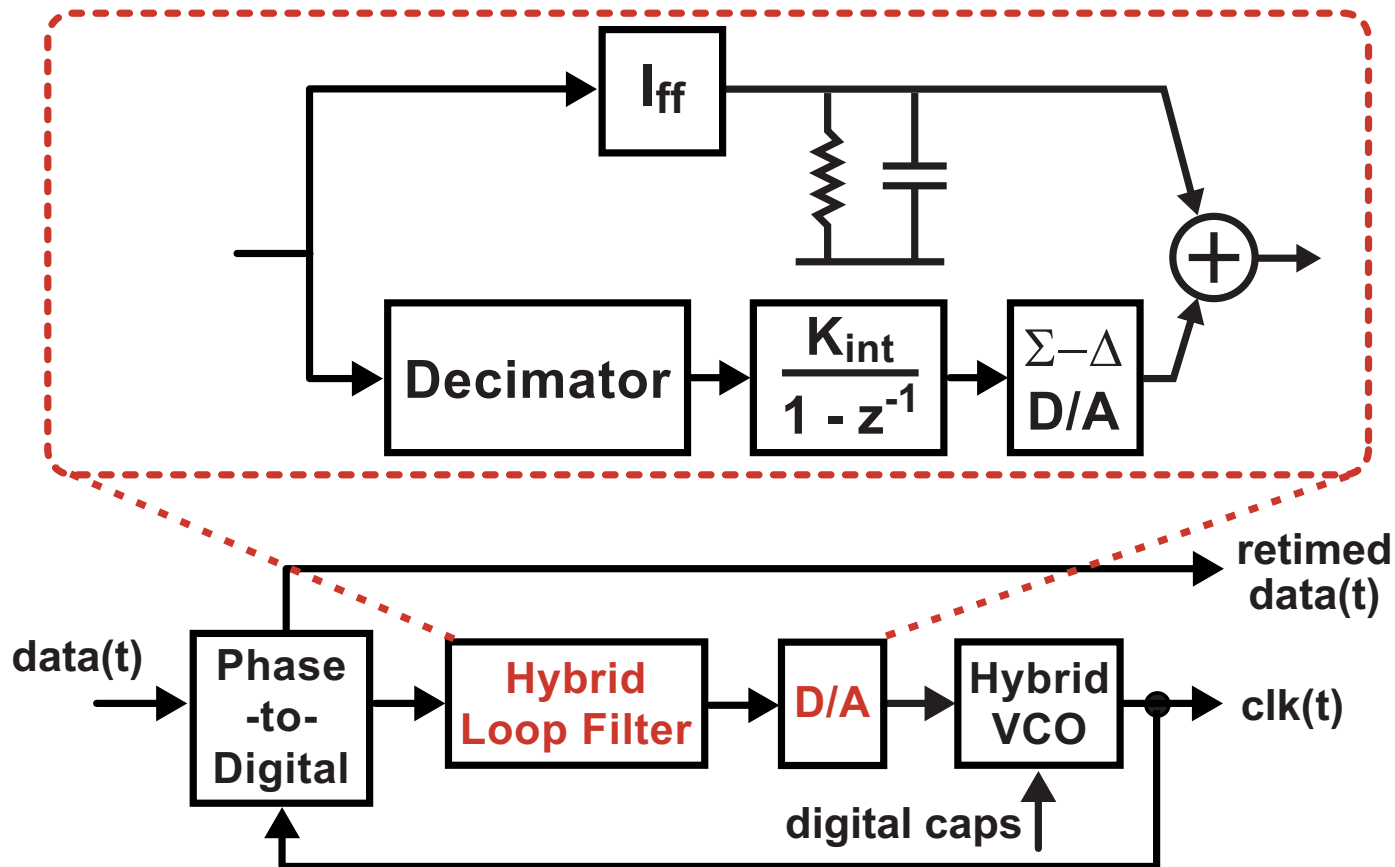


- Accumulator acts as digital integrator
- Sigma-Delta D/A allows high resolution with easy implementation
- Decimator lowers operating speed of accumulator and D/A

Walk Through of Decimator Implementation

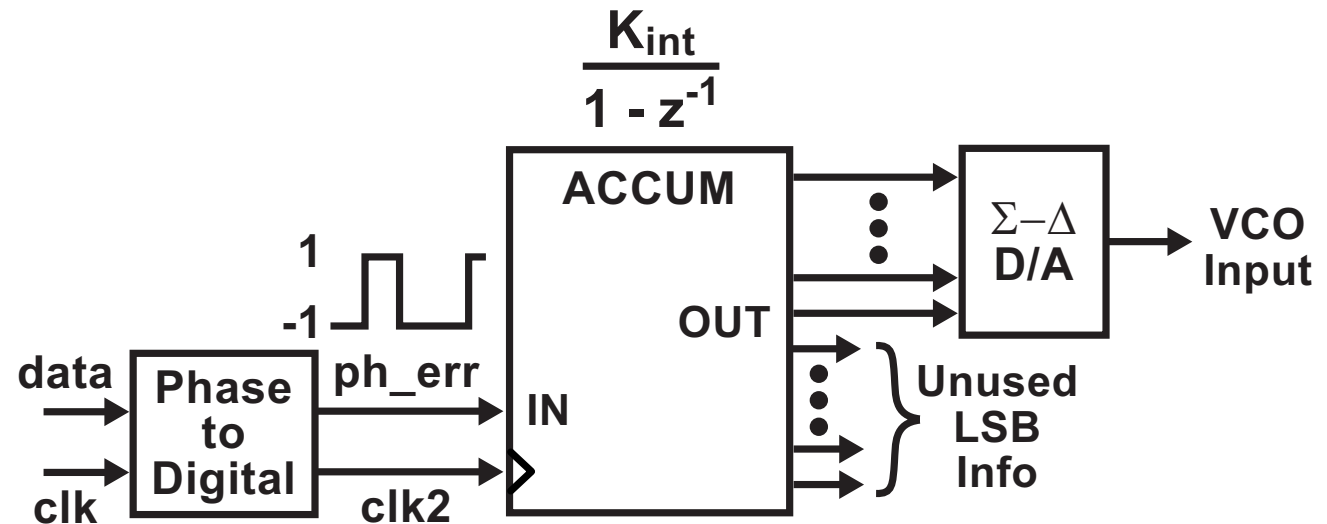

- Consider simply running accumulator at full rate
 - Would need to run at GHz speeds in 0.25u CMOS
 - High power!
- Key observations
 - Accumulator output has higher resolution than needed by VCO input
 - We do not need the LSB portion of the accumulator output

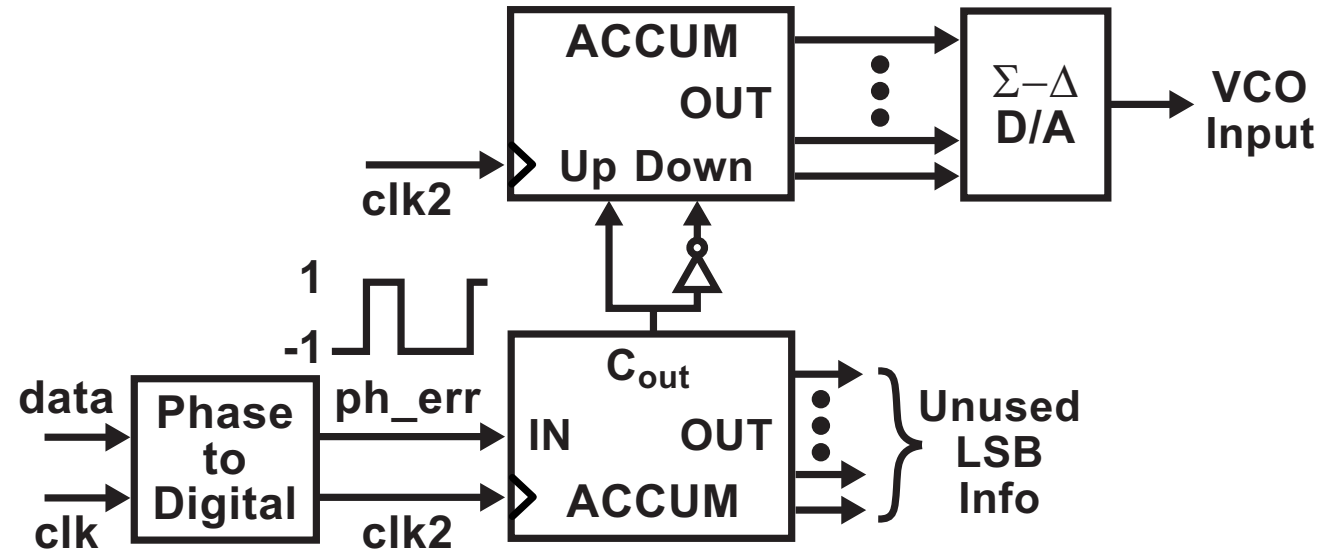
Split Accumulator into LSB and MSB Sections



■ Key observations:


- We only need one line of communication between LSB and MSB sections (i.e., carry signals)
- We only need to generate the carry out signal of the LSB section
- We can replace the LSB section with a decimator structure and still preserve all relevant information

First Pass at Decimator Implementation

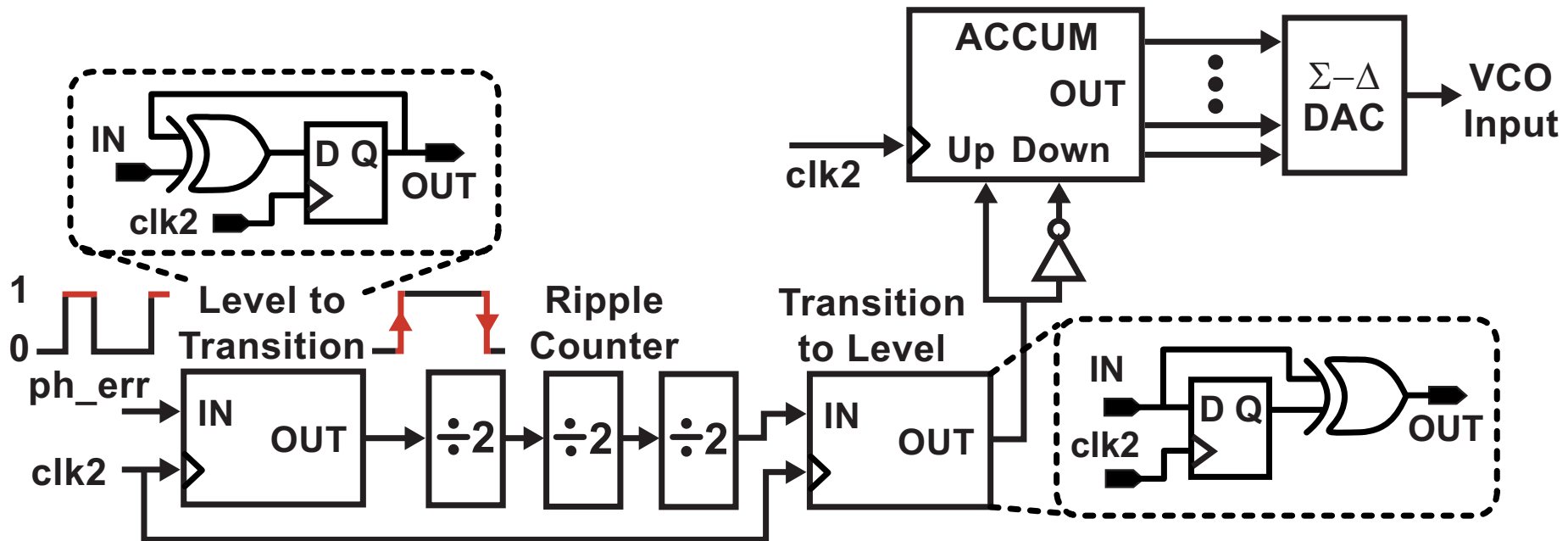


- We can implement the LSB accumulator with a ripple counter
 - Issue: ripple counter counts transitions
 - Solution: use appropriate translators to convert between voltage levels and transitions
- Next step: we have achieved an efficient LSB accumulator, but not a lower operating frequency

Final Decimator Architecture

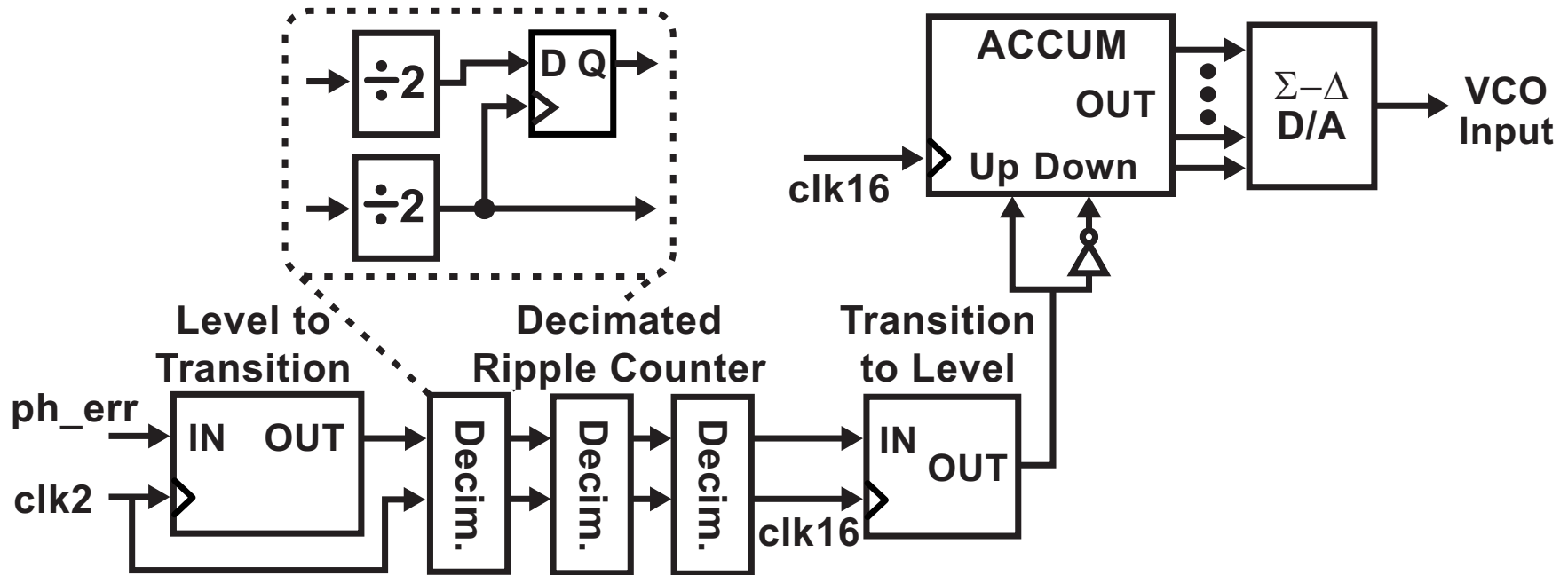

- Re-clock divide-by-2 stages of ripple counter at progressively lower clock frequencies
 - Aligns ripple counter transitions to lower frequency clock boundaries
- MSB Accumulator now runs at 1/16 of the original frequency in the above example


Overall CDR Architecture

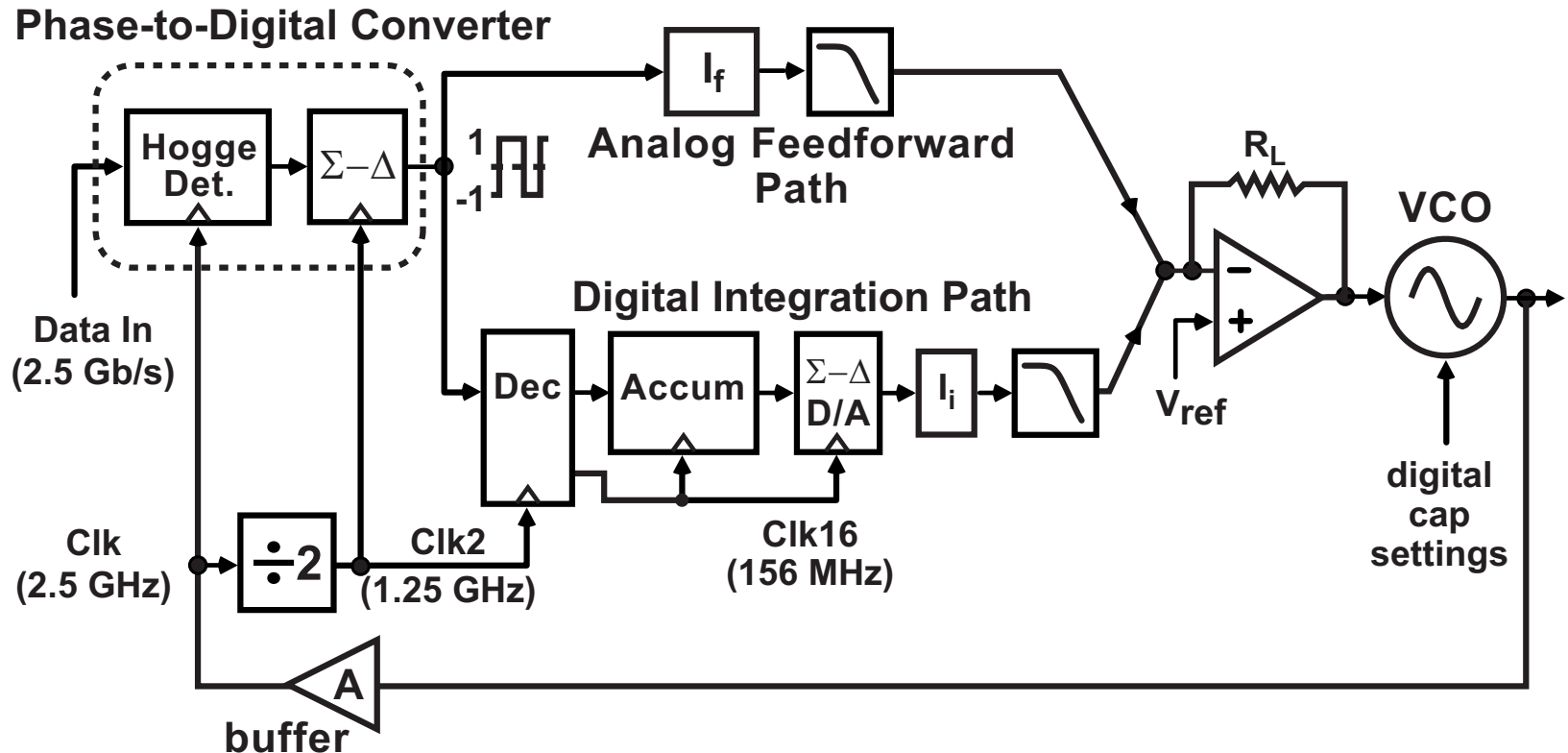

■ We have achieved:


- A low power, compact, highly linear phase-to-digital structure
- A low power, compact, highly configurable hybrid loop filter
- Compatible with existing hybrid VCO structures achieving excellent phase noise in 0.25u CMOS

Die Photo

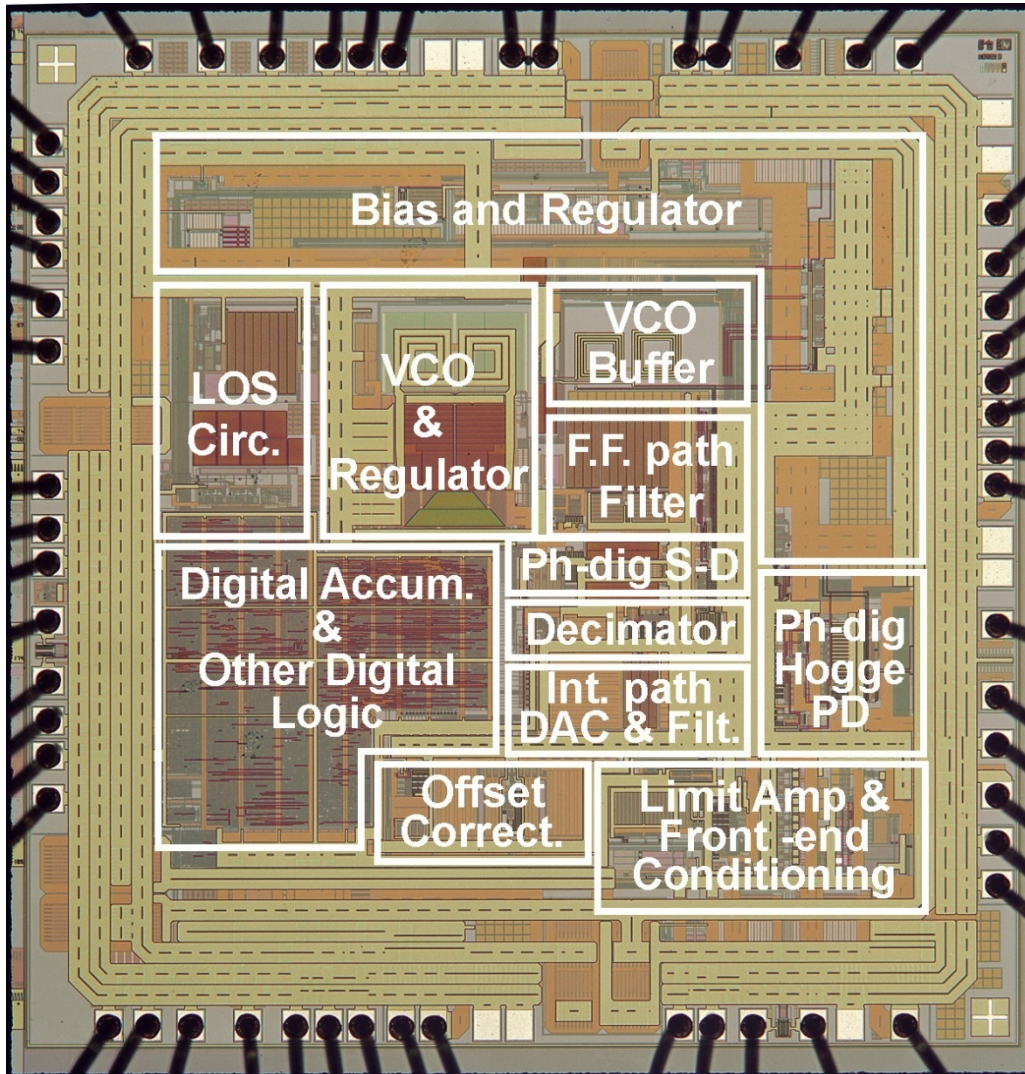

- **Supply Voltage**
 - 2.5 V or 3.3 V
- **Typical current**
 - 170 mA (2.5 Gb/s)
- **Supported data rates**
 - 2.7 Gb/s (FEC)
 - 2.5 Gb/s (OC-48)
 - Gigabit Ethernet
 - 622 Mb/s (OC-12)
 - 155 Mb/s (OC-3)
- **Minimum input**
 - 10 mV (differential)
- **Package size**
 - 5mm X 5mm


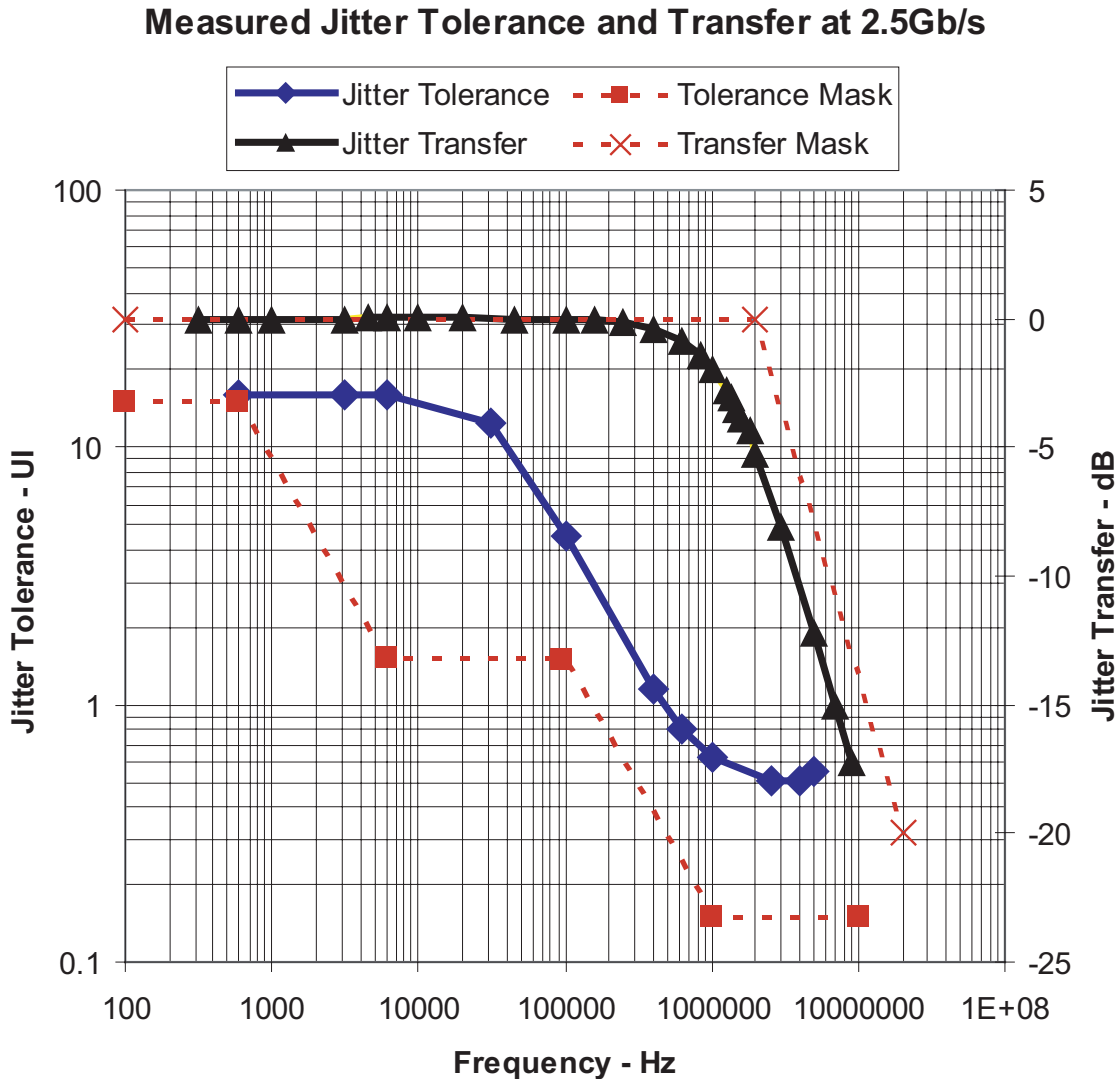
Measured Jitter Tolerance and Transfer at 2.5 Gb/s



■ **SONET performance specifications met at all data rates:**

- **Jitter transfer (typ.)**
 - Peaking < 0.03 dB
- **Jitter tolerance (min)**
 - > 0.3 UI_{pp} (> 1 MHz)
- **Jitter generation**
 - 3 mUI rms (typ.)
 - 25 mUI pp (typ.)

Measured Eye Diagrams at 2.5 Gb/s

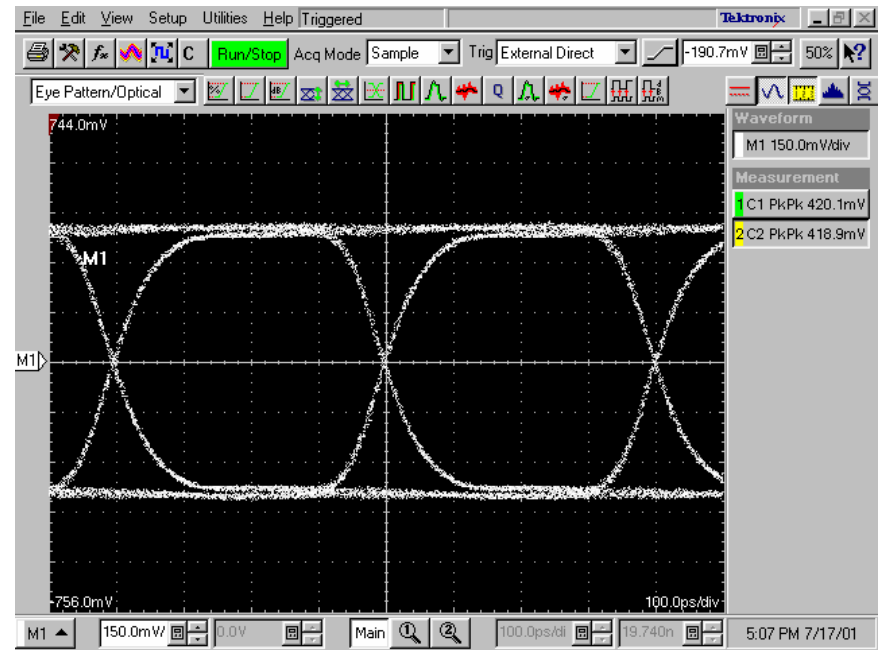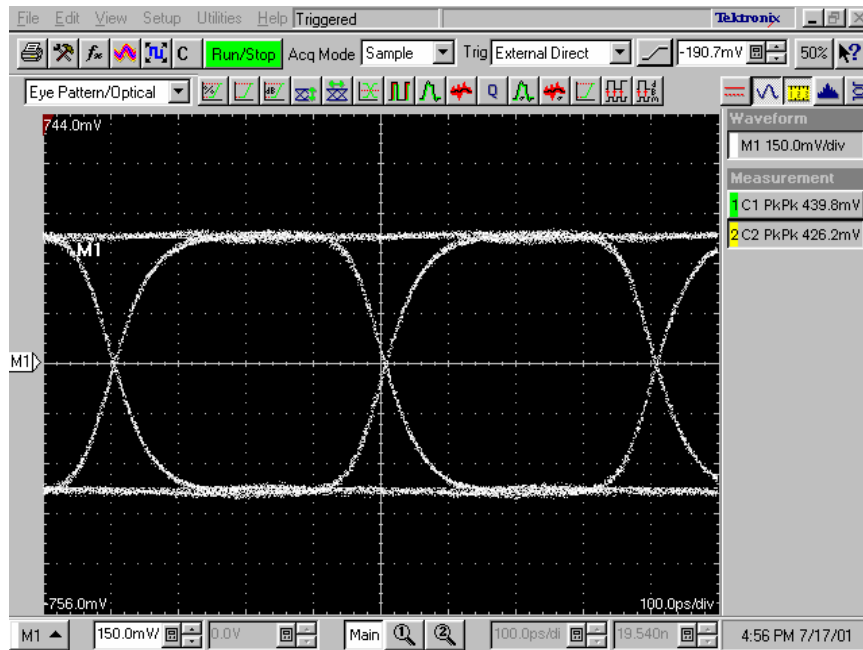

■ Best Case Conditions

- Input data: 2 Vp-p diff.
- Pattern: PRBS 2^7-1
- Temperature: 25° C
- Jitter: 1.2 ps RMS


■ Worst Case Conditions

- Input data: 10 mVppd
- Pattern: PRBS $2^{31}-1$
- Temperature: 100° C
- Jitter: 1.4 ps RMS

What about the digital cap settings?


--- Digital frequency acquisition example ---

Referenceless Frequency Acquisition

 


- Utilize a “Forbidden Zone” to infer frequency lock
 - Use this information to determine digital cap settings

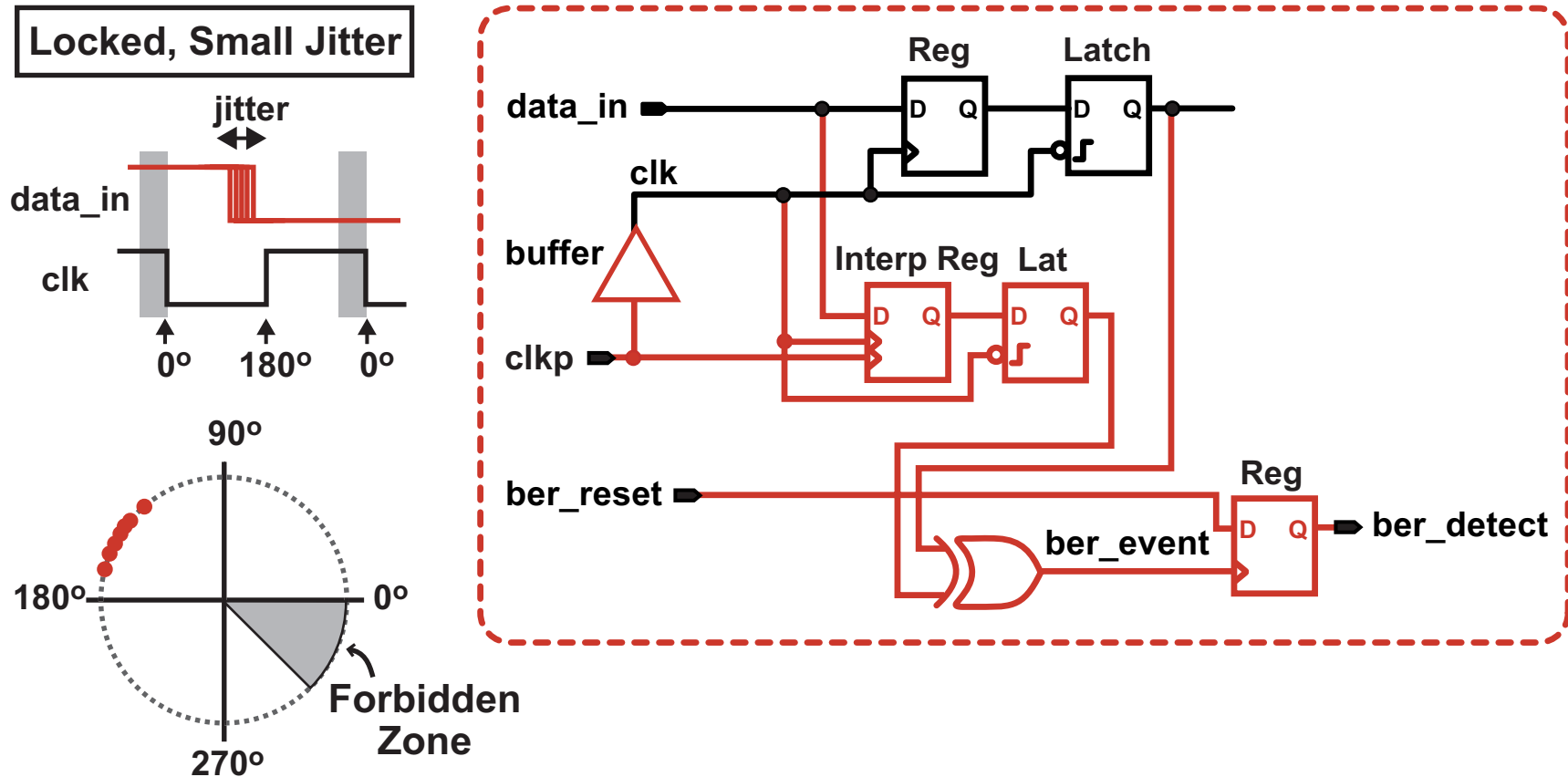A Bit Error Detector Based on Forbidden Zone




- **Key idea: sample input data at two different times**
 - Change `ber_detect` value if the two results are different
- **Implementation: achieve delayed clock with less than one buffer delay by using interpolative register**

Interpolative Latch

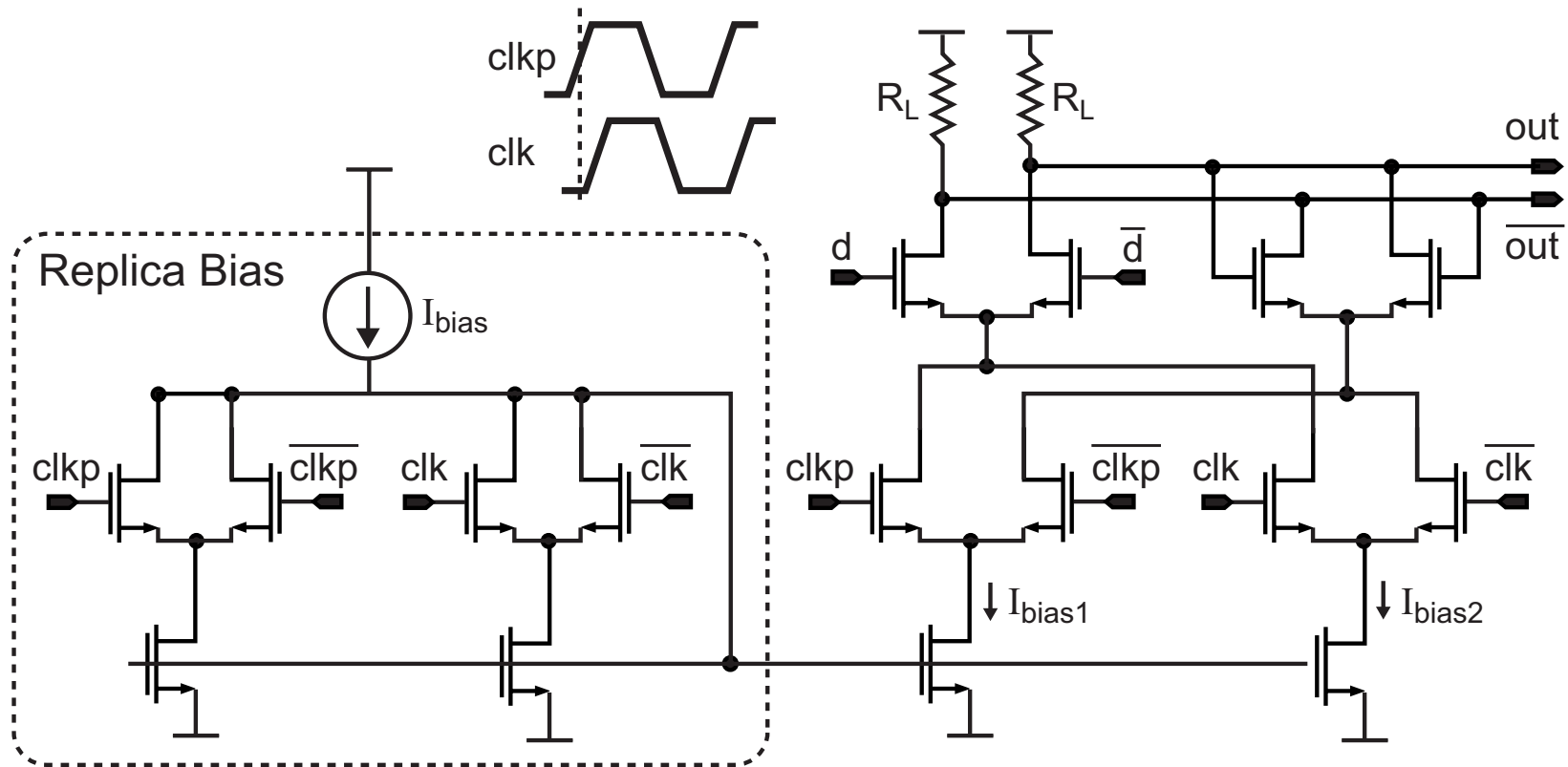


- **Effective latch time occurs *between* rising edges of input clocks (i.e., *clk* and *clkp*)**
 - **Adjustment of I_{bias1}/I_{bias2} allows adjustment of latch time**
 - **Choose $I_{bias1} = I_{bias2}$ in this application**

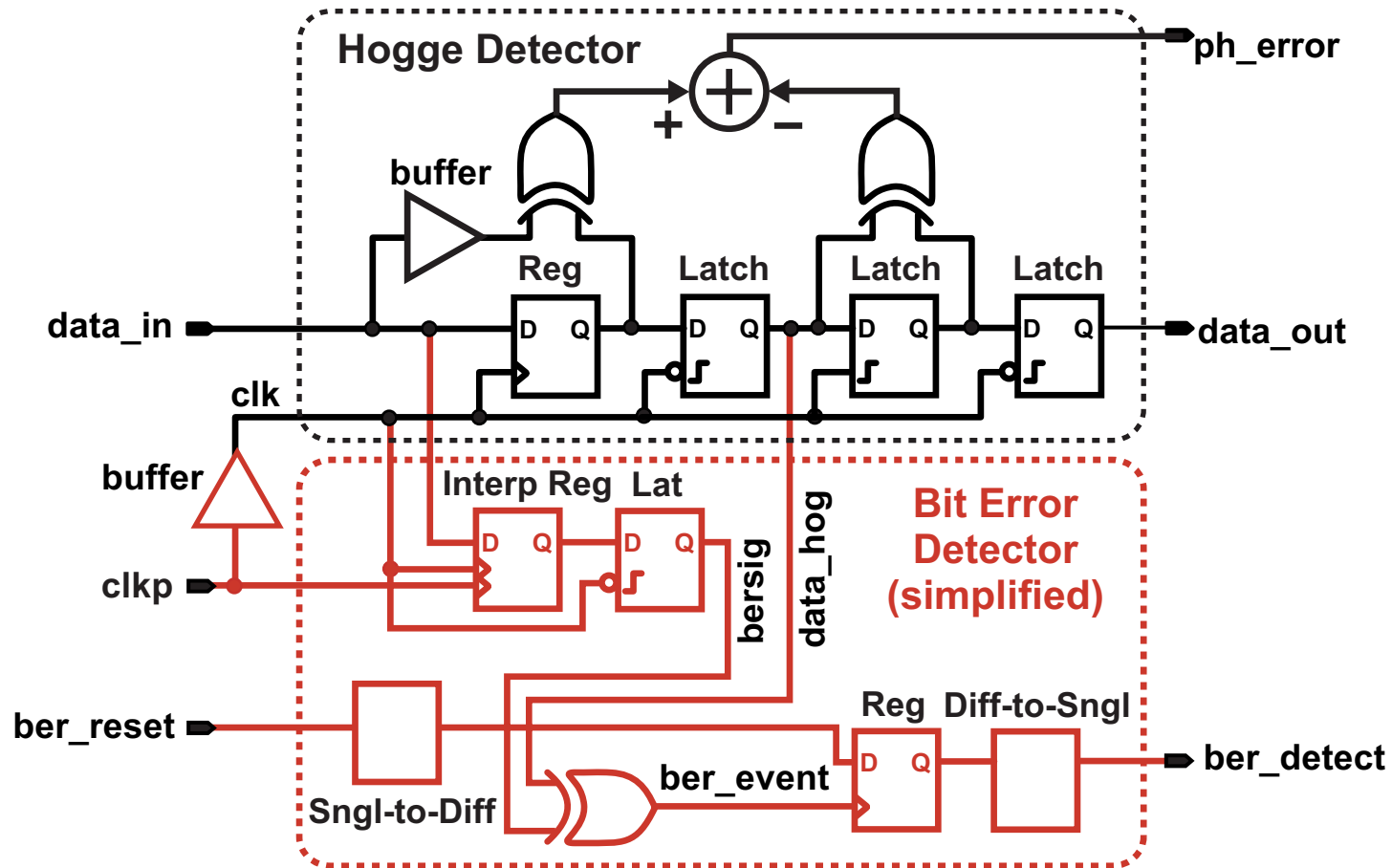Combined Hogge Detector and Bit Error Detector




- Sensing of bit errors adds minimal overhead to Hogge Det.
 - Note: Diff-to-Sngl and Sngl-to-Diff converters interface to lower speed signals (`ber_reset` and `ber_detect`)

Sensing Bit Errors

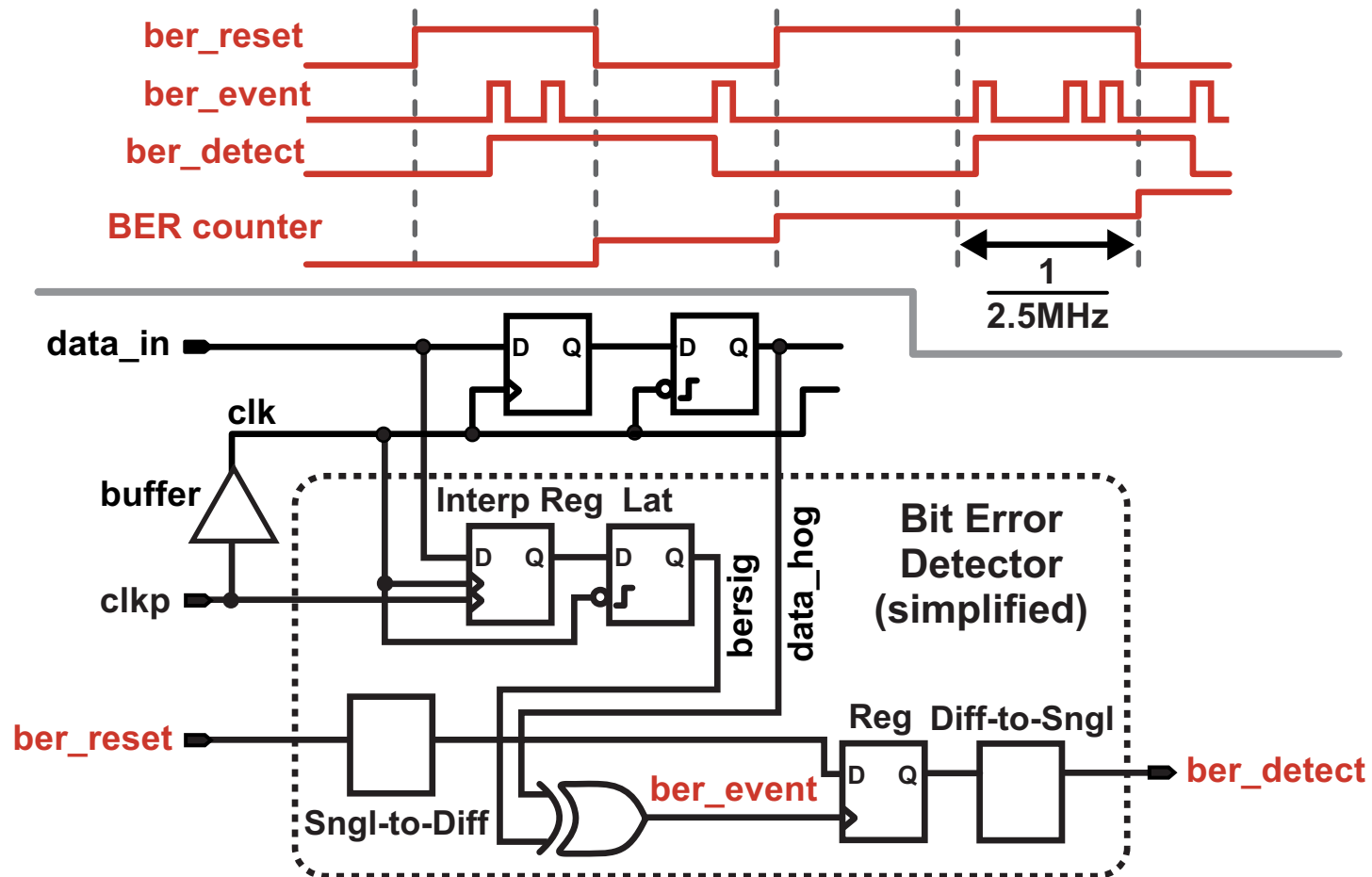

- For robust operation, only detect whether *at least one* bit error occurs within period of 2.5 MHz clock
 - BER Counter increases by one if the above occurs

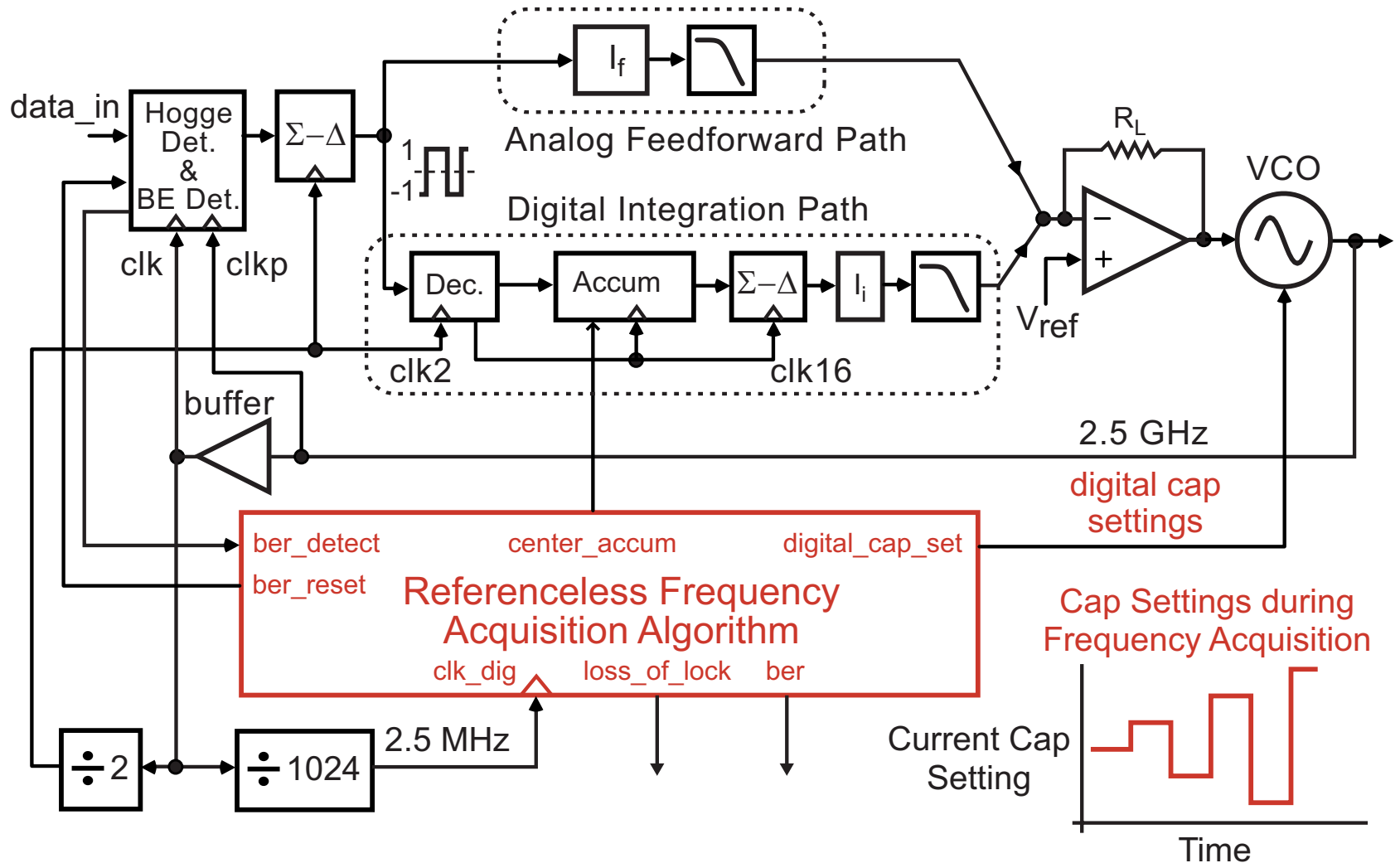
Overall System with Referenceless Frequency Acq.




- **Digital cap settings are updated as shown when bit error counts exceed a threshold value**

State Diagram for Referenceless Frequency Acq.

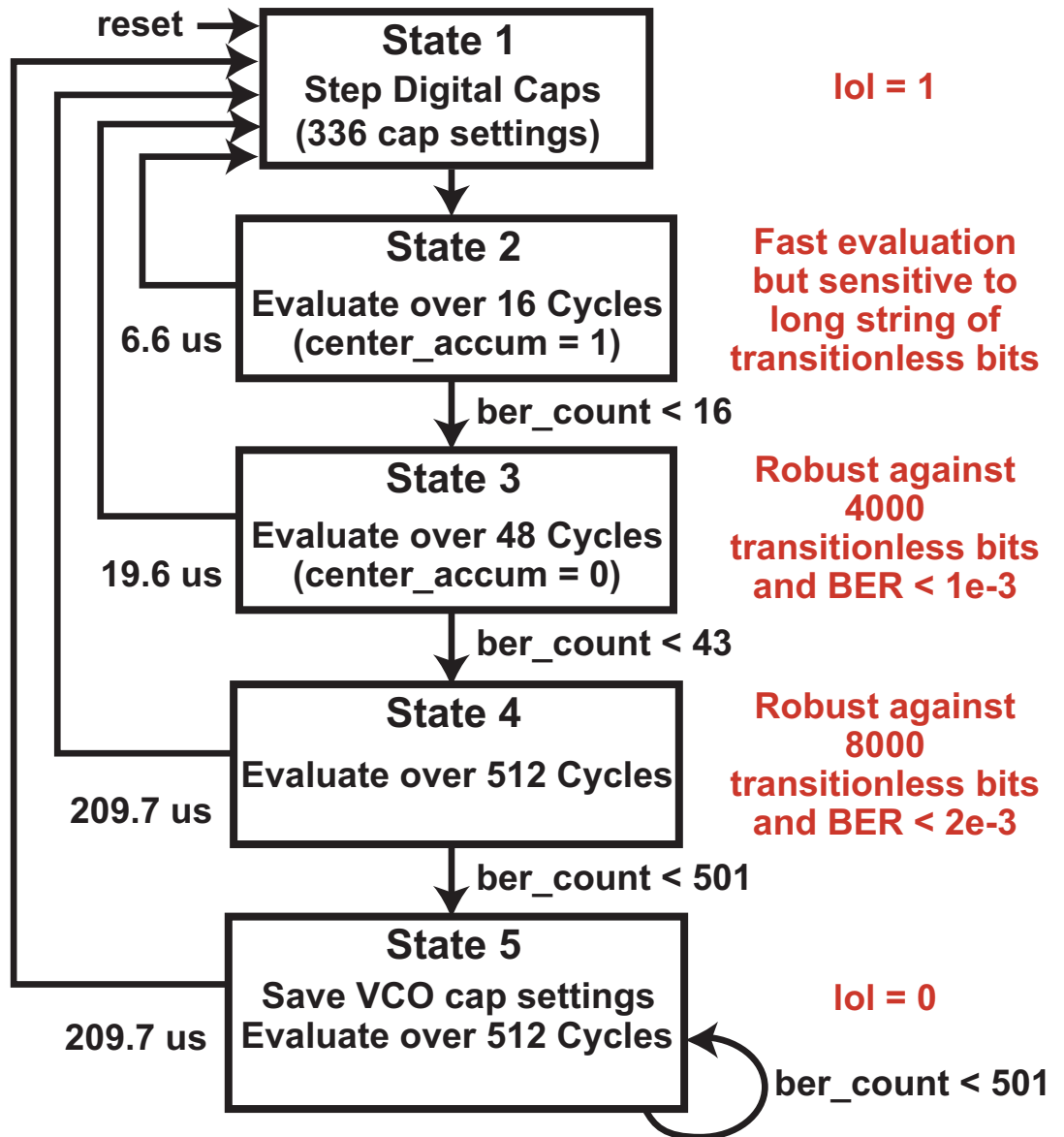- **Fast initial check of cap setting**
 - Allows speedy visitation of all cap settings
 - Assumes a wrong cap setting will usually yield a high BER count
- **Progressively slower checks of cap setting**
 - Protects against false selection of a cap setting




 Example: No Jitter, High Transition Density




- **BER counter goes to zero when correct digital cap setting is achieved**

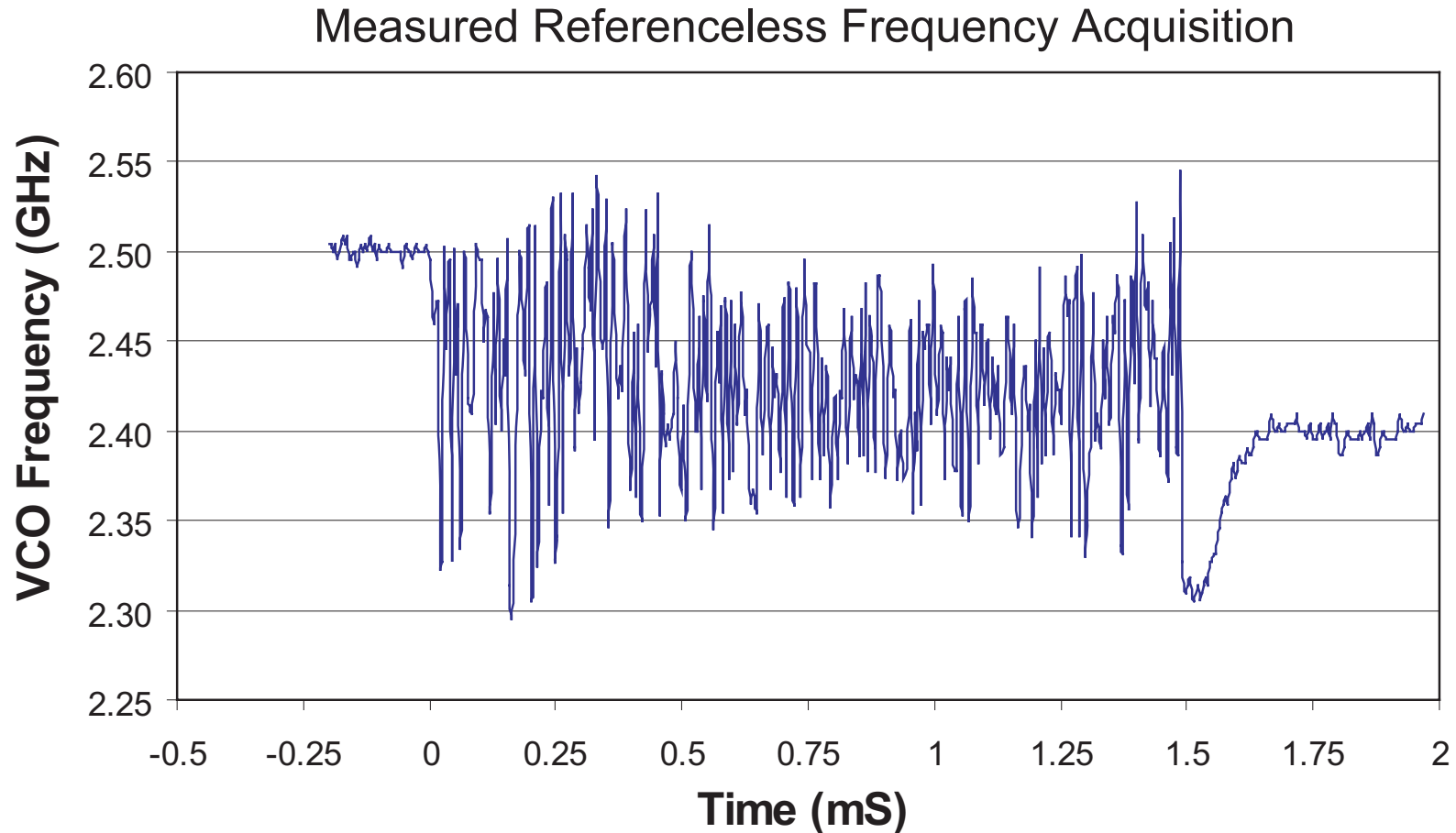Measured Referenceless Frequency Acquisition



- **Change data input from 2.5 Gbit/s to 2.4 Gbit/s**
 - In this case, frequency acquisition completes in < 2 ms

 
Example: High Jitter, Low Transition Density



- **BER Counter continues to have non-zero values even after correct digital cap setting is achieved**
 - This information can be used to estimate BER of CDR

Measured BER Estimation versus Actual BER

Measured BER Estimate Vs Actual BER

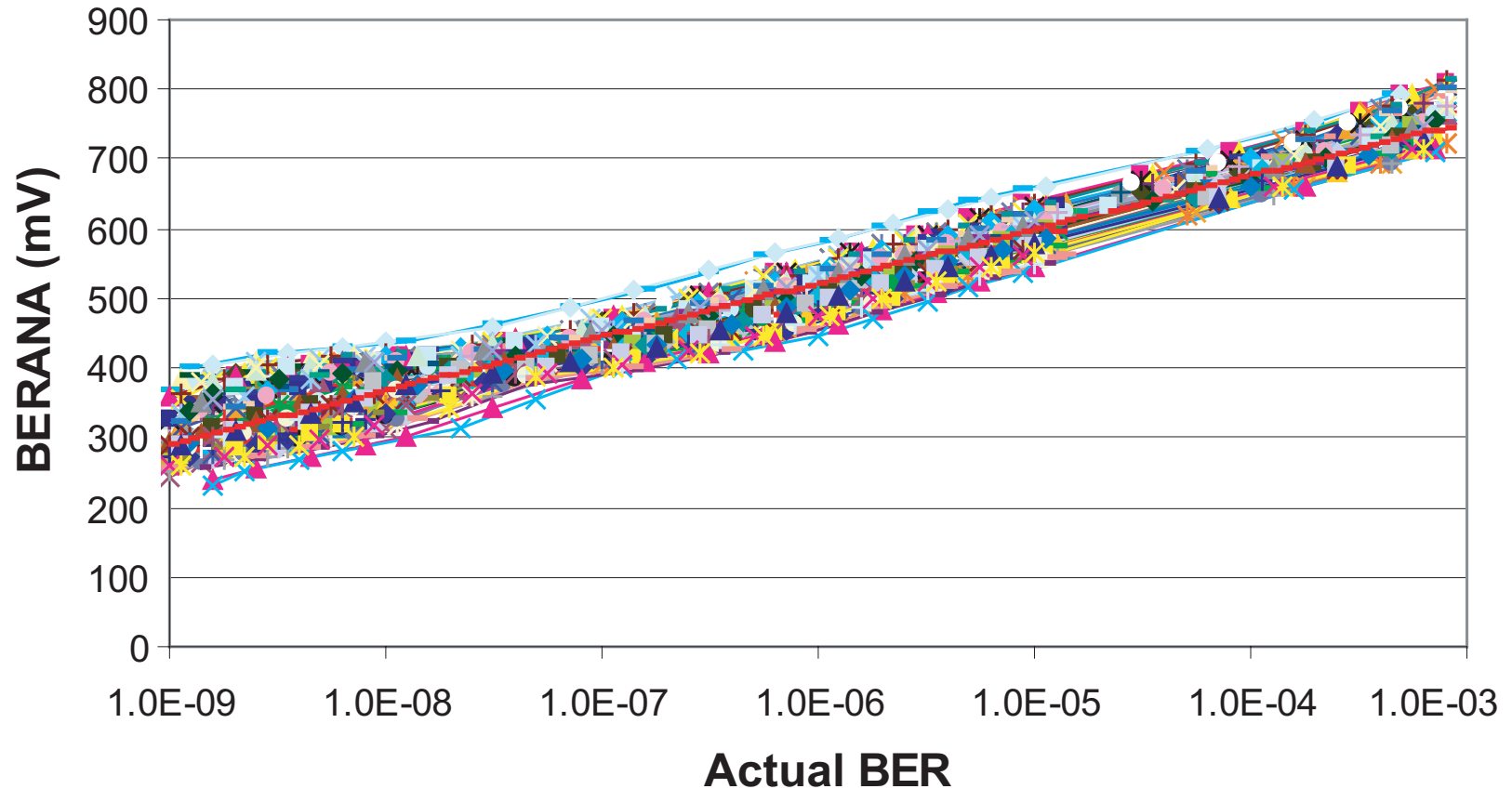

- **Above measured results occur across:**
 - **Worst case split lot corners**
 - **Temp: -40 to 85 degrees C, Voltage supply: 1.62 to 3.63 V**

Conclusion

- **Mixed-signal techniques allow high performance to be achieved with low power and compact area**
 - Phase-to-digital converter: combined Hogge PD and First Order Sigma-Delta A/D
 - Hybrid Loop Filter
 - All-digital frequency acquisition with minimal overhead
- **Measured results confirm high performance**
 - All SONET specifications met with 1.2 ps typical rms jitter
 - Referenceless frequency detection with BER monitor

**Mixed-signal design philosophy:
Leverage *both* analog and digital circuits such that
their relative strengths are fully utilized**