

***Short Course On  
Phase-Locked Loops and Their Applications  
Day 5, PM Lecture***

***Advanced PLL Examples (Part II)***

**Michael Perrott**

**August 15, 2008**

**Copyright © 2008 by Michael H. Perrott**

**All rights reserved.**


# Outline

---

- **Optical/Electrical Phase-Locked Loops**
- **High Speed CDR Techniques**
- **VCO-based A/D Conversion**
- **MEMS-based clocking**

# Optical/Electrical Phase Locking


---

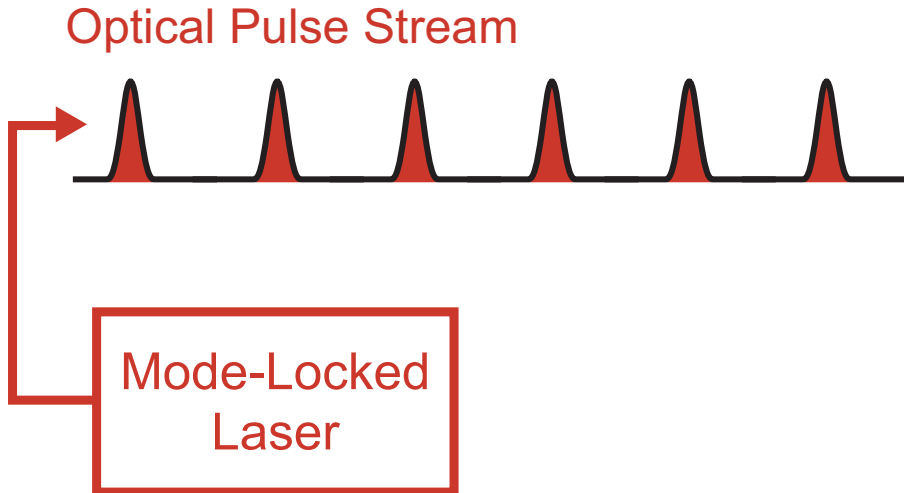

- **Mode-locked lasers provide optical clock streams with excellent jitter characteristics**
  - **14 fs jitter (10 Hz to 375 MHz) has been achieved**  
J.B. Schlager et. al, Opt. Lett. 28, 2411-2413 (2003)


**Can we lock an electrical clock to the optical pulse stream AND maintain low jitter?**

# Optical/Electrical Phase Locked Loops

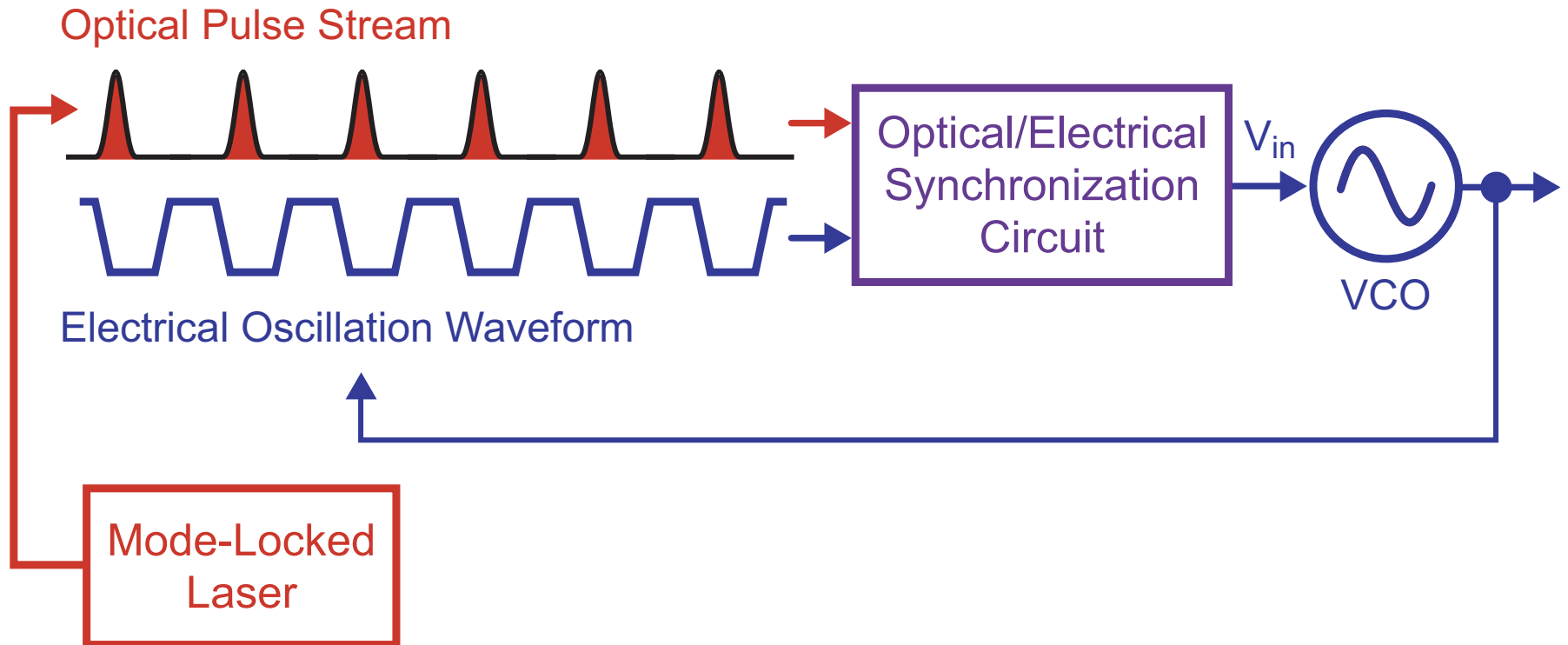


- **Generate a frequency tunable electronic clock source by using a voltage controlled oscillator (VCO)**
- **Lock VCO output to pulse stream using an optical/electrical synchronization circuit**
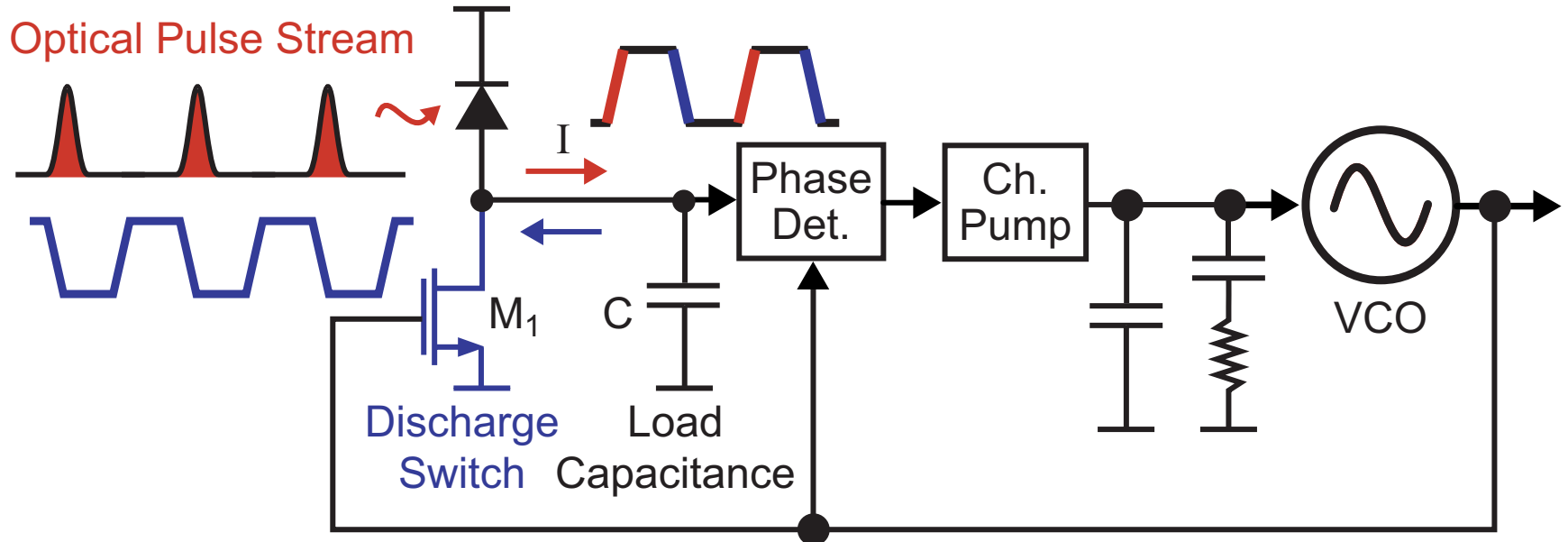
# Method 1 of Implementing the Synchronization Circuit




- Create an electrical square wave reference signal by using a photodiode and discharge switch
- Lock the VCO output to the electrical reference signal by using a conventional electronic phase locked loop
 
# Key Idea of Method 1: Measure Phase Based on Edges



- Relative phase positions of optical pulses are captured by the edge locations of the electrical reference waveform


# Issue 1: Noise

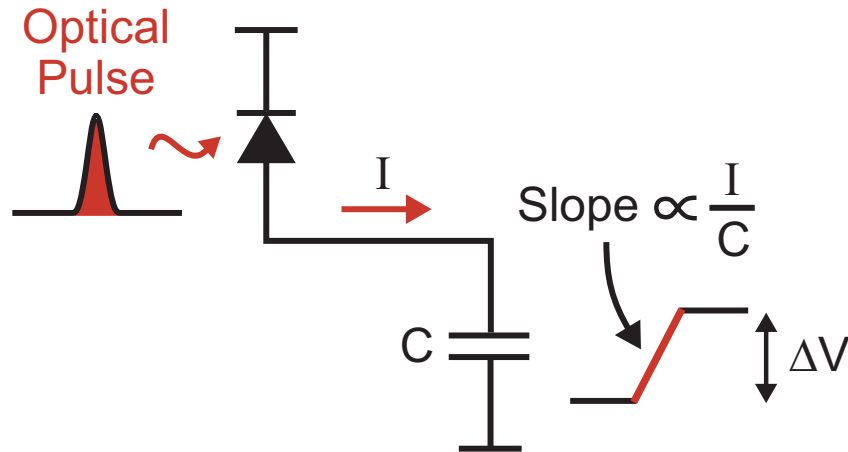

- The slope of the transition edges is limited by the current/capacitance ratio at the photodetector output
- Higher edge slopes are desirable to achieve low noise
  - Voltage noise present in the reference waveform translates to timing jitter according to the edge slope

Achievable noise performance is limited by the  $I/C$  ratio of the electronics (i.e., photodiode and the capacitive load it drives)
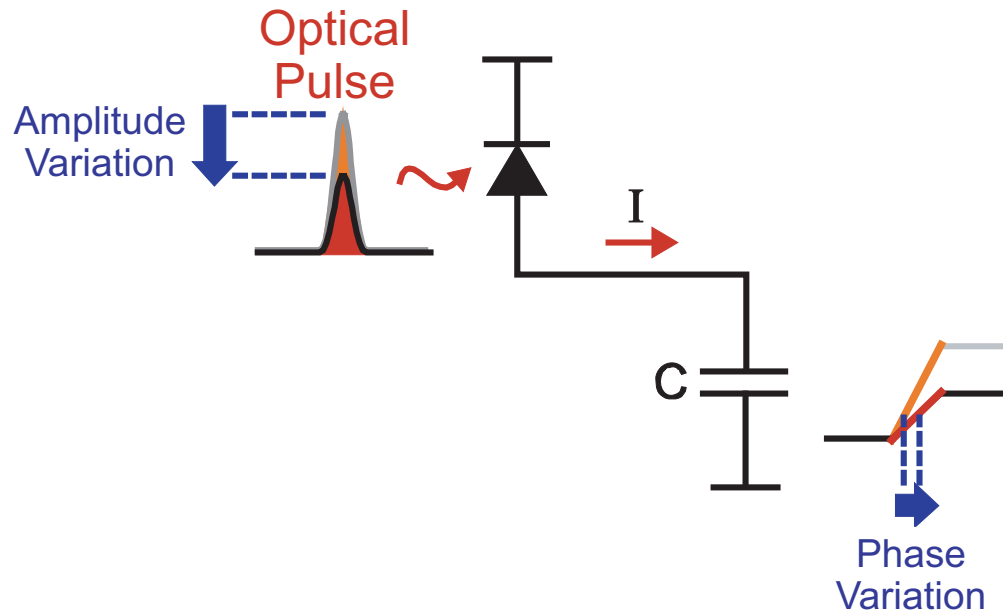
## Issue 2: Sensitivity to Amplitude Variation




- Practical pulse streams from mode-locked lasers exhibit undesired amplitude variation
- Phase detection based on the edge-based approach above translate pulse amplitude variation into phase variation




***Can We Do Better?***

# Proposed Approach

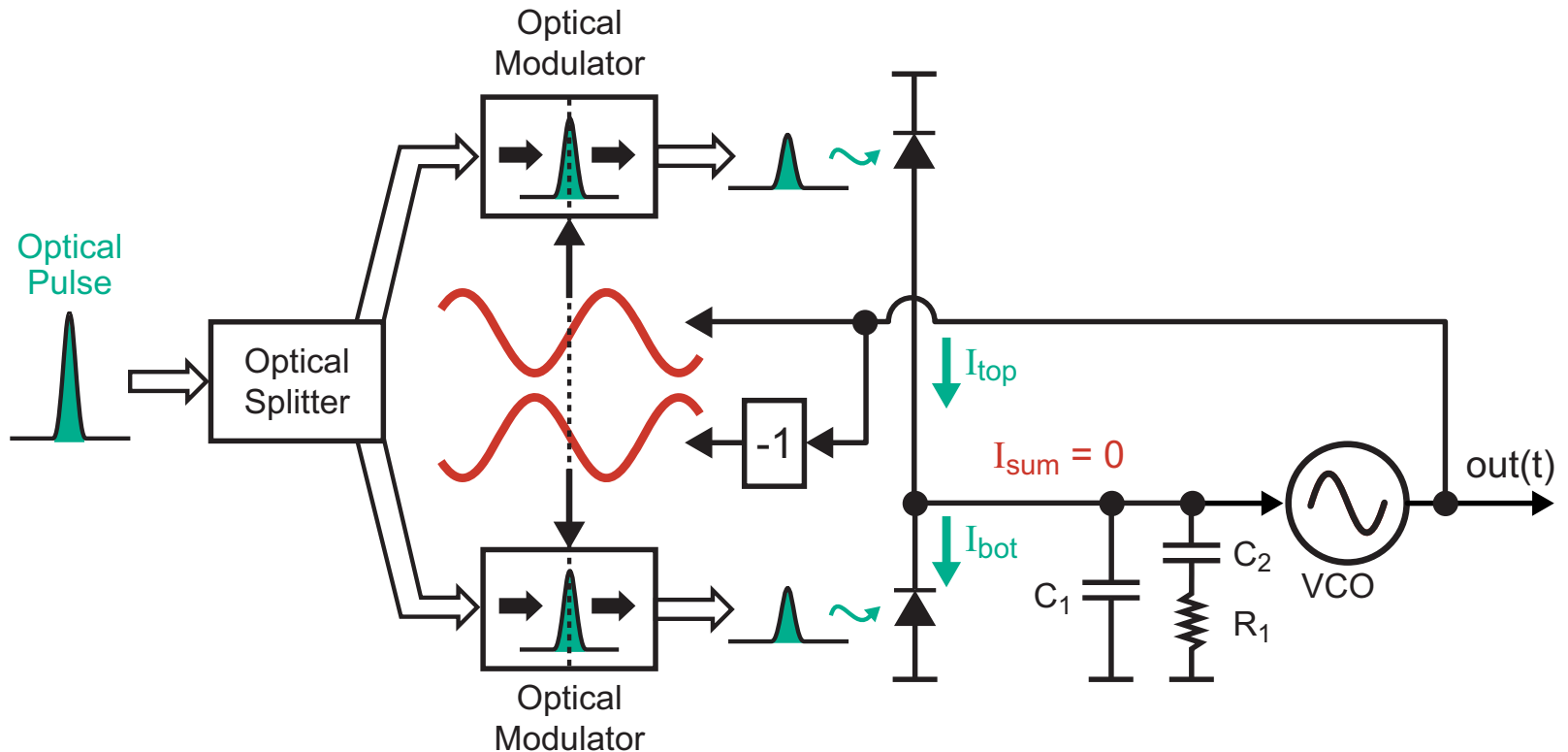


- **Move phase comparison into the optical domain**
  - Passing an optical pulse through an optical modulator effectively samples its input value at the time
- **Use photodetectors to detect the average *power* of the modulator outputs**
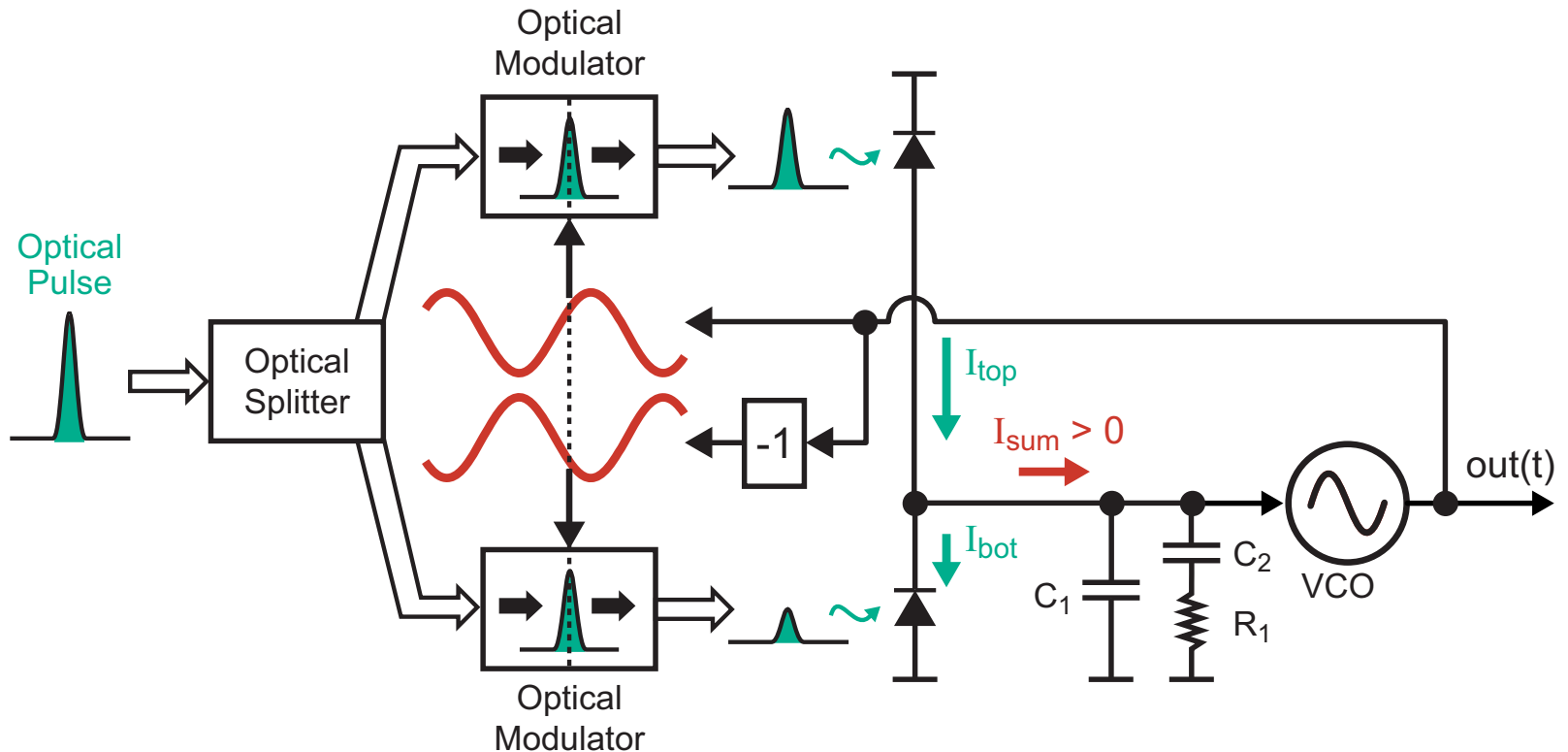
# Impact of VCO Output Phase Being Too Early



- An imbalance of modulator output power levels causes a difference in current between the top and bottom photodetectors
  - The resulting current causes the VCO input voltage to rise

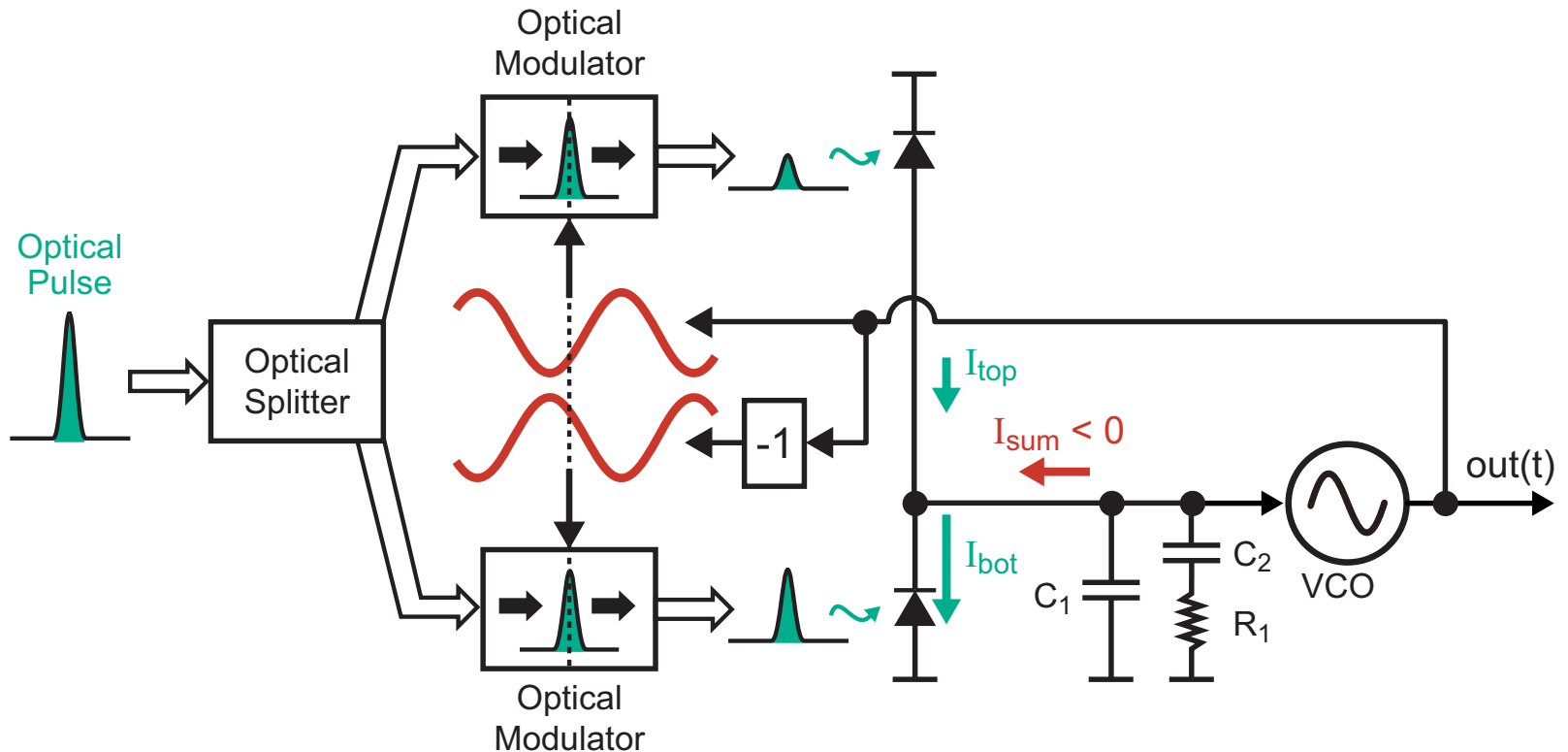
## Impact of VCO Output Phase Being Too Late



- **Current imbalance shifts the opposite way, so that the VCO control voltage now starts to fall**

**Accurate measurement of phase error is achieved**

 
# Approach is Insensitive to Amplitude Variations



- **Amplitude fluctuations impact the top and bottom currents equally (at least to first order)**
  - The VCO control voltage remains undisturbed
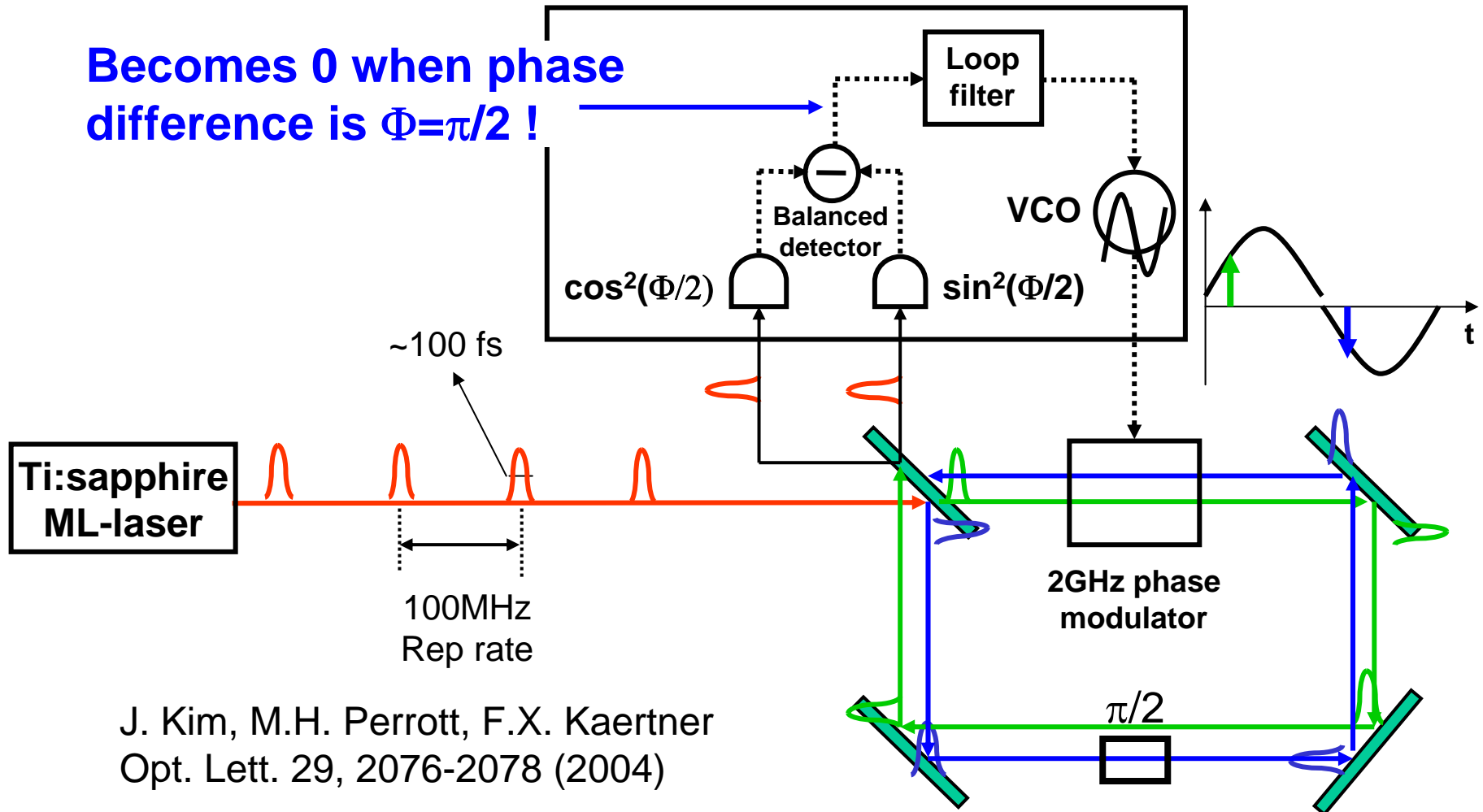
# Actual Implementation (Jung-Won Kim)

Becomes 0 when phase difference is  $\Phi = \pi/2$  !




J. Kim, M.H. Perrott, F.X. Kaertner  
Opt. Lett. 29, 2076-2078 (2004)

- Use Mach-Zehnder interferometer within Sagnac-loop
  - Robust against temperature fluctuations

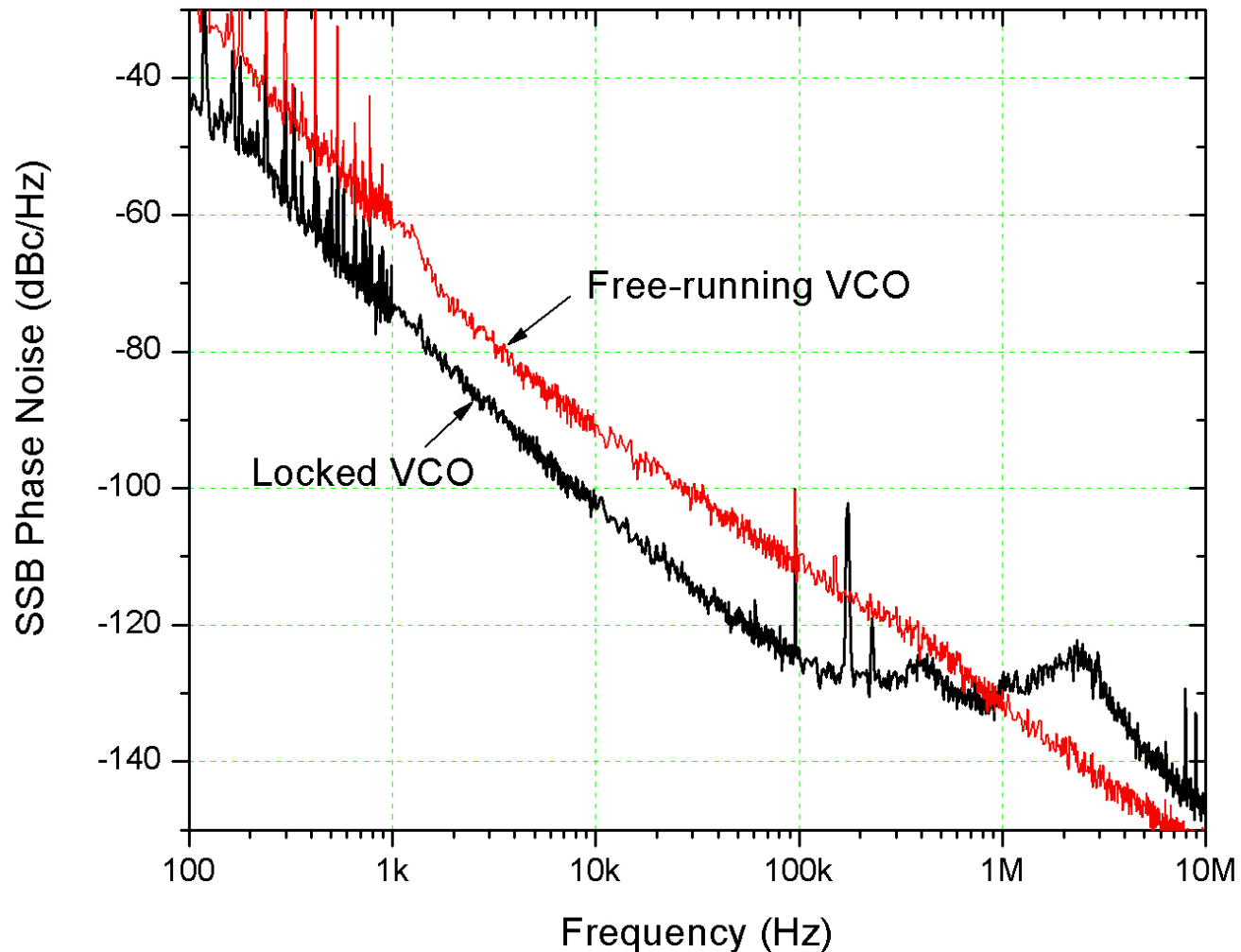
# Measured Results

- Locking is achieved with  $> 1$  MHz bandwidth


 
# Limitation in Achieving Low Absolute Jitter


- Noise of laser noise dominates at low frequencies




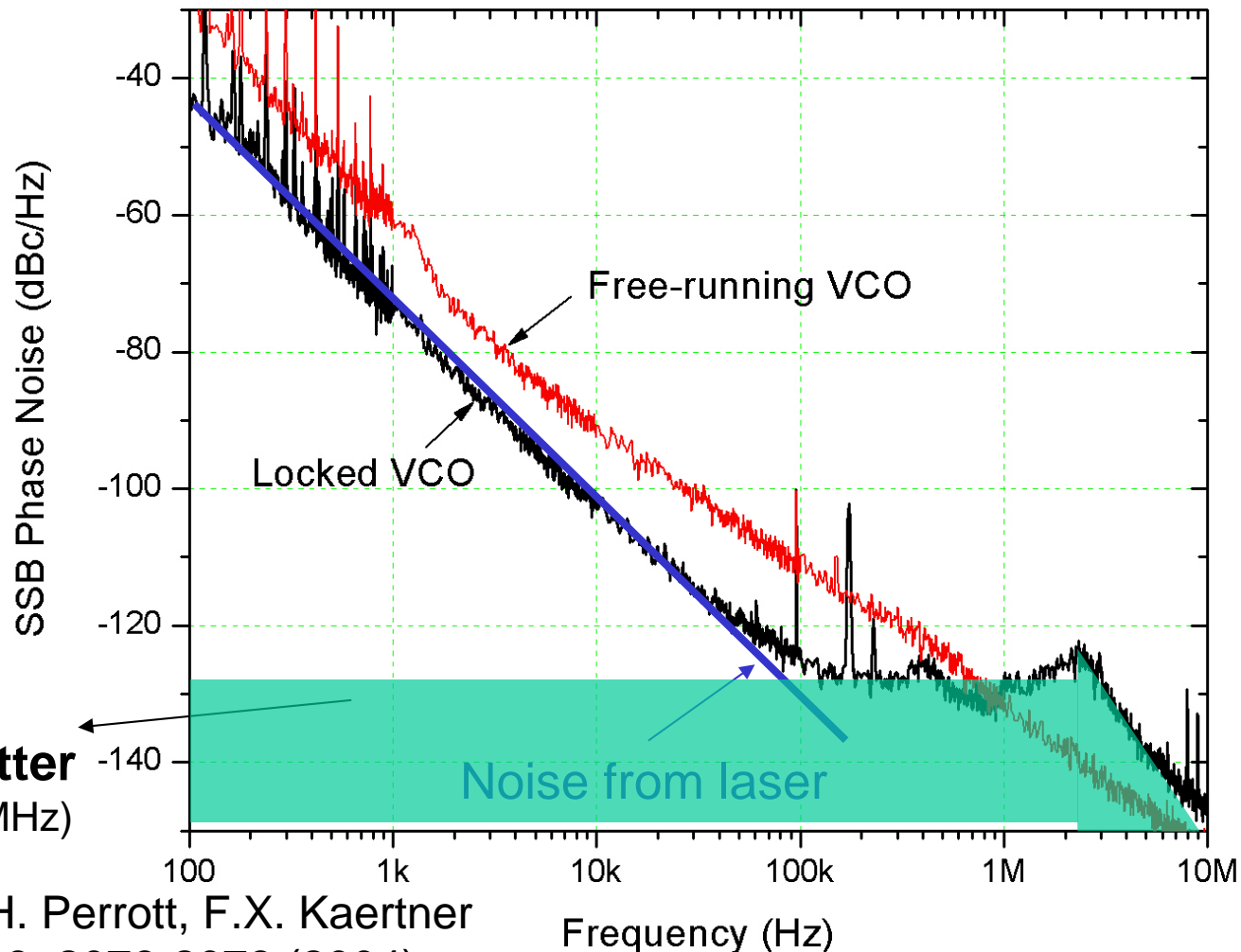
# Estimate of Relative Noise Between VCO and Laser

- A separate experiment led to the estimate below



J. Kim, M.H. Perrott, F.X. Kaertner  
Opt. Lett. 29, 2076-2078 (2004)

# Conclusions


---

- **Optical components have the following benefits for phase-locked loops:**
  - **Mode-locked lasers provide extremely low jitter pulse sequences**
  - **Optical channels provide extremely high bandwidth**
  - **Optical components allow extremely fast memoryless processing of signals (such as multiplication)**
- **We demonstrated a low jitter phase-locked loop leveraging optical pulses as input and optical/electronic phase detection**

**Many more exciting opportunities will arise as we obtain higher integration levels for optical components**


***High Speed Clock and Data Recovery  
Circuit Techniques***
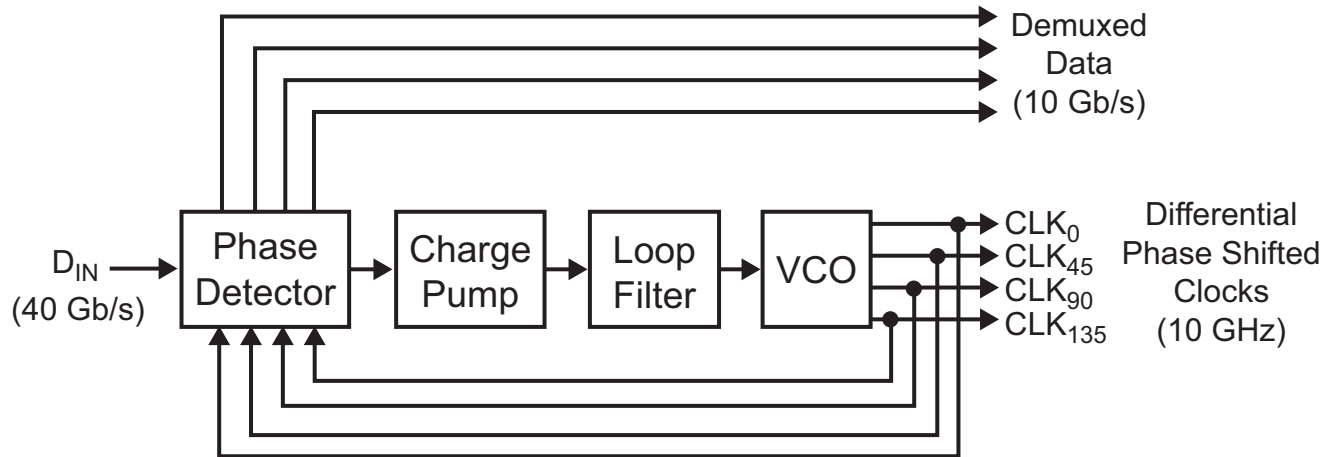
# A 40 Gb/s CDR in 0.18u CMOS! (Lee and Razavi)



- **Achieves high speed operation using interleaving**
  - 4 parallel 10 Gb/s detectors are fed by an 8-phase VCO
    - 4 phases used for sampling registers
    - 4 phases used for bang-bang phase detection registers
- **Key challenges**
  - **Low jitter and low mismatch between clock phases**
    - We will look at this issue in detail here
  - **Achievement of 10 Gb/s sampling/bang-bang detection**

 
# The Need for Low Mismatch Between Clock Phases



- **8-phases generated by 4 VCO clock signals and their complements**
- **Desired spacing between clock signals is only 12.5 ps!**
  - **Must meet setup and hold times of each 10 Gb/s sampler and phase detector register (limited by 0.18u technology)**
  - **Mismatch and jitter on clock phases quickly eats into any margin left over after meeting setup/hold times**
    - Unacceptable bit error rates can easily result


# A Method to Generate Clock Phases

---

 

- Use transmission delay lines to generate each phase
- Advantage over using buffers as delay elements
  - Wide bandwidth and lower noise
  - Mismatch only a function of geometry variation
    - Buffer mismatch a function of both geometry and device variation (i.e., doping variation, etc.)
- Issue: transmission line is big
  - Loss (and finite bandwidth) due to finite resistance of metal
  - Long distance between clock phase outputs undesirable

 
# Realize a Lumped Parameter Version of Trans. Line



- Approximate transmission line as an LC ladder network
  - Allows a much more compact implementation
  - Offers the same advantage of having mismatch depend only on geometry
- Issue: now that mismatch has been dealt with, how do we achieve low jitter?

# Combine VCO and Phase Generator


---

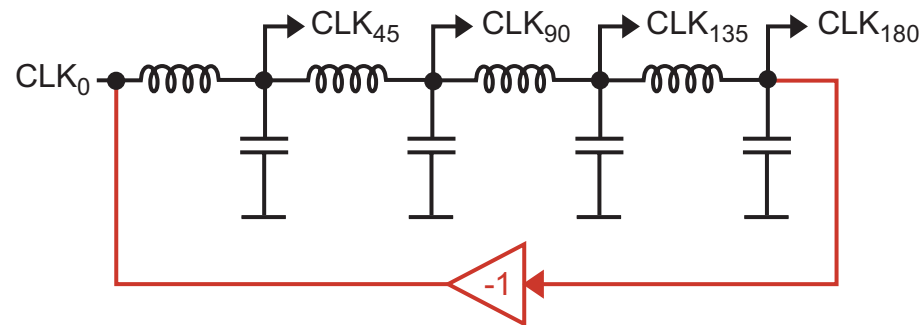

- Can satisfy Barkhausen criterion by inverting output of line and feeding back to the input
  - Looks a bit like a ring oscillator, but much better phase noise performance



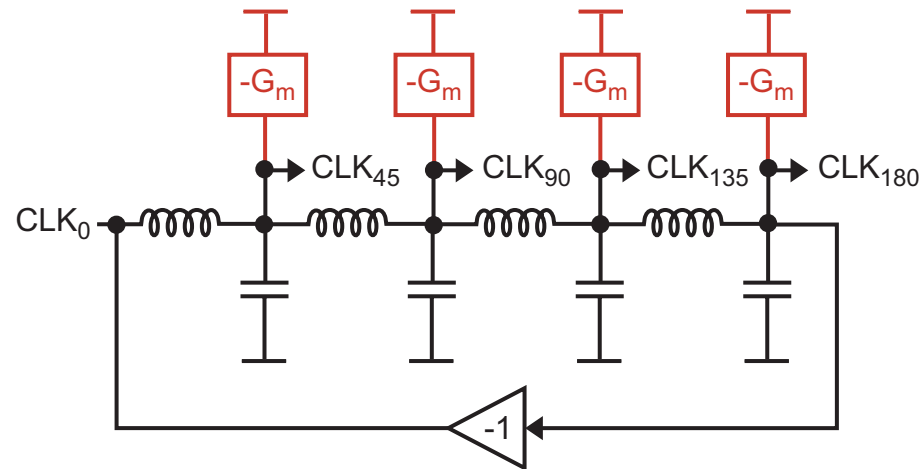
# Sustain Oscillation by Including Negative Resistance



- Place negative resistance at each phase to keep amplitudes identical
  - Must be careful to minimize impact on mismatch
- Issue: how do you match feedback path from  $CLK_{180}$  to  $CLK_0$  with other phases?

# Use a Circular Geometry!

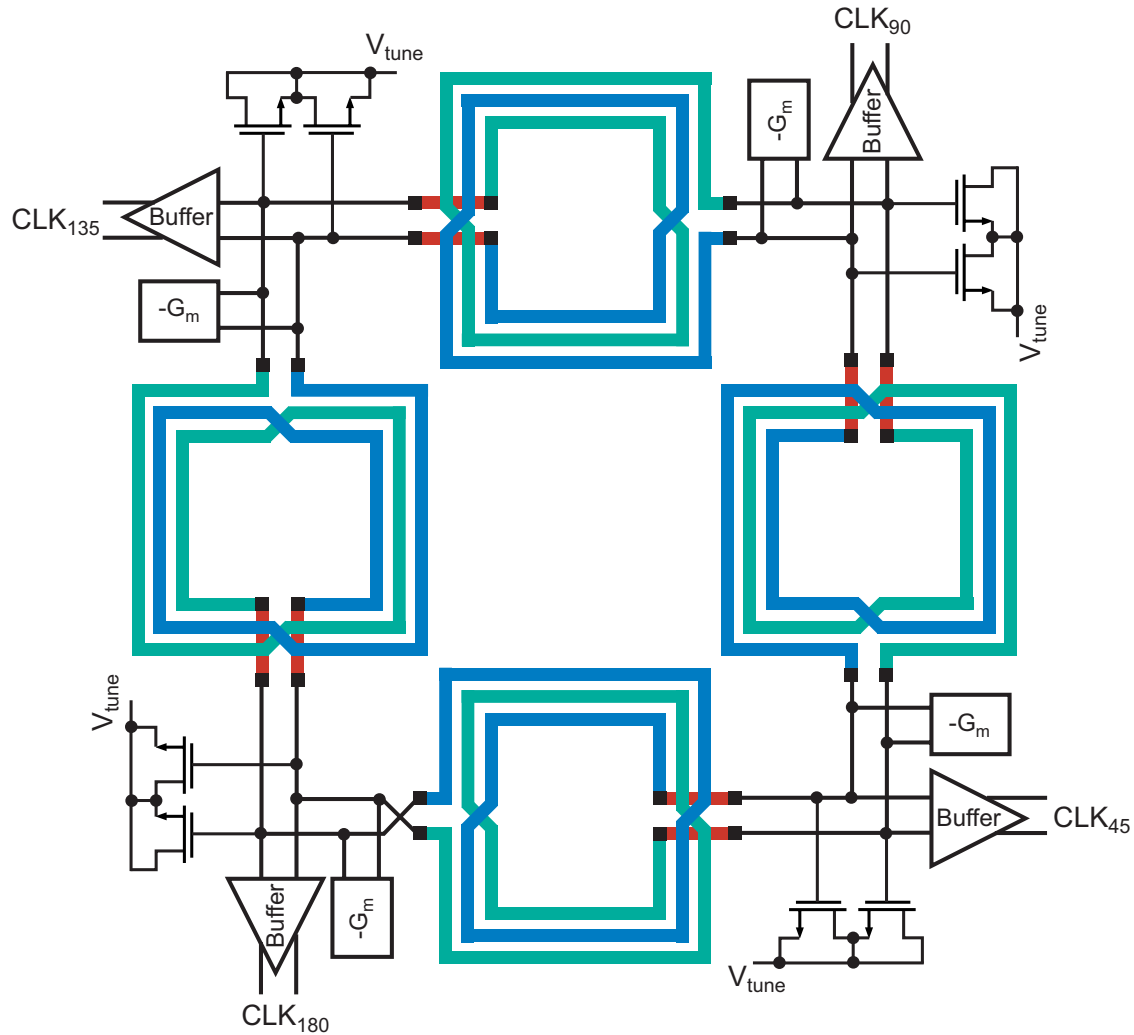

- Note use of differential inductors, etc.

## ***Other Nice Nuggets in the Lee and Razavi Paper***


---

- **Phase detection using 4 bang-bang detectors**
  - Clever combining of individual detectors to create an overall control voltage
  - Note: Bang-bang detection linearized by metastable behavior of registers
- **Achievement of 10 Gb/s registers in 0.18u CMOS**
  - Leverages a large amplitude clock signal using a tuned VCO buffer
  - Uses SCL registers with resistor loads – bottom current sources eliminated to leverage large amplitude clock
- **Fast XOR gate and amplifier structures**

**Take a look at the paper for more details:  
“A 40-Gb/s Clock and Data Recovery Circuit in 0.18-um  
CMOS Technology”, Jri Lee and Behzad Razavi, JSSC, Dec. 2003**

***Leveraging VCO-based Quantization to  
Achieve Low Power, Wideband A/D  
Conversion for Multi-Standard RF Front-ends***


# Motivation

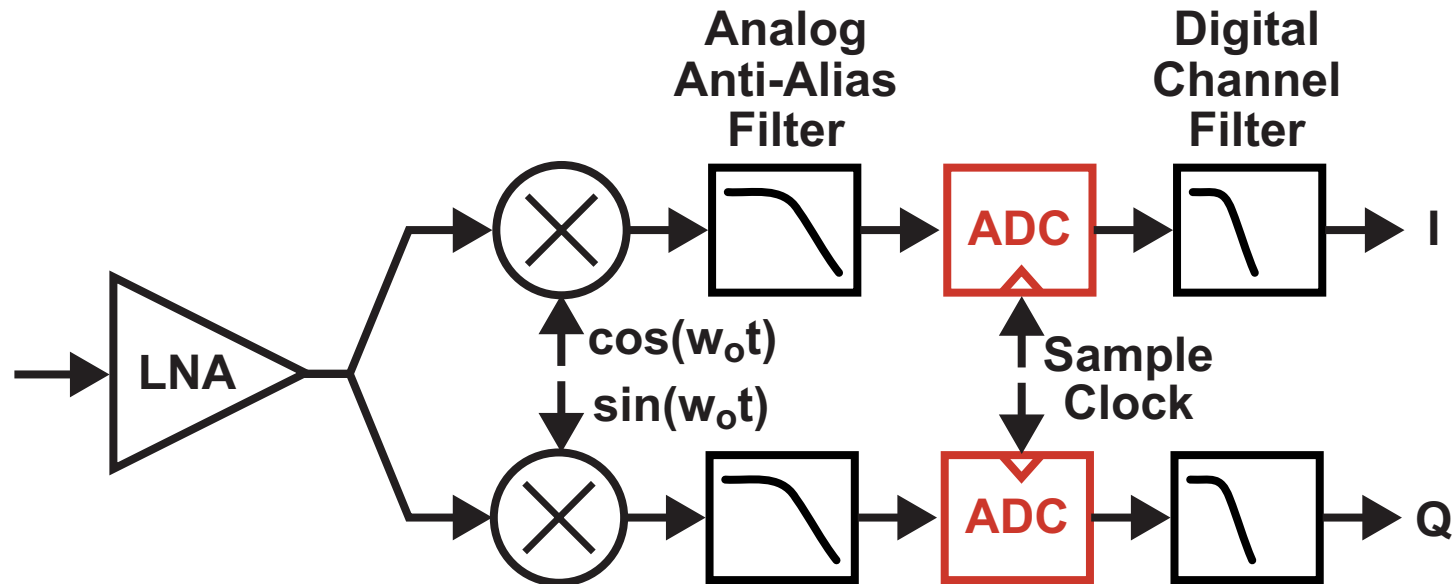

- A highly digital receive path is very attractive for achieving multi-standard functionality
- A key issue is achieving a wide bandwidth ADC with high resolution and low power
  - Minimal anti-alias requirements are desirable for simplicity

**Continuous-Time Sigma-Delta ADC structures have very attractive characteristics for this space**
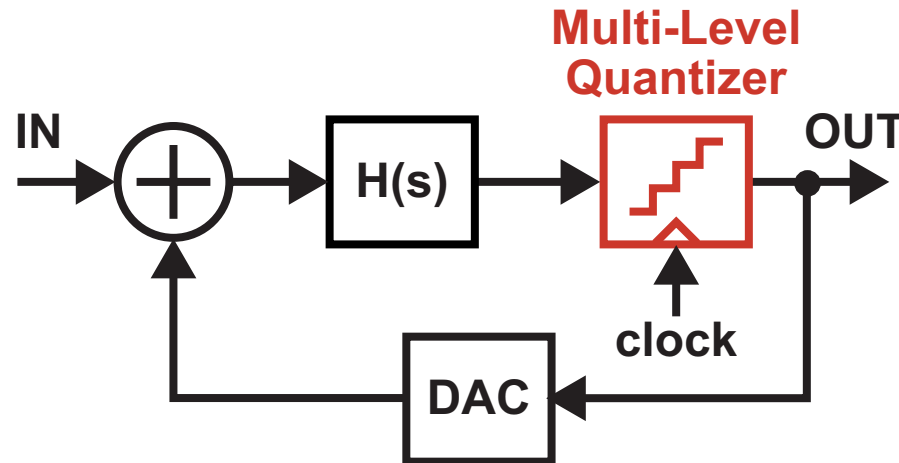
# A Basic Continuous-Time Sigma-Delta ADC Structure



## ■ Key characteristics

- Operation based on oversampling and feedback
- Sampling occurs at the quantizer *after* filtering by  $H(s)$
- Quantizer noise is shaped according to choice of  $H(s)$ 
  - High open loop gain required to achieve high SNR
  - Digital filtering/decimation required for signal extraction

**We will focus on achieving an efficient implementation of the multi-level quantizer by using a ring oscillator**

## ***Why are VCO-based converters interesting?***

---

- **Converters are building blocks for mixed-signal systems**
  - Communication systems (both wireless and wireline)
  - Frequency synthesizers
- **Standard implementations are problematic**
  - High-performance analog functionality is becoming more difficult to achieve using traditional methods
  - Shrinking power supply, limited intrinsic gain, etc.
- **Voltage controlled oscillators are inherently mixed-signal**
  - Analog input voltage
  - Binary (digital) output levels
  - Highly digital implementation


**Can voltage controlled oscillators offer excellent analog performance with a highly digital implementation?**

***A 10-bit 20MHz 38mW 950MHz CT  $\Sigma\Delta$  ADC with a  
5-bit noise-shaping VCO-based Quantizer and  
DEM circuit in 0.13 $\mu$  CMOS***

**Matthew Z. Straayer, Michael H Perrott**



 
# Voltage Controlled Oscillator (VCO) fundamentals



$$F_{\text{out}}(t) = K_v \cdot V_{\text{tune}}(t)$$
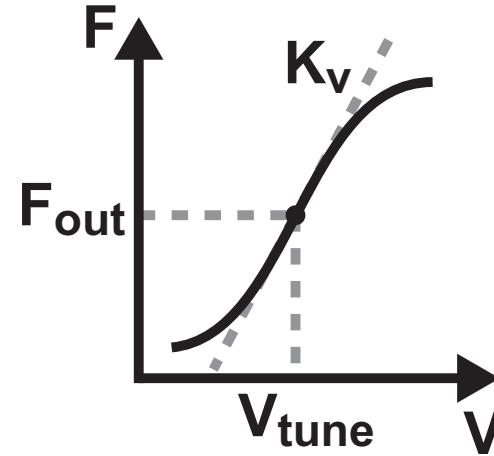
$$\Phi_{\text{out}}(t) = \int_0^t 2\pi \cdot K_v \cdot V_{\text{tune}}(\tau) \cdot d\tau$$




$$K_v = \frac{dF_{\text{out}}}{dV_{\text{tune}}}$$


- Voltage-to-frequency is a linear relationship
- Voltage-to-phase is an integration

Can we leverage these analog signal processing functions?

# Concept of VCO-based converters

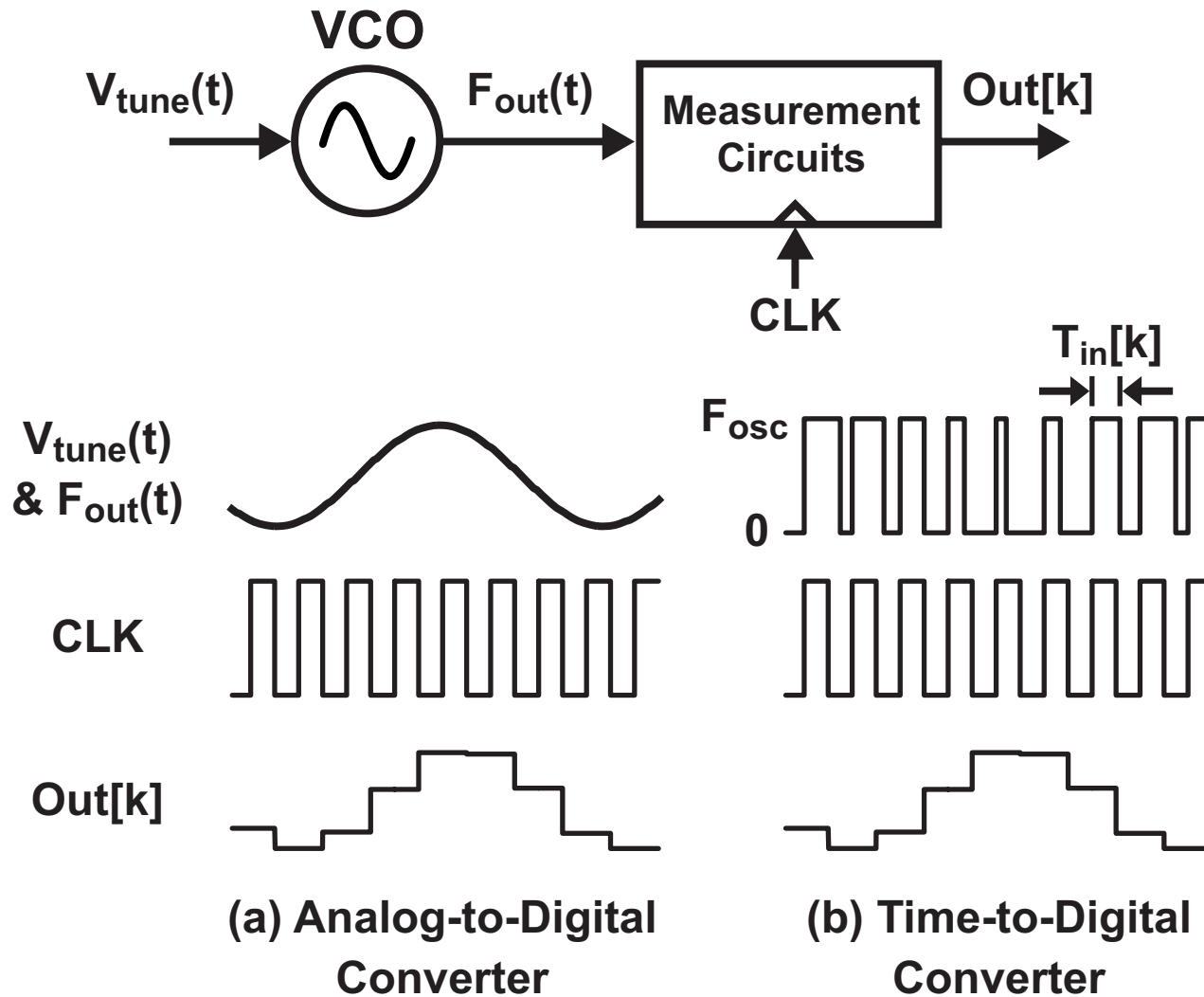

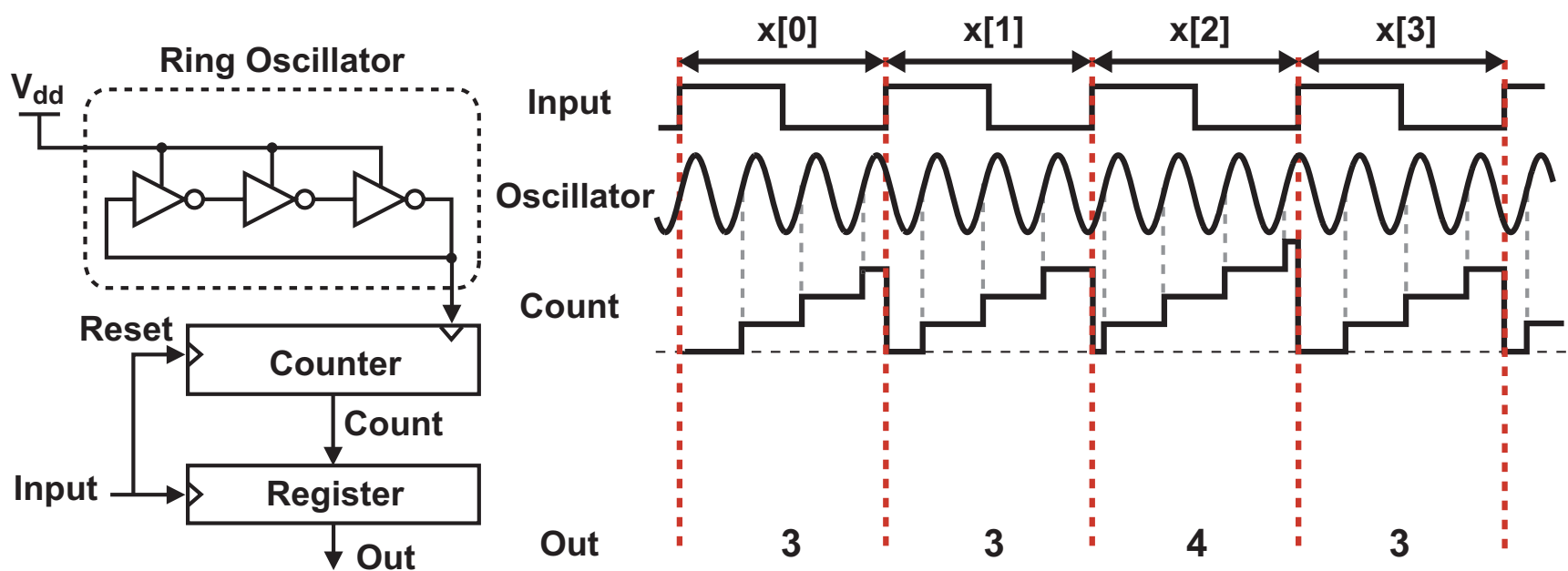
# Consider Measurement of the Period of a Signal




- Use digital logic to count number of oscillator cycles during each input period
  - Assume that oscillator period is much smaller than that of the input
- Note: output count per period is not consistent
  - Depends on starting phase of oscillator within a given measurement period
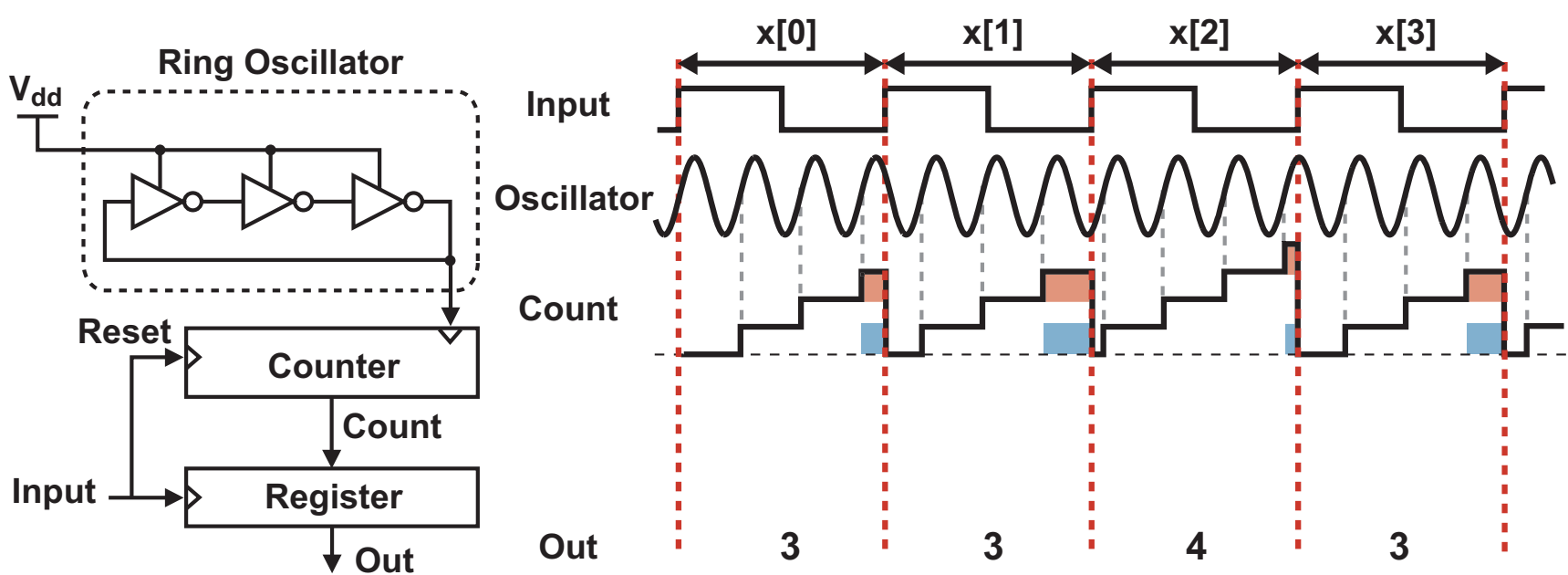
# Examine Quantization Error in Measurements



- Quantization error varies according to starting phase of the oscillator within a given measurement period
  - Leads to *scrambling* of the quantization noise
- But there is something rather special about the scrambling action ...
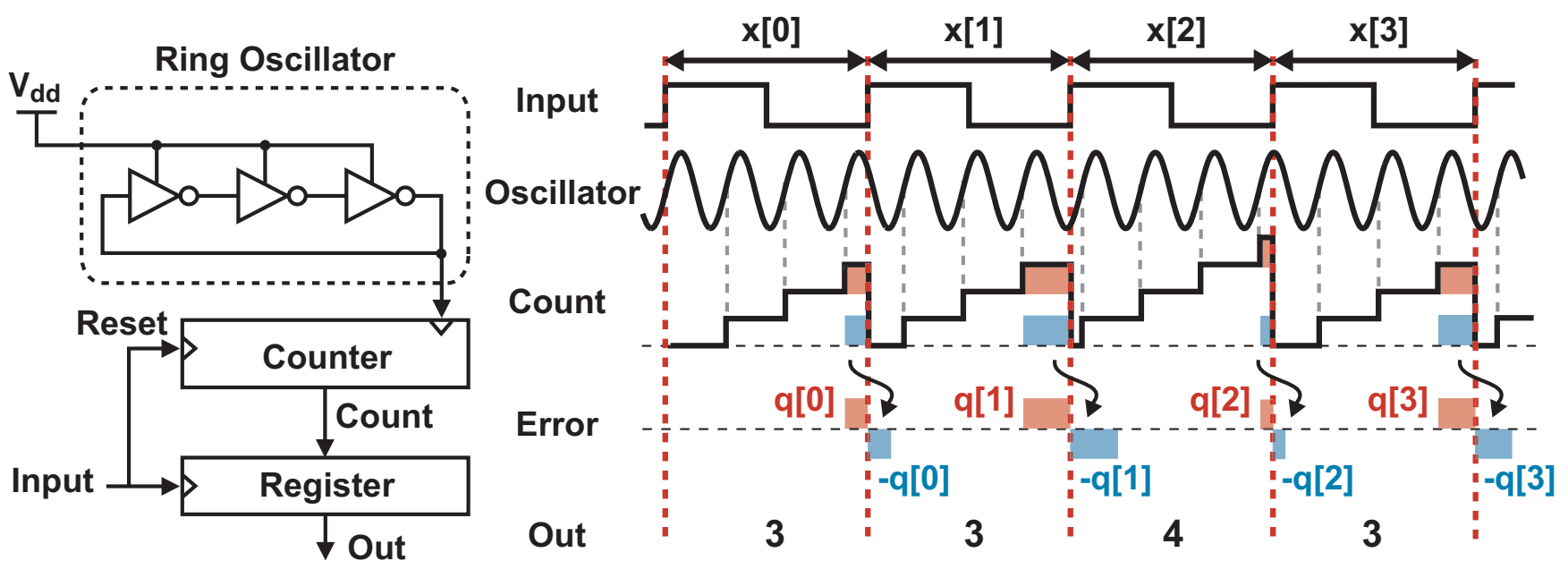
# A Closer Examination of Quantization Noise



- Calculate impact of quantization noise in time:


$$\begin{aligned} out[k] &= x[k] + error[k] \\ &= x[k] + q[k] - q[k-1] \end{aligned}$$

- Take Z-transform:

$$Out(z) = X(z) + (1 - z^{-1})Q(z)$$

**Quantization noise is first order noise shaped!**

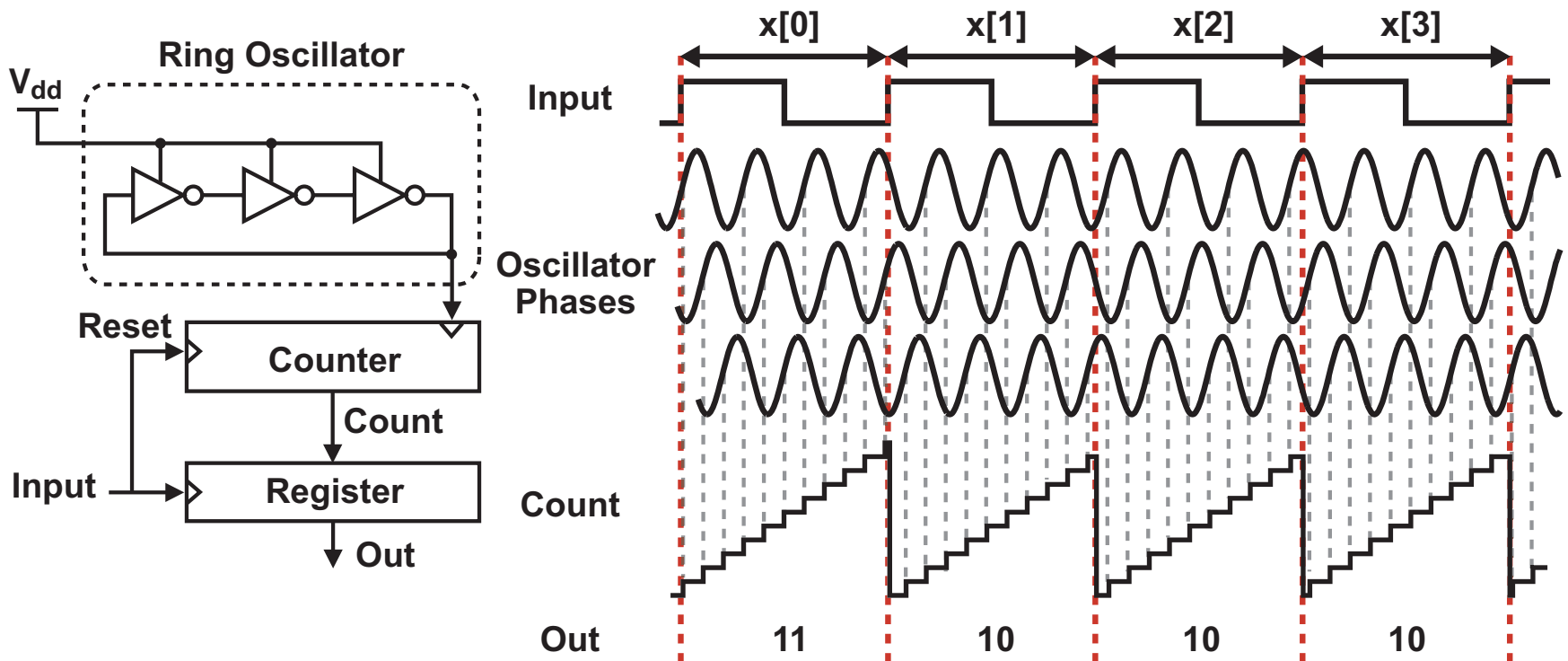
# Improve Resolution By Using All Oscillator Phases




- **Step size in time is reduced to one inverter delay**
  - Quantization noise is still scrambled and first order noise shaped
  - Mismatch between delay elements is *barrel-shifted*

# A Closer Look at Barrel Shifting Property


Measurement 1

 


Measurement 2

 

Measurement 3

 


Measurement 4

 


- Barrel shifting is seen as steady progression through delay elements across measurements
  - Mismatch between delay elements is first order shaped!
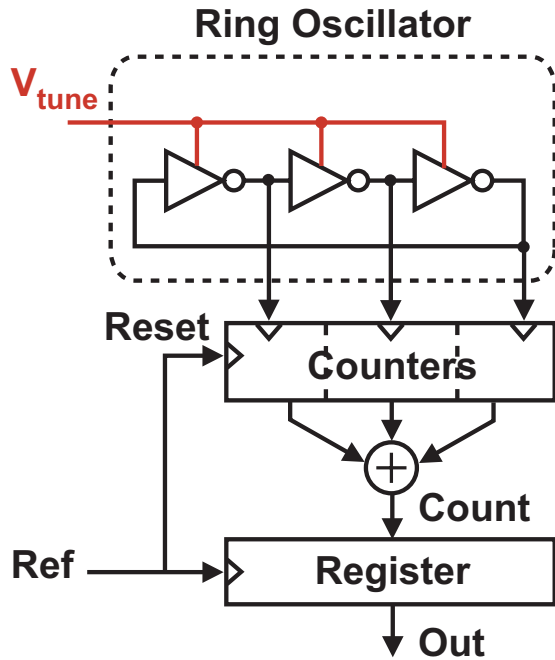
# Application of Ring Oscillator as an ADC Quantizer



 Similar approaches:  
Alon, Stojanovic, Horowitz  
JSSC 2005  
Kim, Cho, ISCAS 2006





- **Input:** analog tuning of ring oscillator frequency
- **Output:** count of oscillator cycles per Ref clock period

**Quantization noise is first order noise shaped!**



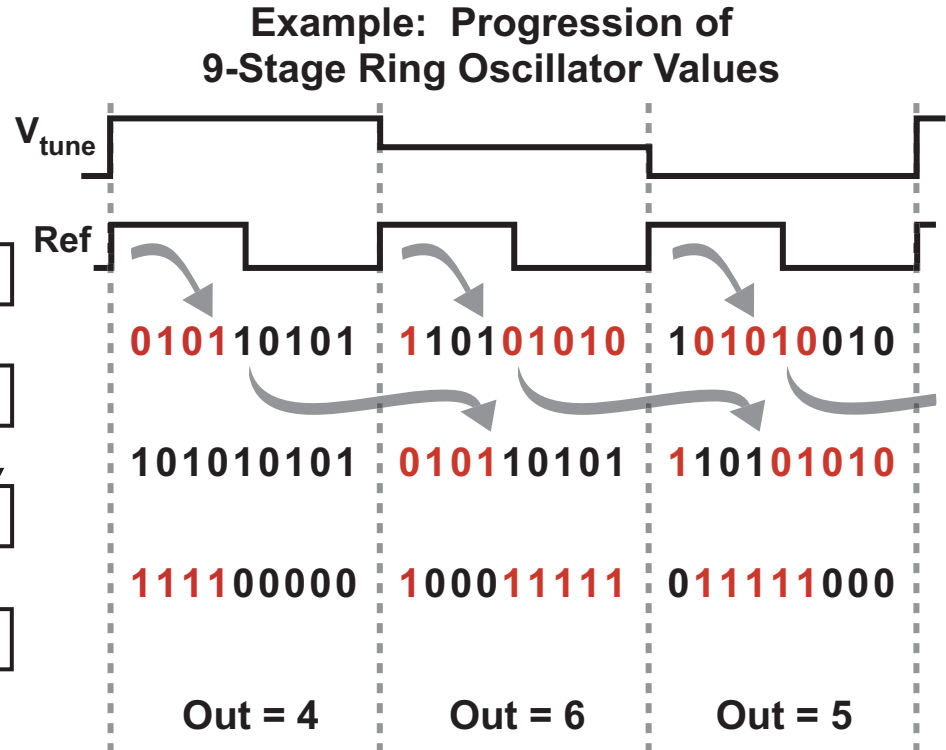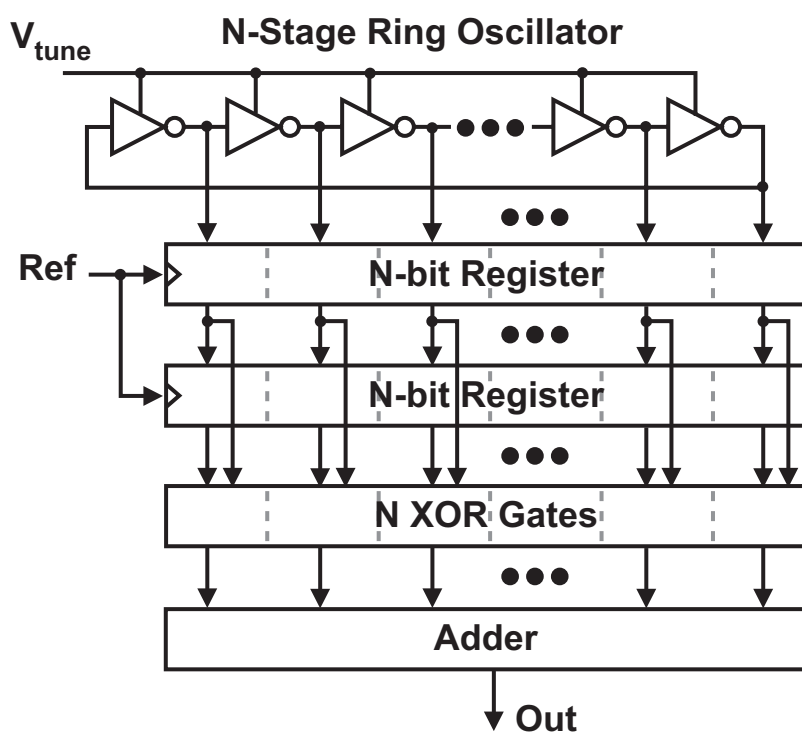
# A Better Implementation for High Speed Conversion



- Assume a high Ref clock frequency (i.e., 1 GHz)
- Increase number of stages,  $N$ , such that transitions never cycle through any stage more than once per Ref clock period
- Use registers and XOR gates to determine transition count
- Avoidance of reset action improves operating speed


# A First Step Toward Modeling

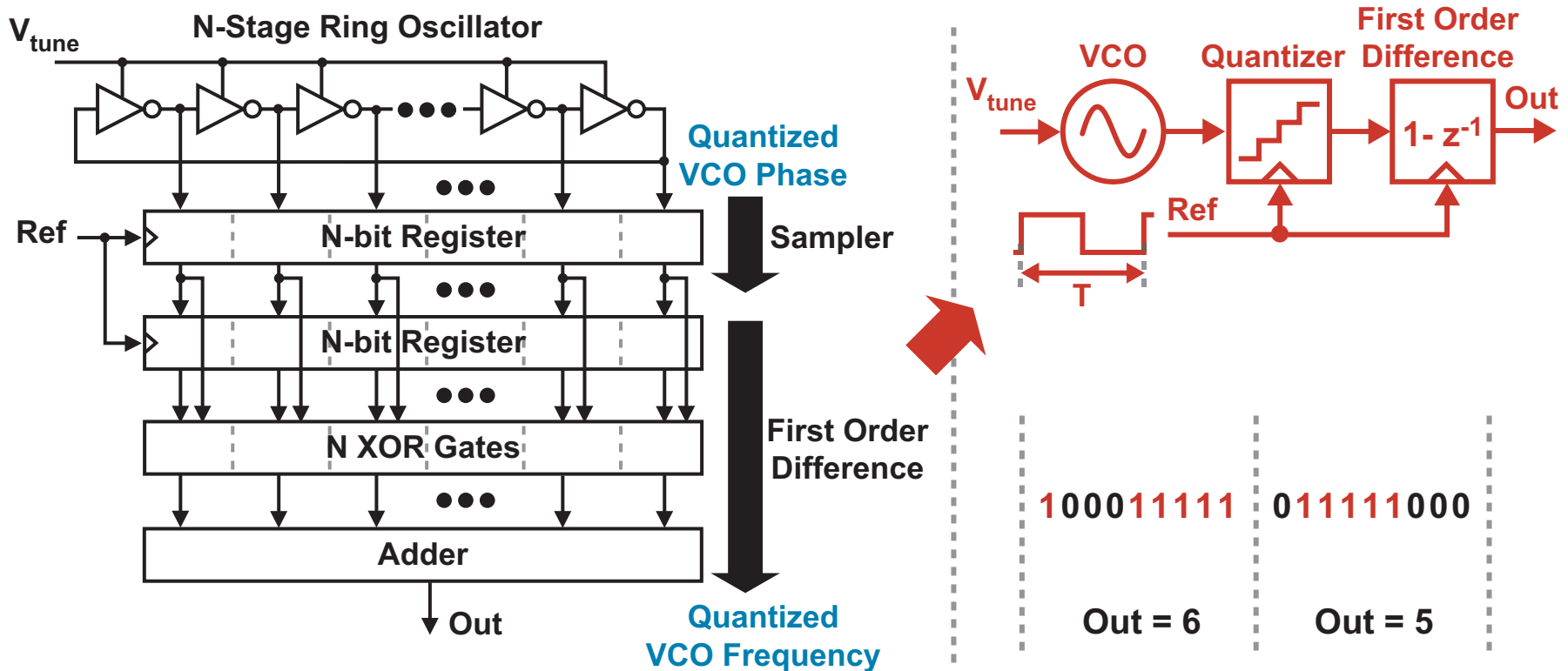



- **VCO provides quantization, register provides sampling**
  - Model as separate blocks for convenience
- **Addition of XOR operation on current and previous samples corresponds to a first order difference operation**
  - Extracts VCO frequency from the sampled VCO phase signal
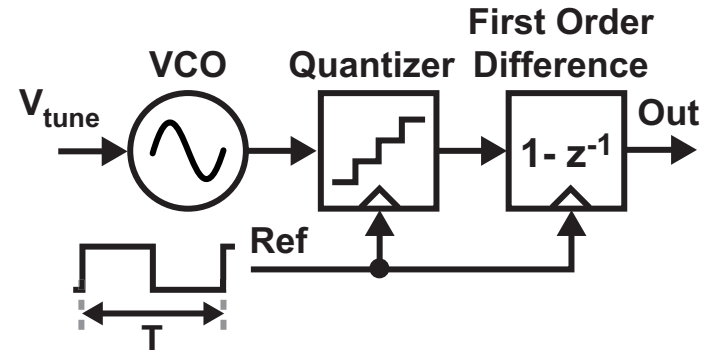
# Corresponding Frequency Domain Model

- VCO modeled as integrator and  $K_V$  nonlinearity
- Sampling of VCO phase modeled as scale factor of  $1/T$
- Quantizer modeled as addition of quantization noise




  - Key non-idealities:
  - VCO  $K_V$  nonlinearity
  - VCO noise
  - Quantization noise





# Example Design Point for Illustration

## Simulated ADC Output Spectrum

 


  - Ref clk:  $1/T = 1$  GHz
- 31 stage ring oscillator
  - Nominal delay per stage: 65 ps
- $K_{VCO} = 500$  MHz/V
  - $\pm 5\%$  linearity
- VCO noise: -100 dBc/Hz at 10 MHz offset




# SNR/SNDR Calculations with 20 MHz Bandwidth


## Simulated ADC Output Spectrum

 


Conditions	SNDR
<b>Ideal</b>	<b>68.2 dB</b>
<b>VCO Thermal Noise</b>	<b>65.4 dB</b>
<b>VCO Thermal + Nonlinearity</b>	<b>32.2 dB</b>

 

 
**VCO  $K_v$  nonlinearity is the key performance bottleneck**


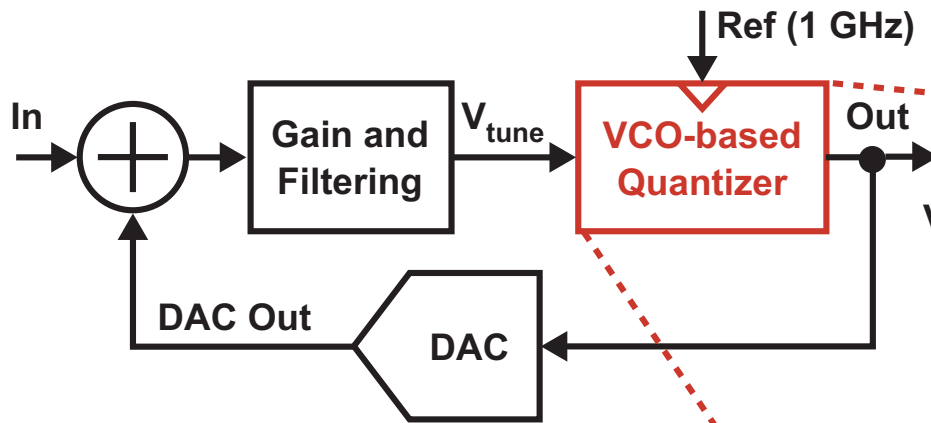
# Reducing the Impact of Nonlinearity using Feedback




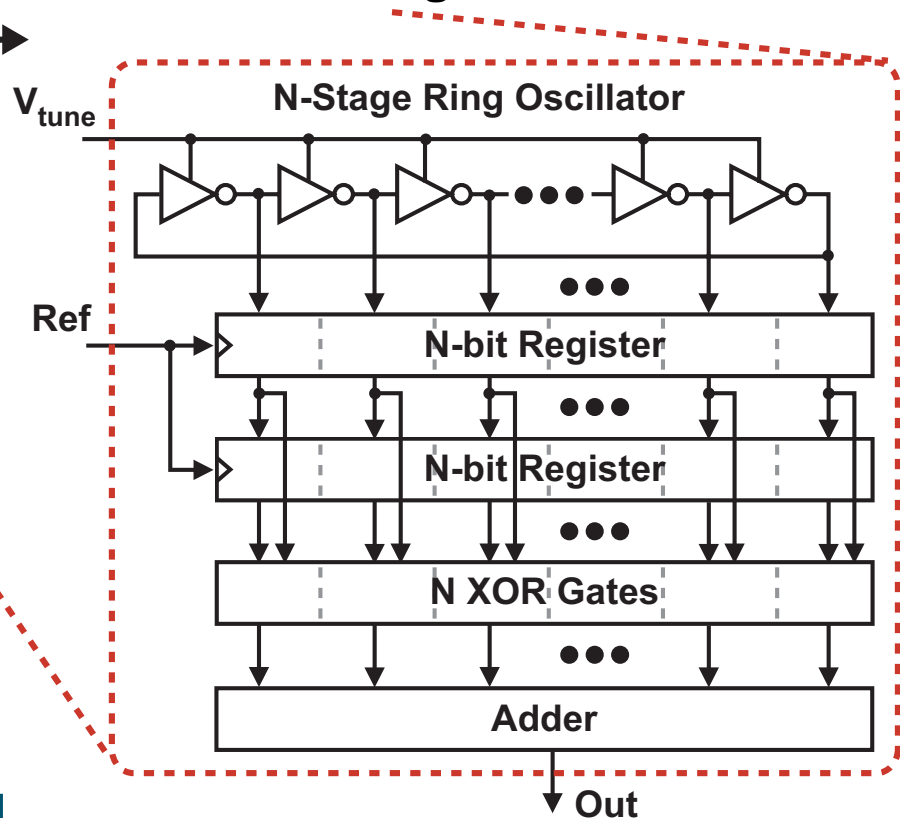Iwata, Sakimura, TCAS II, 1999  
Naiknaware, Tang, Fiez, TCAS II, 2000



- Place VCO-based quantizer within a continuous-time Sigma-Delta ADC structure
  - Quantizer nonlinearity suppressed by preceding gain stage
- Must achieve a highly linear DAC structure
  - Otherwise, noise folding and other bad things happen ...

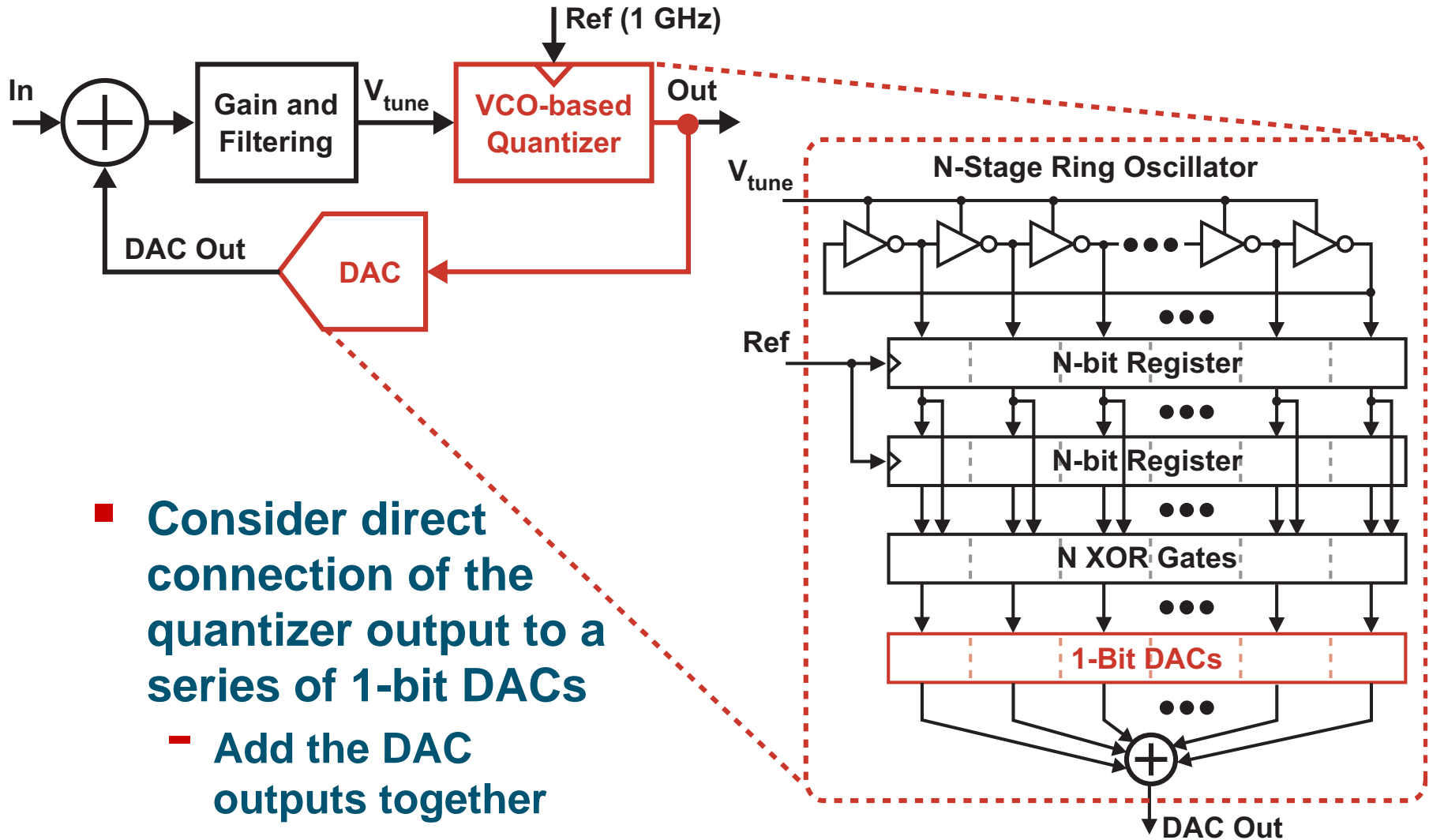
# A Closer Look at the DAC Implementation



- Consider direct connection of the quantizer output to a series of 1-bit DACs
  - Add the DAC outputs together

**What is so special about doing this?**
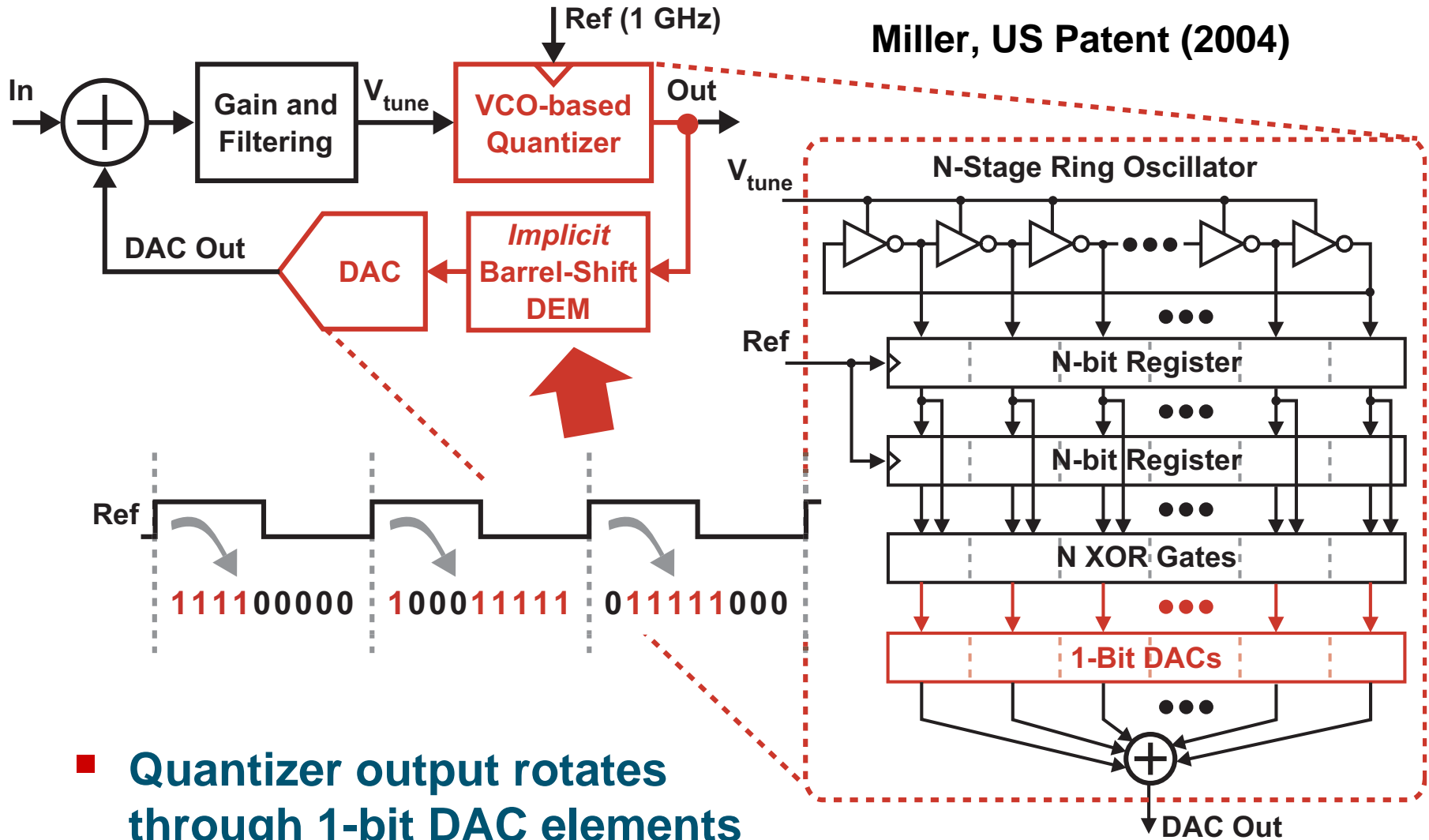
# Key Insight: Quantizer Acts as a Barrel-Shifter




- Quantizer output rotates through 1-bit DAC elements


- Acts to shape DAC mismatch and linearize its behavior


 
# A Geometric View of the VCO Quantizer/DEM and DAC




## Our Prototype

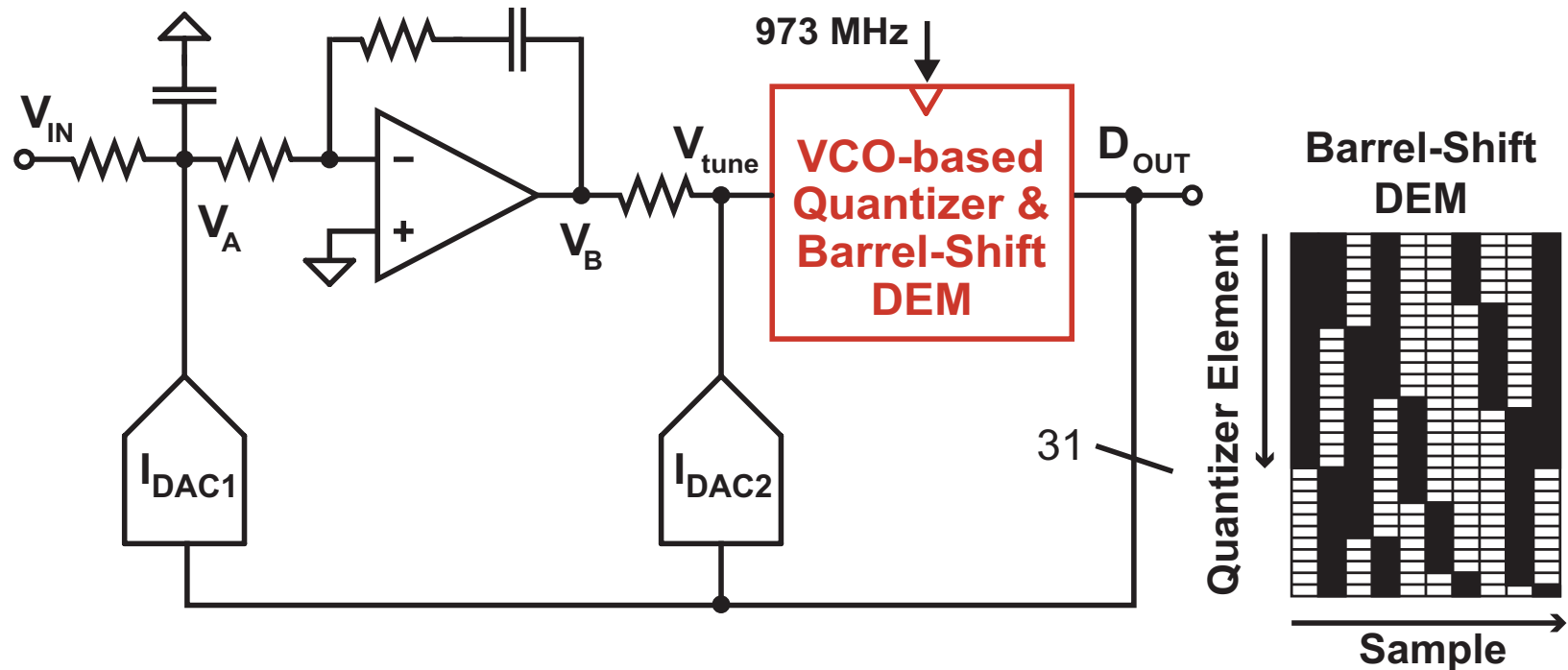


- **Second order dynamics achieved with only *one* op-amp**
  - Op-amp forms one integrator
  - $I_{dac1}$  and passive network form the other (lossy) integrator
  - Minor loop feedback compensates delay through quantizer
- ***Third order* noise shaping is achieved!**
  - VCO-based quantizer adds an extra order of noise shaping



# Custom IC Implementing the Prototype

 

 - 0.13u CMOS
- Power: 40 mW
- Active area: 700u X 700u
- Peak SNDR: 67 dB (20 MHz BW)
- Conversion efficiency: 0.5 pJ/conv. step




# Design of the VCO Core Inverter Cell

  

- 31 stages
- Fast for good resolution ( $< 100$  psec / stage)
- Large  $K_{VCO}$  (600-700 MHz) with good dynamic range
- 2 bits of coarse tuning for process variations
- $< 8$  mW for 1 GSPS 5-bit quantizer / DEM


# Opamp Design is Straightforward

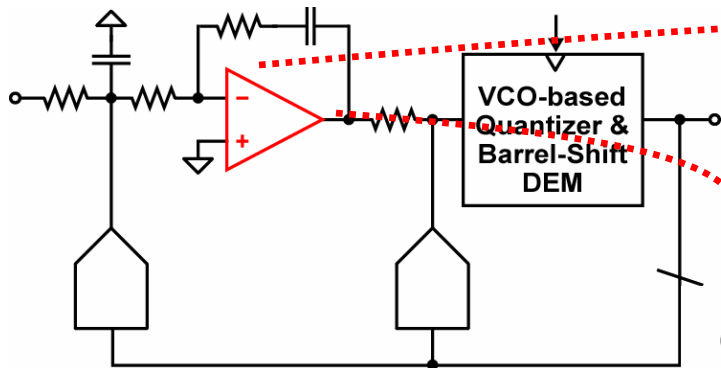
 
## Simulated Performance:


- $A_v = 55$  dB
- $GBW = 2$  GHz
- $P_{DISS} = 15$  mW

High SNR of VCO-based quantizer allows reduced opamp gain ( $A_v$ )



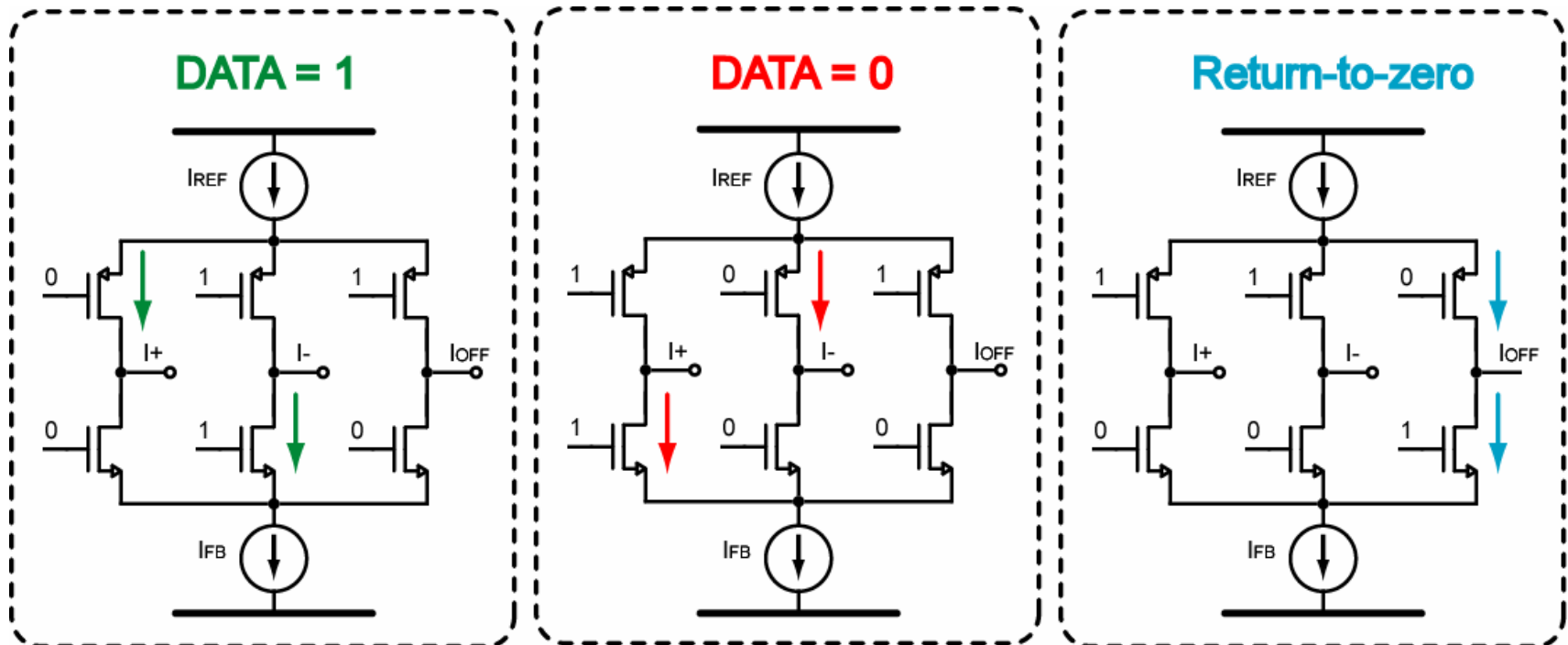
# Primary Feedback DAC Schematic


- Fully differential RZ pulses
- Triple-source current steering
- $I_{\text{OFF}}$  is terminated off-chip



# Measured Spectrum From Prototype

 


# Measured SNR/SNDR Vs. Input Amplitude

 


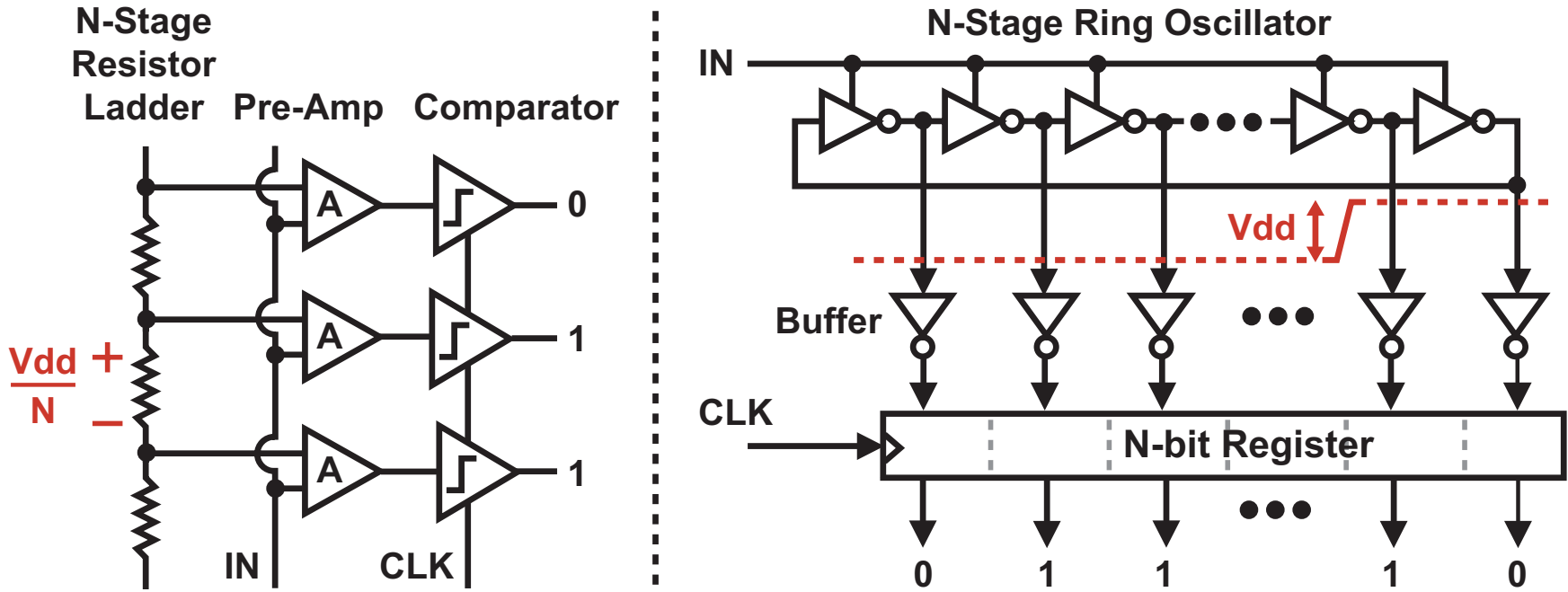
# Summarizing the Benefits of VCO-based Quantization




- **Much more digital implementation**
  - No resistor ladder or differential gain stages
- **Offset and mismatch is not of concern in the design**
- **Metastability behavior is improved**



**Implementation is high speed, low power, low area**
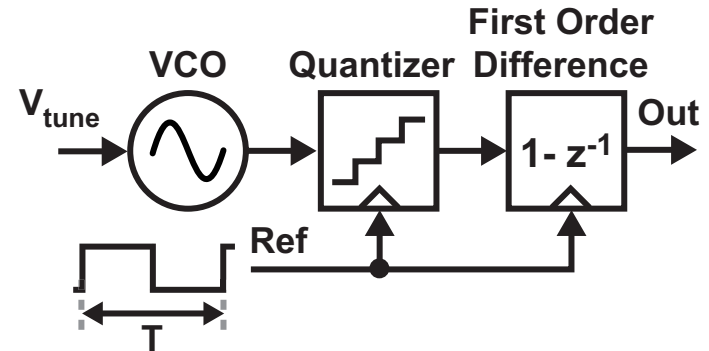
# How Do We Get Better Performance in the Future?

- Key issue: VCO voltage to frequency nonlinearity
- Possible paths to improvement
  - Analog calibration
  - Digital calibration
  - A more appropriate CT Sigma-Delta ADC topology



  System and algorithm innovation hold much promise



# Conclusions

---


- **VCO-based quantization is a promising component for achieving low power, high resolution, analog-to-digital conversion**
  - High speed, low power, low area implementation since offset and mismatch is not of concern
  - First order noise shaping of quantization noise
    - Lowers open loop gain requirements in CT Sigma-Delta ADC since quantizer has high SNR
  - Improved metastability behavior
- **12-bit ENOB, 10 MHz bandwidth ADC was demonstrated with 40 mW of power consumption**
- **Key focus for future designs: reduce impact of VCO nonlinearity**

# ***MEMS-based Clocking***


***Aaron Partridge, SiTime, Inc.***
 
# Early Developments

- Early MEMS resonator, 1965
  - The “Resonant Gate Transistor”



H.C. Nathanson, App. Phys. Lett. 1965

 


H.C. Nathanson, Trans. Elec. Des. 1967
 
## Early Developments

---

- **Early MEMS resonator, 1965**
  - The “Resonant Gate Transistor”
- **Poly resonators and integrated electronics**
  - True MEMS oscillators on a chip




C.T.C. Nguyen, R.T. Howe, JSSC 1999
 
## Early Developments

---

- **Early MEMS resonator, 1965**
  - The “Resonant Gate Transistor”
- **Poly resonators and integrated electronics**
  - True MEMS oscillators on a chip
- **Sometimes exotic materials**
  - Diamond, Silicon Carbide




J. Wang, C.T.C. Nguyen, MEMS'2004

 
# Early Developments

---

- **Early MEMS resonator, 1965**
  - The “Resonant Gate Transistor”
- **Poly resonators and integrated electronics**
  - True MEMS oscillators on a chip
- **Sometimes exotic materials**
  - Diamond, Silicon Carbide
- **Now often trenched into SOI**
  - Single Crystal Material



 Tuning fork resonator trenched into SOI wafer surface.




S. Pourkamali, F. Ayazi, 2004


 
# Early Developments


---

- **Early MEMS resonator, 1965**
  - The “Resonant Gate Transistor”
- **Poly resonators and integrated electronics**
  - True MEMS oscillators on a chip
- **Sometimes exotic materials**
  - Diamond, Silicon Carbide
- **Now often trenched into SOI**
  - Single Crystal Material
- **After 40 years, MEMS oscillators are on the market**



Tuning fork resonator in SOI with encapsulation cover.

# Key MEMS Fabrication Process Steps

 


- **MEMS First™** invented by Markus Lutz, SiTime founder.
- **EpiSeal™** invented by Dr. Aaron Partridge, SiTime founder.
- The process took more than seven years to develop at Bosch, Stanford, and SiTime.
 
# Completed Resonators



---

- **Size**
  - 140 micron thin
  - 0.8 x 0.6 mm footprint
- **Mechanically robust**
  - Quad structure of resonator
  - SiTime's patented EpiSeal™ protects the resonator at the wafer level
- **Low cost**
  - Standard IC packaging
  - 50,000 resonators per wafer




# Stacked Die Construction

Fabrication Solid Model

  


De-lid die photo




# Frequency Stability Over Temperature

 

# Frequency Stability: Aging 1year

 
  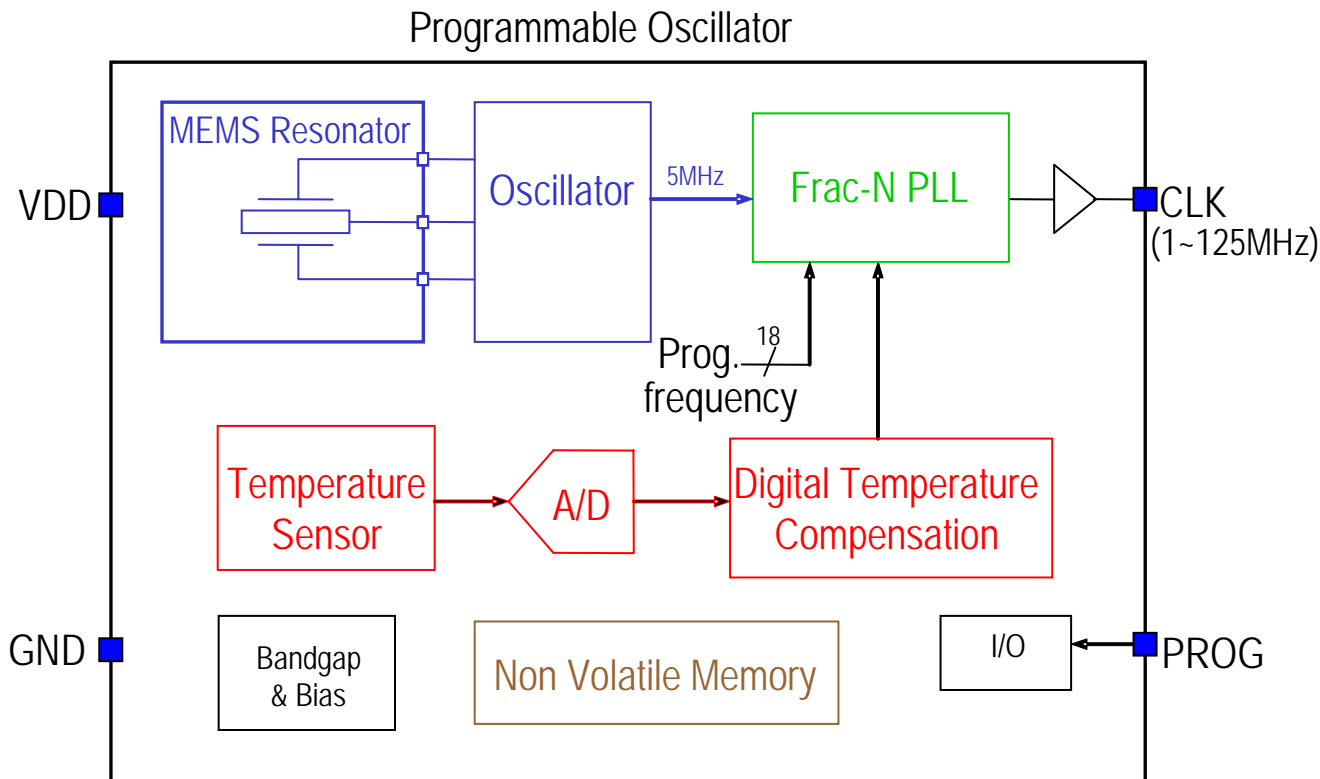
# Enough MEMS, What About the System Design?



1.4 mm


# SiT8002 General Purpose Programmable Oscillators

**In Mass Production!**

- Drop-in replacements for quartz-based oscillators
  - Pin-out compatible
  - Footprint compatible
- Flexible architecture
  - Any Frequency: 1 MHz to 125 MHz
  - Any Voltage: 1.8 V, 2.5 V, or 3.3 V
  - Standby or Output Enable Modes
  - +/- 50 ppm over -40 to +85 C
- Always-in-stock: 3 week lead time
- Highly Mechanically Robust
  - 50,000G Shock test
  - 70G Vibration test from 20 to 1 kHz



Pin Number	Pin Name	Pin Type	Pin Description
1	ST	Digital In	Standby
2	GND	Power	Connect to Ground
3	CLK	Digital Out	Clock Output
4	VDD	Power	Connect 1.8V, 2.5V or 3.3V

 


Frequency Range	Accuracy	Jitter	Current Consumption	Startup Time	VDD	Packages	Temp. Range
1 – 125 MHz	+/- 50 ppm +/- 100 ppm	20 ps rms period jitter	< 15 mA (no load)	Typical 12 ms	1.8, 2.5, 3.3 +/- 5%	2520, 3225, 5032, 7050	-40 to +85 C -10 to +70 C




# SiT8002UT World's Thinnest Programmable Osc.

Samples  
NOW!

 

SiT8002UT: Flexible Timing Solution in a Tiny Package

 - Package thickness of <400 micron
  - Footprint: 3.5 x 3.0 mm
  - +/- 100 ppm over -40 to +85 C




Frequency Range	Accuracy	Jitter	Current Consumption	Startup Time	VDD	Packages	Temp. Range
1 – 125 MHz	+/- 100 ppm	20 ps rms period jitter	< 15 mA (no load)	Typical 12 ms	1.8, 2.5, 3.3 +/- 5%	3.5 x 3.0 x 0.37 mm	-40 to +85 C

# SiT8102 Lowest Jitter Programmable Oscillator

In Pre-Production!
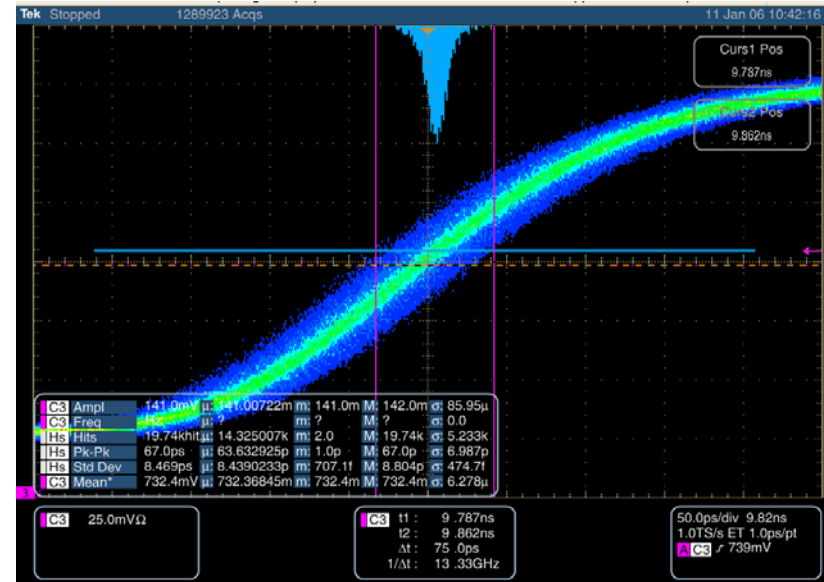
## SiT8102: High Performance Oscillator

- <1ps rms phase jitter (random)
- < 4 ps rms Period jitter
- Typical programmable quartz oscillators:
  - 15-25 ps rms Period jitter
- Small size: 2.5x2.0x0.8 mm
- Typical applications:
  - SATA, SAS, FibreChannel, Firewire (1394), Ethernet, 10G Ethernet, PCI Express



Frequency Range	Accuracy	Period Jitter	Current Consumption	Startup Time	VDD	Packages	Temp. Range
1 – 200 MHz	+/- 25ppm +/-50ppm +/-100ppm	<4 ps rms period jitter	< 17 mA (no load)	10 ms max	1.8, 2.5, 3.3V +/- 5%	2520, 3225, 5032, 7050	-40 to +85 C -10 to +70 C

# Conclusions

---

- **Clock generation is required in all communication and computation systems**
  - Quartz crystals have provided accurate timing for 40 years
    - Present a barrier to achieving higher levels of integration
- **MEMS-based clocking allows higher levels of integration**
  - Temperature and process variations can be handled through circuit design and calibration
  - Provides a platform for clocking solutions with expanded functionality and very high levels of integration

# Summary of Short Course

---

- **PLLs have been around for over 70 years, but still present an exciting research area**
  - **Digital phase-locked loops provide an exciting platform for improving PLL performance**
    - Joint circuit/algorithm approaches
    - New TDC designs will be key to excellent performance
  - **Analog circuits will continue to play an important role**
    - Achieve high resolution and speed much more efficiently than digital circuits
  - **New technologies will allow better performance and higher levels of integration**
    - Optical/electrical integration
    - MEMS-based resonator technology